

Time-Domain Analysis of Switching Transitions

Buck

Assume: (i) C_{ds} is linear (through an equiv. or otherwise)
 (ii) $V \approx \text{const}$ during t_{dt}

During t_{dt}

AC-equivalent

Buck-Boost

AC equivalent

Resonant Circuit Solution

general example

(1) $V_{bc} - v_c = L \frac{di_c}{dt}$
 (2) $i_c - I_{dc} = C \frac{dv_c}{dt}$

$$V_{bc} - v_c = L \frac{d}{dt} \left(C \frac{dv_c}{dt} + I_{dc} \right)$$

$$V_{bc} - v_c = LC \frac{d^2 v_c}{dt^2}$$

$$LC \frac{d^2 v_c}{dt^2} + v_c - V_{bc} = 0$$

ICs:
 @ $t=0$ $v_c(0) = V_0$
 $i_c(0) = I_0$

$$v_c(t) = V_{bc} + (V_0 - V_{bc}) \cos\left(\frac{t}{\sqrt{LC}}\right) + (I_0 - I_{dc}) \sqrt{\frac{L}{C}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_c(t) = I_{dc} + (I_0 - I_{dc}) \cos\left(\frac{t}{\sqrt{LC}}\right) + \sqrt{\frac{C}{L}} (V_{bc} - V_0) \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$\underbrace{\hspace{10em}}_{\text{DC solution}} \quad \text{Define:} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad f_0 = \frac{1}{2\pi\sqrt{LC}} \quad R_0 = \sqrt{\frac{L}{C}}$



Normalization and Notation

$$v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos(\omega_0 t) + (I_0 - I_{DC}) R_0 \sin(\omega_0 t)$$

$$i_c(t) = I_{DC} + (I_0 - I_{DC}) \cos(\omega_0 t) + \frac{V_0 - V_0}{R_0} \sin(\omega_0 t)$$

→ Normalizing $v_c(t)$ & $i_c(t)$ according to:

- $m_c(t) = \frac{v_c(t)}{V_{base}}$, V_{base} is an ("arbitrary") constant voltage
- $j_c(t) = \frac{i_c(t)}{I_{base}}$, $I_{base} = \frac{V_{base}}{R_0}$ ←
- $\theta = \omega_0 t$

$$v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos\left(\frac{\omega_0 t}{\sqrt{LC}}\right) + (I_0 - I_{DC}) \frac{R_0}{\sqrt{LC}} \sin\left(\frac{\omega_0 t}{\sqrt{LC}}\right)$$

$$i_c(t) = I_{DC} + (I_0 - I_{DC}) \cos\left(\frac{\omega_0 t}{\sqrt{LC}}\right) + (V_{DC} - V_0) \frac{1}{\sqrt{LC}} \sin\left(\frac{\omega_0 t}{\sqrt{LC}}\right)$$

Pick $V_{base} = V_{DC} \rightarrow I_{base} = \frac{V_{base}}{R_0} = \frac{V_{DC}}{R_0} = \frac{V_{DC}}{1/LC}$

$$m_c(t) = \frac{v_c(t)}{V_{base}} = 1 + \frac{(V_0 - V_{DC})}{V_{DC}} \cos(\omega_0 t) + \frac{(I_0 - I_{DC}) R_0}{V_{DC}} \sin(\omega_0 t)$$

$$j_c(t) = \frac{i_c(t)}{I_{base}} = \frac{I_{DC}}{I_{base}} + \frac{(I_0 - I_{DC}) R_0}{V_{DC}} \cos(\omega_0 t) + \frac{V_{DC} - V_0}{R_0} \frac{R_0}{V_{DC}} \sin(\omega_0 t)$$

try: $(m_c - 1)^2 + \left(j_c - \frac{I_{DC}}{I_{base}}\right)^2$

$$= \left(\frac{V_0 - V_{DC}}{V_{DC}} \cos(\omega_0 t) + \frac{(I_0 - I_{DC}) R_0}{V_{DC}} \sin(\omega_0 t)\right)^2 + \left(\frac{(I_0 - I_{DC}) R_0}{V_{DC}} \cos(\omega_0 t) - \frac{V_0 - V_{DC}}{V_{DC}} \sin(\omega_0 t)\right)^2$$

$$= \left(\frac{V_0 - V_{DC}}{V_{DC}}\right)^2 (\cos^2 \omega_0 t + \sin^2 \omega_0 t) + \left(\frac{(I_0 - I_{DC}) R_0}{V_{DC}}\right)^2 (\sin^2 \omega_0 t + \cos^2 \omega_0 t)$$

$$(m_c(r)-1)^2 + (j_c(r) - \frac{I_{oc}}{I_{base}})^2 = \left(\frac{V_o - V_{bc}}{V_{bc}}\right)^2 + \left(\frac{I_o - I_{oc}}{I_{base}}\right)^2$$

↓

Circle centered @ $m_c=1, j_c = \frac{I_{oc}}{I_{base}}$
w/ radius of r

$$\rightarrow \sqrt{\left(\frac{V_o - V_{bc}}{V_{bc}}\right)^2 + \left(\frac{I_o - I_{oc}}{I_{base}}\right)^2} = r$$

Normalization

Differential equations \rightarrow geometric equation

- for linear LL, LC circuits (w/ DC voltage & current sources)

UT

State Plane Analysis

if lossless, r is constant

ex: what is $i_{c,max}$?
 $j_{c,max} = I_{oc} + r$

Denormalize
 $i_{c,max} = j_{c,max} I_{base}$

$= I_{oc} + r I_{base}$

[1] R. Oruganti and F. C. Lee, "Resonant Power Processors, Part I - State Plane Analysis", Industry Applications, IEEE Tran. on, vol. 21, no. 6, nov 1985.

[2] D. P. Atherton, Nonlinear Control Engineering. London: Van Nostrand Reinhold, 1982, Ch. 2.