



Announcements

- Presentation from General Motors (electrification and controls)
 - Thursday (tomorrow) at 3:40 in MK 524


a) Buck-Boost: $\frac{V}{V_g} = \frac{D}{D'} = \frac{1}{2} \rightarrow \boxed{D = \frac{1}{3}}$


b) To get $P_{out} = \frac{V^2}{R} = 1000W$,
 $\rightarrow I = \frac{I_{out}}{D'} = \frac{3}{2} \frac{1000W}{200V} = 7.5A$ ~~15A~~

7.5 A – Note: values for the remainder of the problem are affected



Assume $R_{ds} = 100m\Omega$ still applies at 15A current at any time, I_c flows through two devices, so

$P_{cond} = I_c^2 (R_{ds} \cdot 2) = \boxed{45W}$

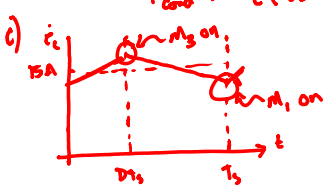c) 

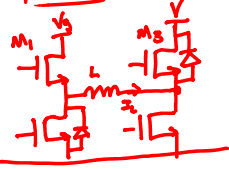

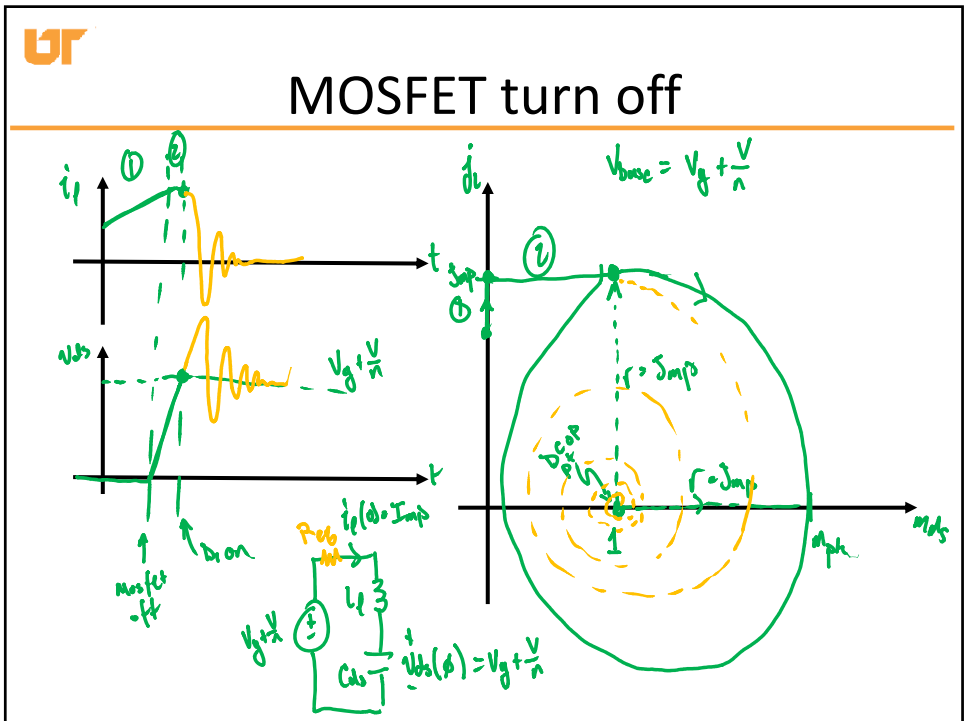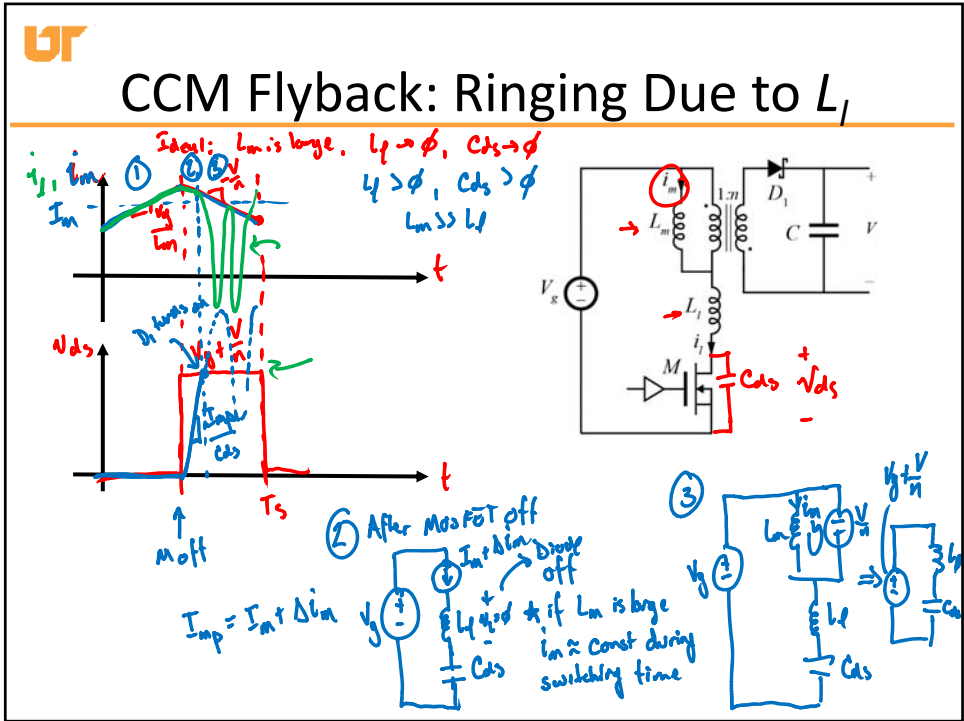w) constant I_g . V_g tracks Q_g waveform under hard-switched conditions. When soft-switched, the "Miller plateau" will disappear. Because of direction of I_c & adequate t_{dt} , D_2 & D_3 are conducting during all turn-on transitions





Leakage Voltage Stress

$$m_{pk} = 1 + \Delta i_{mp}$$

$$V_{pk} = V_{base} m_{pk} = \left(V_g + \frac{V}{n} \right) \left(1 + (I_{mr} \Delta i_m) \frac{R_o}{V_g + \frac{V}{n}} \right)$$

$$= V_g + \frac{V}{n} + R_o (I_{mr} \Delta i_m)$$

ex
Similar to Avb

$$V_g = 400V$$

$$r = 10V$$

$$P = 100W$$

$$f_s = 1MHz$$

$$D = 0.5$$

$$n = \frac{1}{40}$$

$$C_{ds} = 100pF$$

$$L_m = 1.8mH$$

$$L_f = 35\mu H$$

(2% of L_m)

$$R_o = \sqrt{\frac{L_f}{C_{ds}}} \approx 600\Omega$$

$$I_m = \frac{I_{out} n}{D}$$

$$2 \Delta i_m = \frac{V_g}{L_m} \Delta T_s$$

$$I_{mp} = 550mA$$

$$V_{base} = V_g + \frac{V}{n} = 800V$$

Voltage stress in ideal case

$$V_{pk} = 800V + 600\Omega (550mA)$$

$$V_{pk} \hat{=} 1150V!$$

Risk of destruction or higher rating necessary



Leakage Switching Loss

$$E_{start} = \frac{1}{2} C_{ds} \left(V_g + \frac{V}{n} \right)^2 + \frac{1}{2} L_f I_{mp}^2$$

$$E_{end} = \frac{1}{2} C_{ds} \left(V_g + \frac{V}{n} \right)^2$$

$$E_{loss} = \frac{1}{2} L_f I_{mp}^2$$

$$= \frac{1}{2} (35\mu H) (550mA)^2$$

* Assuming ringing dies out before the end of the switching period.



$$\approx 5.29 \mu J$$

$$@ 1MHz = f_s$$

$$P_{loss} = 5.29W$$



CCM Flyback: Clamping Circuit

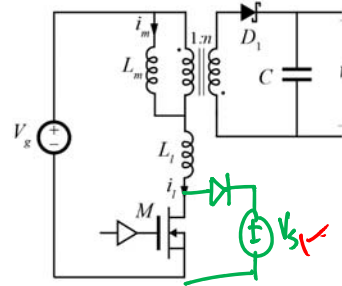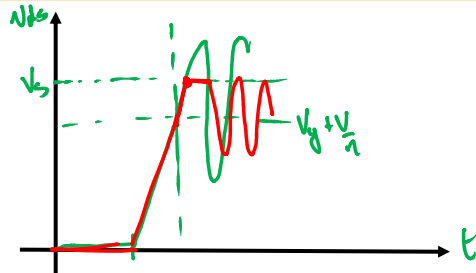

$V_g + \frac{V}{n} < V_c < V_{pk}$
 $V_c = 1000V$



Clamped State Plane

