
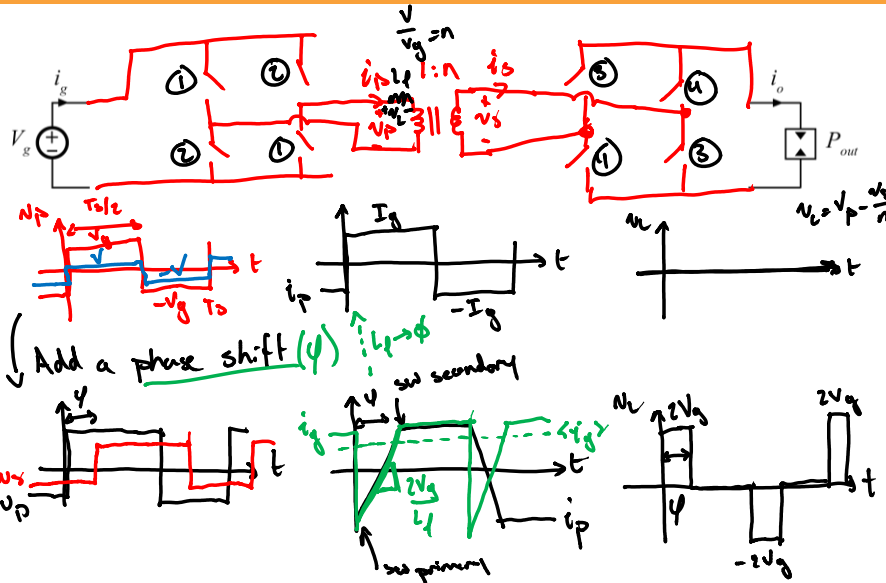



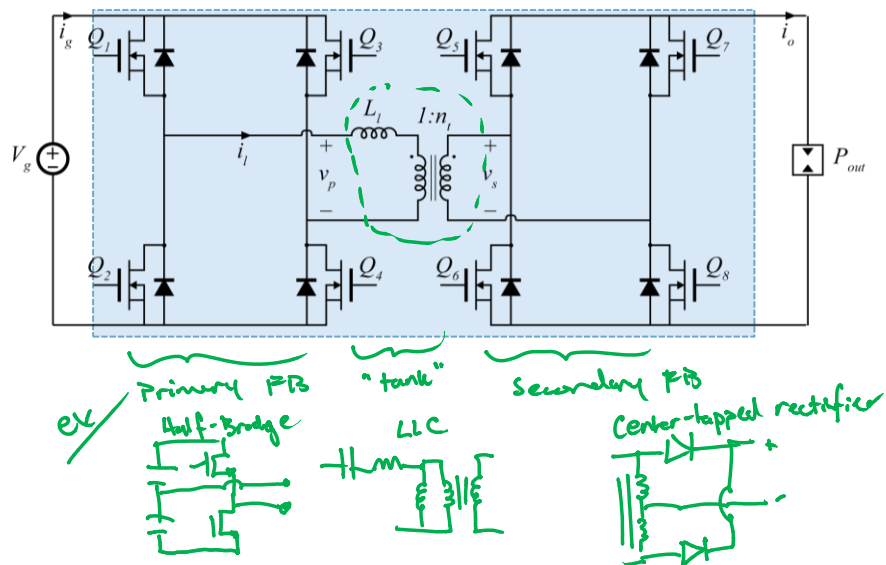


Introduction to AC-link topologies



DAB Converter "Quasi-resonant"



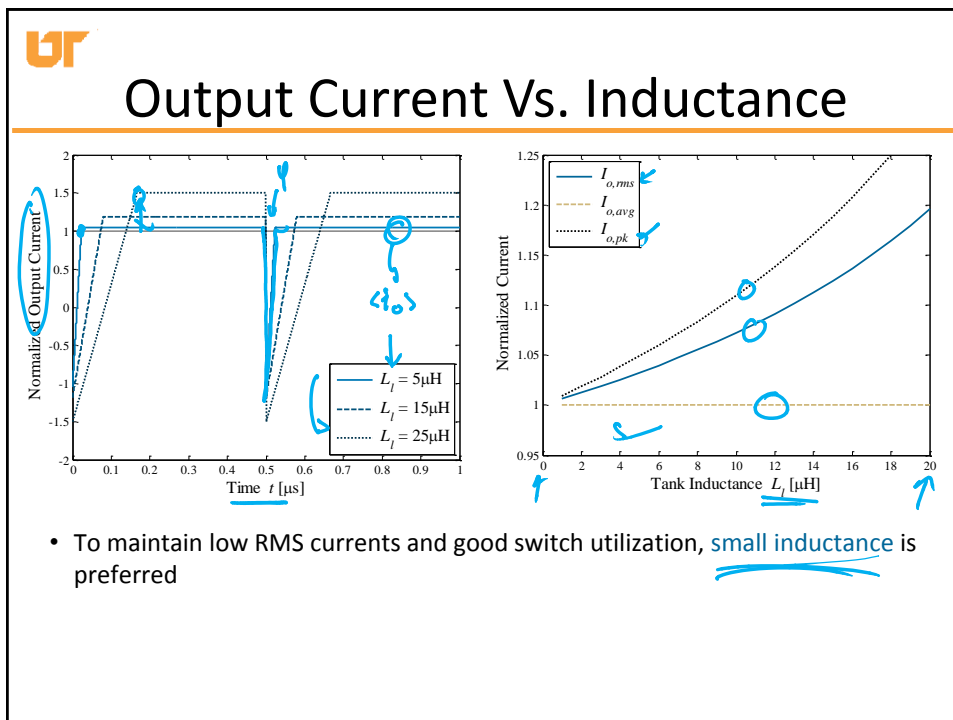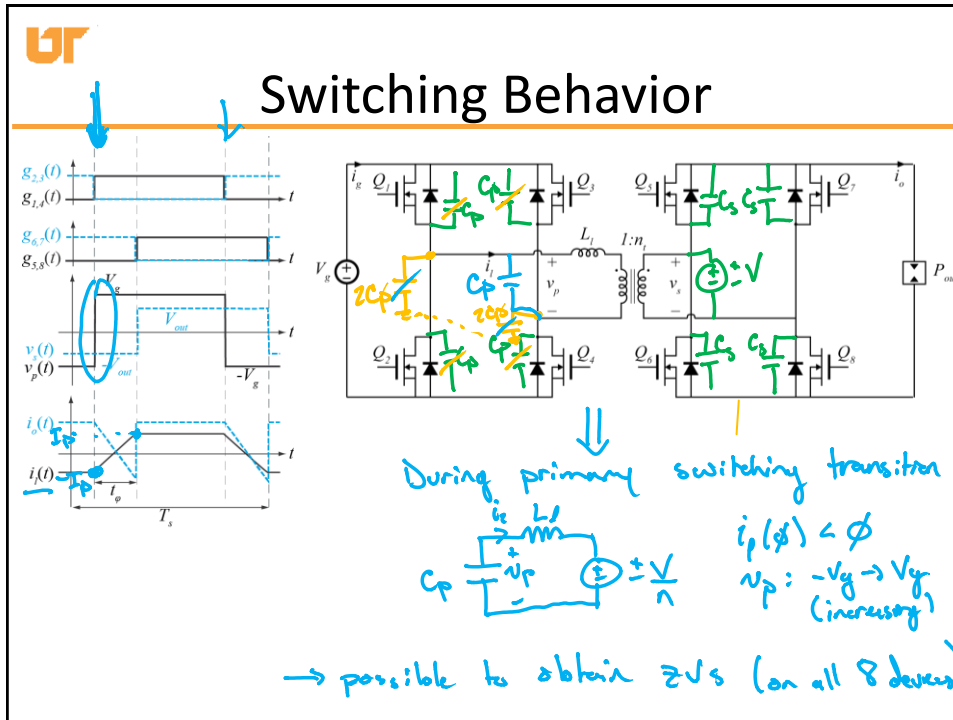



Dual Active Bridge Converter

