



Averaging Step

$$\eta_t \langle i_{out} \rangle = \frac{2}{T_s} \int_{t_1}^{t_2} i_{out}(t) dt = \frac{2}{T_s} [f_1 + f_2 + f_3 + f_4]$$

$$\frac{1}{I_{base}} \cdot \eta_t \langle i_{out} \rangle = \frac{2}{T_s} \left[2C_p V_g + t_2 \frac{J_1 - J_2}{2} + \phi + t_4 J_p \right] \cdot \frac{1}{I_{base}}$$

$$J = \eta_t \frac{\langle i_{out} \rangle}{I_{base}} = \frac{2}{T_s} \left[2C_p V_g \frac{z_0}{\sqrt{f_0}} + t_2 \frac{J_1 - J_2}{2} + t_4 J_p \right]$$

$$J = 2f_3 \left[\frac{z_0}{\omega_0} + t_2 \frac{J_1 - J_2}{2} + t_4 J_p \right] \cdot \frac{\omega_0}{\omega_0}$$

$$J = \frac{2f_3}{z_0 f_0} \left[z + \beta \frac{J_1 - J_2}{2} + h J_p \right]$$

$$J = \frac{r}{\pi} \left[z + \frac{h}{2} (J_1 - J_2) + h J_p \right]$$

↑ ↑



Output Plane

$$J = \frac{n \langle i_{out} \rangle}{I_{base}} = \frac{F}{\pi} \left[2 + \frac{1}{4} (J_1^2 - J_2^2) + J_p \left(\frac{\pi}{F} - \alpha - \beta - \delta \right) \right]$$


← ↓

$$F = \frac{f_s}{f_0}$$

$$F \rightarrow 1 \quad f_0 = f_s$$

$F \rightarrow 0 \quad f_0 \gg f_s$

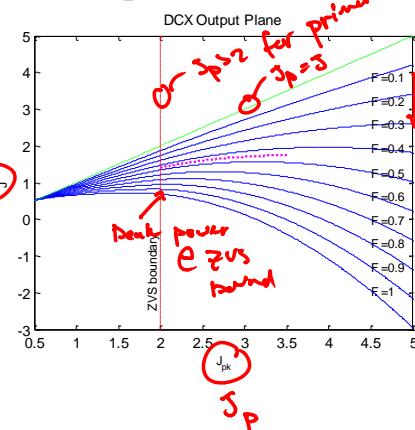$\approx v_s \approx \text{very fast wrt } T_s$





Selection of Tank Inductance


- State plane analysis gives equation of the form:

$$P_{out} = f(L_i, C_p, C_s, f_s, J_p) \rightarrow f(\text{design, } J_p)$$

- If we select some minimum power P_{min} for ZVS design to place ZVS boundary ($J_p = 2$), at P_{min}

$$P_{min} = f(L_i, \text{devices, } f_s)$$

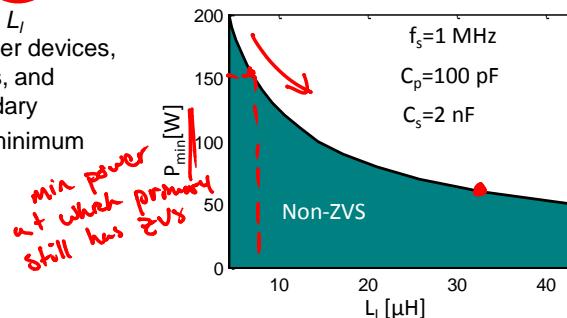- From resulting equation, L_i determined from converter devices, application requirements, and placement of ZVS boundary
- Now select devices for minimum loss in converter



Selecting MOSFETs for DAB

150 V FETS

Device Variant	Type	r_{on} [mΩ]	C_{oss} [pF]	Q_g [nC]
EPC1012	GaN	70	80	1.9
EPC1010	GaN	18	310	7.5
FDMS2672	MOS	64	95	30
IPD320N	MOS	35	135	12.0
IRFS4020	MOS	85	91	18.0

12V FETS

Device Variant	Type	r_{on} [mΩ]	C_{oss} [pF]	Q_g [nC]
EPC1014	GaN	12.0	150	3.0
EPC1015	GaN	3.2	575	11.6
CSD16325Q5C	MOS	1.7	2190	18.0
STD60N3LH5	MOS	8.8	265	8.8
CSD16411Q3	MOS	12.0	330	2.9


- Representative sample of HV and LV devices, including Si and GaN devices
- Above P_{min} , all devices have no switching loss, so efficiency only depends on conduction losses


$$P_{cond} = P_{cond,p} + P_{cond,s} = 2r_{on,p}i_{g,rms}^2 + 2r_{on,s}i_{out,rms}^2$$

Selecting MOSFETs for DAB

150 V FETS					12V FETS				
Device Variant	Type	r_{on} [mΩ]	C_p [pF]	Q_g [nC]	Device Variant	Type	r_{on} [mΩ]	C_s [pF]	Q_g [nC]
EPC1012	GaN	70	87	1.9	EPC1014	GaN	12.0	241	3.0
EPC1010	GaN	18	353	7.5	EPC1015	GaN	3.2	1000	11.6
FDMS2672	MOS	64	177	30	CSD16325Q5C	MOS	1.7	3200	18.0
IPD320N	MOS	35	379	12.0	STD60N3LH5	MOS	8.8	713	8.8
IRFS4020	MOS	85	140	18.0	CSD16411Q3	MOS	12.0	486	2.9

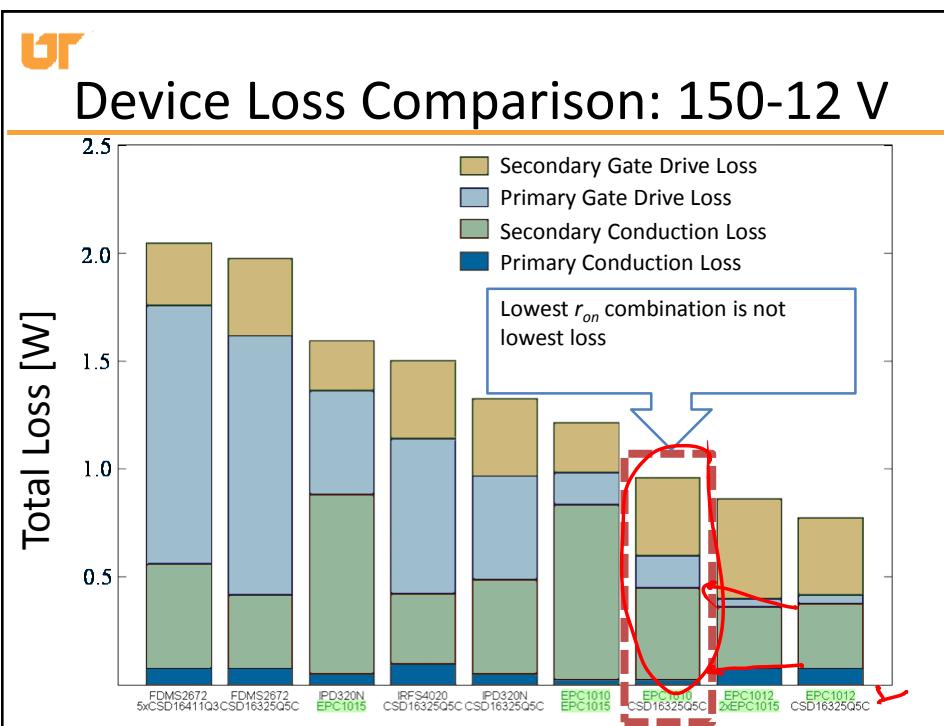- Representative sample of HV and LV devices, including Si and GaN devices
- Above P_{min} , all devices have no switching loss, so efficiency only depends on conduction losses
- Initial conclusion is to select lowest r_{on} devices
- Can solve analytical loss model from state plane analysis





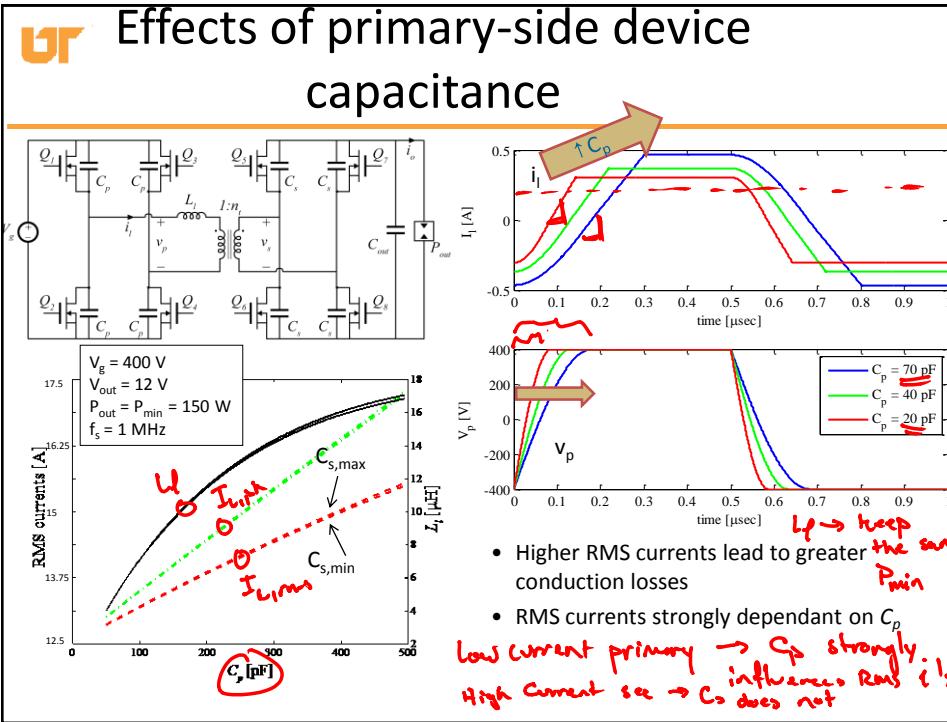

Selecting MOSFETs for DAB

150 V FETs					12V FETs				
Device Variant	Type	r_{on} [mΩ]	C_p [pF]	Q_g [nC]	Device Variant	Type	r_{on} [mΩ]	C_s [pF]	Q_g [nC]
EPC1012	GaN	70	17	1.9	EPC1014	GaN	12.0	241	3.0
EPC1010	GaN	18	353	7.5	EPC1015	GaN	3.2	1000	11.6
FDMS2672	MOS	64	177	30	CSD1632505C	MOS	1.7	3200	18.0
IPD320N	MOS	35	379	12.0	STD60N3LH5	MOS	8.8	713	8.8
IRFS4020	MOS	85	140	18.0	CSD16411Q3	MOS	12.0	486	2.9

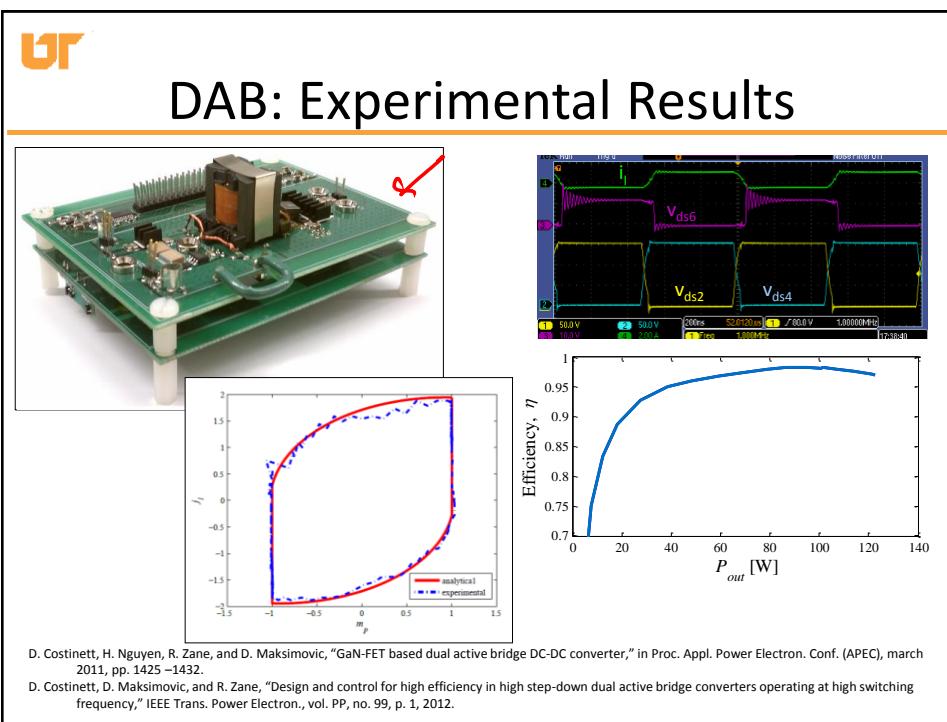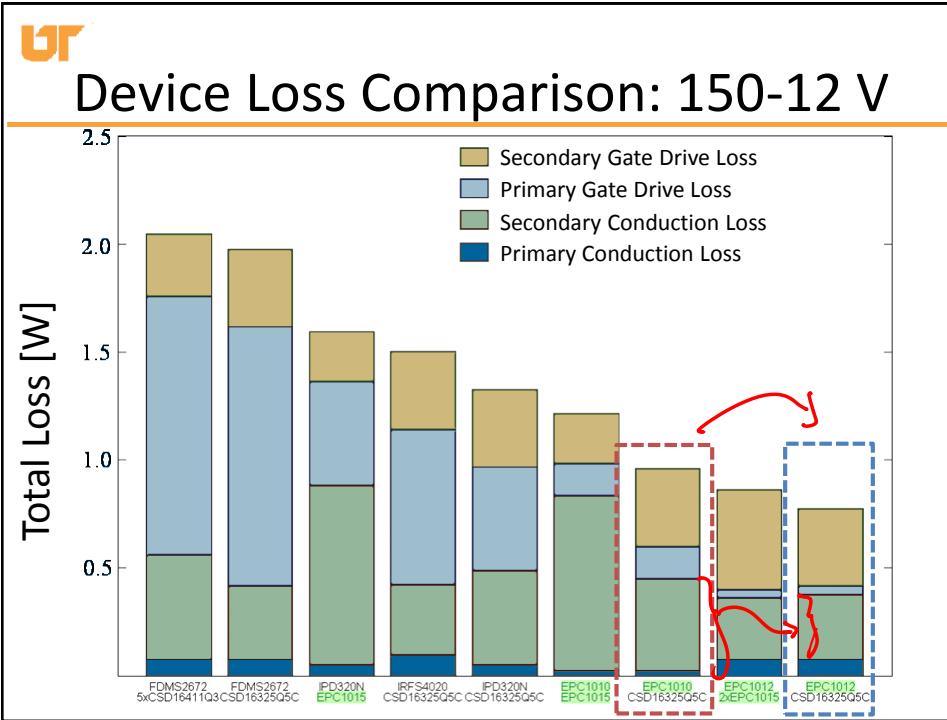
- Analysis predicts that optimal selection consists of lowest C_p primary device and lowest r_{on} secondary device






Linear Model Comparison to Simulation

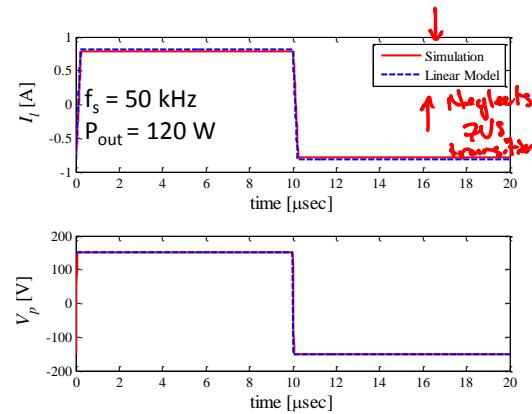- At high output power and low switching frequency, square wave model of DAB converter accurately predicts behavior of full circuit simulation



High Frequency, Low Power Operation

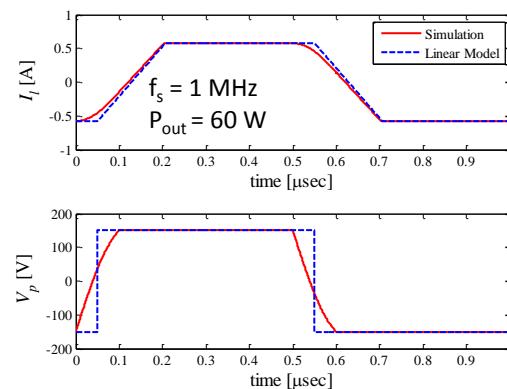- At low output power and high switching frequency, square wave model is poor fit to circuit behavior
- Effect of switching transitions need to be considered




Application Example: Automotive

Fig. 1. Converter operating voltage ranges required for automotive application.

Fig. 3. Automotive DAB converter ($273 \times 90 \times 53$ mm).

Fig. 13. Calculated distribution of the power losses for operation at $V_1 = 340$ V, $V_2 = 12$ V, and $P_2 = 2$ kW.

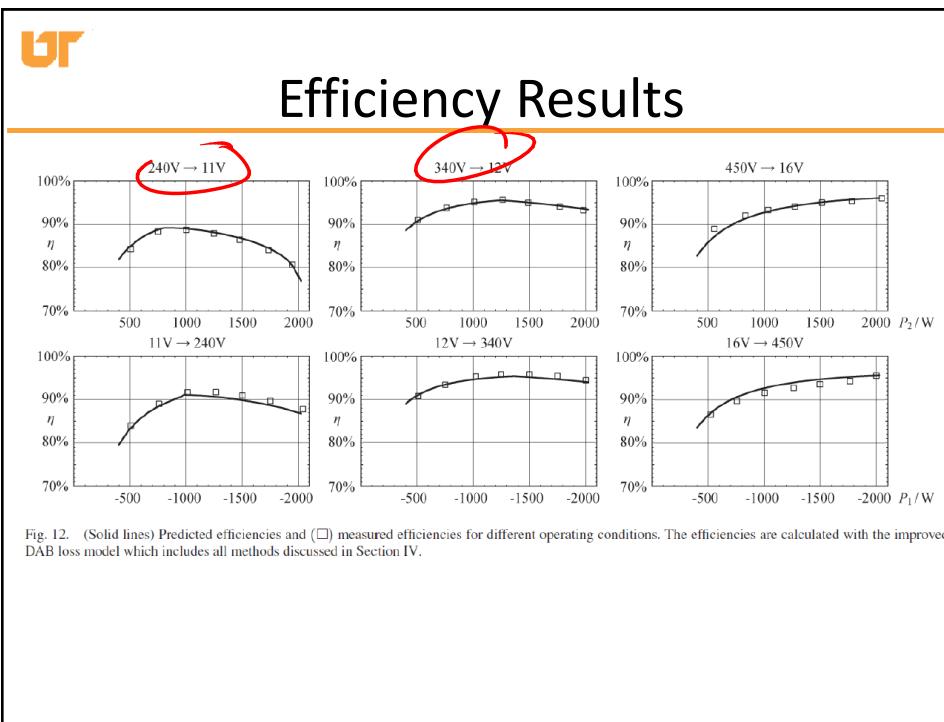*F. Krismer, J.W.Kolar, "Accurate Power Loss Model Derivation of a High-Current Dual Active Bridge Converter for an Automotive Application, IEEE Trans. On Industrial Electronics, March 2010





Alternate Modulation Schemes

