

**UF** **Series Resonant Converter**  
*(one of many modes of operation)*

*phase-shift modulation*

$g_{2,3}(t)$   
 $g_{1,4}(t)$   
 $g_{6,7}(t)$   
 $g_{5,8}(t)$   
 $v_p(t)$   
 $v_s(t)$   
 $i_o(t)$   
 $i_l(t)$   
 $v_r(t)$

$V_g$   
 $C_{in}$   
 $v_p$   
 $C_r$   
 $i_l$   
 $L_r$   
 $1:n$   
 $v_s$   
 $C_{out}$   
 $V_{out}$   
 $I_{load}$

$n i_o(t)$   
 $I_1$   
 $I_2$   
 $I_3$   
 $I_4$   
 $V_{r2}$   
 $V_{r1}$   
 $T_s$

Design so that  $f_0 = \frac{1}{2\pi\sqrt{L_r C_r}} \ll f_s$   
 (otherwise may lose ZVS)

In next few slides, neglect ZVS transitions  $\rightarrow$  analyze same as before

$\log(f\omega)$   
 $f_s$   
 $\frac{1}{5C_r}$   
 $\frac{1}{5L_r}$

**UF** **Complete State Plane – Phase Shift Modulation**  $\phi \geq 1$

$r_1^2 = M_{r1}^2 + J_1^2 = M_{r2}^2 + J_2^2$   
 $\alpha = \pi - \tan^{-1}\left(\frac{J_1}{M_{r1}}\right) - \tan^{-1}\left(\frac{J_2}{M_{r2}}\right)$

$r_2^2 = (M_{r2} + 2)^2 + J_2^2 = (M_{r1} + 2)^2 + J_1^2$   
 $\beta = \tan^{-1}\left(\frac{J_2}{M_{r2} + 2}\right) + \tan^{-1}\left(\frac{J_1}{2 + M_{r1}}\right)$

unknowns:  $M_{r1}, M_{r2}, J_1, J_2, \alpha, \beta$



## Averaging Step

Complete sw. period

$$\omega_0 \frac{T_s}{2} = (t_\alpha + t_\beta) \omega_0$$

$$\alpha + \beta = \frac{\pi}{F}$$

$$n \langle i_{out} \rangle = \frac{2}{T_s} \int i_p(t) dt = \frac{2}{T_s} [g_1 + g_2]$$

$$= \frac{2}{T_s} [C_r (V_{r2} + V_{r1}) + C_r (V_{r1} - V_{r2})]$$

$$\frac{1}{I_{base}} n \langle i_{out} \rangle = \frac{2}{T_s} 2C_r V_{r1} \cdot \frac{R_o}{V_{base}}$$


$$J = M_{r1} 2 \frac{F}{\pi}$$

$$M_{r1} = \frac{\cos(\frac{\pi}{2F} - \beta)}{\cos(\frac{\pi}{2F})} - 1$$

Y. Cheron, "Soft Commutation"





## SRC Simulation

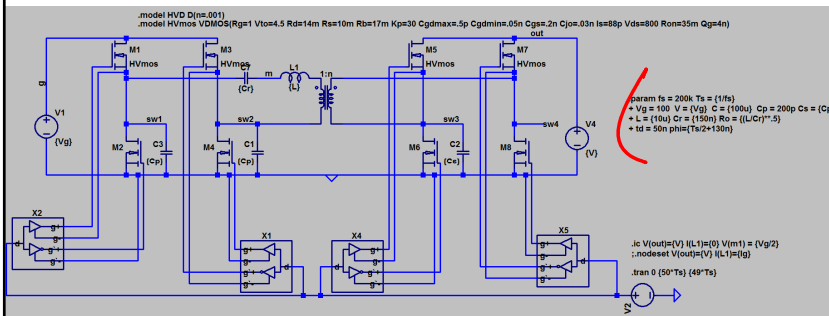

$f_s = 200kHz$   
 $V = V_g = 100V$   
 $L = 10\mu H$   
 $C_r = 150nF$




$F \approx 1.5$

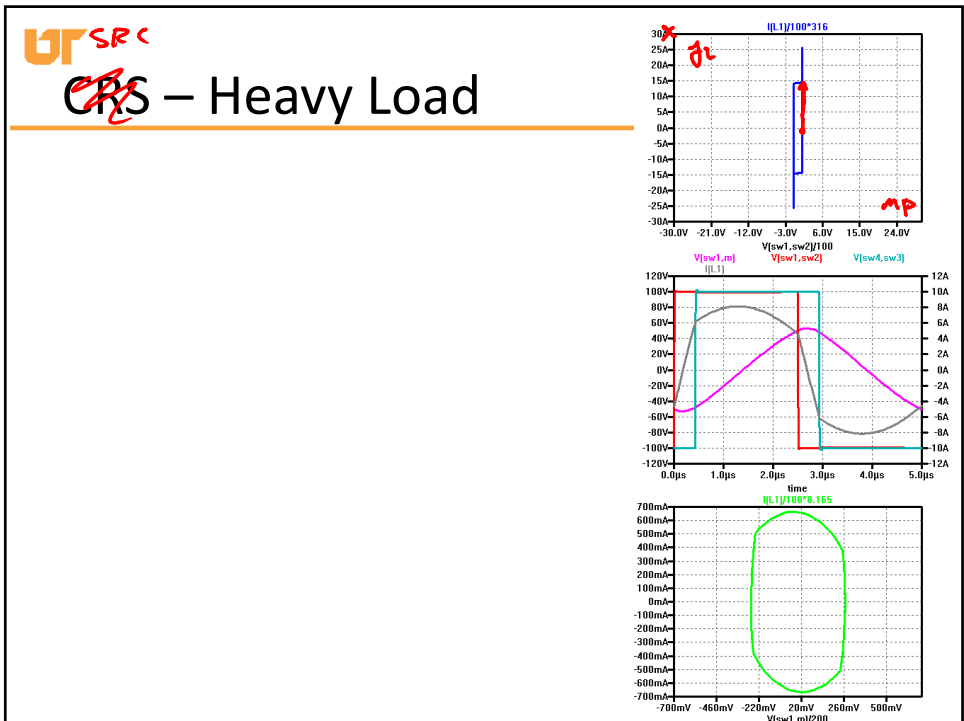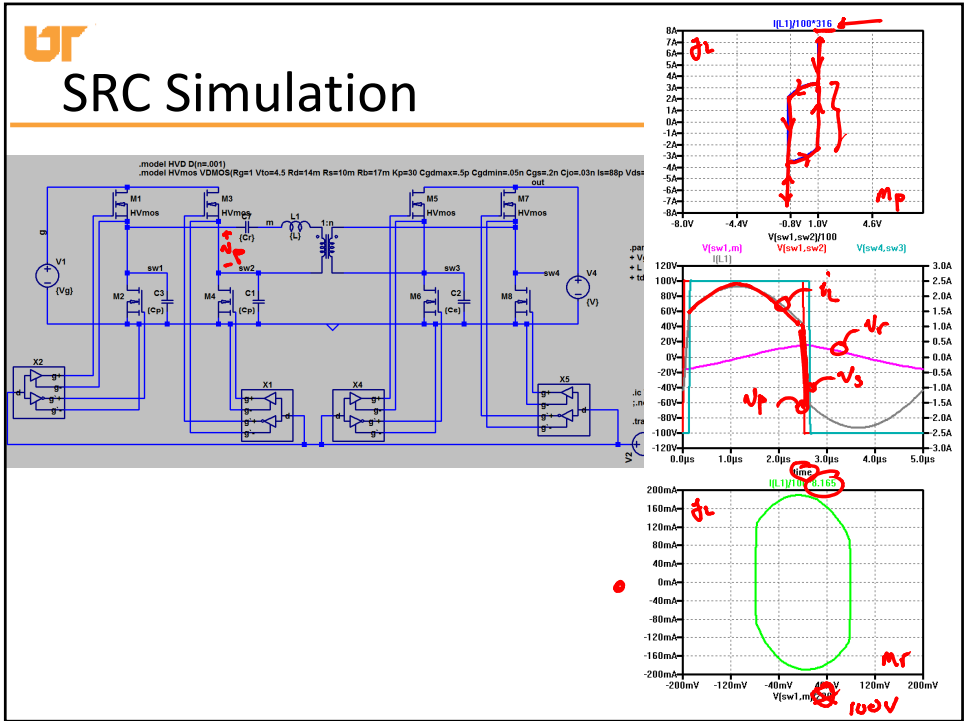






# SRC – Light Load



$F \approx 1.5$

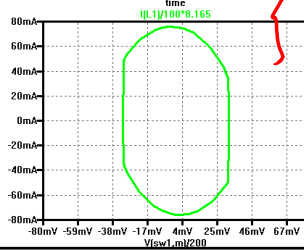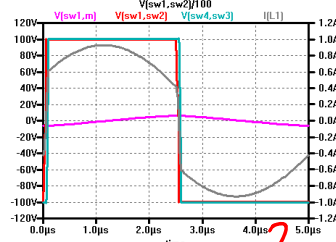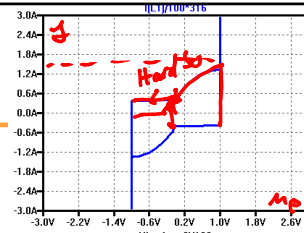

# SRC Near Resonance

$F = 1.05$

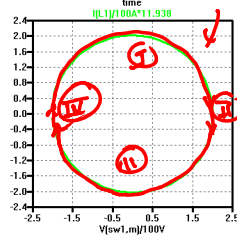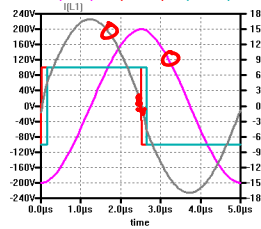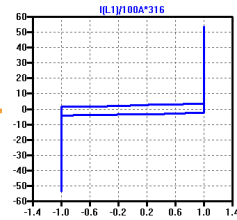

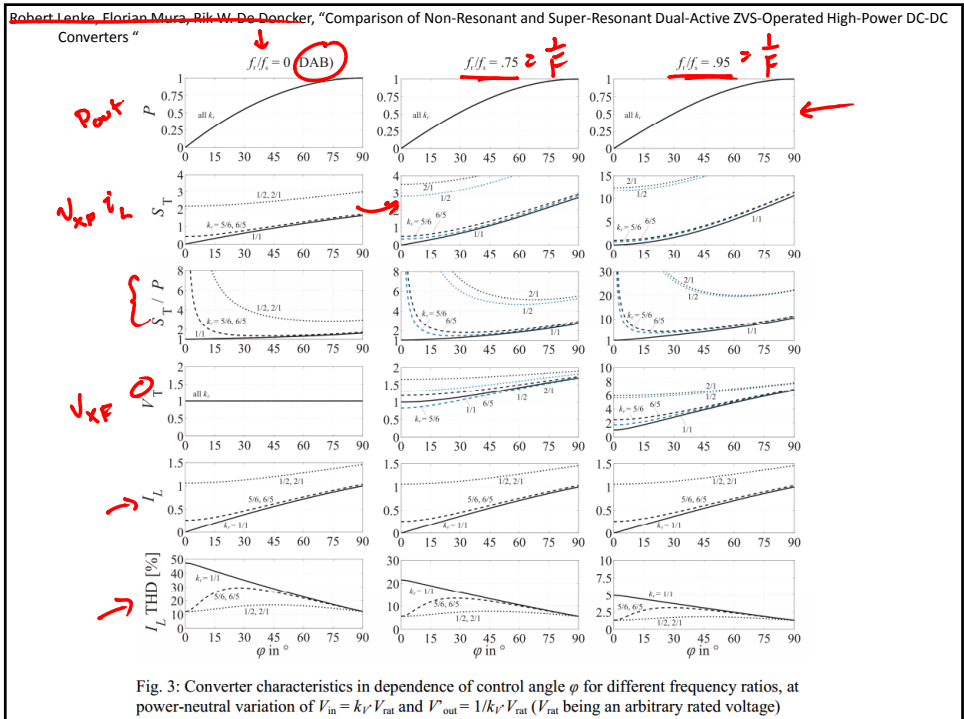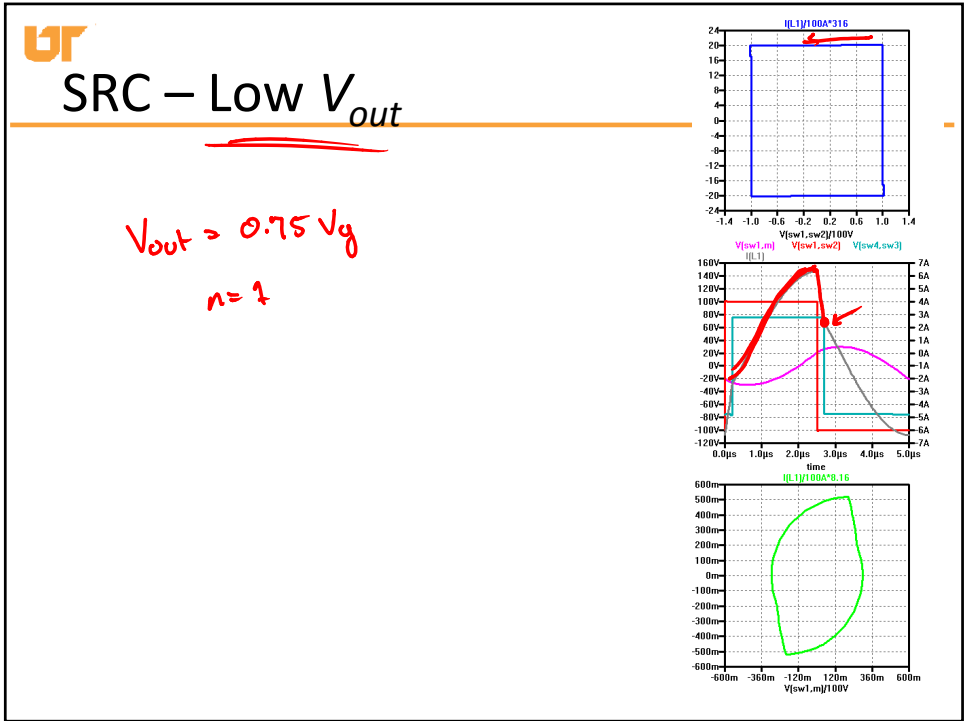

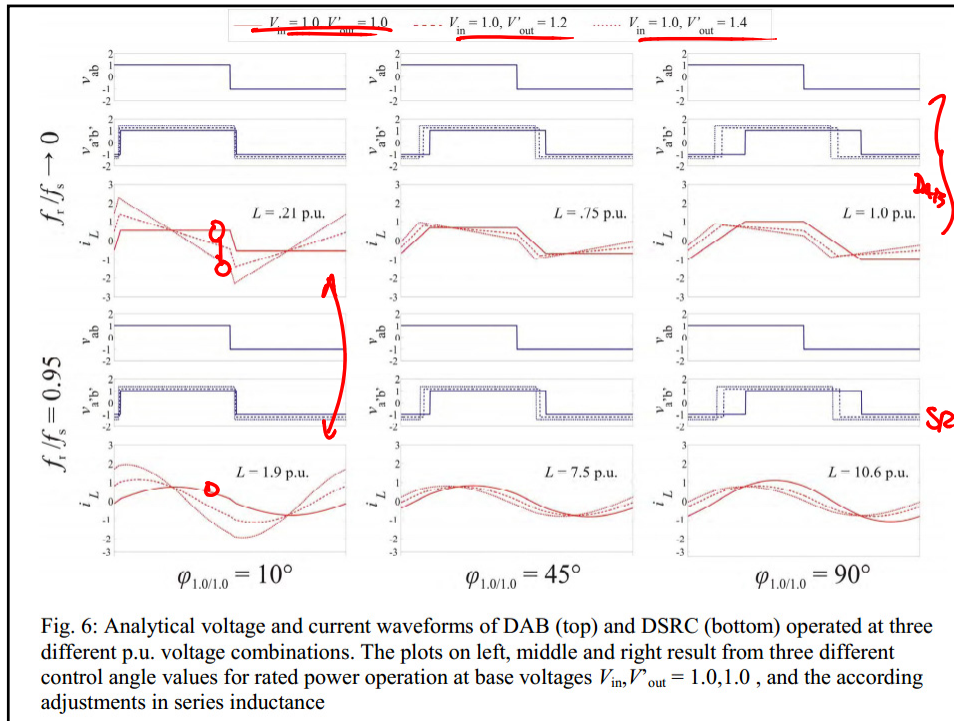


Fig. 6: Analytical voltage and current waveforms of DAB (top) and DSRC (bottom) operated at three different p.u. voltage combinations. The plots on left, middle and right result from three different control angle values for rated power operation at base voltages  $V_{in}, V'_{out} = 1.0, 1.0$ , and the according adjustments in series inductance

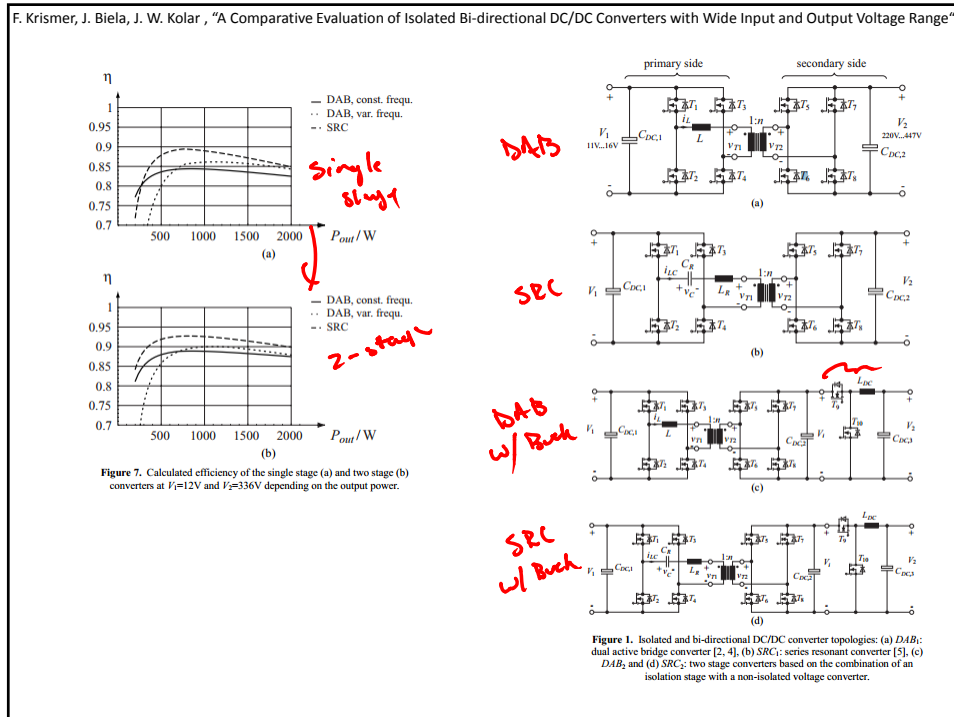


Figure 7. Calculated efficiency of the single stage (a) and two stage (b) converters at  $V_1=12V$  and  $V_2=336V$  depending on the output power.

Figure 1. Isolated and bi-directional DC/DC converter topologies: (a) DAB; dual active bridge converter [2, 4], (b) SRC; series resonant converter [5], (c) DAB; and (d) SRC; two stage converters based on the combination of an isolation stage with a non-isolated voltage converter.