


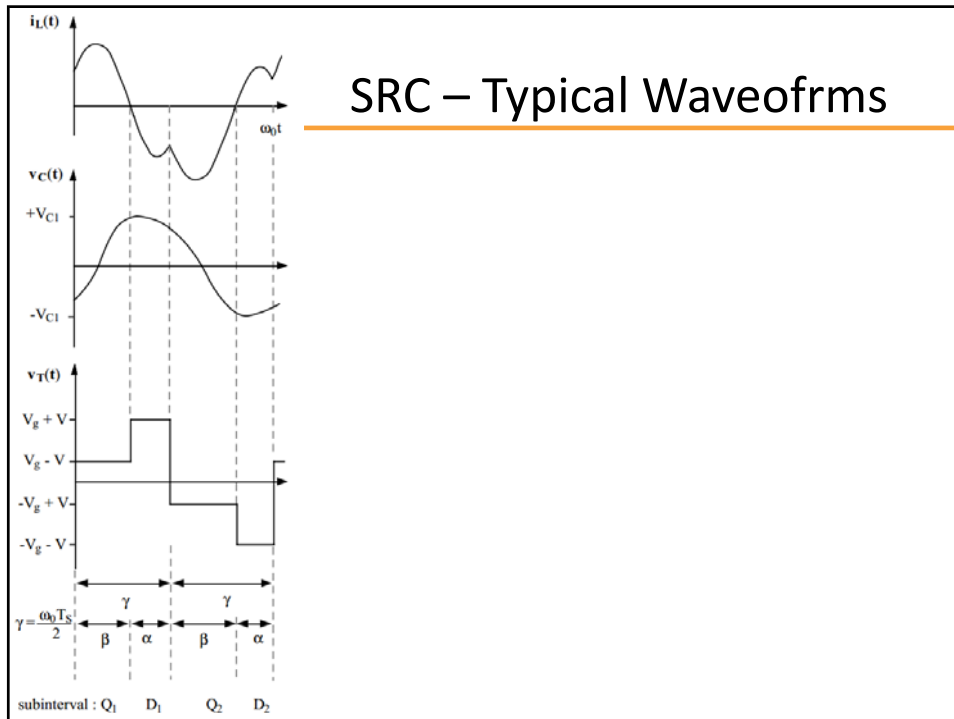


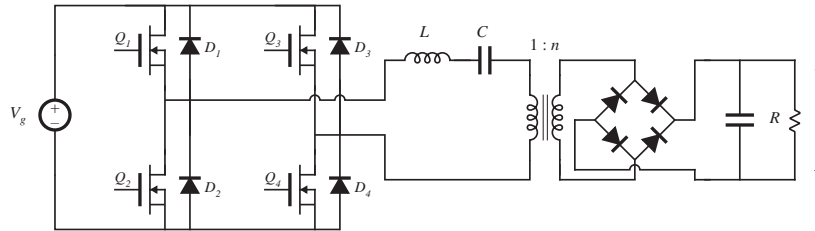

SRC: Diode Rectifier

 

 



State Plane Solution




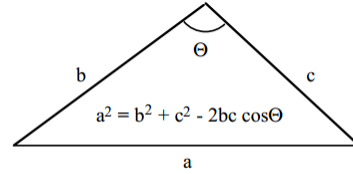


Fig. 4.14 The Law of Cosines

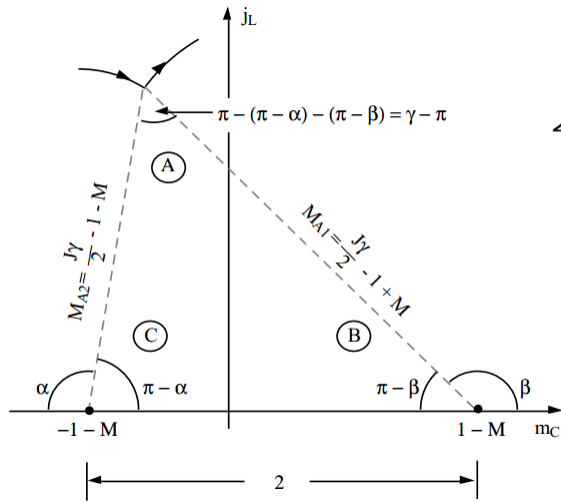


 

Elliptical Output Characteristic

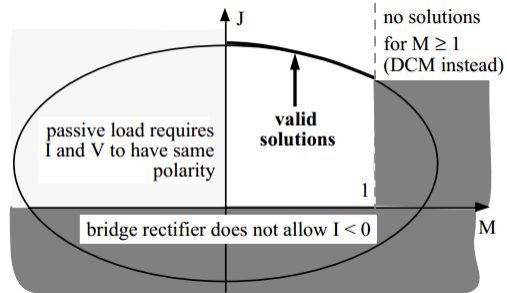

Output Plane

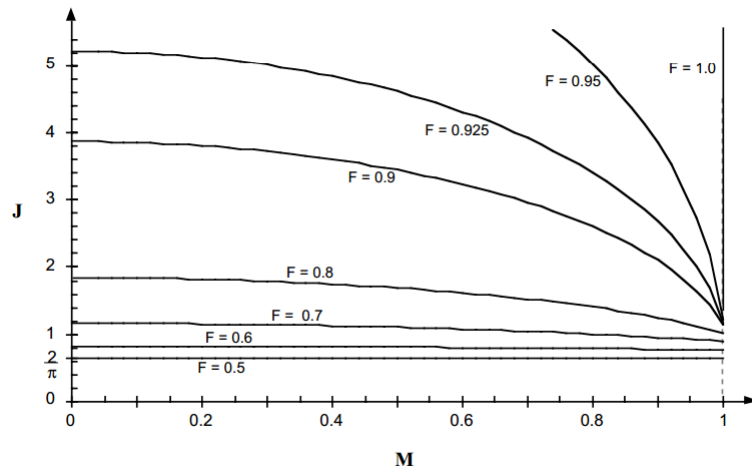



Frequency Modulation

