
 


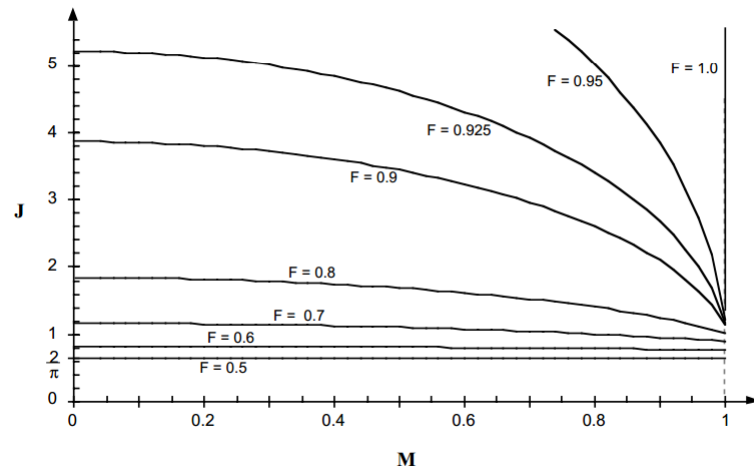


## Output Plane











# Frequency Modulation

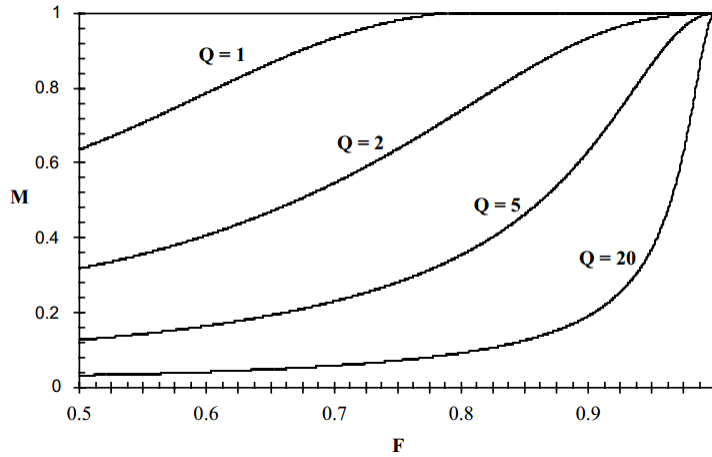

# Issues with $k=1$ CCM

$M = \frac{1}{2}$   
 $F = 0.69$

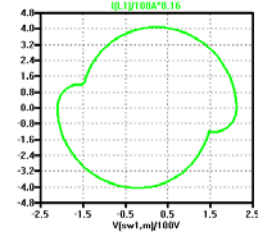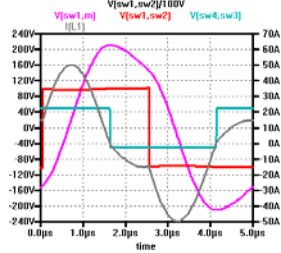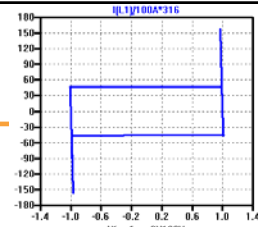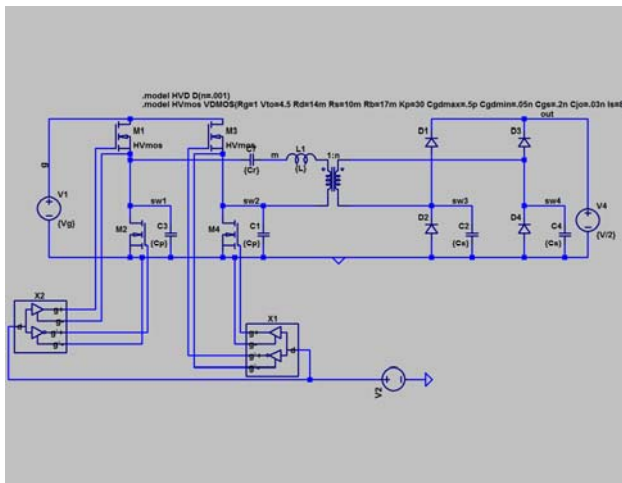


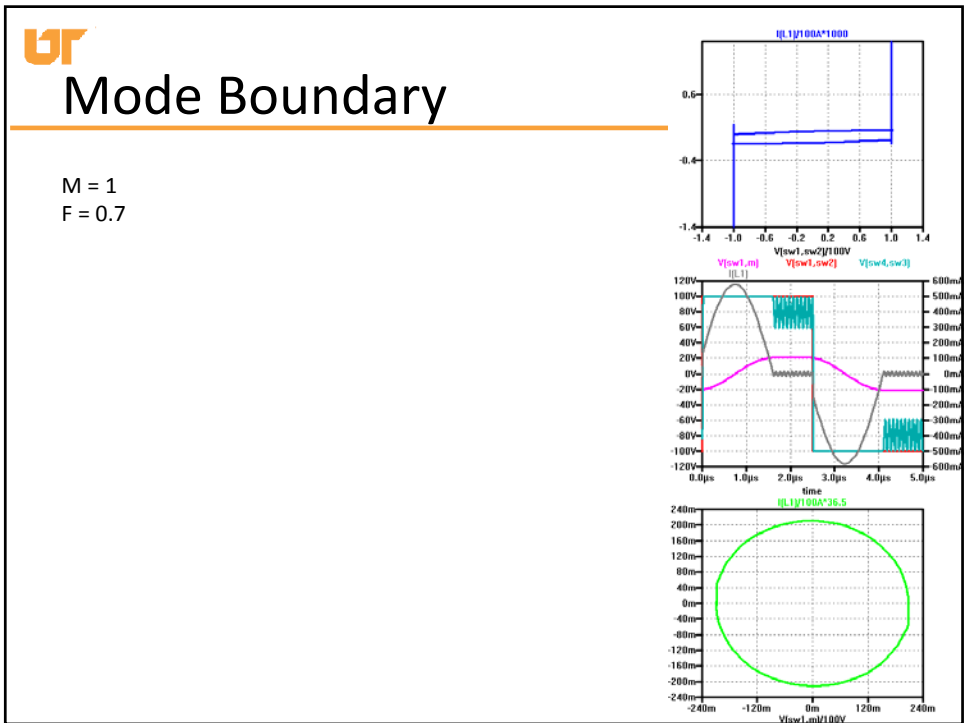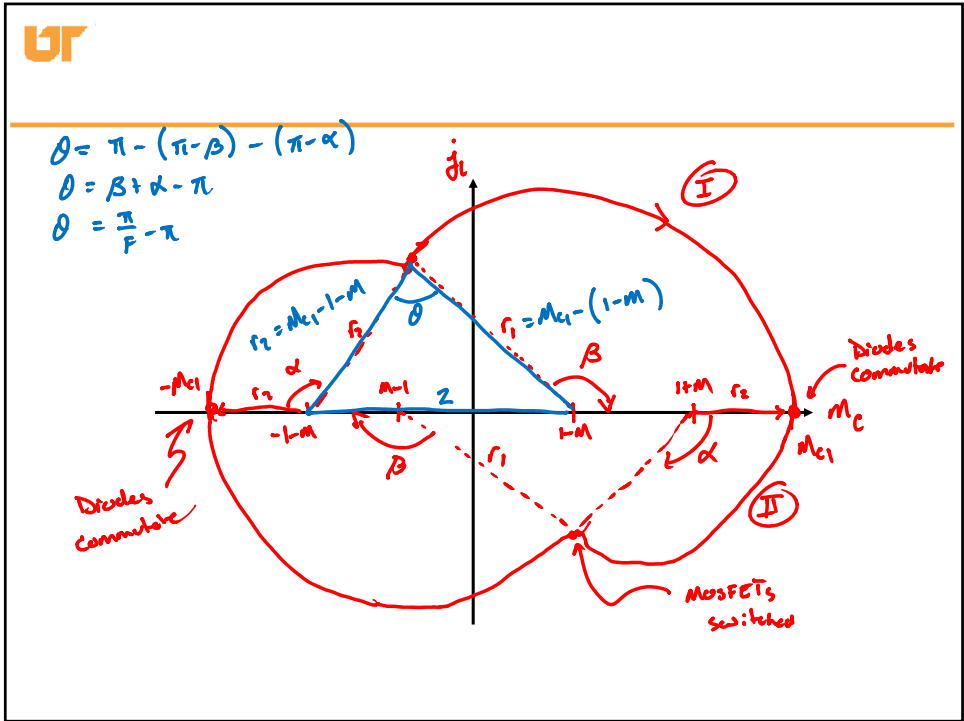




# Mode Boundary



$M = \frac{1}{2}$   
 $F = \frac{1}{2}$

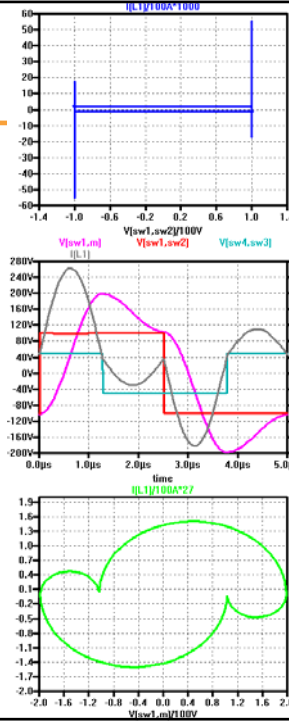

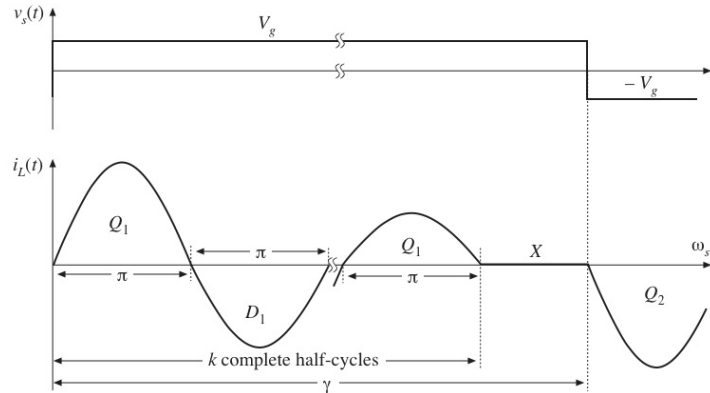
# Discontinuous Conduction Modes

• In the “type  $k$ ” discontinuous conduction mode, the tank rings through  $k$  complete half cycles during each half switching period. The output diode rectifiers then become reverse-biased, and remain off until the input bridge transistors switch to initiate the next half switching period.



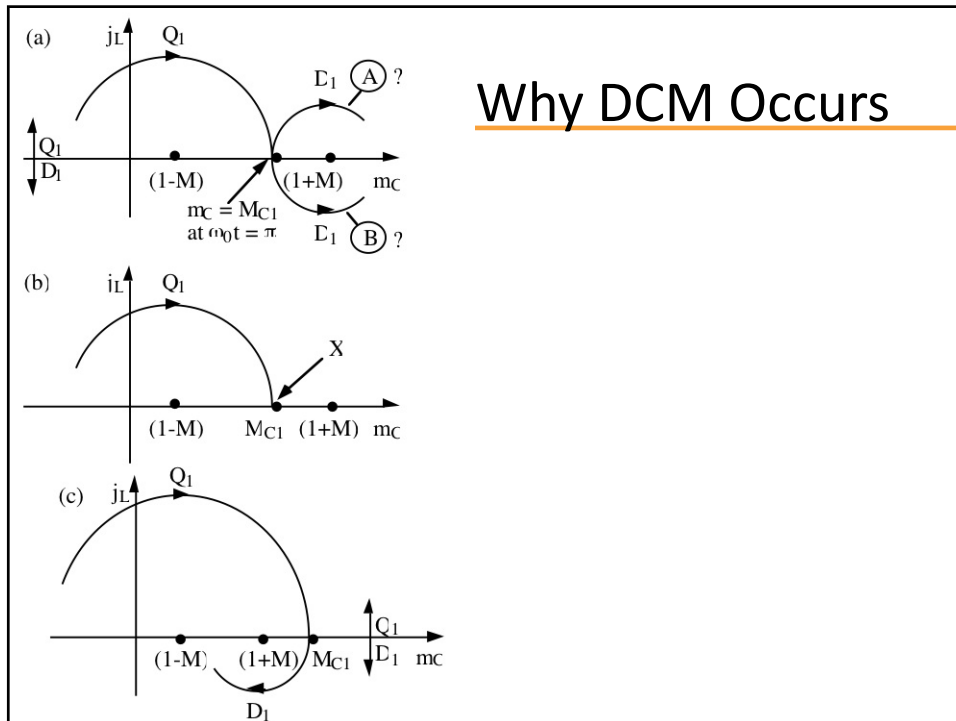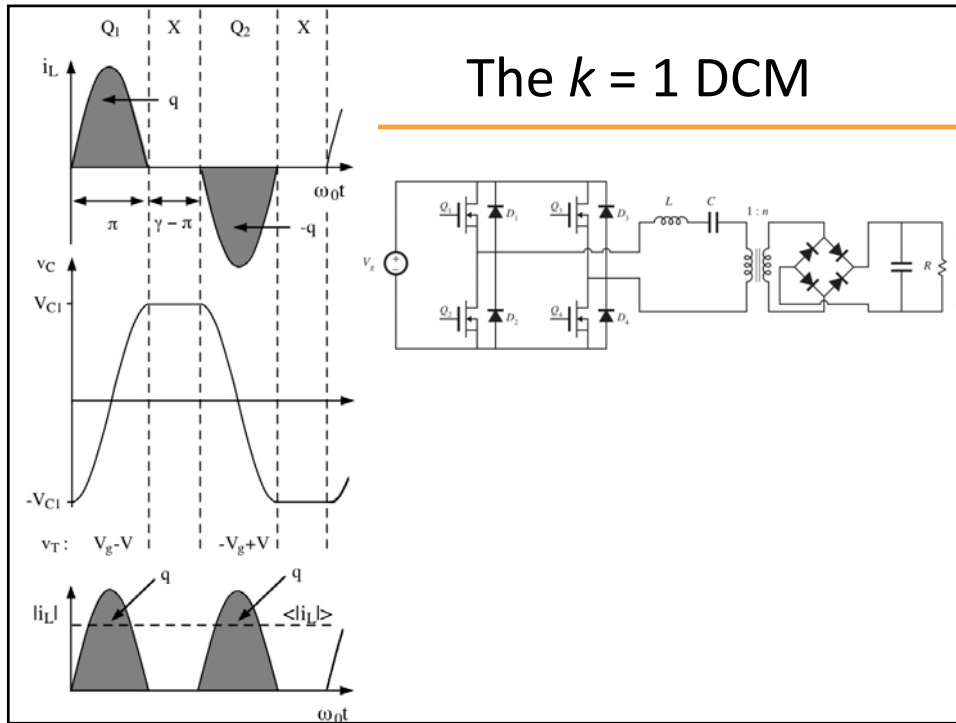

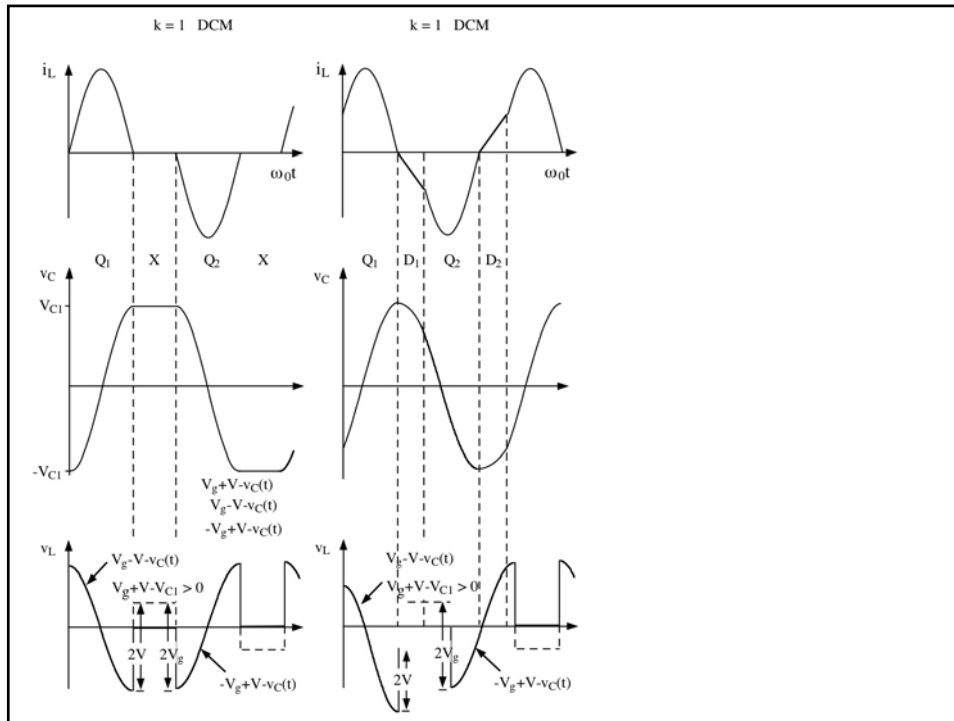

## Summary of results $k = 1$ DCM

