




## Quasi-Resonant Converters

*Doesn't use state plane analysis*

- Introduction
- 20.1 The zero-current-switching quasi-resonant switch cell
  - 20.1.1 Waveforms of the half-wave ZCS quasi-resonant switch cell
  - 20.1.2 The average terminal waveforms
  - 20.1.3 The full-wave ZCS quasi-resonant switch cell
- 20.2 Resonant switch topologies
  - 20.2.1 The zero-voltage-switching quasi-resonant switch
  - 20.2.2 The zero-voltage-switching multiresonant switch
  - 20.2.3 Quasi-square-wave resonant switches
- 20.3 Ac modeling of quasi-resonant converters
- 20.4 Summary of key points



## A quasi-square-wave ZVS buck

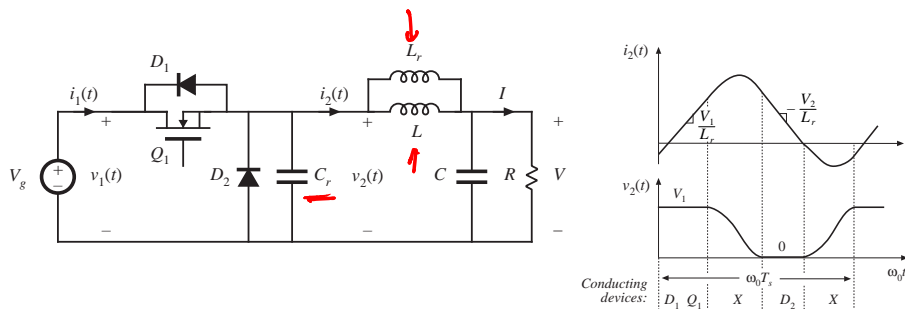


- Peak transistor voltage is equal to peak transistor voltage of PWM cell
- Peak transistor current is increased
- Zero-voltage switching in all semiconductor devices


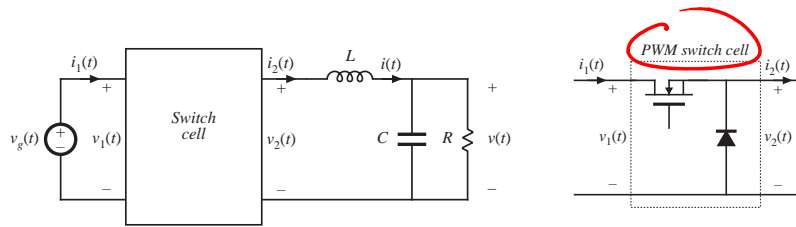
# The resonant switch concept


- A quite general idea:
  1. PWM switch network is replaced by a resonant switch network
  2. This leads to a quasi-resonant version of the original PWM converter




Example: realization of the switch cell in the buck converter



# Two quasi-resonant switch cells

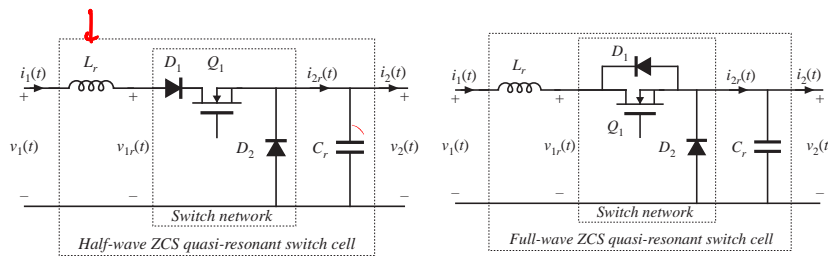

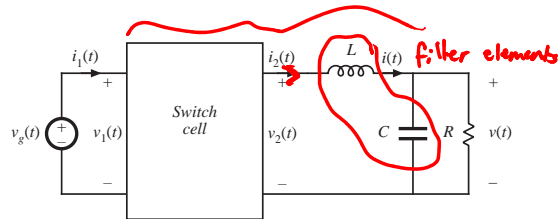Insert either of the above switch cells into the buck converter, to obtain a ZCS quasi-resonant version of the buck converter.  $L_r$  and  $C_r$  are small in value, and their resonant frequency  $f_0$  is greater than the switching frequency  $f_s$ .





## 20.1 The zero-current-switching quasi-resonant switch cell

Tank inductor  $L_r$  in series with transistor: transistor switches at zero crossings of inductor current waveform



Tank capacitor  $C_r$  in parallel with diode  $D_2$ : diode switches at zero crossings of capacitor voltage waveform

Two-quadrant switch is required:

*Half-wave:*  $Q_1$  and  $D_1$  in series, transistor turns off at first zero crossing of current waveform

*Full-wave:*  $Q_1$  and  $D_1$  in parallel, transistor turns off at second zero crossing of current waveform

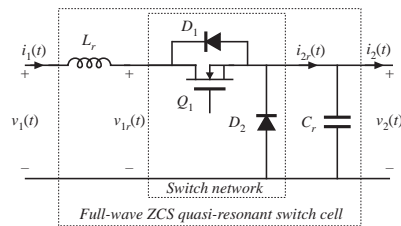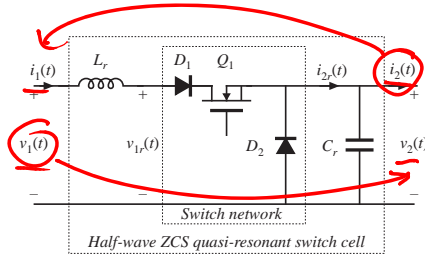Performances of half-wave and full-wave cells differ significantly.





## The switch conversion ratio $\mu$

A generalization of the duty cycle  $d(t)$

The switch conversion ratio  $\mu$  is the ratio of the average terminal voltages of the switch network. It can be applied to non-PWM switch networks. For the CCM PWM case,  $\mu = d$ .

If  $V/V_g = M(d)$  for a PWM CCM converter, then  $V/V_g = M(\mu)$  for the same converter with a switch network having conversion ratio  $\mu$ .

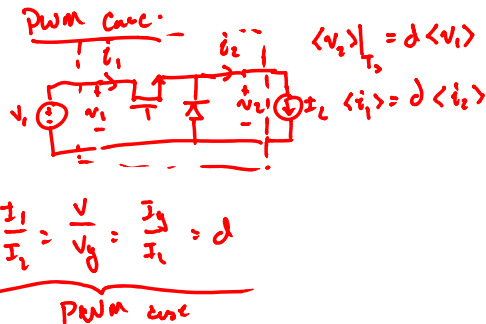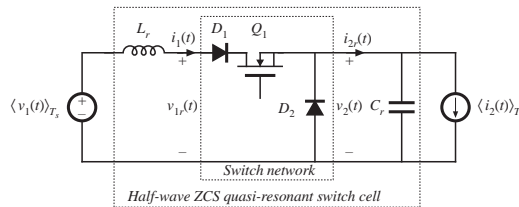
Generalized switch averaging, and  $\mu$ , are defined and discussed in Section 10.3.






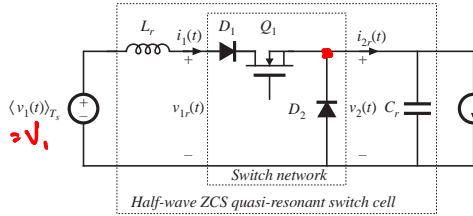
## 20.1.1 Waveforms of the half-wave ZCS quasi-resonant switch cell

The half-wave ZCS quasi-resonant switch cell, driven by the terminal quantities  $\langle v_1(t) \rangle_{T_S}$  and  $\langle i_2(t) \rangle_{T_S}$ .



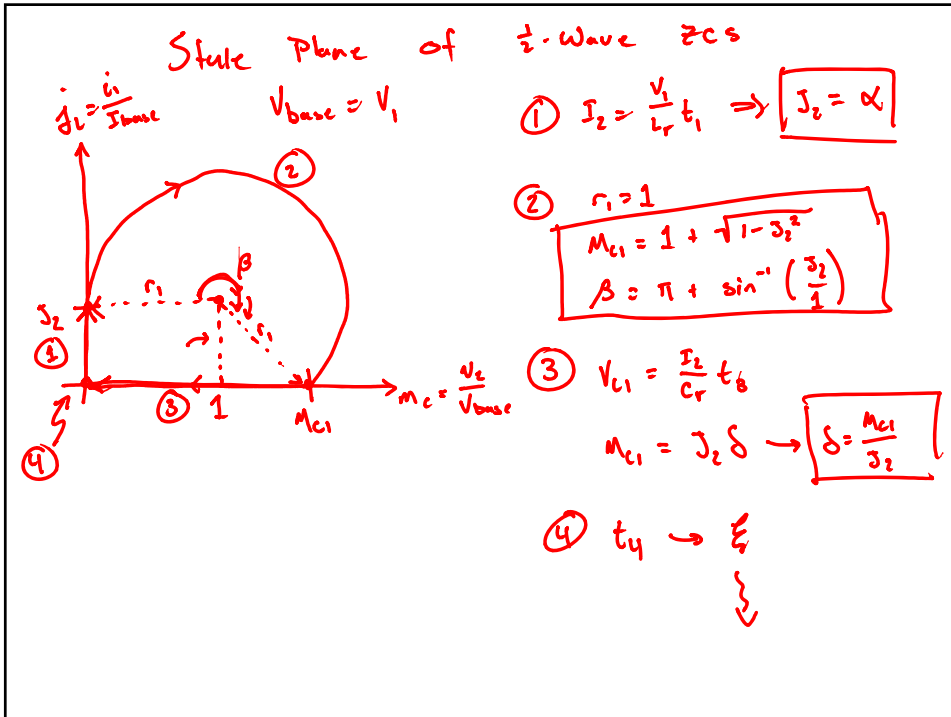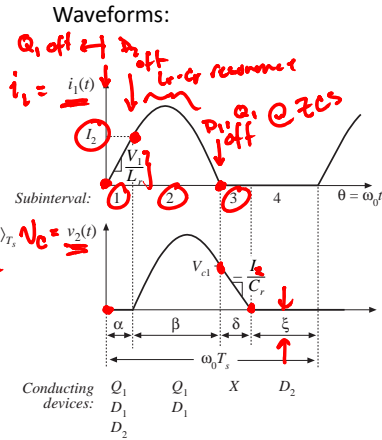Each switching period contains four subintervals





## Boundary of zero current switching

$$T_s = t_1 + t_2 + t_3 + t_4$$

$$\frac{2\pi}{F} = \alpha + \beta + \delta + \xi$$

What is needed to obtain ZCS?

① enough time

② Large enough  $r_s$

From ref level

(20.21)

②  $\beta_2 < 1 \rightarrow$

$$I_2 < \frac{V_1}{R_0}$$

①  $\xi \geq \phi$

$$\rightarrow \frac{2\pi}{F} \geq \alpha + \beta + \delta$$

(20.31)

$$\frac{2\pi}{F} \geq \beta_2 + \pi + \sin^{-1}(\beta_2) + \frac{1 + \sqrt{1 - \beta_2^2}}{\beta_2}$$



## 20.1.2 The average terminal Waveforms



Averaged switch modeling: we need to determine the average values of  $i_1(t)$  and  $v_2(t)$ .

$$\langle i_1 \rangle = \frac{1}{T_s} [\beta_1 + \beta_2]$$

$$\beta_1 = \frac{1}{2} \frac{\alpha}{\omega_0} I_2$$



$$\beta_2 = \underbrace{C_r V_{c1}}_{\beta_{2a}} + \underbrace{I_2 t_2}_{\beta_{2b}}$$
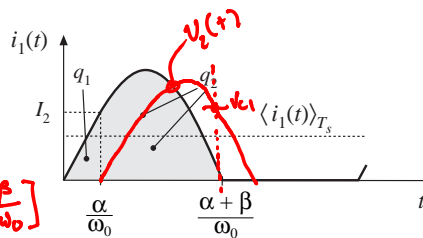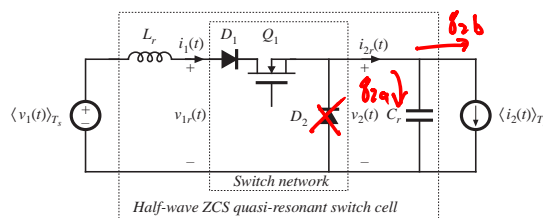
$$\langle i_1 \rangle = \frac{1}{T_s} \left[ \frac{1}{2} \frac{\alpha}{\omega_0} I_2 + C_r V_{c1} + I_2 \frac{\beta}{\omega_0} \right]$$




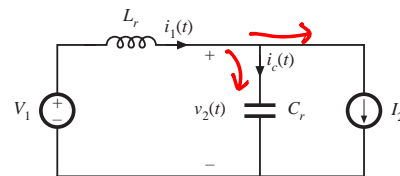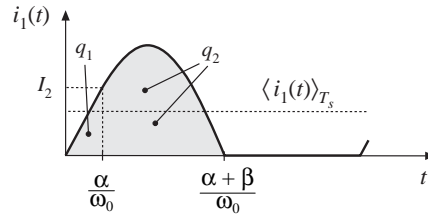
## Charge arguments: computation of $q_2$



Circuit during subinterval 2



## Switch conversion ratio $\mu$

$$\langle i_1 \rangle = \frac{1}{T_s} \left[ \frac{1}{2} \frac{\alpha}{\omega_0} I_2 + C_r V_{c1} + \frac{\beta}{\omega_0} I_2 \right]$$

$$\mu = \frac{\langle i_1 \rangle}{I_2} = \frac{1}{T_s} \left[ \frac{1}{2} \frac{\alpha}{\omega_0} + \frac{C_r V_{c1}}{I_2} \left( \frac{\omega_0}{\omega_0} \right) + \frac{\beta}{\omega_0} \right]$$

$$\mu = \frac{F}{2\pi} \left[ \frac{\alpha}{2} + \beta + \frac{\mu_{c1}}{\mathcal{J}_2} \right]$$

$$\mu = F \frac{1}{2\pi} \left[ \frac{\mathcal{J}_2}{2} + \pi + \sin^{-1}(\mathcal{J}_2) + \frac{\sqrt{1-\mathcal{J}_2^2} + 1}{\mathcal{J}_2} \right]$$

$$\mu = F P_{1/2}(\mathcal{J}_2) + P_h(\mathcal{J}_2)$$

↑ from book  
(20.43)