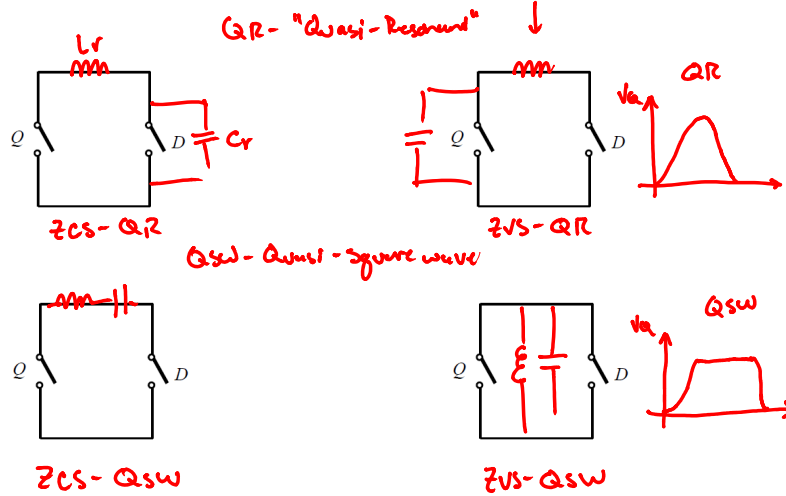






Classification of Resonant-Switch Converters



ZVS-QR

Converter examples

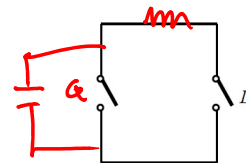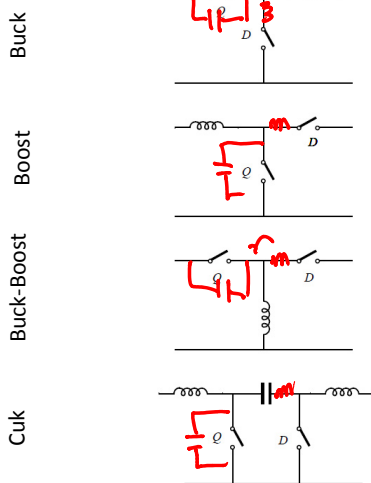High-frequency view of the switch network






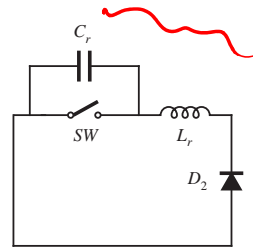
20.3.1 The zero-voltage-switching quasi-resonant switch cell

ZVS-QR

When the previously-described operations are followed, then the converter reduces to



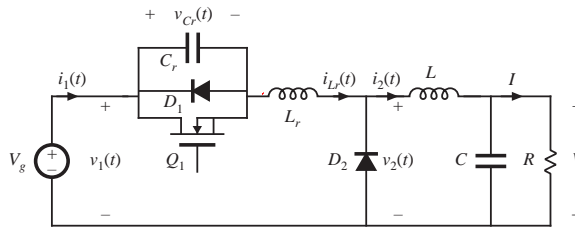A full-wave version based on the PWM buck converter:



ZVS-QR

$$J_s \geq J_s \geq J_T$$

Switch conversion ratio

$$\mu = 1 - FP_{\frac{1}{2}} \left(\frac{1}{J_s} \right) \quad \text{half-wave}$$

$$\mu = 1 - FP_1 \left(\frac{1}{J_s} \right) \quad \text{full-wave}$$


ZVS boundary

$$J_s \geq 1$$

$$\text{peak transistor voltage } V_{cr, pk} = (1 + J_s) V_1$$

A problem with the quasi-resonant ZVS switch cell: peak transistor voltage becomes very large when zero voltage switching is required for a large range of load currents.



Tank waveforms

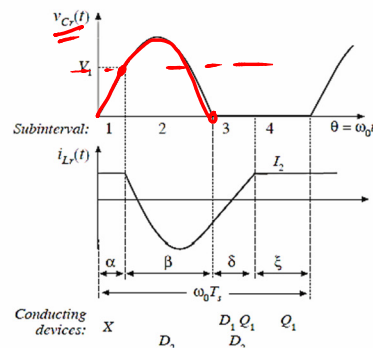



ZVS-QR State Plane Trajectory

normalized phase plane:

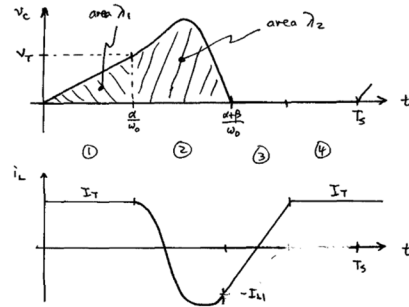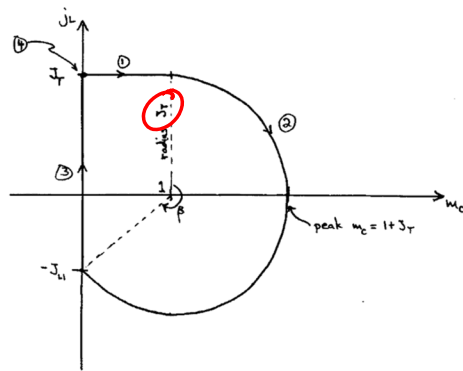

The average output voltage

Average output voltage:

$$\langle m_s \rangle = 1 - \langle m_c \rangle$$

$$\langle v_s \rangle = \mu V_T \quad \text{with} \quad \mu = 1 - F_P(J_T)$$

$$P = \frac{1}{2\pi} \left[\frac{1}{2} \frac{1}{J_T} + \pi + \sin^{-1} \frac{1}{J_T} + J_T + \sqrt{J_T^2 - 1} \right]$$

$$\text{type b } P(J_T) = \text{type a } P\left(\frac{1}{J_T}\right)$$

$$\begin{bmatrix} \langle v_s \rangle \\ \langle i_s \rangle \end{bmatrix} = \mu \begin{bmatrix} V_T \\ I_T \end{bmatrix}$$

$$\underline{x}_S = \mu \underline{x}_T$$




dc transformer
 μ controlled by F , but
 also depends on
 V_T and I_T

UT Results: Quasi-resonant switches

	Switch	μ	$P(J_T)$	load current range	voltage conversion range
	<u> PWM</u>	D	—	nearly infinite	$0 \leq \mu \leq 1$
"type a" 2CS	→ type a 1/2 wave	$F P(\frac{J_T})$	$k_2(J_T)$	$0 \leq J_T \leq 1$	$0 \leq \mu \leq 1$
"type b" 2VS	type a full wave	$FP \approx F$	$k_1(J_T) \approx 1$	$0 \leq J_T \leq 1$	$0 \leq \mu \leq 1$
	type b 1/2 wave	$1-FP(J_T)$	$k_2(\frac{1}{J_T})$	$1 \leq J_T \leq \infty$	$0 \leq \mu \leq 1$
$J_T \equiv J_T$	type b full wave	$1-FP \approx 1-F$	$k_1(\frac{1}{J_T}) \approx 1$	$1 \leq J_T \leq \infty$	$0 \leq \mu \leq 1$

with $k_2(x) = \frac{1}{2\pi} \left[\frac{1}{2}x + \pi + \sin^{-1}x + \frac{1}{x} (1 + \sqrt{1-x^2}) \right]$

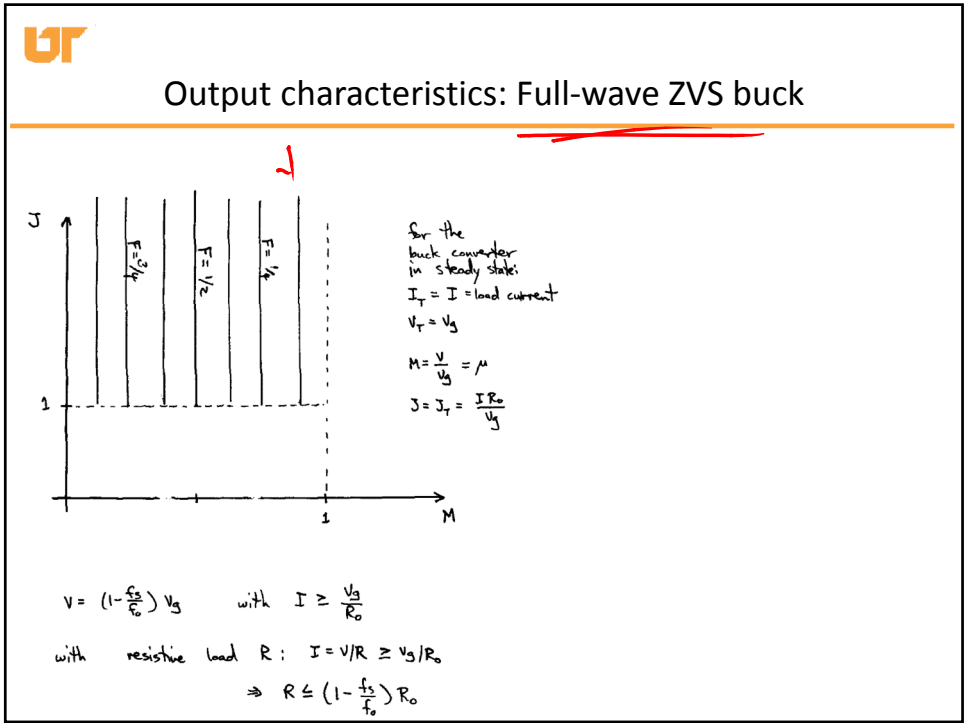
$k_1(x) = \frac{1}{2\pi} \left[\frac{1}{2}x + 2\pi - \sin^{-1}x + \frac{1}{x} (1 - \sqrt{1-x^2}) \right]$






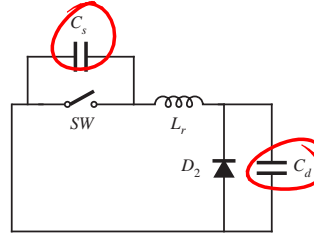20.3.2 The ZVS multiresonant switch

When the previously-described operations are followed, then the converter reduces to



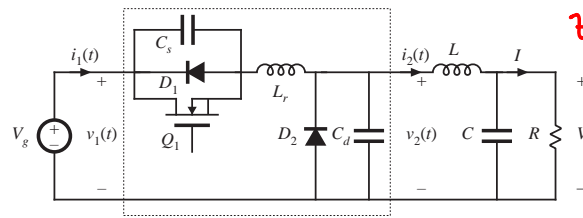A half-wave version based on the PWM buck converter:



ZVS-MR Operating Modes

D Maksimovic, "Synthesis of PWM and Quasi-Resonant DC-to-DC Power Converters," Ph.D. thesis, California Institute of Technology, 1989.

- ① $I = i_{r0} + \frac{V}{L_r} t_1$
- ② $i_{r2} = I + \frac{V}{R_d} \sin(\omega_s t_2)$
 $v_{d2} = V_d (1 - \cos(\omega_s t_2))$
 $\omega_s = \frac{1}{\sqrt{L_r C_d}}$, $R_d = \sqrt{\frac{L_r}{C_d}}$
- ③ $v_{d3} = I R_o \omega_s t_3 - k v_{d2}$
 $\omega_s t_3 = \pi + \tan^{-1} \left(\frac{V_d - V_{d2}}{i_{r2} R_o - I R_o / (1+k)} \right) + \tan^{-1} \left(\frac{V_d - V_{d3}}{i_{r3} R_o + I R_o / (1+k)} \right)$
 $(V_d - V_{d2})^2 + (i_{r2} R_o - I R_o / (1+k))^2 = (V_d - V_{d3})^2 + (i_{r3} R_o + I R_o / (1+k))^2$
 with $R_o = \sqrt{\frac{L_r}{C_d (1+k)}}$, $k = \frac{C_d}{C_t}$, $\omega_s = \frac{1}{\sqrt{L_r (C_d (1+k))}}$
- ④ $(V_d - V_{d3})^2 + (i_{r3} R_t)^2 = V_d^2 + (i_{r0} R_t)^2$
 $\omega_s t_4 = \tan^{-1} \left(\frac{-i_{r3} R_t}{V_d - V_{d3}} \right) - \tan^{-1} \left(\frac{-i_{r0} R_t}{V_d} \right)$
 with $\omega_s = \frac{1}{\sqrt{L_r C_t}}$, $R_t = \sqrt{\frac{L_r}{C_t}}$

averaging

$$\mu = \frac{t_2}{T_s} - \frac{L_r i_{r2}}{V_d T_s} + \frac{L_r I}{V_d T_s} + \frac{t_3}{(1+k) T_s} + \frac{L_r (i_{r2} - i_{r3})}{(1+k) V_d T_s} + \frac{R}{1+k} \frac{\omega_s t_3}{V_d T_s} - \frac{I t_3^2}{(1+k) \cdot 2 C_t V_d T_s}$$


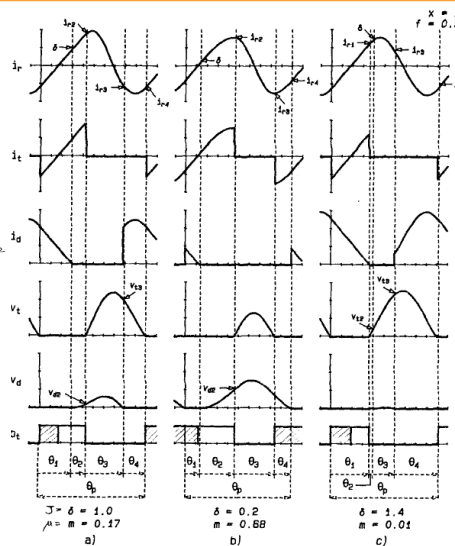


Figure 10.2: Typical waveforms for a ZV-MR converter operating in modes I₁, II₁, III₁. (a)

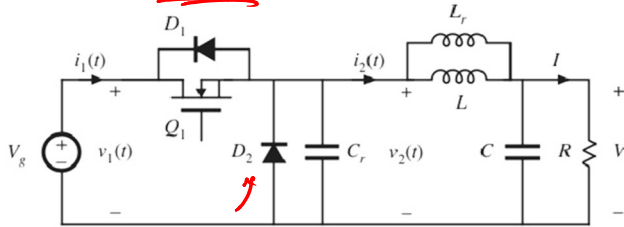


ZVS QSW Converters: Already Studied


Original one-switch version



Add synchronous rectifier


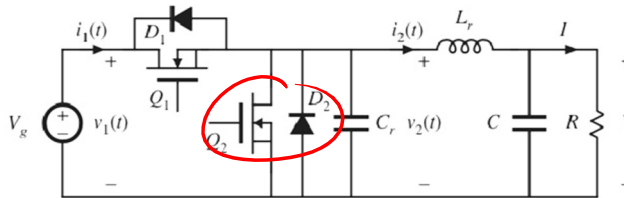


Lecture 21

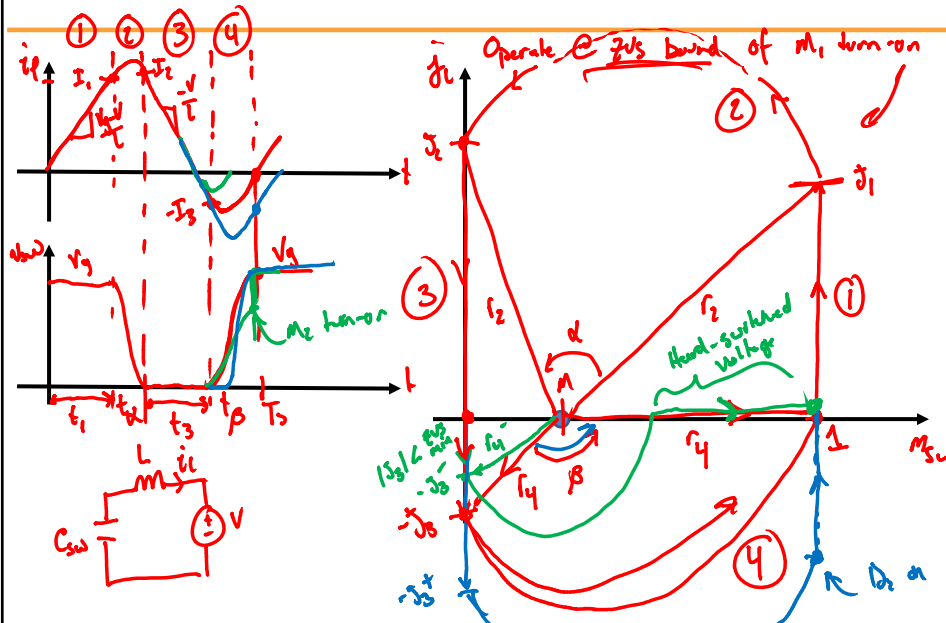


UF 20.2.3 Quasi-square-wave resonant switches

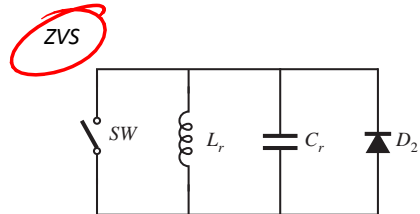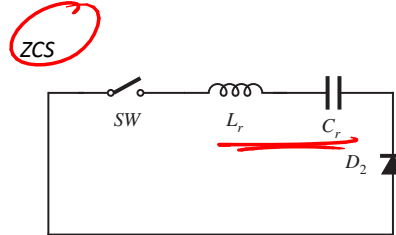When the previously-described operations are followed, then the converter reduces to



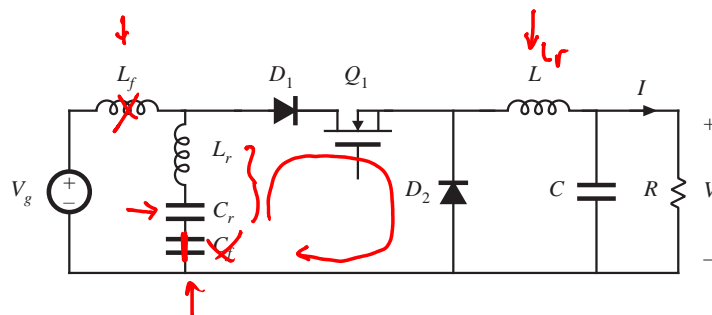UF A quasi-square-wave ZCS buck with input filter



- The basic ZCS QSW switch cell is restricted to $0 \leq \mu \leq 0.5$
- Peak transistor current is equal to peak transistor current of PWM cell
- Peak transistor voltage is increased
- Zero-current switching in all semiconductor devices




Ac modeling of quasi-resonant converters

Use averaged switch modeling technique: apply averaged PWM model, with d replaced by μ



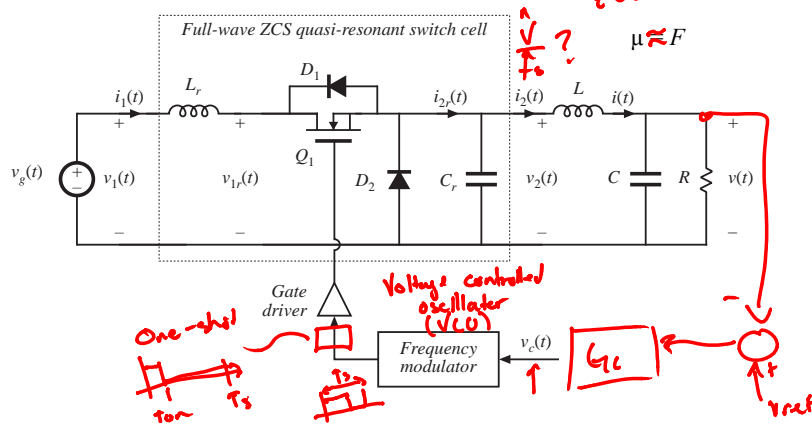Buck example with full-wave ZCS quasi-resonant cell:



Ac modeling of QR converters

Quasi-resonant converters inherit properties of PWM parents, with switch conversion ratio μ playing the role of the PWM switch duty cycle d

AC modeling approach:

- Start from $\mu(v, i, f_s)$ found for the resonant switch
- Perturb and linearize

$$\hat{\mu} = \frac{\partial \mu}{\partial v} \Big|_{\hat{v}} + \frac{\partial \mu}{\partial i} \Big|_{\hat{i}} + \frac{\partial \mu}{\partial f_s} \Big|_{\hat{f}_s}$$


\nearrow dc op. pt.
 \nearrow dc op.
 \nearrow dc op. pt.

- Replace d with μ in the small-signal AC dynamic model of the PWM parent converter

$$\hat{d} \rightarrow \hat{\mu}$$



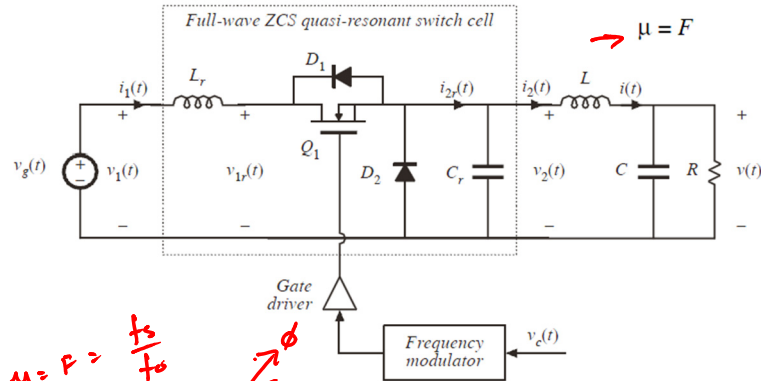
Example 1: Half-wave ZCS quasi-resonant buck




$\mu = F = \frac{f_s}{f_0}$
 $\hat{\mu} = \frac{\partial \mu}{\partial f_s} \Big|_{f_0} \hat{f}_s + \dots$
 $\hat{\mu} = \frac{1}{f_0} \hat{f}_s$ → replace d in normal PWM SSM



Buck Converter Small Signal Model

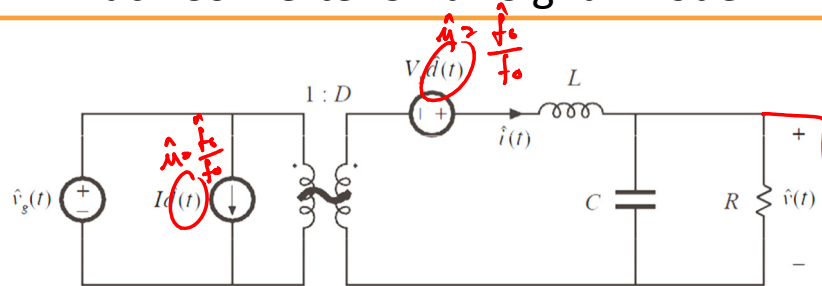


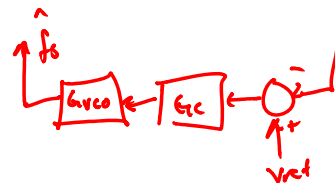Averaged SSM model by:
 { waveform averaging
 state space averaging
 switch averaging






ZVS-QR buck AC model

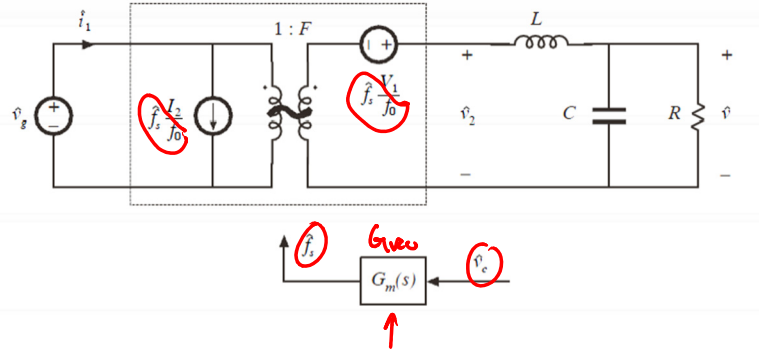

Example 2: Half-wave ZCS-QR buck

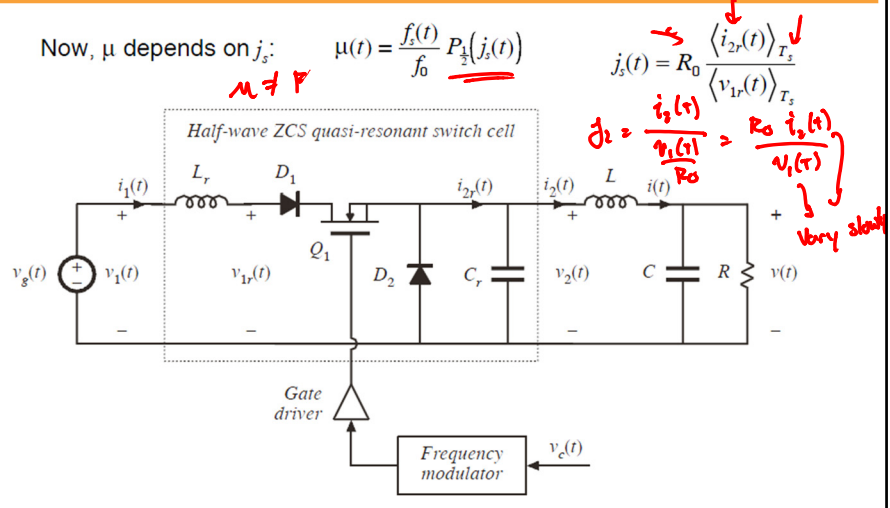



Perturb and Linearize

Perturbation and linearization of $\mu(v_{1r}, i_{2r}, f_s)$:

$$\hat{\mu}(t) = K_v \hat{v}_{1r}(t) + K_i \hat{i}_{2r}(t) + K_c \hat{f}_s(t)$$

with

$$K_v = -\frac{\partial \mu}{\partial j_s} \frac{R_0 L_2}{V_1^2}$$

$$K_i = -\frac{\partial \mu}{\partial j_s} \frac{R_0}{V_1}$$


$$K_c = \frac{\mu_0}{F_s}$$

$$\frac{\partial \mu}{\partial j_s} = \frac{F_s}{2\pi f_0} \left(\frac{1}{2} - \frac{1 + \sqrt{1 - J_s^2}}{J_s^2} \right)$$

$$K_v = \left. \frac{\partial \mu}{\partial v} \right|_{v=v} = \frac{\partial \mu}{\partial i_2} \frac{\partial i_2}{\partial n_1} = \frac{\partial \mu}{\partial j_s} \cdot \left(-R_0 \frac{F_s}{V_1^2} \right)$$



AC SSM of half-wave ZCS-QR buck

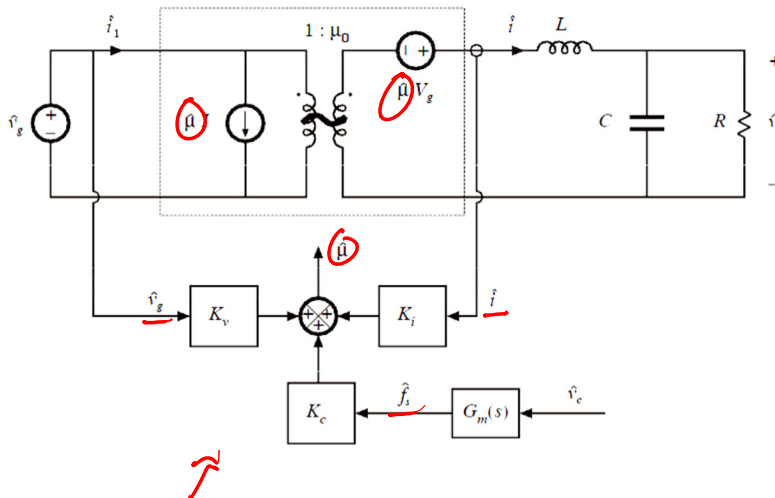



$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{1}{Q} \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

$$G_{vc}(s) = G_{c0} \frac{1}{1 + \frac{1}{Q} \frac{s}{\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Full-wave: poles and zeroes are same as PWM

Half-wave: effective feedback reduces Q-factor and dc gains

$$G_{g0} = \frac{\mu_0 + K_v V_g}{1 + \frac{K_i V_g}{R}}$$

$$G_{c0} = \frac{K_c V_g}{1 + \frac{K_i V_g}{R}}$$

$$\omega_0 = \sqrt{\frac{1 + \frac{K_i V_g}{R}}{L_r C_r}}$$

$$Q = \frac{\sqrt{1 + \frac{K_i V_g}{R}}}{\frac{R_0}{R} + K_i V_g \frac{R}{R_0}}$$

$$R_0 = \sqrt{\frac{L_r}{C_r}}$$



Summary of results

Switch	μ_0	$\frac{\partial \mu}{\partial J_r}$	K_i	K_v	K_c
PWM	D	0	0	0	$K_d = 1$
ZCS HW	$\frac{F}{2\pi} \left(\frac{J_r}{2} + \pi \sin^{-1} \left(\frac{J_r}{J_r} \right) + \frac{1}{J_r} (1 + \sqrt{1 - J_r^2}) \right)$	$\frac{\partial \mu}{\partial J_r} = \frac{F}{2\pi} \left(\frac{1}{2} \frac{(1 + \sqrt{1 - J_r^2})}{J_r^2} \right)$	$\frac{\partial \mu}{\partial J_r} \frac{R_0}{V_{T0}}$	$-\frac{\partial \mu}{\partial J_r} \frac{R_0 I_{T0}}{V_{T0}^2}$	$K_f = \frac{\mu_0}{F_{d0}}$
ZCS FW	$\frac{F}{2\pi} \left(\frac{J_r}{2} + 2\pi \sin^{-1} \left(\frac{J_r}{J_r} \right) + \frac{1}{J_r} (1 - \sqrt{1 - J_r^2}) \right)$	$\frac{\partial \mu}{\partial J_r} = \frac{F}{2\pi} \left(\frac{1}{2} \frac{(1 - \sqrt{1 - J_r^2})}{J_r^2} \right)$	0	0	$K_f = \frac{\mu_0}{F_{d0}}$
ZVS HW	$1 - \frac{F}{2\pi} \left(\frac{J_r}{2} + \pi \sin^{-1} \left(\frac{J_r}{J_r} \right) + J_r \left(1 + \sqrt{1 - \frac{1}{J_r^2}} \right) \right)$	$\frac{\partial \mu}{\partial J_r} = \frac{1}{J_r^2} \frac{F}{2\pi} \left(\frac{1}{2} \frac{(1 + \sqrt{1 - J_r^2})}{J_r^2} \right)$	$\frac{\partial \mu}{\partial J_r} \frac{R_0}{V_{T0}}$	$-\frac{\partial \mu}{\partial J_r} \frac{R_0 I_{T0}}{V_{T0}^2}$	$K_f = \frac{\mu_0}{F_{d0}}$
ZVS FW	$1 - \frac{F}{2\pi} \left(\frac{J_r}{2} + 2\pi \sin^{-1} \left(\frac{J_r}{J_r} \right) + J_r \left(1 - \sqrt{1 - \frac{1}{J_r^2}} \right) \right)$	$\frac{\partial \mu}{\partial J_r} = \frac{1}{J_r^2} \frac{F}{2\pi} \left(\frac{1}{2} \frac{(1 - \sqrt{1 - J_r^2})}{J_r^2} \right)$	0	0	$K_f = \frac{\mu_0}{F_{d0}}$