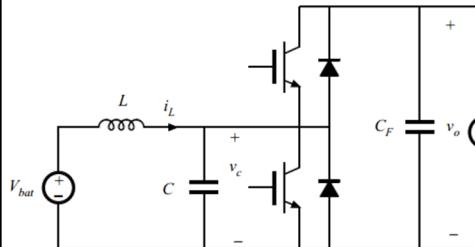




Example 3: ZVS-QSW Boost Converter



Bidirectional drivetrain boost converter in electric vehicles

- $P_o = 12.5 \text{ kW}$
- $f_s = 100 \text{ kHz}$
- $V_{bat} = 250 \text{ V}$
- $V_o = 500 \text{ V}$
- $F = 0.5$



Goals:


- Find L , C to achieve ZVS for all operating points
- Sketch small-signal model for control design
- Solve $G_{vd}(s)$





IGBT vs. MOSFET

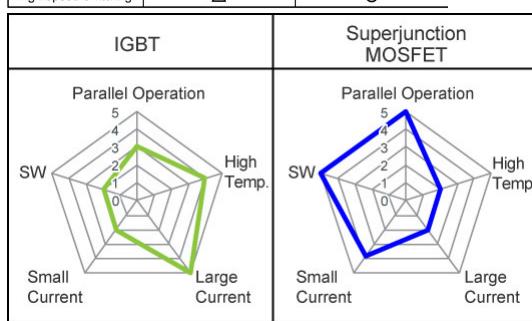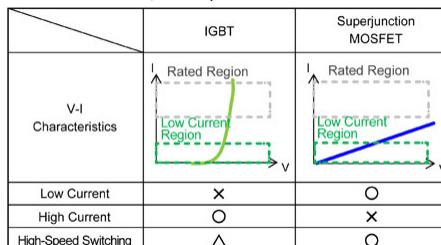Rohm, "New Hybrid MOS Combines the Best Characteristics of MOSFETs and IGBTs Improved energy savings"




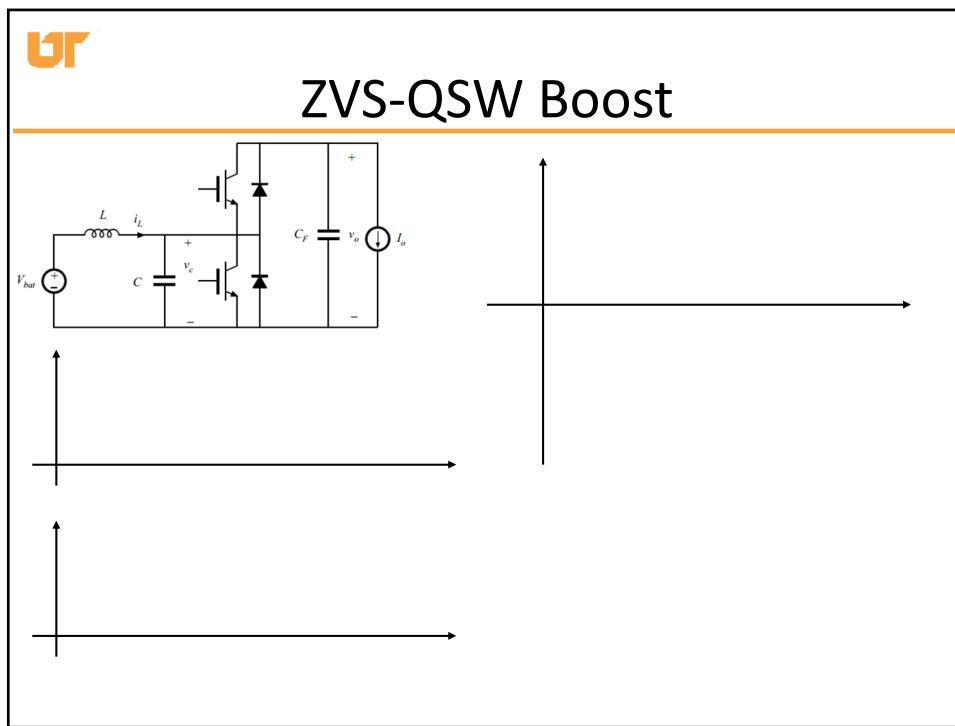

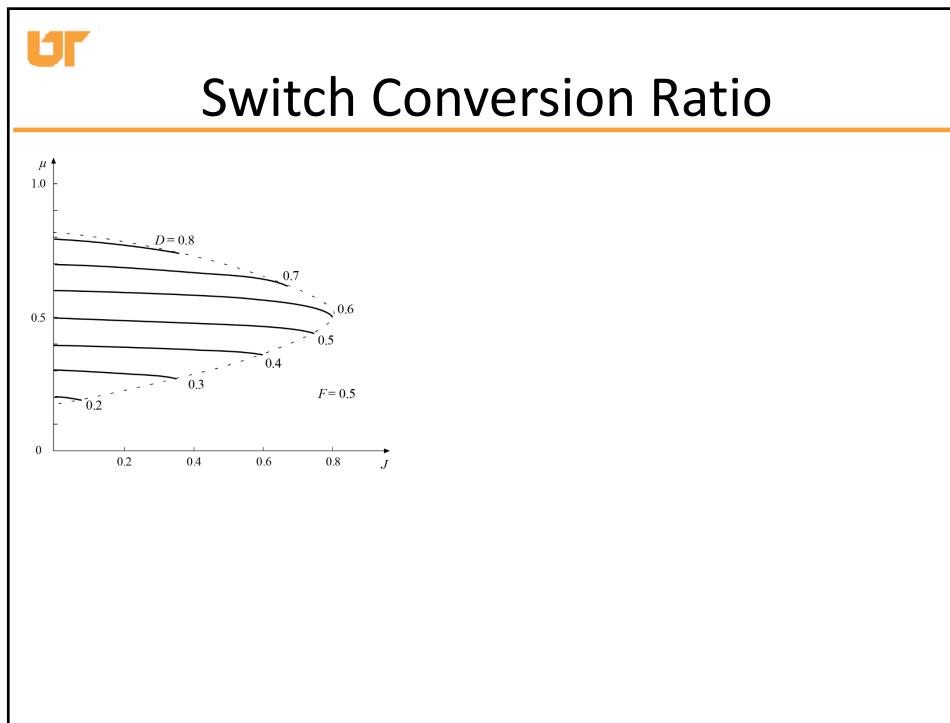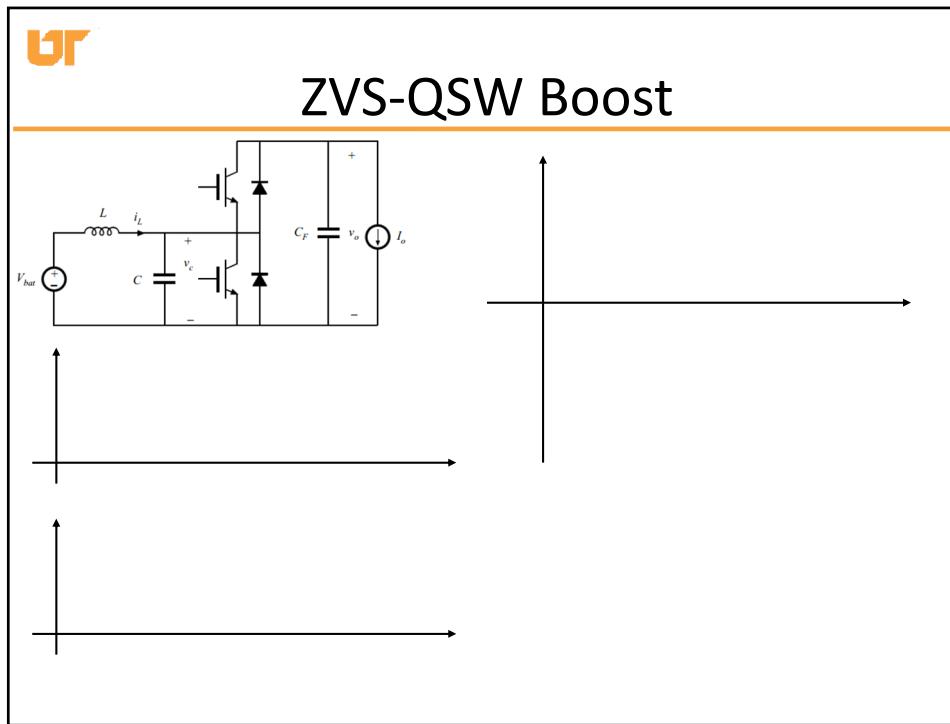



Boost SSM

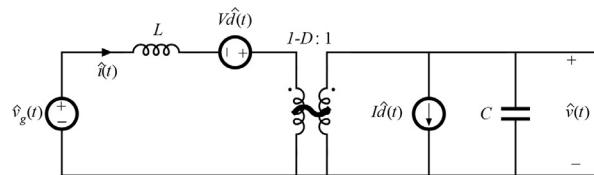

PWM Converter Transfer Functions

