




High Frequency Power Electronics

Prof. Daniel Costinett

ECE 581 Lecture 3
August 25, 2014




Device Capacitances

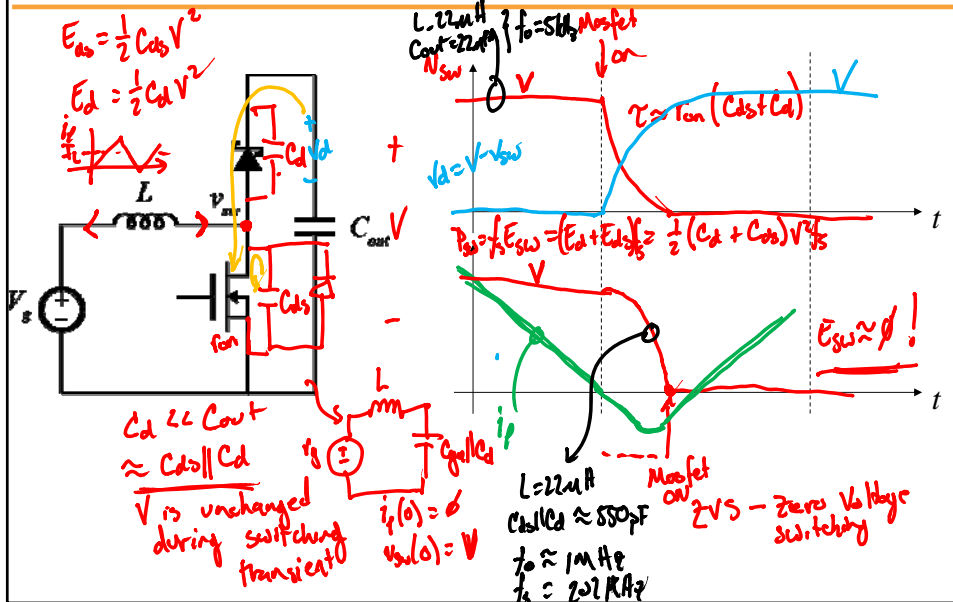





Resonant Circuits

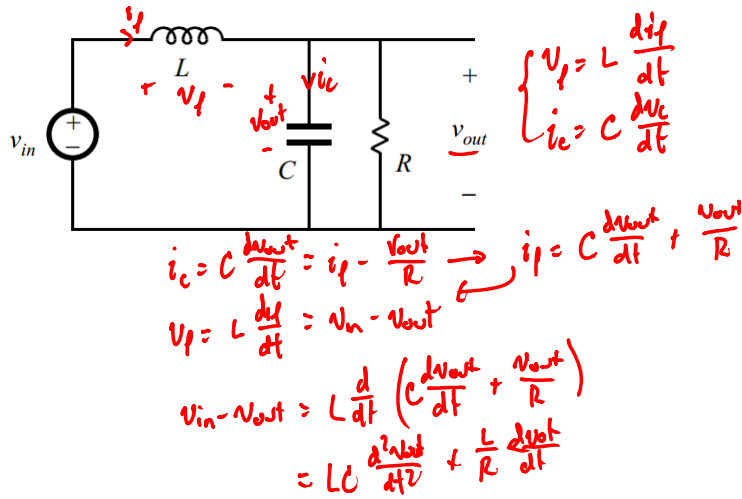

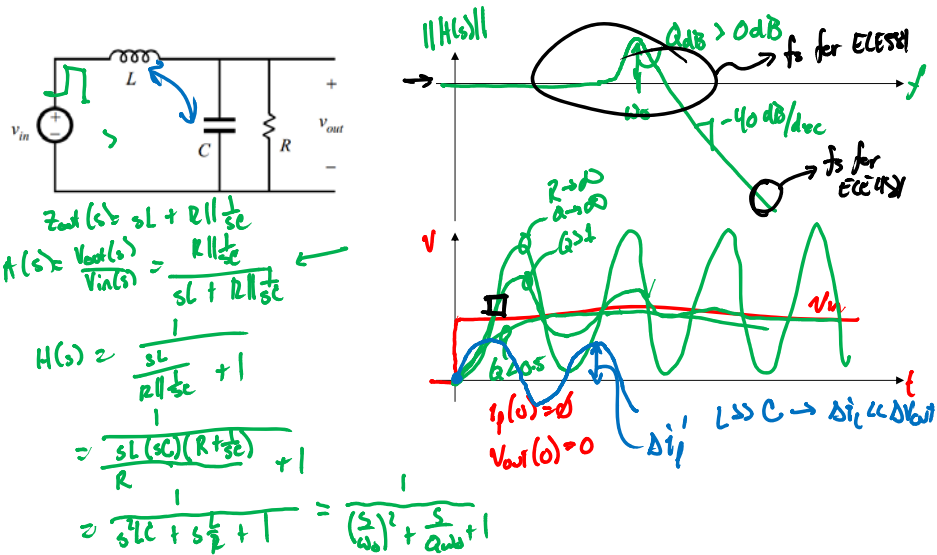
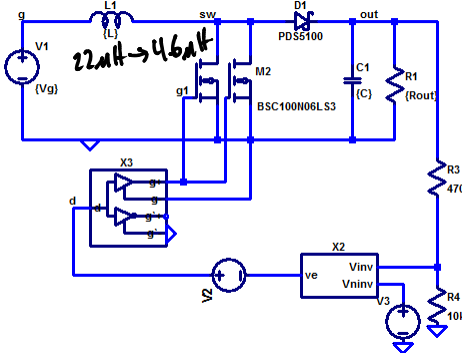
Resonant Circuit Analysis





Soft Switching





$\Delta i_L \geq I_L \rightarrow \text{DCM}$

$\Delta i_L = \frac{1}{2} \frac{V_g}{L} DT_s$


DCM boundary:



$$L = \frac{1}{2} \frac{V_g}{I_L} DT_s = \frac{1}{2} \frac{(12V)}{(4A)} \frac{(0.75)}{202 \text{kHz}}$$

$L = 5.5 \mu\text{H}$

$\Delta i_L \approx 5A$


$L = 4.6 \mu\text{H}$

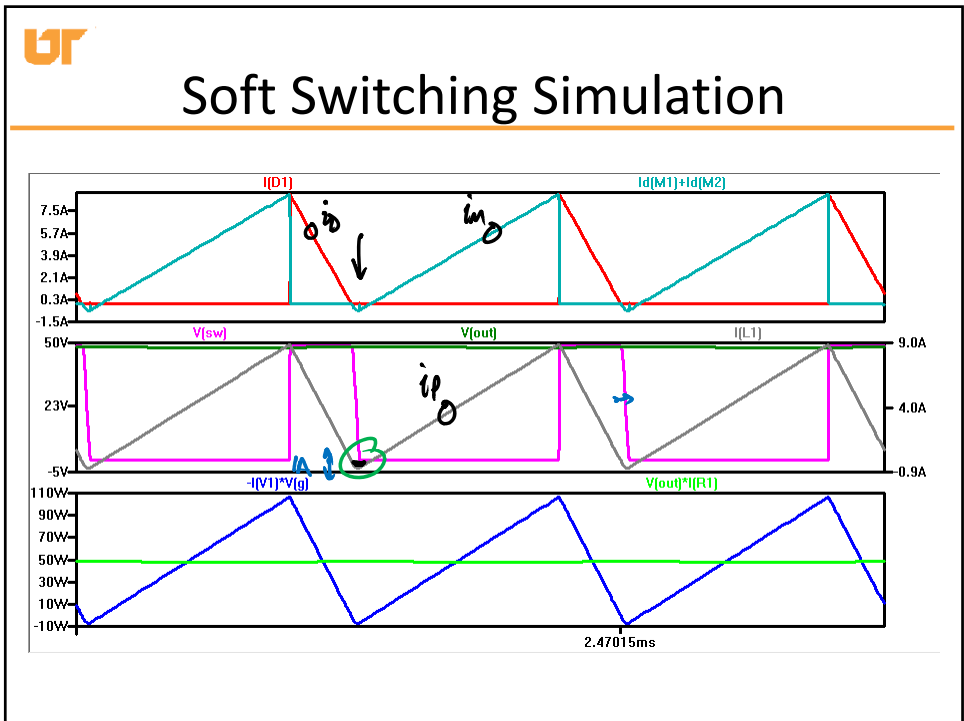

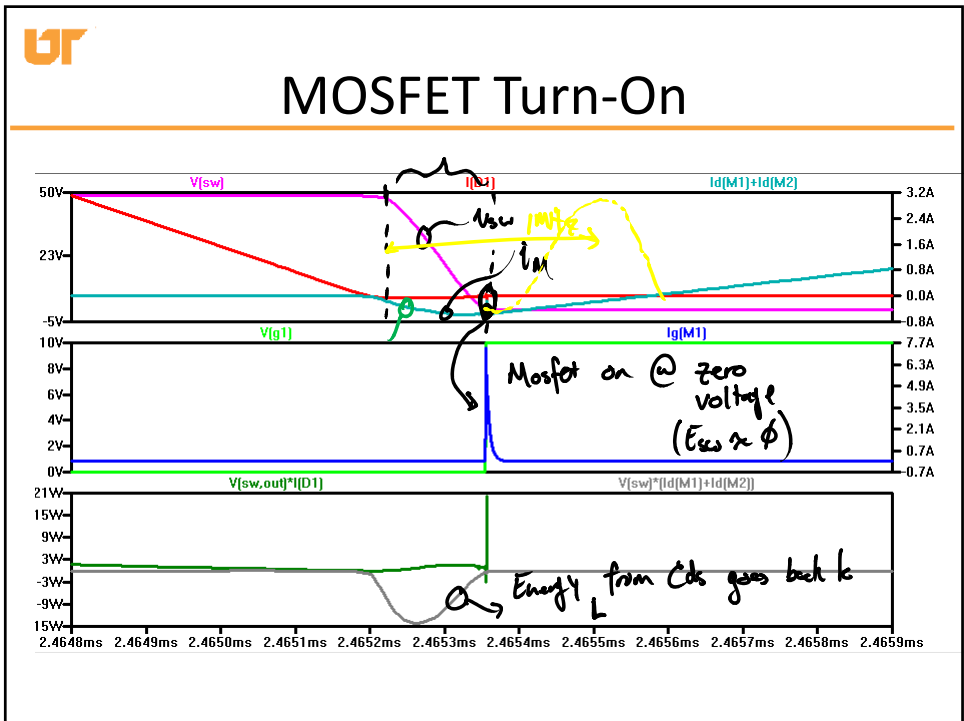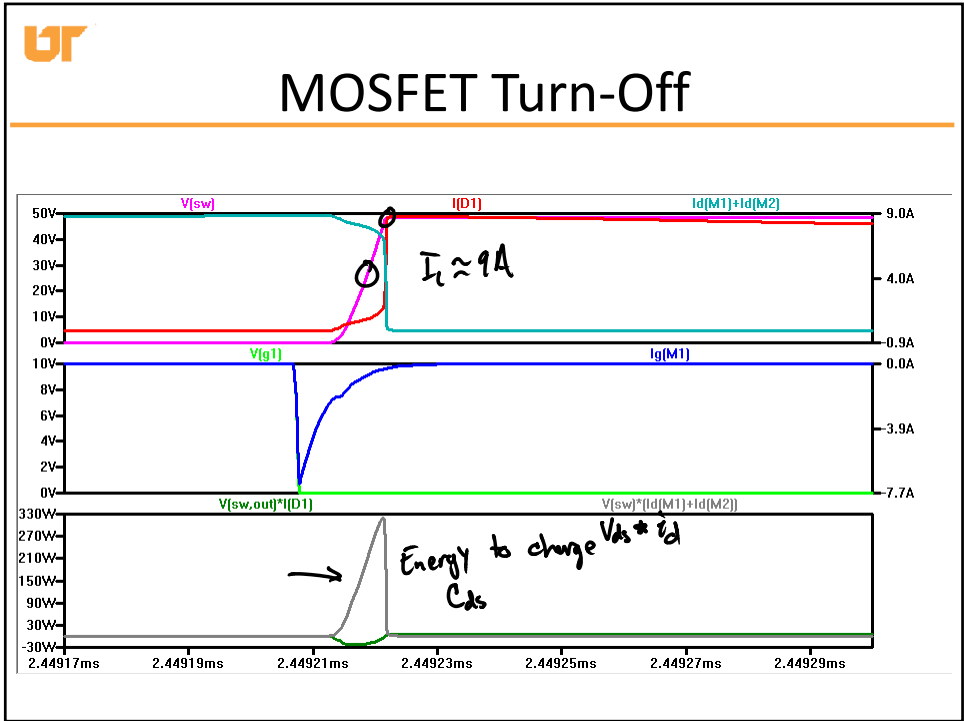




→ 1 MHz Operation

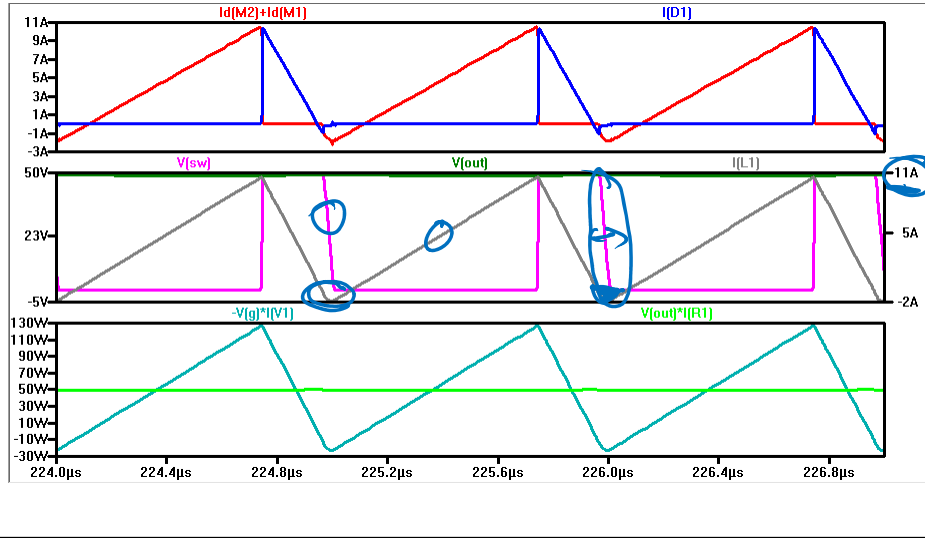


MOSFET Turn-On

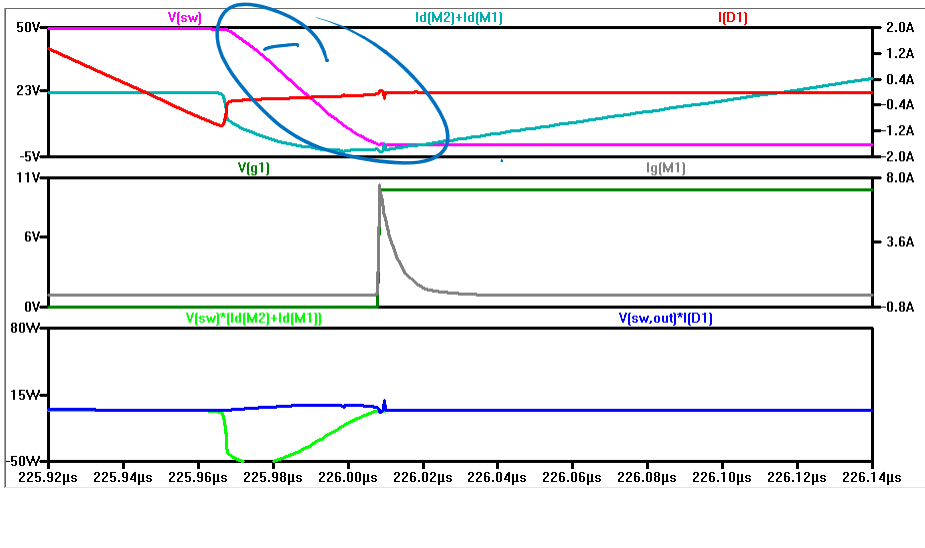



Synchronous Operation

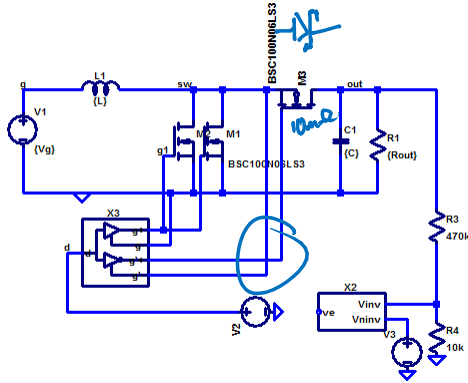

$$i_{cond} \approx I_{out} V_D$$


$$= (1A) (0.75V) \approx 0.75W$$

$$i_{cond} = I_{m,rms}^2 r_{on}$$

$$\approx I_{out}^2 r_{on} \approx 10mW$$




Synchronous Simulation

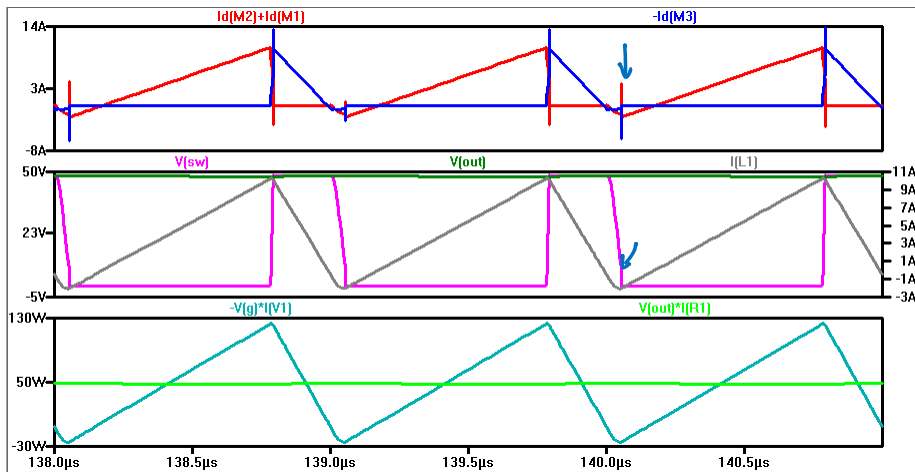



Summary Results

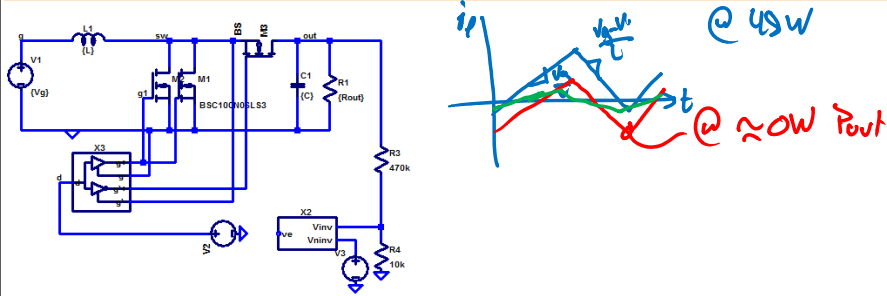

L	C_{out}	f_s	Diode	η (Sim)
22uH	22uF	202k	Si (FR)	93.9%
22uH	22uF	202k	Si Schottky	96.9%
4.65uH	22uF	202k	Si Schottky	98.5%
710nH	4.4uF	1 MHz	Si Schottky	98.4%
710nH	4.4uF	1 MHz	MOSFET	99.8%

Soft Switched