




High Frequency Power Electronics

Prof. Daniel Costinett

ECE 581 Lecture 3
August 25, 2014




Resonant Circuits

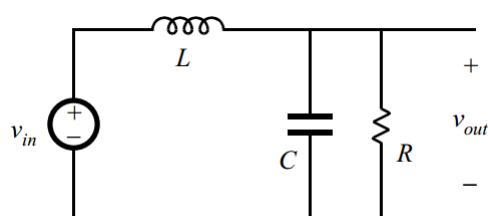








Resonant Circuit Analysis


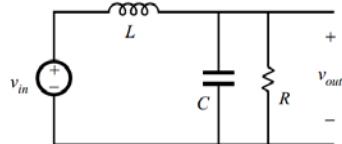




Soft Switching

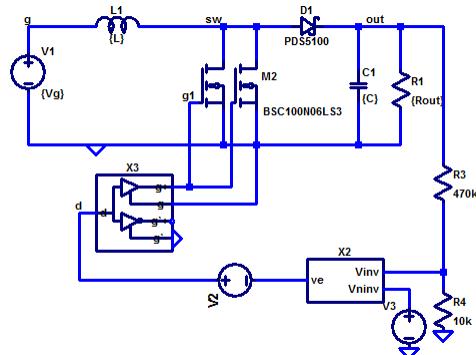

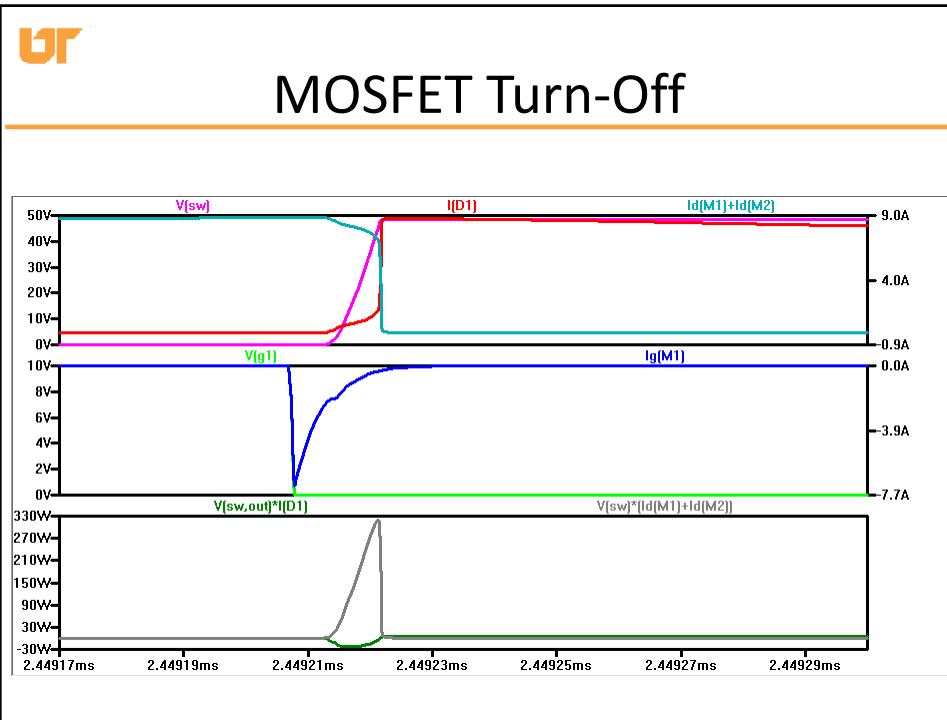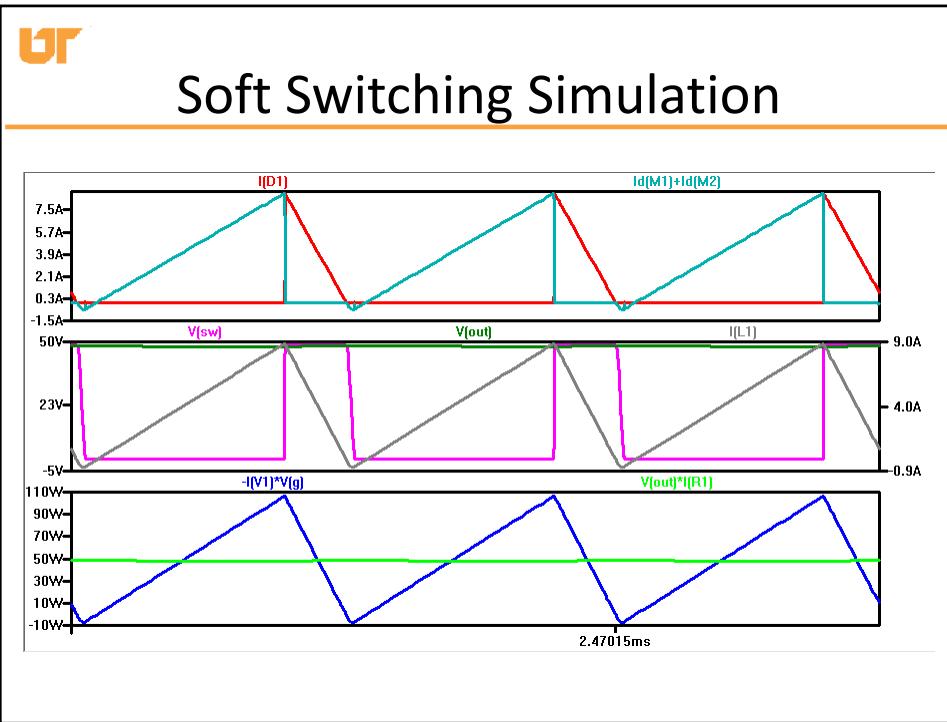

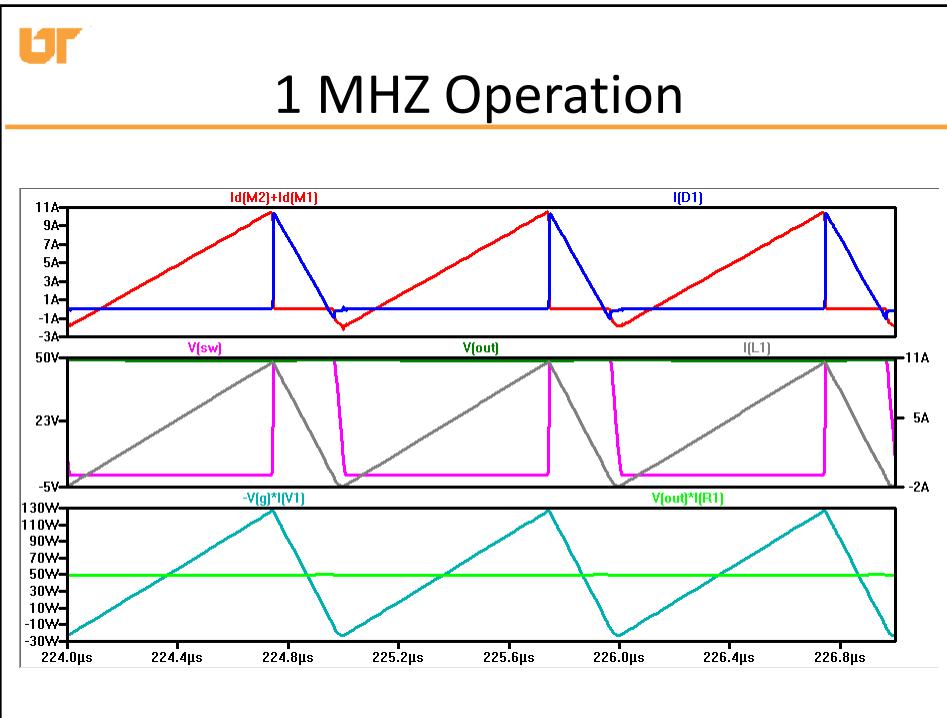
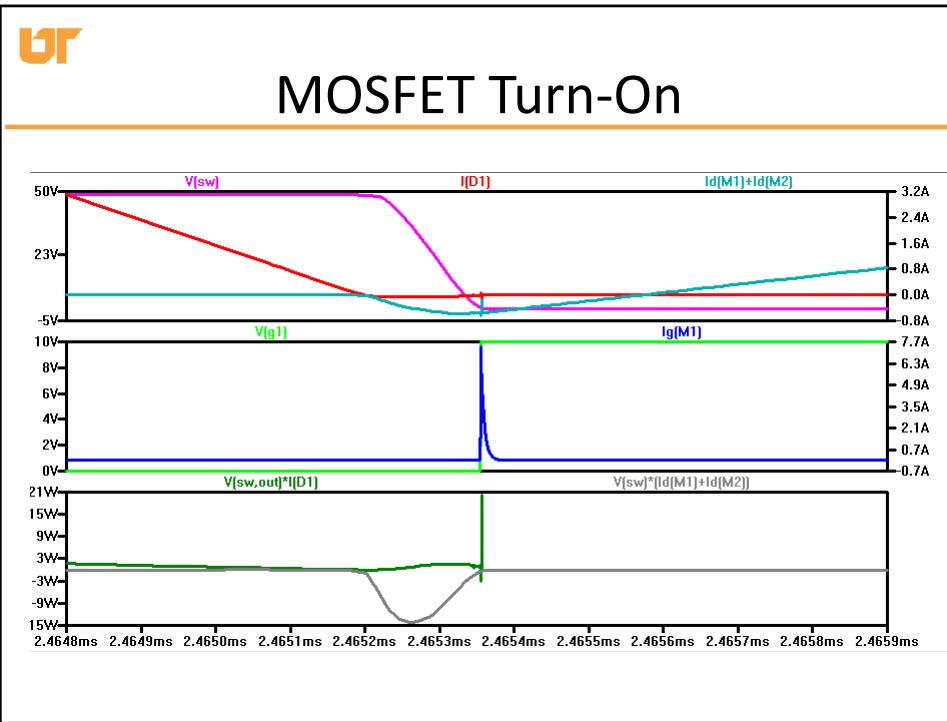


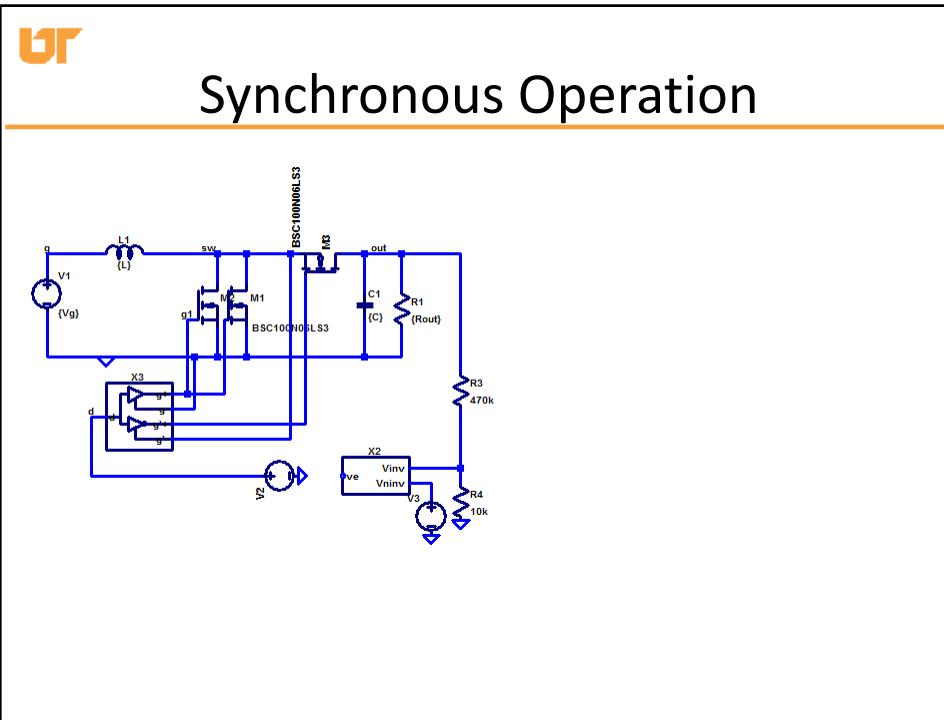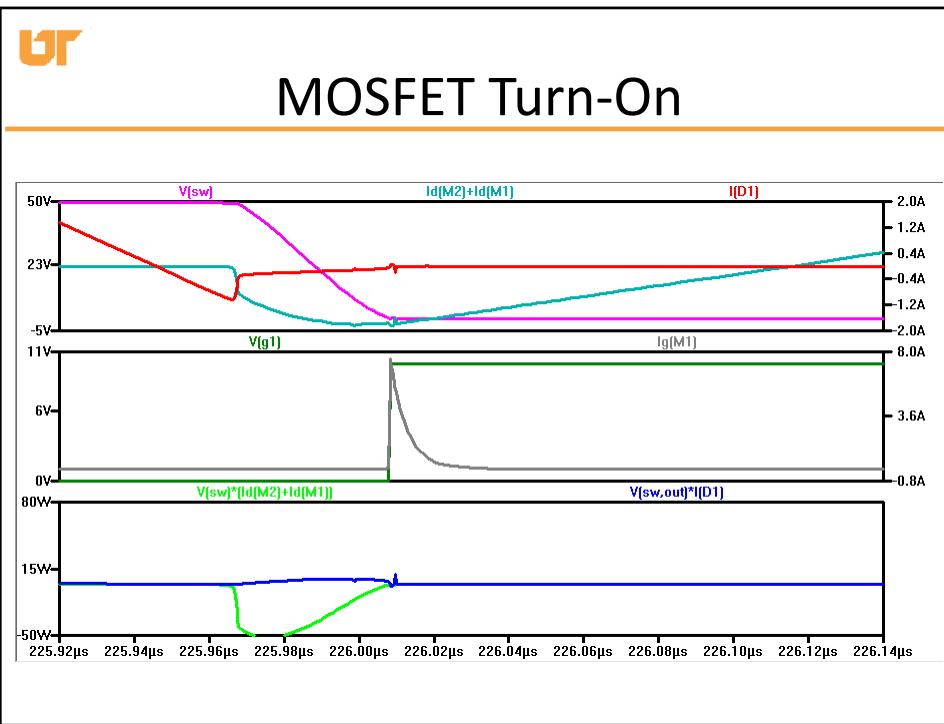

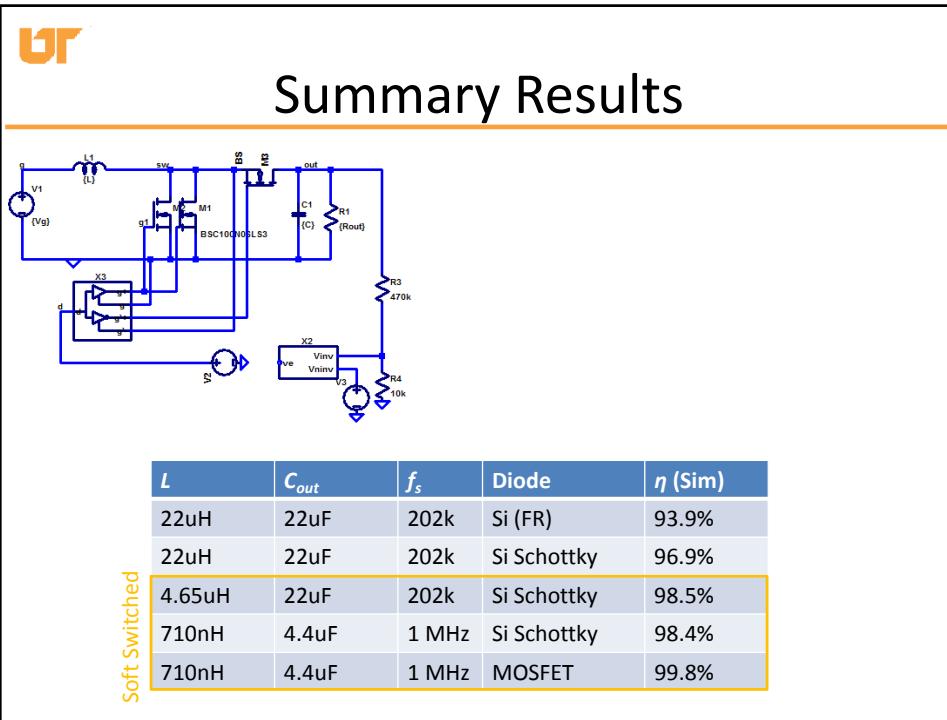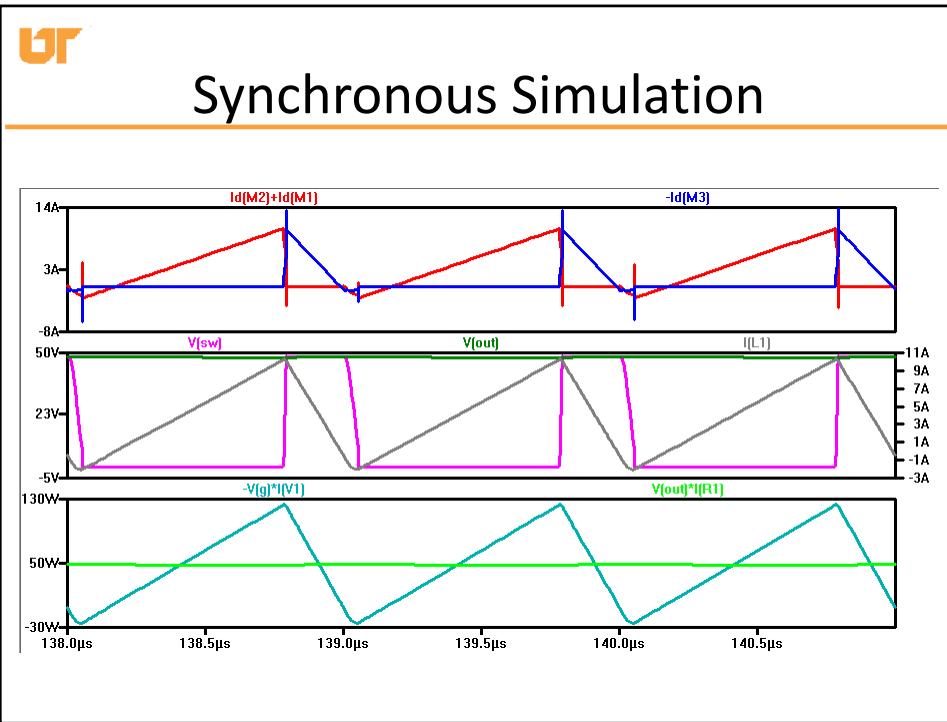




Limitations: Gate Drive

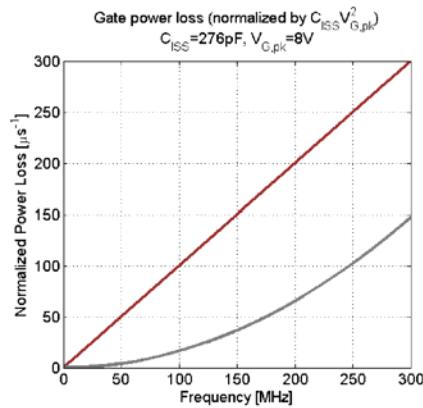
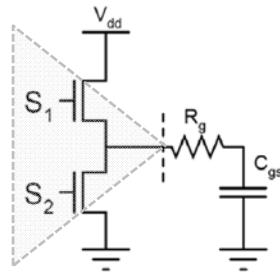


Limitations: t_d/T_s

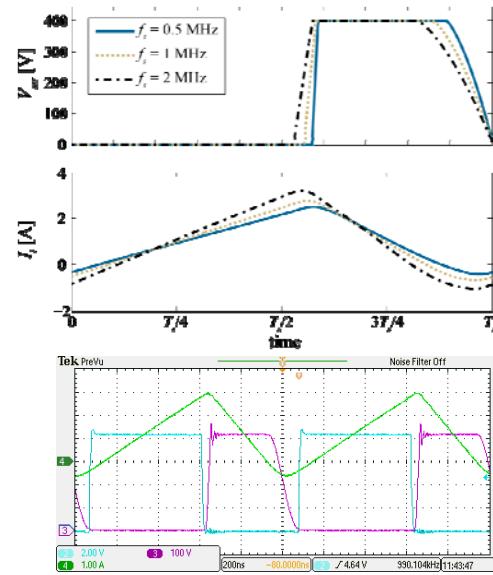



Limitations: Thermal

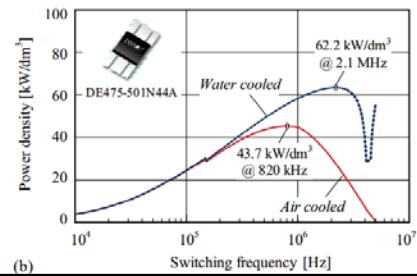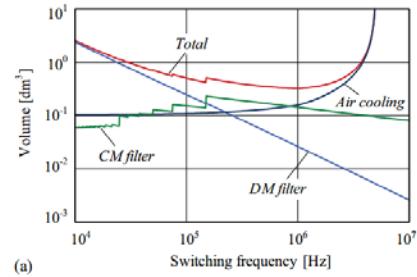

Kolar, J.W.; Drofenik, U.; Biela, J.; Heldwein, M.L.; Ertl, H.; Friedli, T.; Round, S.D., "PWM Converter Power Density Barriers," *Power Conversion Conference - Nagoya, 2007. PCC '07*, vol., no., pp.P-9-P-29, 2-5 April 2007



Limitations: Magnetics Design

