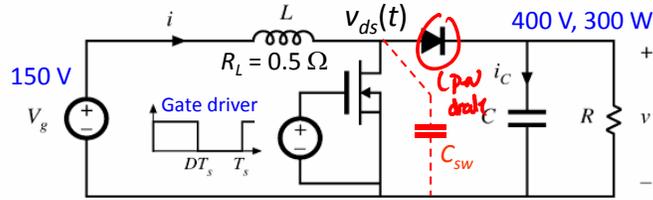




# Hard-switched Si devices




Si devices, standard "hard-switched" operation

MOSFET

- $di_T/dt = 200 \text{ A}/\mu\text{s}$
- $C_{d,eq} = 45 \text{ pF}$
- $R_{on} = 0.15 \Omega$

Si diode

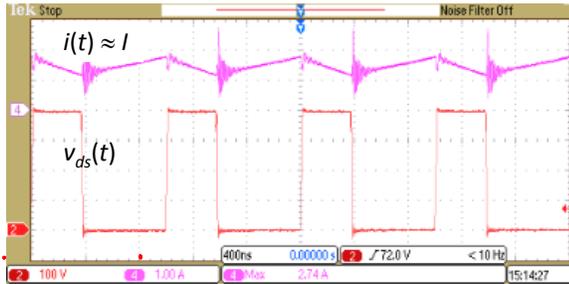- $t_{rr} = 40 \text{ ns}$
- $Q_{rr} = 60 \text{ nC}$
- $2C_{d,eq} - C_{d,eq} = 22 \text{ pF}$
- $V_D = 1.5 \text{ V}$




$f_s = 1 \text{ MHz}$


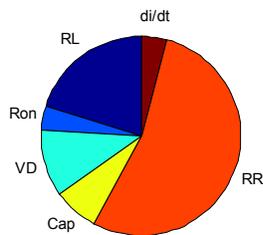
# Loss breakdown: Si Boost


$f_s = 100 \text{ kHz}$   
 $P_{loss} = 10.6 \text{ W}, \eta = 96.6\%$



Reverse-recovery:  
 54% of the total loss

Conduction losses: RL, Ron, VD  
 Switching losses:  
 "RR" reverse recovery,  
 "Cap"  $C_{sw}$  discharge

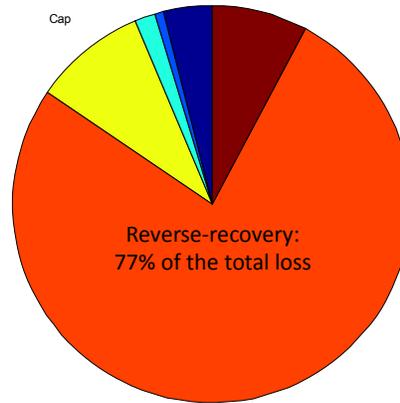$f_s = 1 \text{ MHz}$   
 $P_{loss} = 84.7 \text{ W}, \eta = 78.0\%$   
 Experiment\*  $\eta = 81.2\%$




Reverse-recovery:  
 77% of the total loss


\*Pulsed measurement, continuous operation not feasible due to thermal runaway




## Efficiency: hard-switched Si Boost

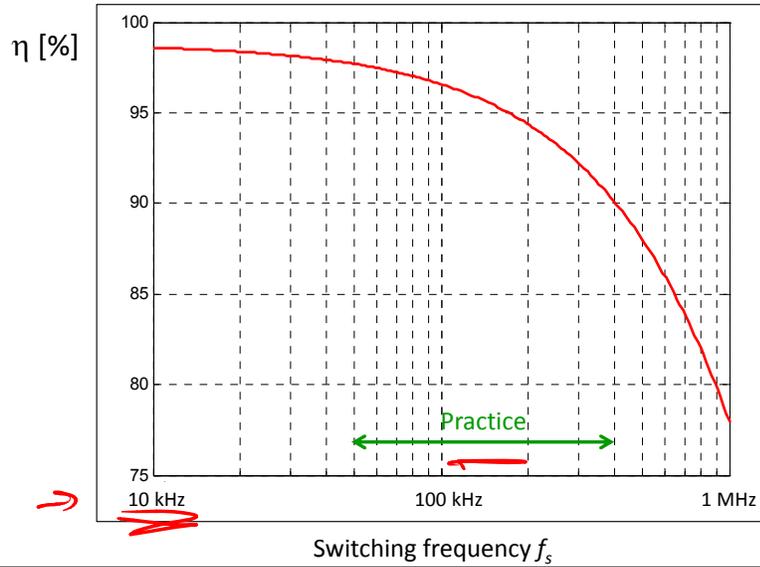

## ZVS with Si diode

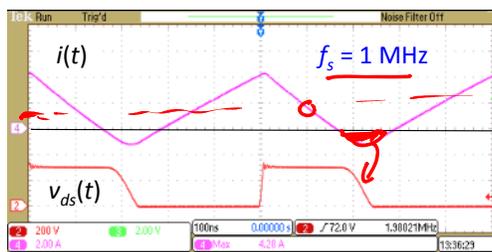

Zoom-in:

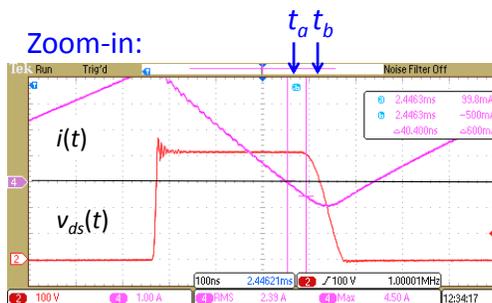



### • ZVS turn-ON

- Eliminated losses due to  $C_{sw}$  discharge during turn-ON transient
- Eliminated losses due to MOSFET  $di_F/dt$  during turn-ON transient

### • Diode reverse recovery still impacts the waveforms and losses

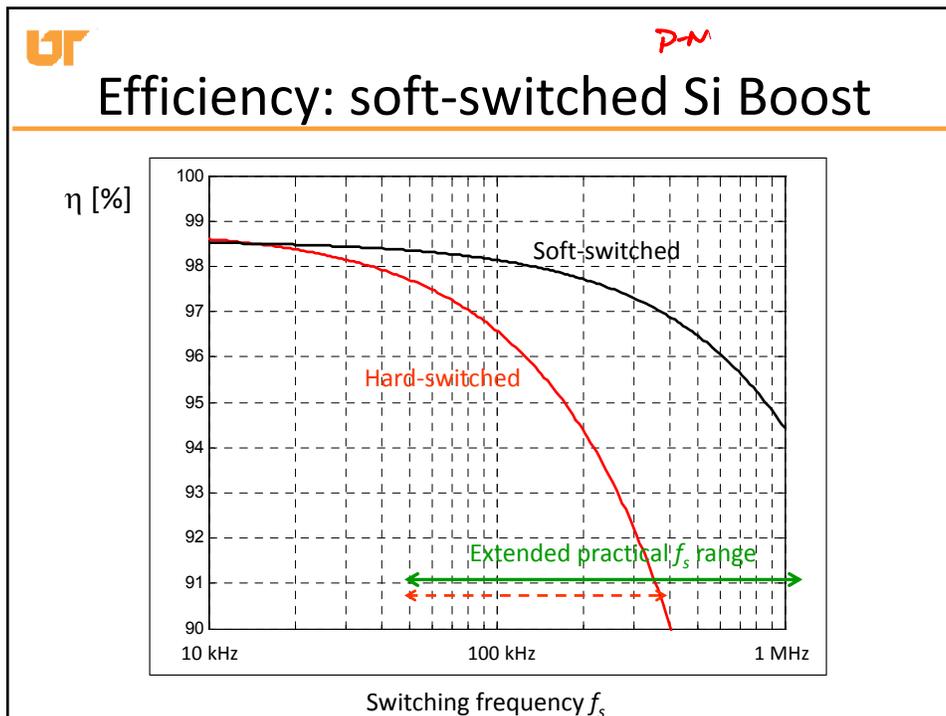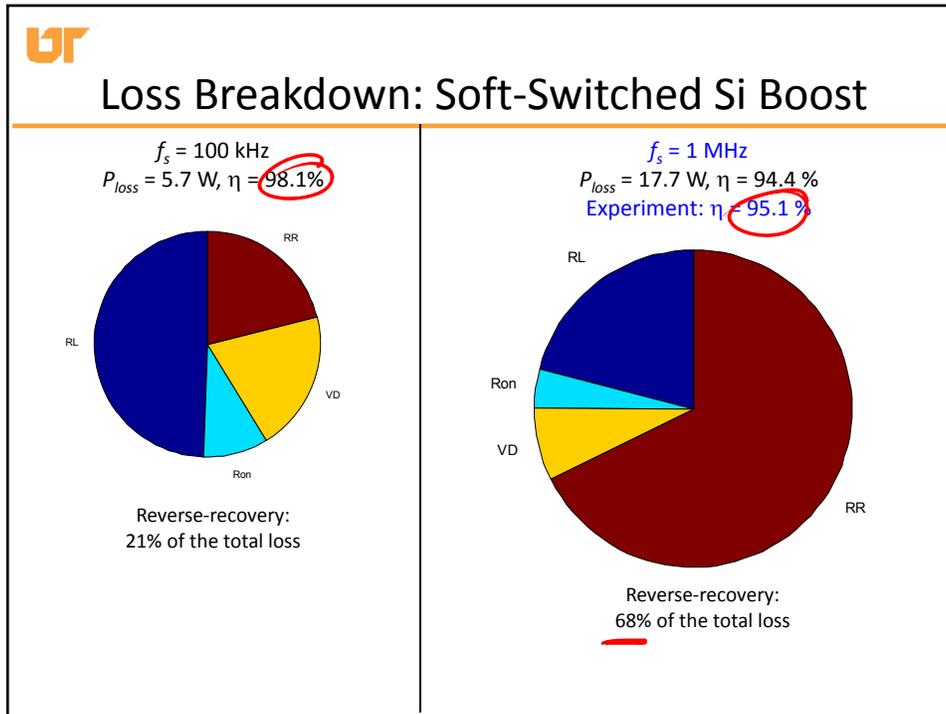
### • Increased current ripple

- Increased conduction losses (by >30%)
- Increased  $dv_{ds}/dt$  upon turn-OFF, MOSFET turn-OFF speed is more important





# Hard-Switched SiC Schottky Diode

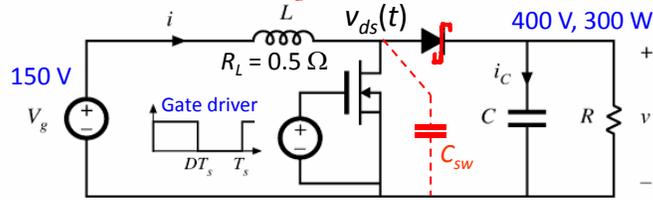


SiC diode, standard "hard-switched" operation

MOSFET

- $di_T/dt = 200 \text{ A}/\mu\text{s}$
- $C_{ds,eq} = 45 \text{ pF}$
- $R_{on} = 0.15 \Omega$

SiC diode

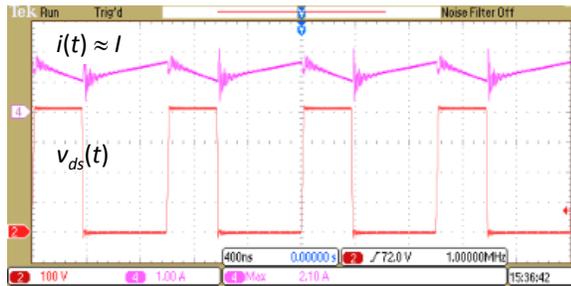- $t_{rr} = 0, Q_{rr} = 0$
- $2C_{d,Qeq} - C_{d,eq} = 64 \text{ pF}$
- $V_D = 1.8 \text{ V}$




$f_s = 1 \text{ MHz}$



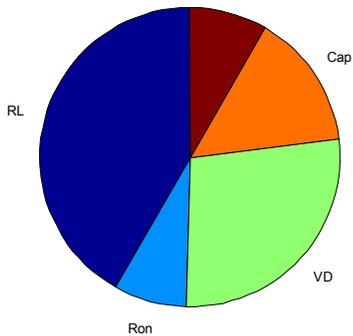
## Loss Breakdown: hard-switched SiC diode



$f_s = 100 \text{ kHz}$   
 $P_{loss} = 5 \text{ W}, \eta = 98.4\%$



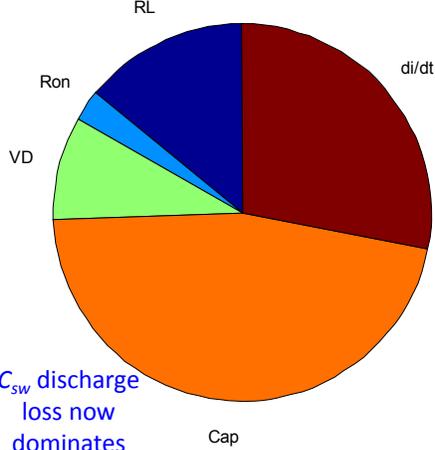$f_s = 1 \text{ MHz}$   
 $P_{loss} = 15.7 \text{ W}, \eta = 95.0\%$   
 Experiment:  $\eta = 94.7\%$




$C_{sw}$  discharge loss now dominates

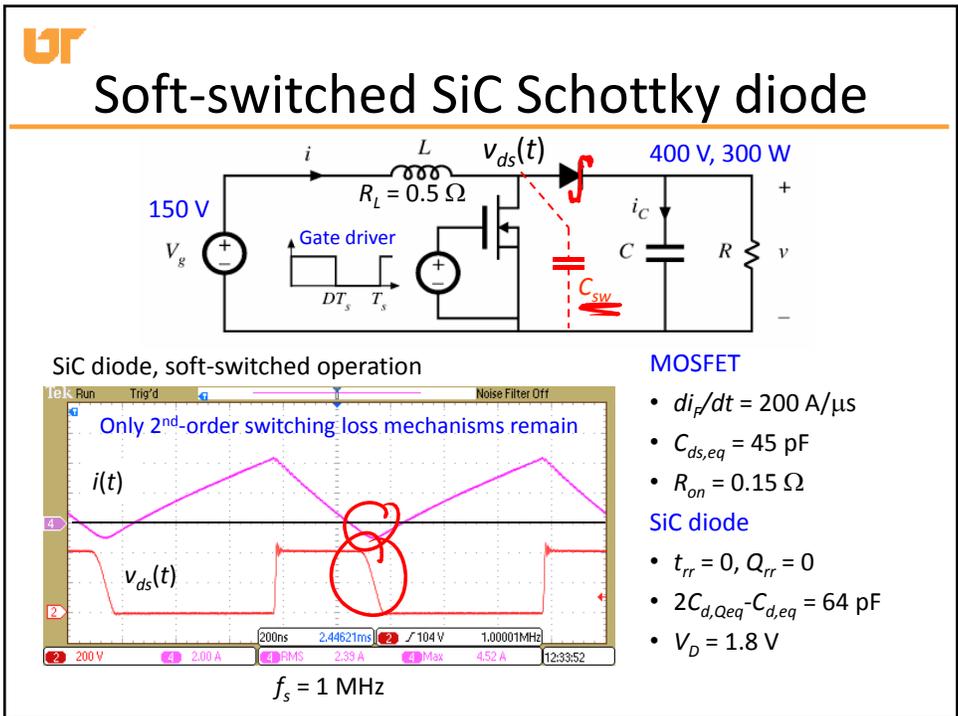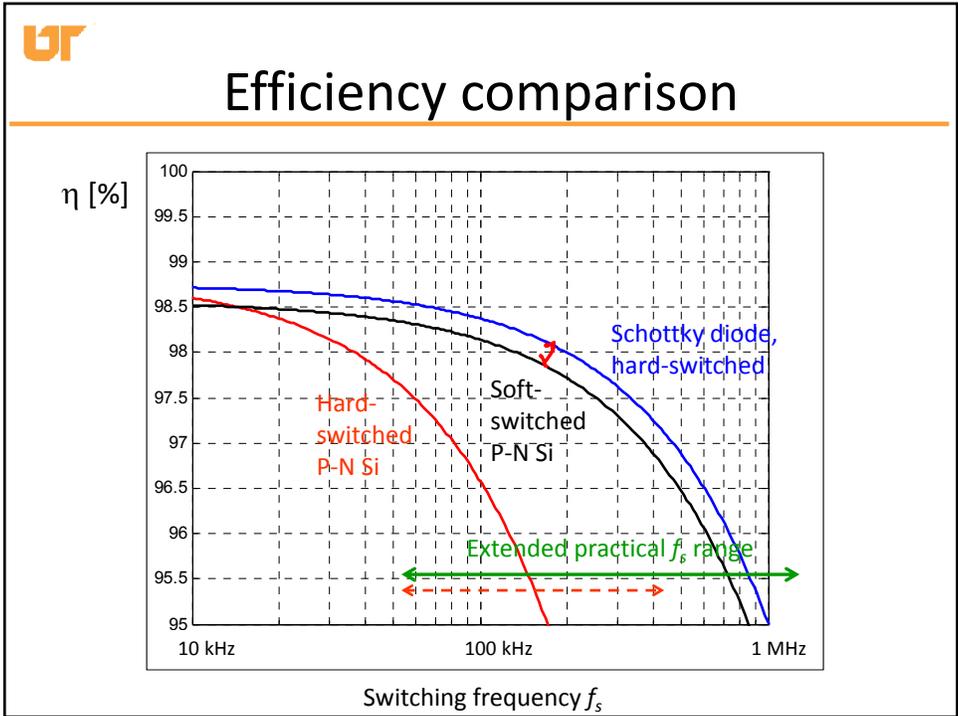


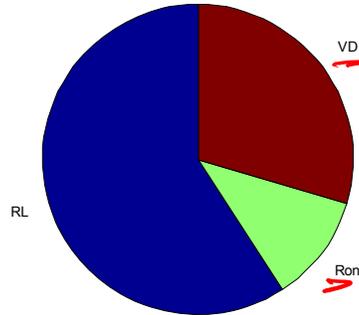
# Soft-switched Boost with SiC diode

Conduction losses only, 2<sup>nd</sup>-order switching losses not included in the model






100 kHz or 1 MHz  
98.5% efficiency  
 $P_{loss} = 4.5 \text{ W}$

Experiments:  
 98.7% at 1 MHz  
 98.0% at 2 MHz



# Efficiency comparison

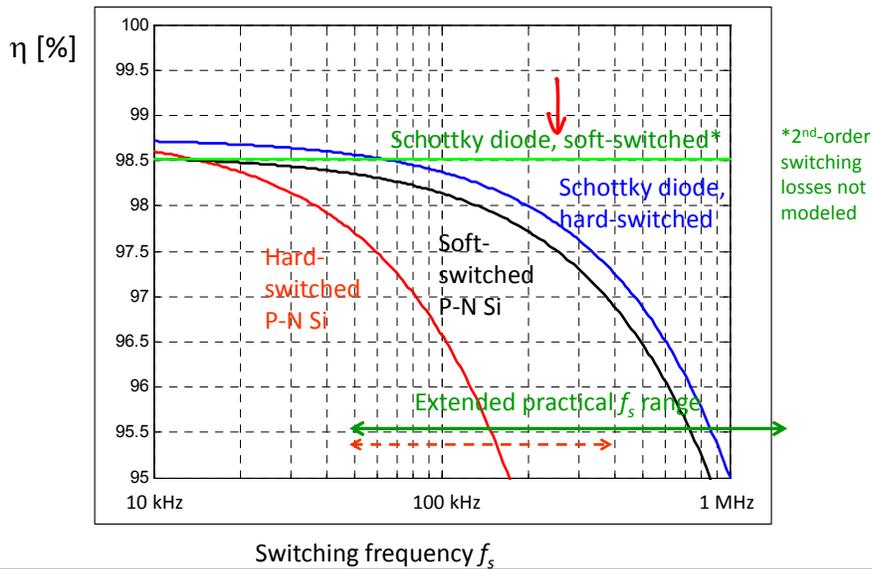

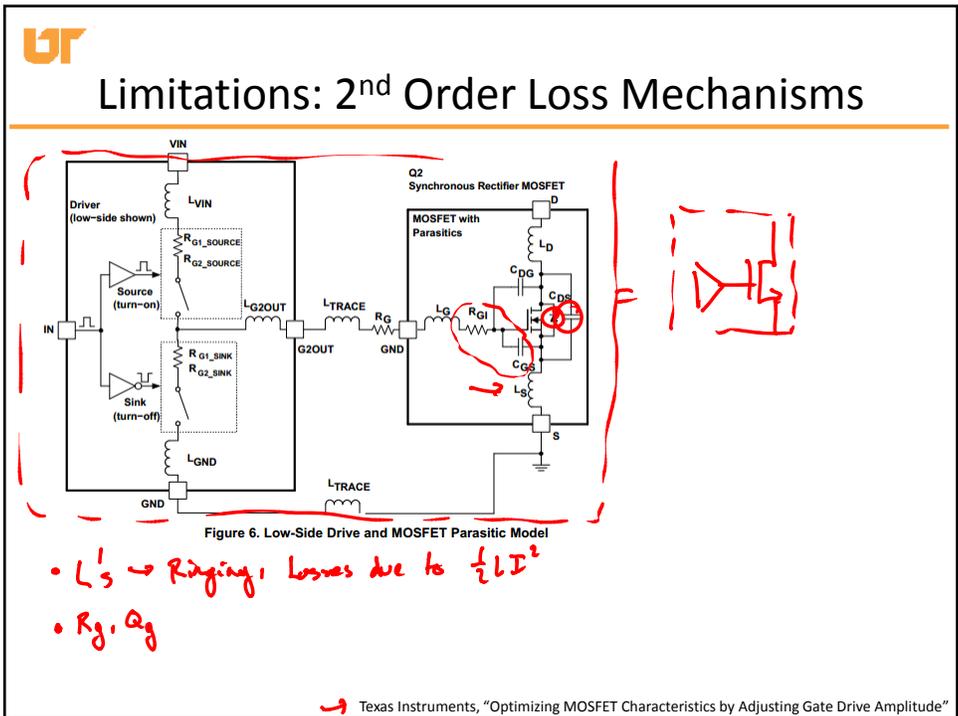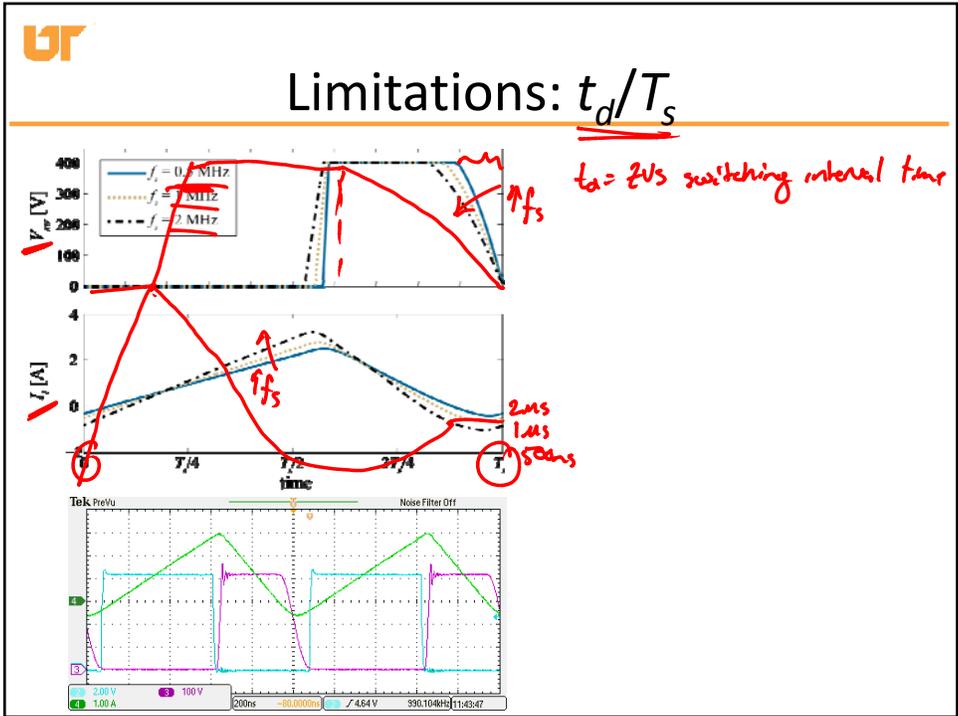



# Limitations: Gate Drive

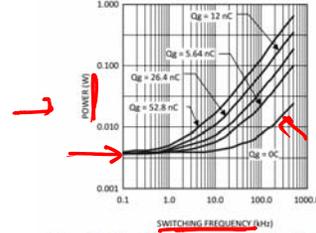
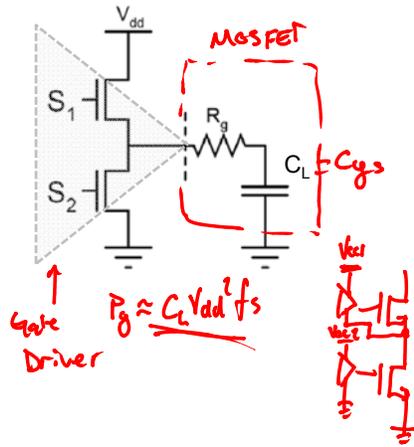


Figure 2. Gate Driver Power Dissipation (LO + HO)  
V<sub>cc</sub> = 12V. Neglecting Diode Losses



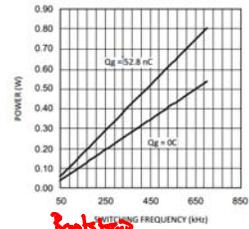


Figure 4. Diode Power Dissipation  
V<sub>in</sub> = 80V

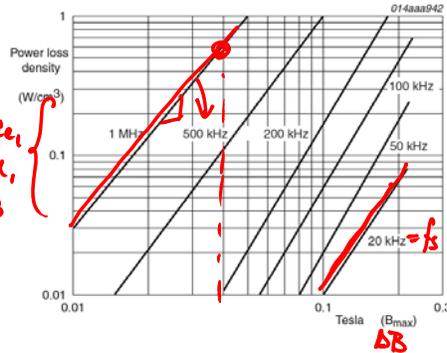Texas Instruments, "Selection of External Bootstrap Diode for LM510X Devices"



# Limitations: Magnetics Design

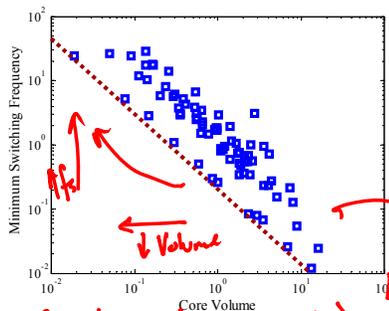

Core loss: (via Steinmetz)


$$P_{core} = K_{fe} (\Delta B)^\alpha (f_s)^\beta V_c$$

$$\Delta B = \int \frac{V}{n A_e} dt \rightarrow \Delta B \downarrow f_s \uparrow$$


- Going to high freq →  $k_{fe}, \alpha, \beta = f(f_s)$
- Additional mechanism: Proximity loss, Skin effect, fringing



# Limitations: Thermal

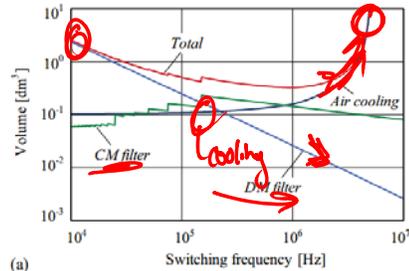

(a)

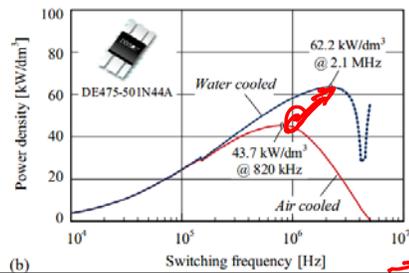

(b)


10kW rectifier 230Vac → 80Vdc  
 ? ≈ cents (big assumption!)  
 ↓ total volume P<sub>loss</sub> ≈ const  
 P<sub>loss</sub> / Volume ↑

Kolar, J.W.; Drofenik, U.; Biela, J.; Heldwein, M.L.; Ertl, H.; Friedli, T.; Round, S.D., "PWM Converter Power Density Barriers," *Power Conversion Conference - Nagoya, 2007. PCC '07*, vol., no., pp.P-9,P-29, 2-5 April 2007




# Example VHF Resonant Boost

## Φ<sub>2</sub> Boost Converter

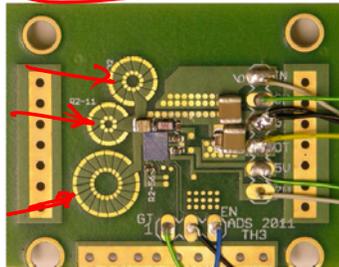

75 MHz, 14W, 85% efficiency

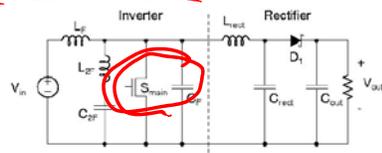

Pilawa-Podgurski, et. al., "Very High-Frequency Resonant Boost Converters," *Trans. P.E.* June 2009



## Topics Covered

---

- **Course Topics**
  - High Frequency Power Conversion
    - Switching losses and device selection
    - Resonance in power electronics
    - Soft switching (ZVS and ZCS)
    - Magnetics design
  - Quasi-resonant soft switching converters
    - Constant frequency control
    - State-plane analysis
    - Resonant switches
    - Modeling and Simulation
    - Discrete time models
  - Resonant Converters
    - Resonant converter topologies
    - Sinusoidal analysis
    - AC-modeling and frequency modulation
    - State-plane analysis
  - Applications and practical issues of high frequency converters