

Simplification

$$J = \frac{2F}{\pi} m_1 \quad \alpha = \pi - 2 \tan^{-1} \left(\frac{J_1}{m_1} \right)$$

$$\frac{\pi}{F} = \alpha + \beta \quad \beta = 2 \tan^{-1} \left(\frac{J_1}{2 + m_1} \right)$$

$$\tan \left(\frac{\beta}{2} \right) (2 + m_1) = J_1$$


$$\tan \left(-\frac{\alpha + \pi}{2} \right) = \frac{J_1}{m_1} = \frac{2 + m_1}{m_1} \tan \frac{\beta}{2}$$

$$m_1 \tan \left(\frac{\pi - \alpha}{2} \right) = \frac{2 \tan \frac{\beta}{2} + m_1 \tan \frac{\beta}{2}}{2 \tan \frac{\beta}{2}}$$


$$m_1 = \frac{2 \tan \frac{\beta}{2}}{\tan \left(\frac{\pi - \alpha}{2} \right) - \tan \frac{\beta}{2}}$$

$$J = \frac{2F}{\pi} \frac{2 \tan \frac{\beta}{2}}{\tan \left(\frac{\pi}{2} - \frac{\pi}{2F} + \frac{\beta}{2} \right) - \tan \frac{\beta}{2}}$$


SRC Control Trajectory

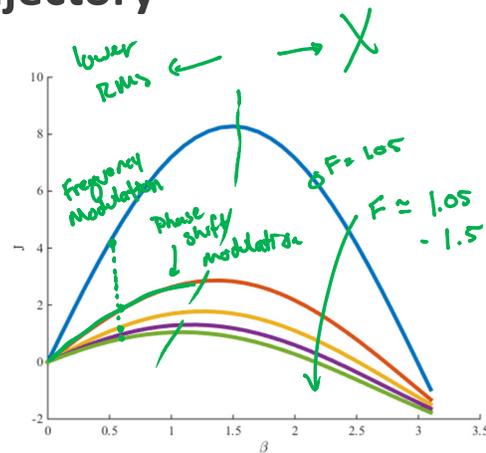


SRC Simulation

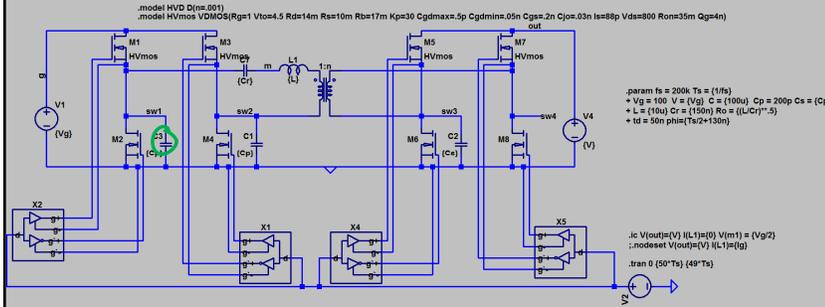



SRC Simulation

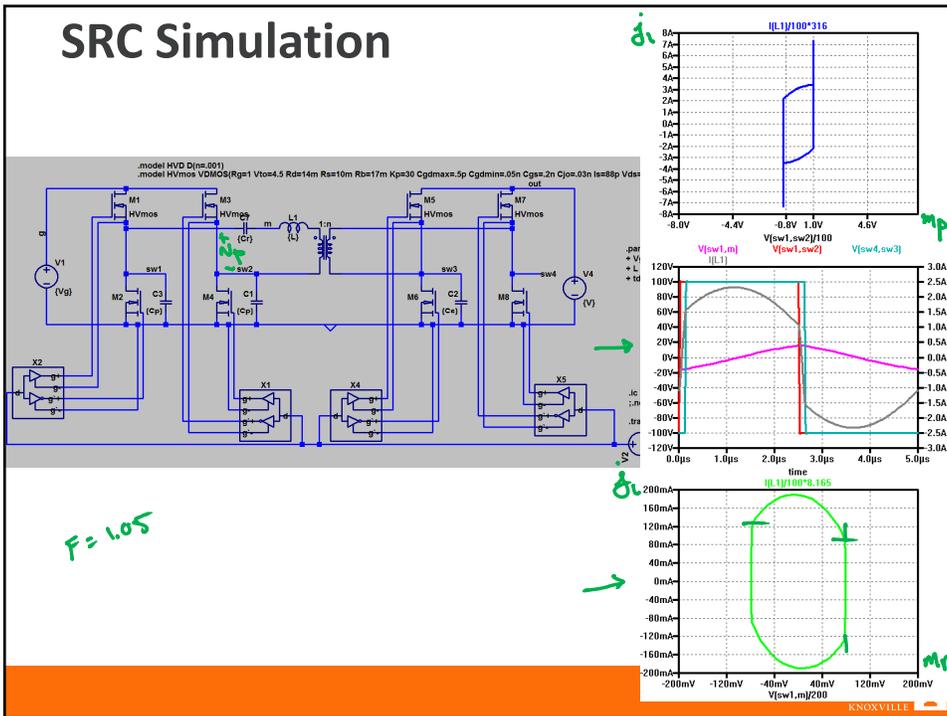

SRC – Heavy Load

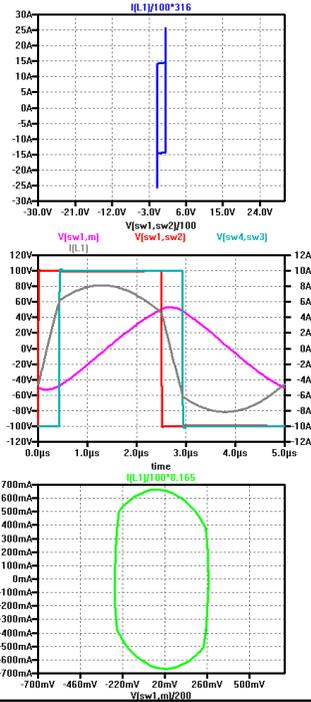


SRC – Light Load

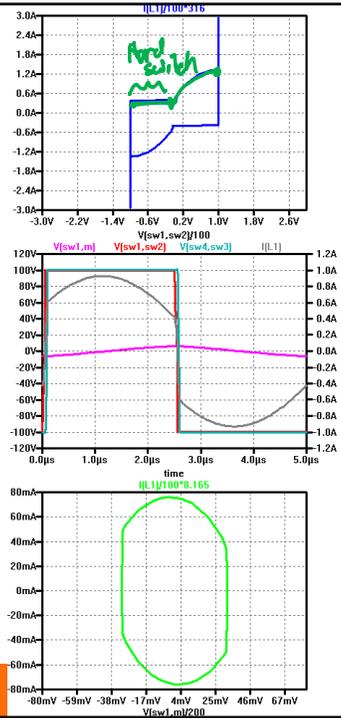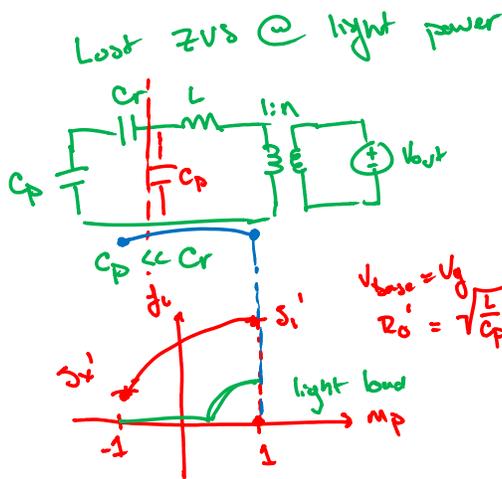


SRC Near Resonance

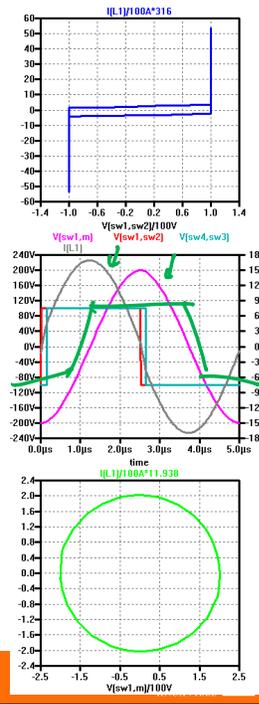$f_s \approx f_0$
 $f_s > f_0$
 ↑
 slightly






SRC – Low V_{out}

$V \neq nV_g$

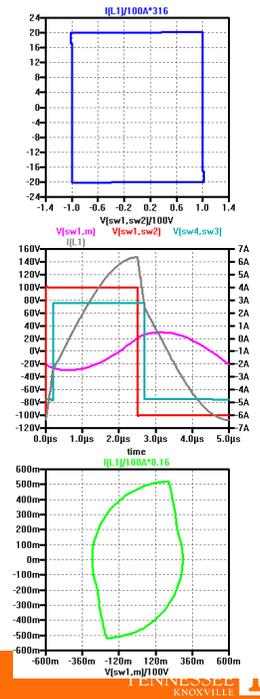


SRC – F >> 1


$$F \gg \rightarrow f_s \gg f_0$$

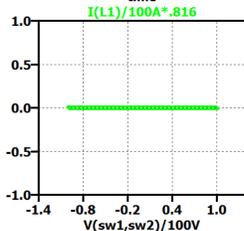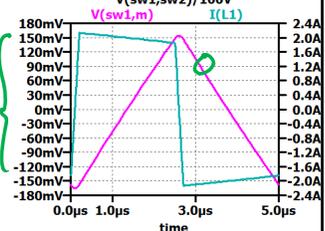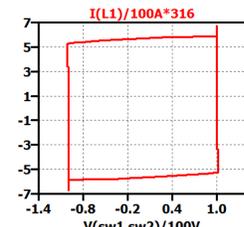

DAB vs SRC

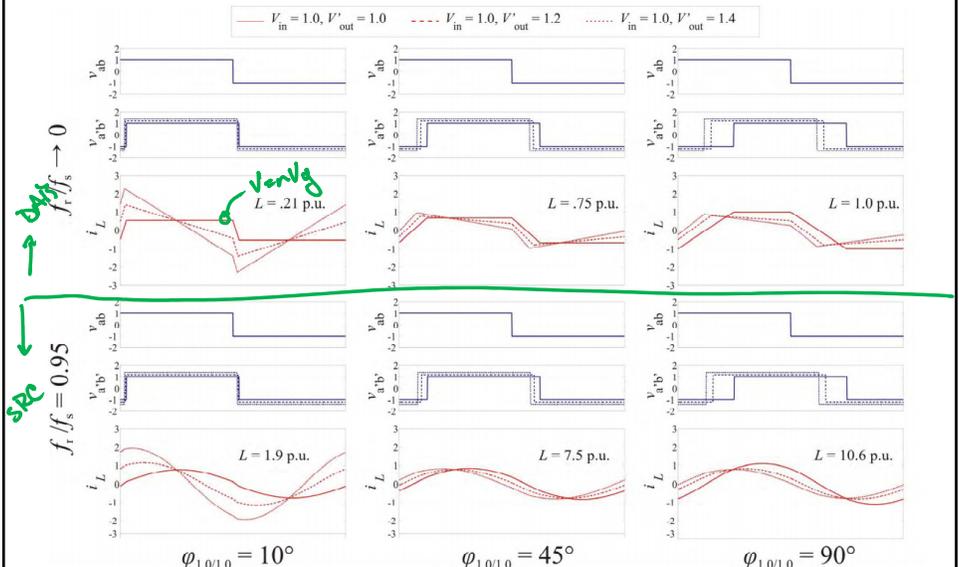

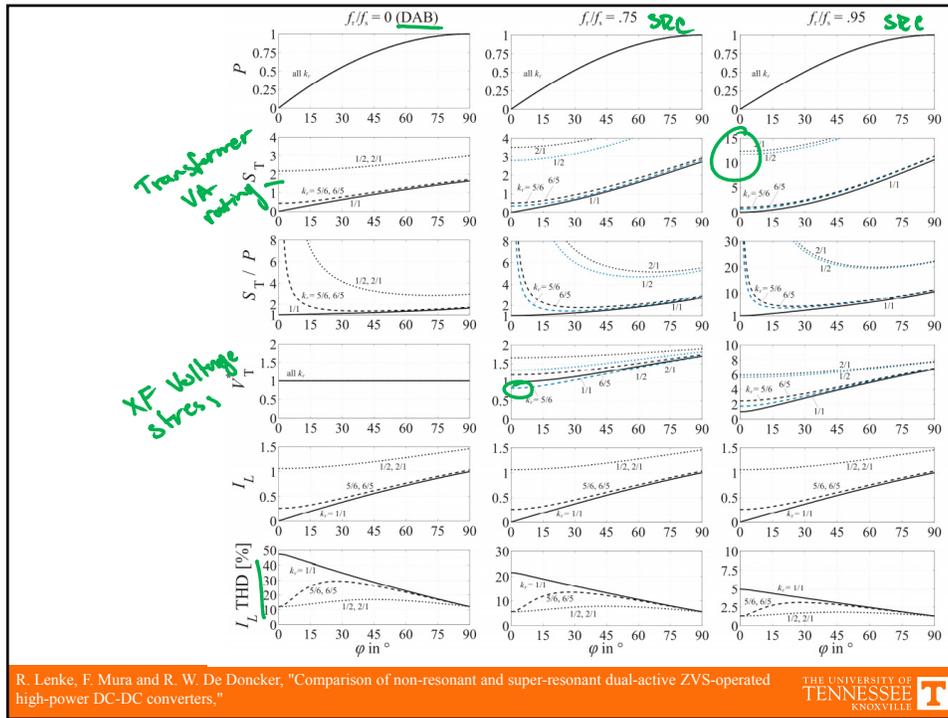R. Lenke, F. Mura and R. W. De Doncker, "Comparison of non-resonant and super-resonant dual-active ZVS-operated high-power DC-DC converters," THE UNIVERSITY OF TENNESSEE KNOXVILLE



R. Lenke, F. Mura and R. W. De Doncker, "Comparison of non-resonant and super-resonant dual-active ZVS-operated high-power DC-DC converters."



DAB vs SRC: Conclusions

DAB

- + Smaller resonant tank
- + Smaller RMS currents
- + Wider Soft-switching range


SRC

- + Can be designed with larger WF inductance
- + Lower AC winding losses
- + Reduced device turn-off losses

R. Lenke, F. Mura and R. W. De Doncker, "Comparison of non-resonant and super-resonant dual-active ZVS-operated high-power DC-DC converters."




Linear Averaged Modeling of DAB

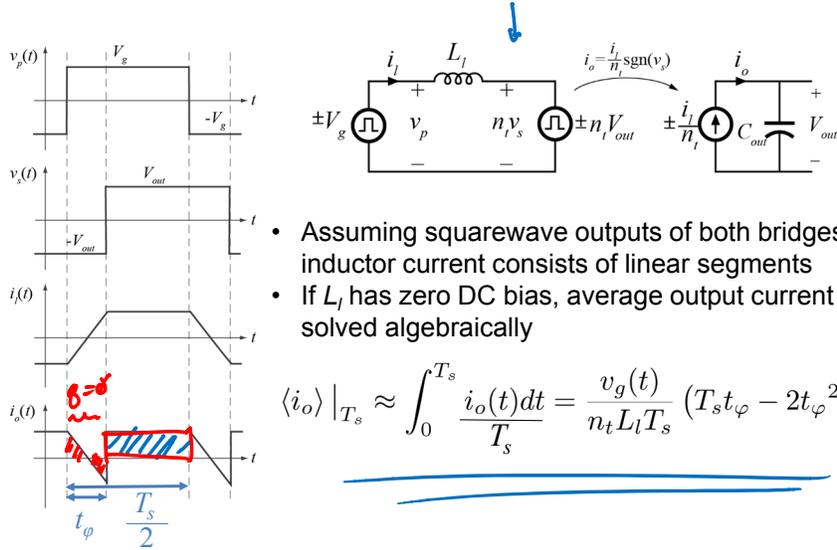


5-19

Superposition of Output Current

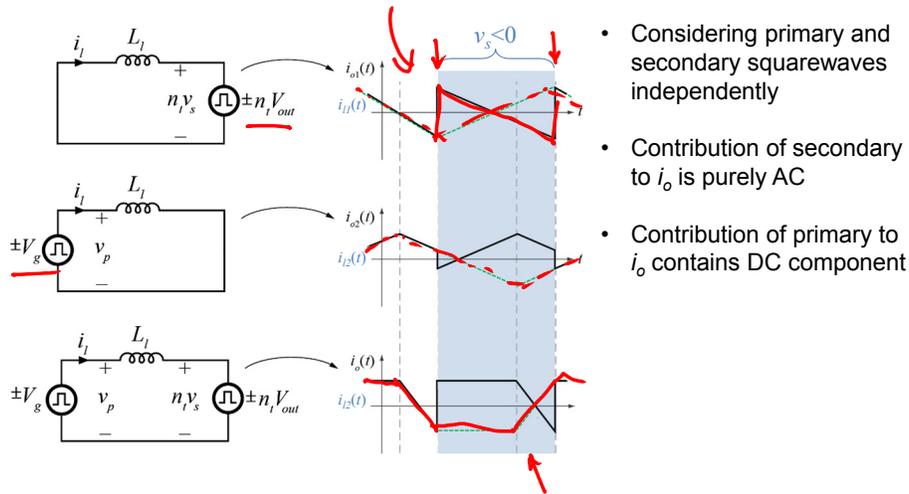

5-20

Superposition of Output Current

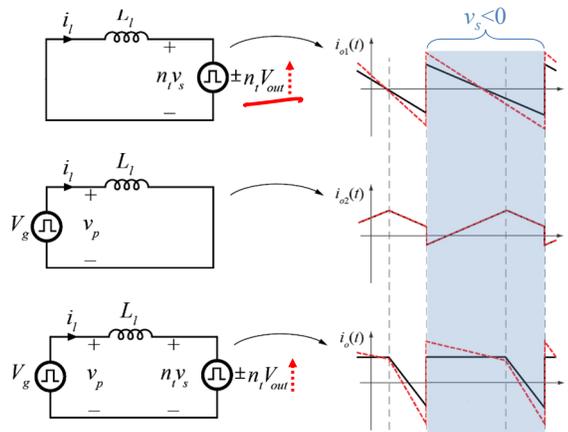

- Considering primary and secondary squarewaves independently
- Contribution of secondary to i_o is purely AC
- Contribution of primary to i_o contains DC component
- As V_{out} increases, only AC component from secondary is increased
- Average current unaffected

5-21