
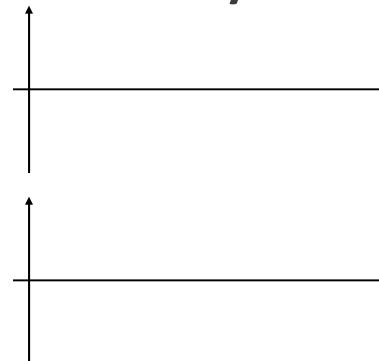



## Diode Rectifier Sinusoidal Analysis

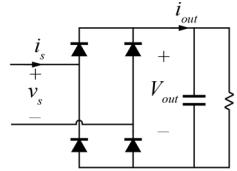

## Diode Rectifier Equivalent Circuit




## Complete Equivalent Circuit

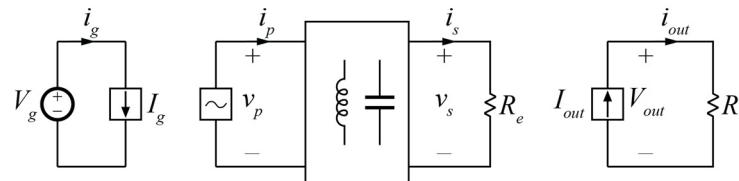

## Construction of Tank Transfer Function



## Output Characteristic

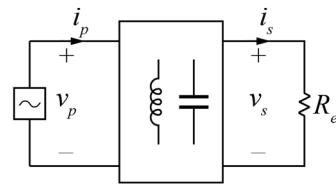

THE UNIVERSITY OF  
TENNESSEE   
KNOXVILLE

## Tank Input Impedance

THE UNIVERSITY OF  
TENNESSEE   
KNOXVILLE