

## Averaging



$$\theta_1 = \frac{1}{J_L}$$

$$J_2 = \sqrt{J_L^2 - 1}$$

$$\beta = \pi + \sin^{-1}\left(\frac{1}{J_L}\right)$$


$$\theta_3 = J_2 + J_L$$

$$\frac{2\pi}{F} = \theta_1 + \beta + \theta_3 + \theta_4$$



## Complete Solution

## MOSFET Voltage Stresses



## Test Circuit

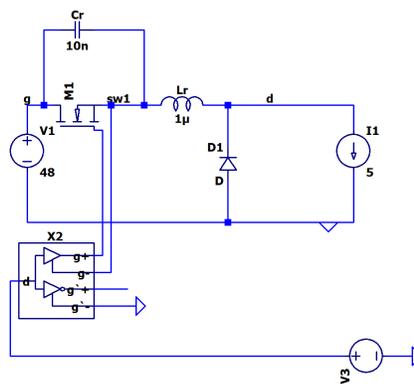



## Simulation Results

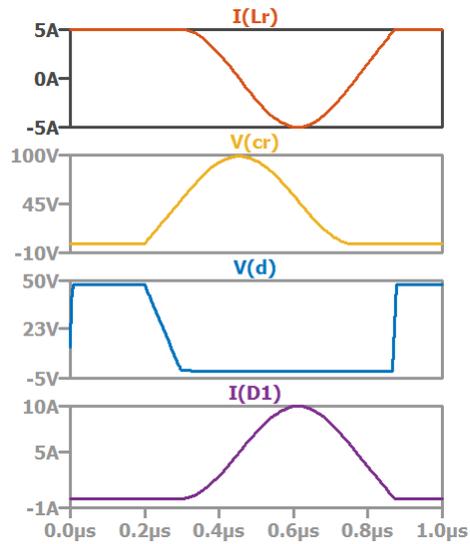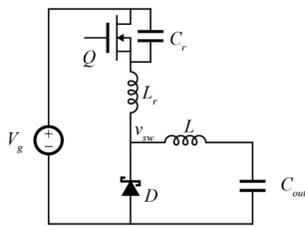


## Diode Capacitance

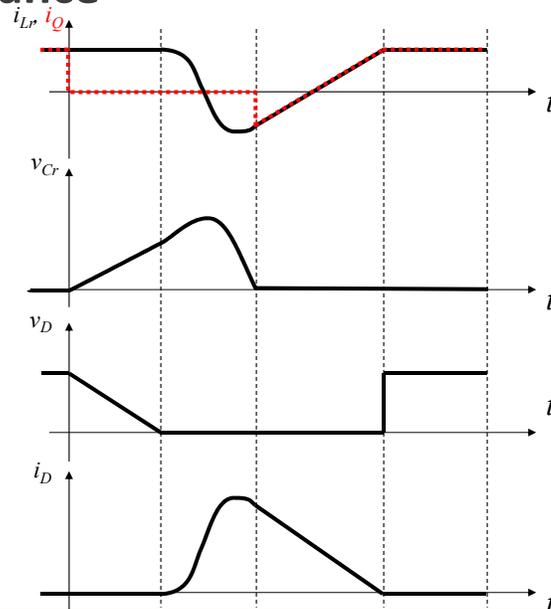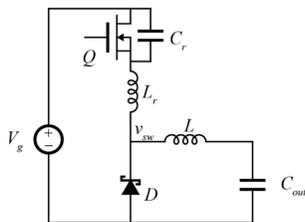


## Simulation Results: Diode Capacitance

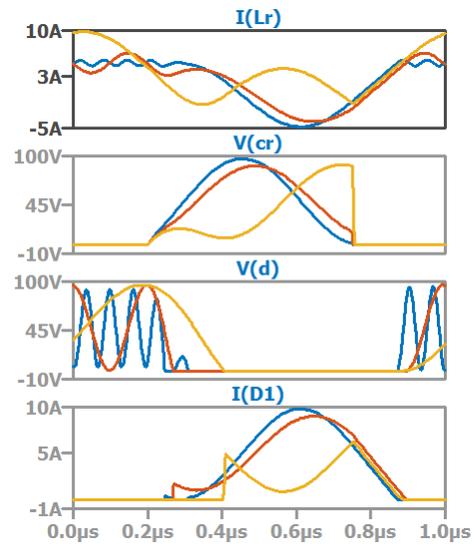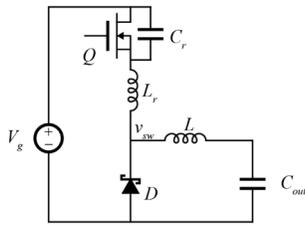

## Wishlist: Multi-Resonant

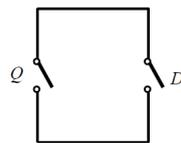

## ZVS-MR Buck

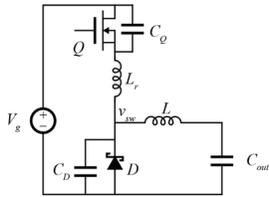

W. A. Tabisz and F. C. Lee, "Zero-voltage-switching multi-resonant technique—a novel approach to improve performance of high frequency quasi-resonant converters," *Power Electronics Specialists Conference, 1988*.

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE



THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE

