

## State Plane Solution: Averaging Step

$$\langle i_{out} \rangle_{T_s} = I_{out} = \langle i_c \rangle_{T_s} = \frac{1}{T_s} \int_0^{T_s} i_c dt$$

$$I_{out} = \frac{1}{T_s} \left[ \int_0^{t_1} i_c dt + \int_{t_1}^{t_2} i_c dt + \dots \right]$$

$$\left(\frac{1}{T_s}\right) I_{out} = \frac{1}{T_s} \left[ \frac{I_1 - I_u}{2} t_1 + \cancel{g_c} + \frac{I_2 - I_3}{2} t_3 + \cancel{g_c} \right] \left(\frac{1}{T_s}\right)$$

(1)                      (2)                      (3)                      (4)

$$S_{out} = \left(\frac{1}{T_s}\right) \frac{1}{T_s} \left[ \frac{J_1 - J_u}{2} t_1 + \frac{J_2 - J_3}{2} t_3 \right] (\omega)$$

$$S_{out} = \frac{F}{2\pi} \left[ \frac{J_1 - J_u}{2} \theta_1 + \frac{J_2 - J_3}{2} \theta_3 \right]$$

## Normalized Period

$$T_s = t_1 + t_2 + t_3 + t_4$$

$$\text{Define } F = \frac{f_s}{f_0}$$

$$\omega_0 T_s = \theta_1 + \alpha + \theta_3 + \beta$$



$$\frac{2\pi f_0}{f_s} = \left[ \frac{2\pi}{F} = \theta_1 + \alpha + \theta_3 + \beta \right]$$

8 total equations

Unknowns:

$\theta_1, \theta_3, \alpha, \beta$

$J_1, J_2, J_3, J_u, I_{out}$

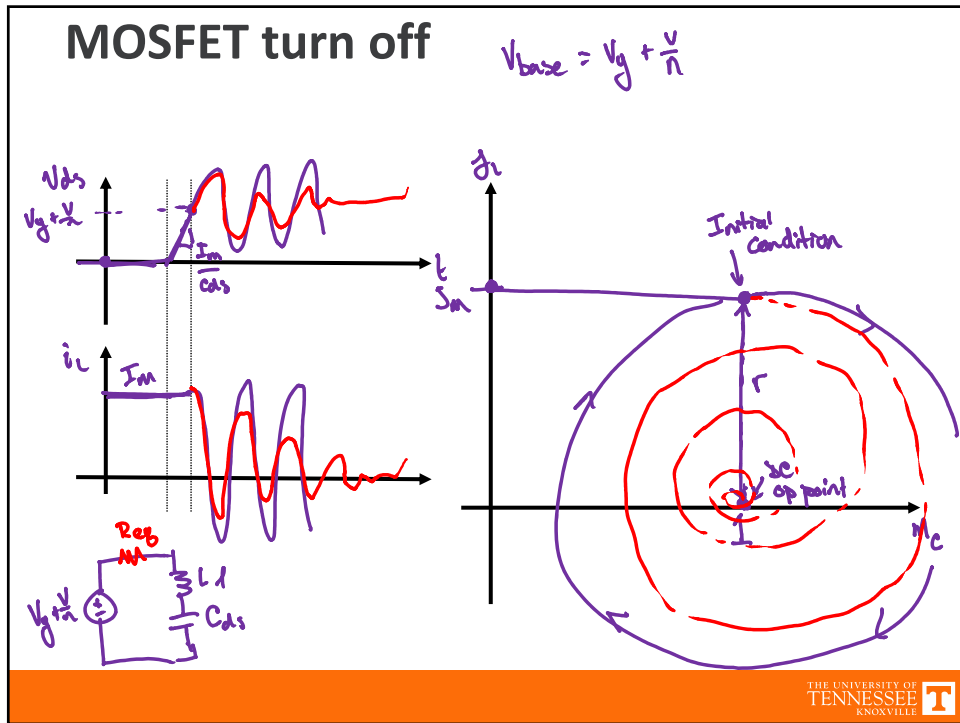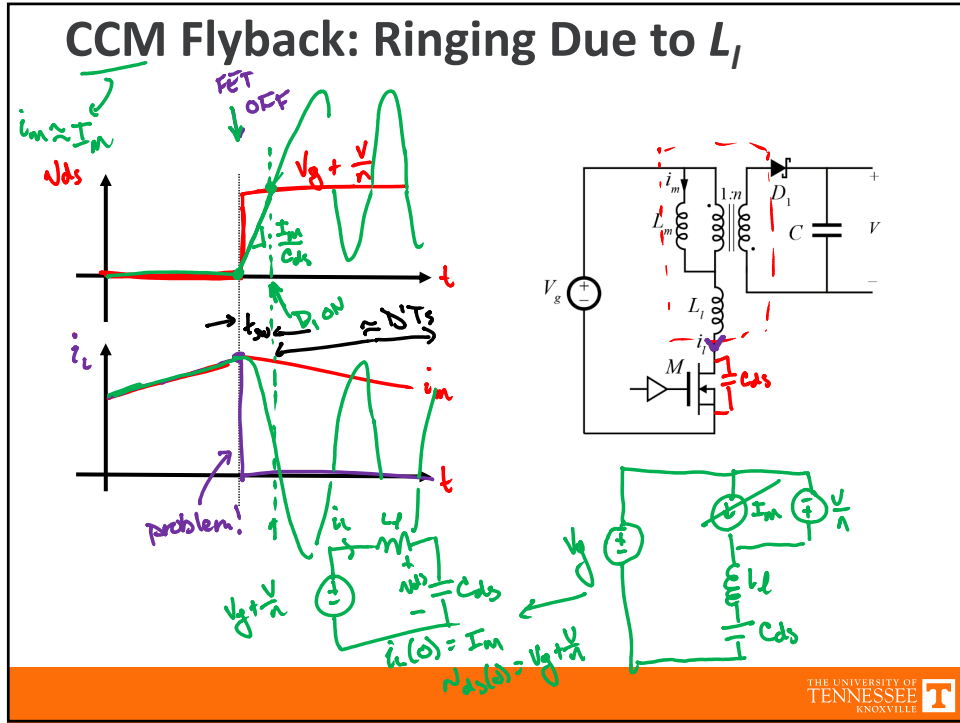

## Leakage Voltage Stress

$$m_{\text{c,ptk}} = 1 + r = 1 + \beta_M$$

$$V_{\text{c,ptk}} = V_{\text{base}} + \beta_M V_{\text{base}}$$

$$V_{\text{c,ptk}} = \left( V_g + \frac{V}{n} \right) + I_M R_o$$

example

$$V_g = 400V$$

$$V = 10V$$

$$P = 100W$$

$$f_s = 1\text{MHz}$$

$$D = 0.5 \quad n = \frac{1}{40}$$

$$C_{ds} = 100\text{pF}$$

$$L_M = 1.8\text{mH}$$

$$L_f = 35\mu\text{H}$$

$$(2\% \text{ of } L_M)$$

$$R_o > \sqrt{\frac{L_f}{C}} = 600\Omega$$

$$\left( \beta_M = \frac{I_M}{I_{\text{base}}} = \frac{I_M R_o}{V_{\text{base}}} \right)$$

$$I_M = \frac{n I_{\text{out}}}{D} = 500\text{mA}$$

$$V_{\text{base}} = V_g + \frac{V}{n} = 800V$$

$$V_{\text{c,ptk}} = 800V + (.5A) 600\Omega$$

$$= \underline{\underline{1100V!}}$$

## Leakage Switching Loss

Assume ringing damps out before the end of  $D \cdot T_s$

$$E_{\text{start}} = \frac{1}{2} L_f I_M^2 + \frac{1}{2} C_{ds} \left( V_g + \frac{V}{n} \right)^2$$



$$E_{\text{end}} = \frac{1}{2} C_{ds} \left( V_g + \frac{V}{n} \right)^2$$

$$E_{\text{loss}} = E_{\text{start}} - E_{\text{end}} = \frac{1}{2} L_f I_M^2$$

$$E_{\text{loss}} = \frac{1}{2} (35\mu\text{H}) (.5\text{A})^2 = 4.4\mu\text{J}$$

$$\text{@ } 1\text{MHz} \quad P_{\text{loss}} = 4.4\text{W}$$

## CCM Flyback: Clamping Circuit

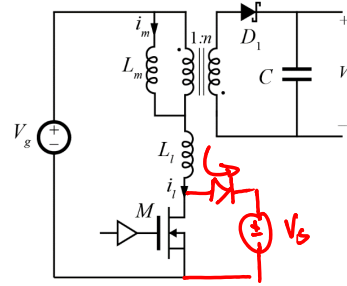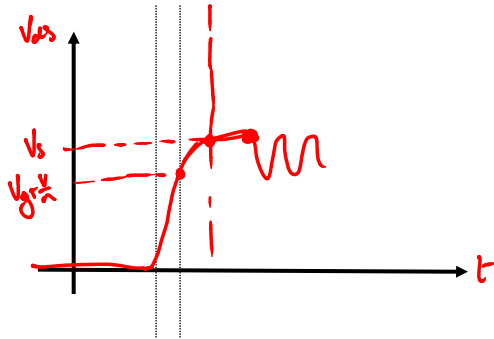

$$V_g + \frac{V}{n} < V_s < V_{ds,max}$$