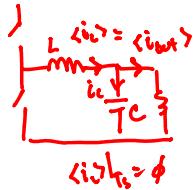



Active Clamp Flyback

Buck:



Capacitor Charge Balance

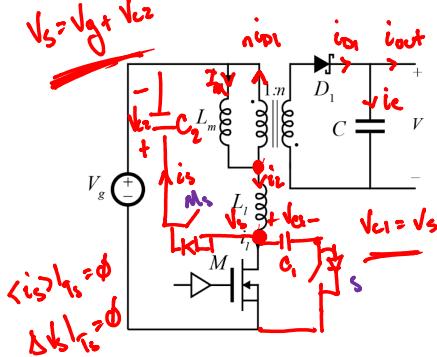
$L_m, C_1, C_S \rightarrow$ larger filter elements



THE UNIVERSITY OF
TENNESSEE KNOXVILLE


Active Clamping

$$V_{base} = V_g + \frac{V}{n}$$

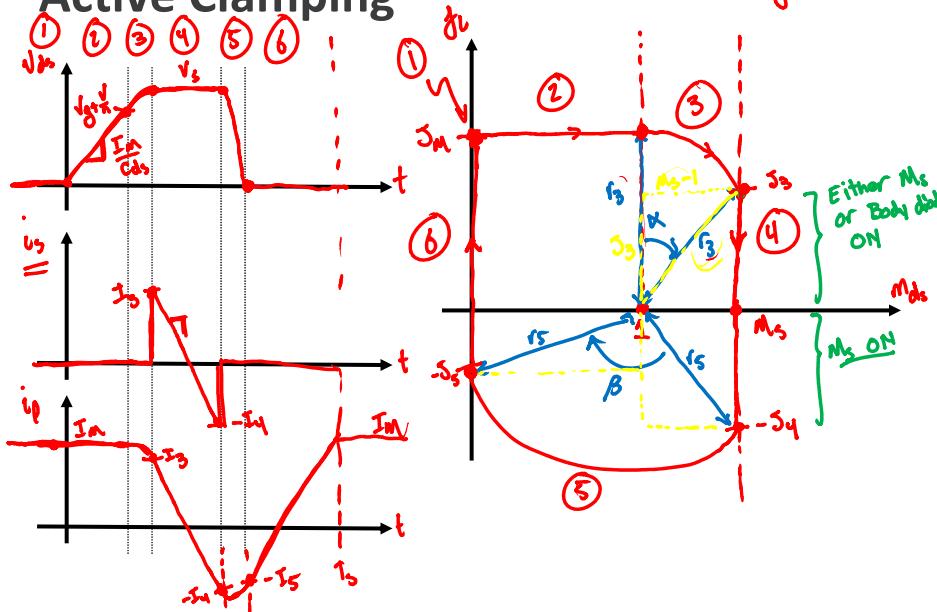

THE UNIVERSITY OF
TENNESSEE KNOXVILLE

Subinterval Equivalent Circuits

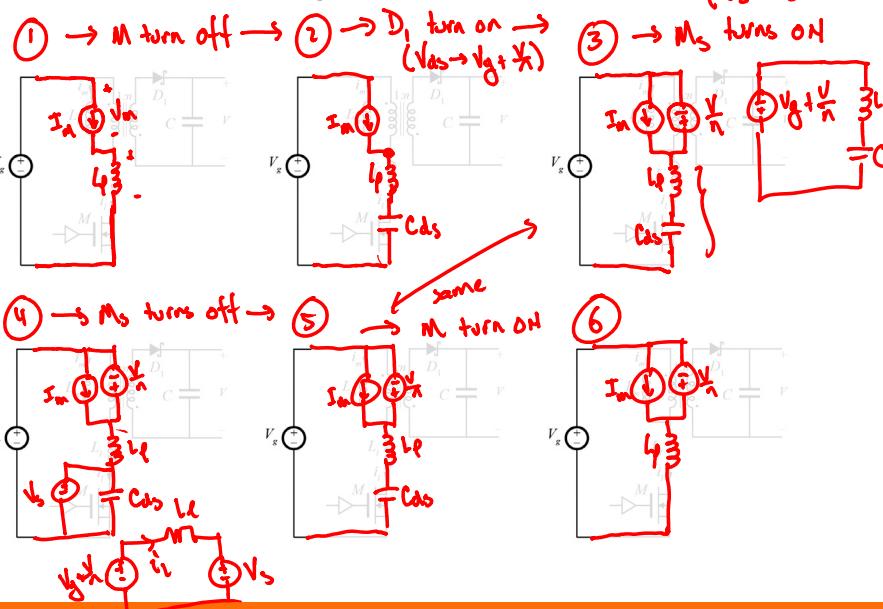

THE UNIVERSITY OF
TENNESSEE 

ZVS Conditions

③ M_s turn-on ZVS condition

$$S_m \geq M_s - 1$$

⑤ M turn-on ZVS condition

$$r_5 \geq 1$$

THE UNIVERSITY OF
TENNESSEE 

Analysis: Intervals 1-3

① Nothing yet

$$\textcircled{2} \quad \left(\frac{1}{I_{\text{base}}}\right) \frac{J_m}{C_{\text{as}}} t_2 = \sqrt{g + \frac{V}{n}} \left(\frac{1}{I_{\text{base}}}\right)$$

$$\frac{J_m}{C_{\text{as}}} t_2 = 1 R_o$$

$$J_m t_2 = \sqrt{\frac{I_2}{C_{\text{as}}}} C_{\text{as}} = \sqrt{4 C_{\text{as}}} = \frac{1}{\omega_0} \rightarrow \boxed{\theta_2 = \frac{1}{J_m}}$$

$$\textcircled{3} \quad \boxed{\alpha = \tan^{-1} \left(\frac{(m_s - 1)}{J_3} \right)}$$

$$r_3^2 = J_m^2 = (m_s - 1)^2 + J_3^2$$



Analysis: Interval 4

$$\textcircled{4} \quad \frac{\sqrt{g + \frac{V}{n}}}{I_p} t_4 = I_3 + I_4$$

$$\boxed{J_3 + J_4 = (m_s - 1) \theta_4}$$



Analysis: Interval 5-6

$$\textcircled{5} \quad r_5^2 = \frac{(m_5-1)^2 + 3_4^2}{3_1^2} = 1 + 3_5^2$$

$$\beta = \tan^{-1}\left(\frac{m_5-1}{3_1}\right) + \tan^{-1}\left(\frac{1}{3_5}\right)$$

$$\textcircled{6} \quad \frac{V_g + \frac{V}{n}}{I_p} t_6 = I_5 + I_m$$

$$\theta_6 = 3_5 + 3_m$$


$$\frac{2\pi}{P} = \theta_1 + \theta_2 + \alpha + \theta_4 + \beta + \theta_6$$

THE UNIVERSITY OF
TENNESSEE 
KNOXVILLE

Analysis: Averaging Cs and Lm

~~Cap or current balance~~
 $i_3 > i_5 \rightarrow I_3 = I_4 \quad \text{or} \quad \underline{\underline{3_3 = 3_4}}$

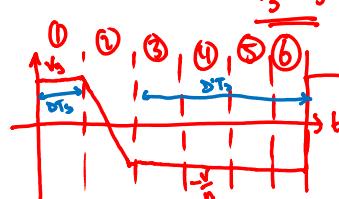~~Volt-second balance on Lm~~
 $\langle N_m \rangle_{t_5} = \phi$



$\langle N_m \rangle_{t_5} = \phi = \frac{1}{t_5} \left[V_g t_1 + \frac{V_g - V}{2} t_2 + -\frac{V}{n} (t_3 + t_4 + t_5 + t_6) \right]$

$\phi = \frac{1}{t_5} \left[V_g (t_1 + \frac{t_2}{2}) - \frac{V}{n} (\frac{t_2}{2} + t_3 + t_4 + t_5 + t_6) \right]$

Conversion ratio

 $\frac{1}{nVg} = \frac{t_1 + \frac{t_2}{2}}{t_2 + t_3 + t_4 + t_5 + t_6} \stackrel{\omega_2}{=} \frac{\theta_1 + \frac{\theta_2}{2}}{\theta_2 + \alpha + \theta_4 + \beta + \theta_6} \approx \frac{\theta_1}{\theta_2}$

THE UNIVERSITY OF
TENNESSEE 
KNOXVILLE

Analysis: Averaging I_{out}

$$n_{i_{out}} = I_m - i_c$$

$$\langle n_{i_{out}} \rangle_{t_0} = n_{i_{out}} = I_m - \langle i_c \rangle$$

$$n_{i_{out}} = \frac{1}{T_s} \left[\int_0^{T_s} n_{i_{out}} dt \right]$$


$$= \frac{1}{T_s} [g_3 + g_4 + g_5 + g_6]$$

$$g_3 = I_m t_3 - C_{ds} (V_s - V_g - \frac{V_s}{2})$$

$$g_4 = I_m t_4$$

$$g_5 = I_m t_5 + C_{ds} (V_s)$$

$$g_6 = \frac{I_m + I_s}{2} t_6$$

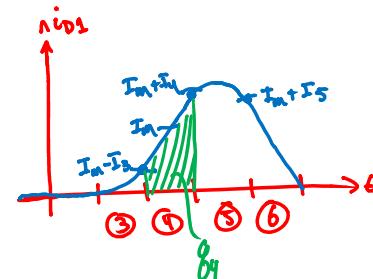

$$J = \frac{n_{i_{out}}}{I_{base}} =$$

$$S = J_m \frac{1}{T_s} \left(K_r \beta + \alpha_1 + \frac{\alpha_2}{2} \right) + \frac{E}{2\pi} + \frac{\partial E}{2\pi} \frac{\partial \beta}{2}$$

THE UNIVERSITY OF
TENNESSEE 
KNOXVILLE