
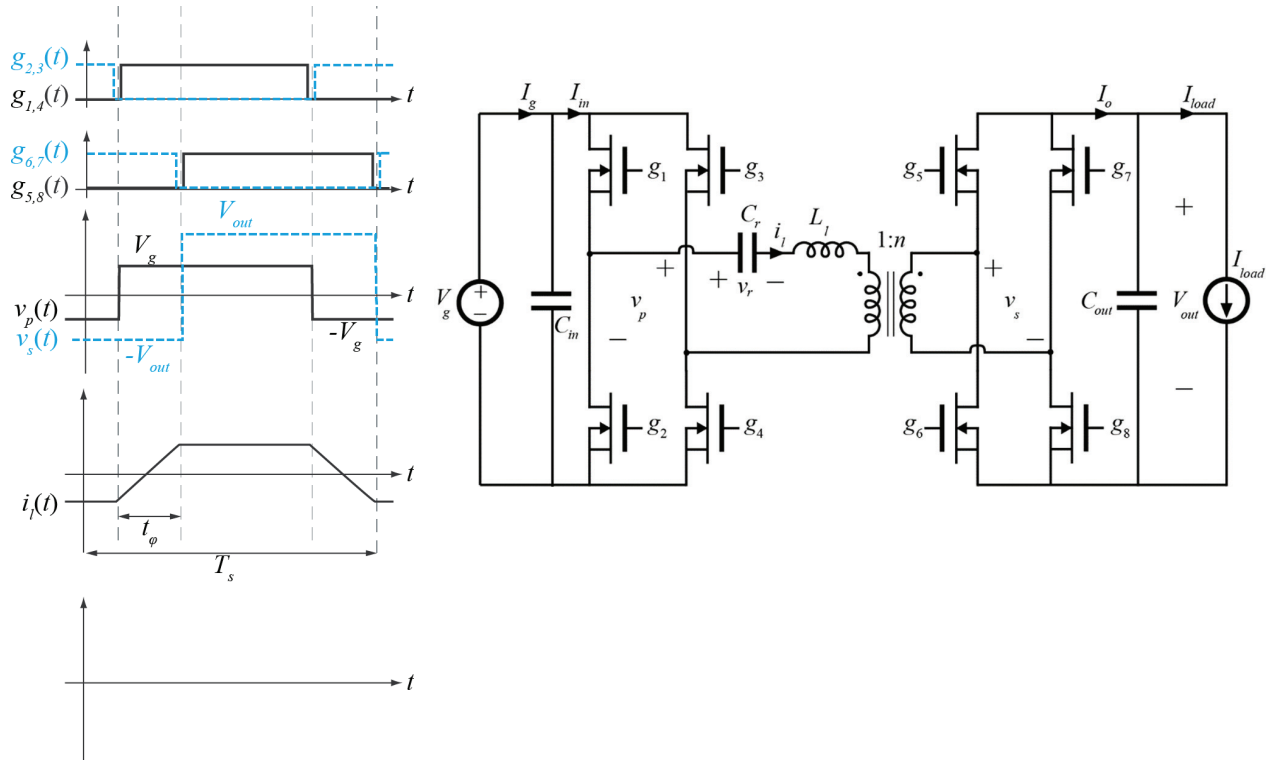



DAB: Transformer Saturation

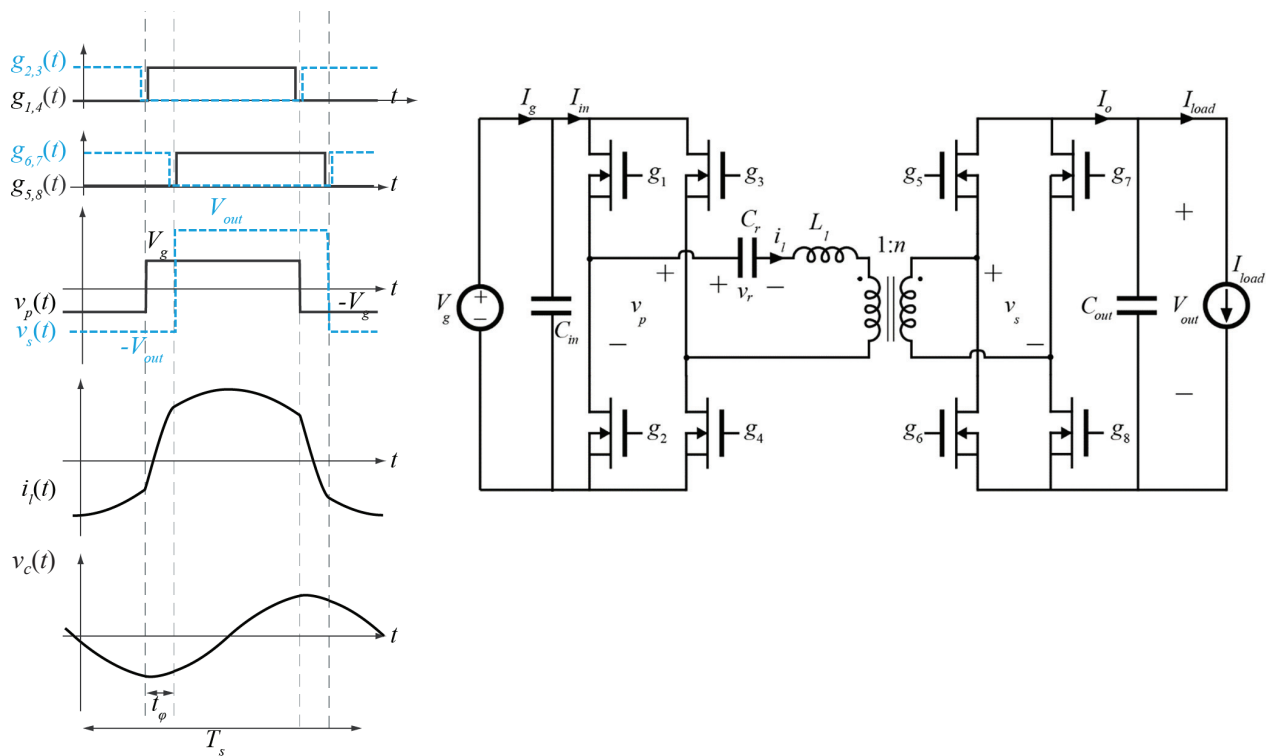


Series Resonant Converter



DAB vs SRC

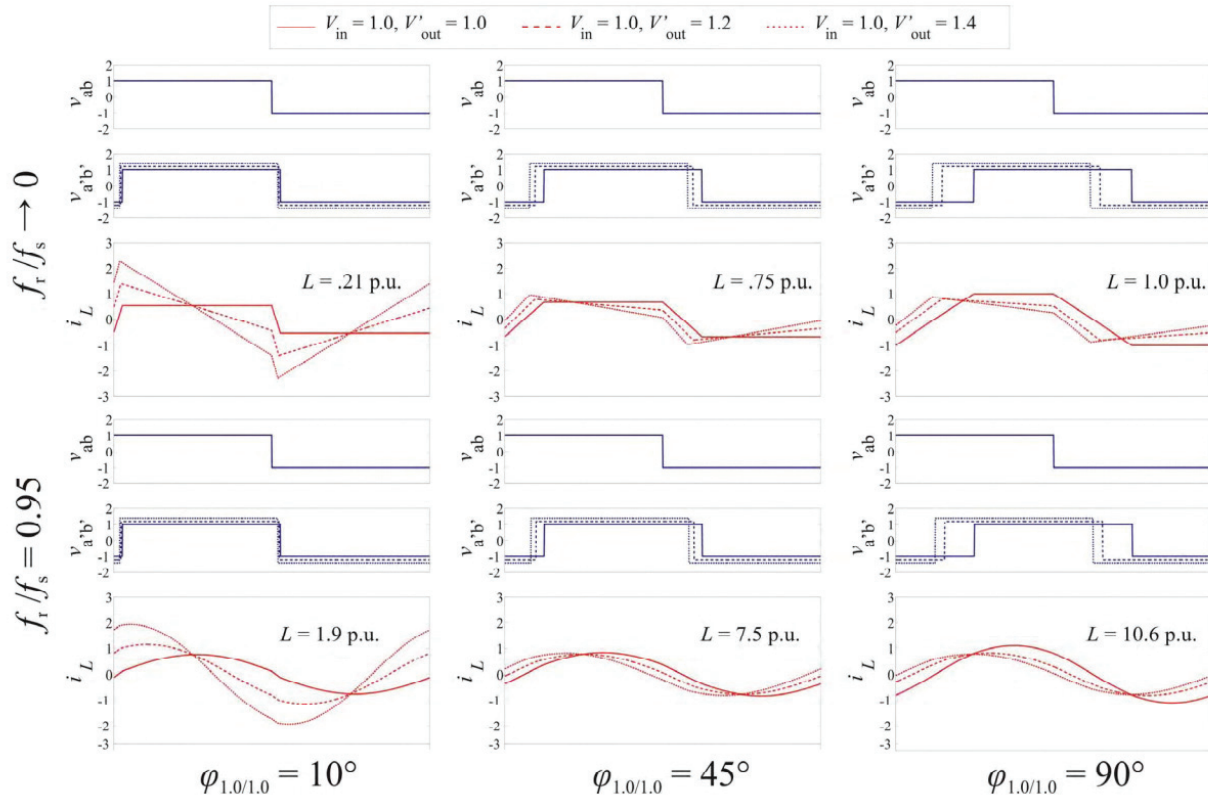

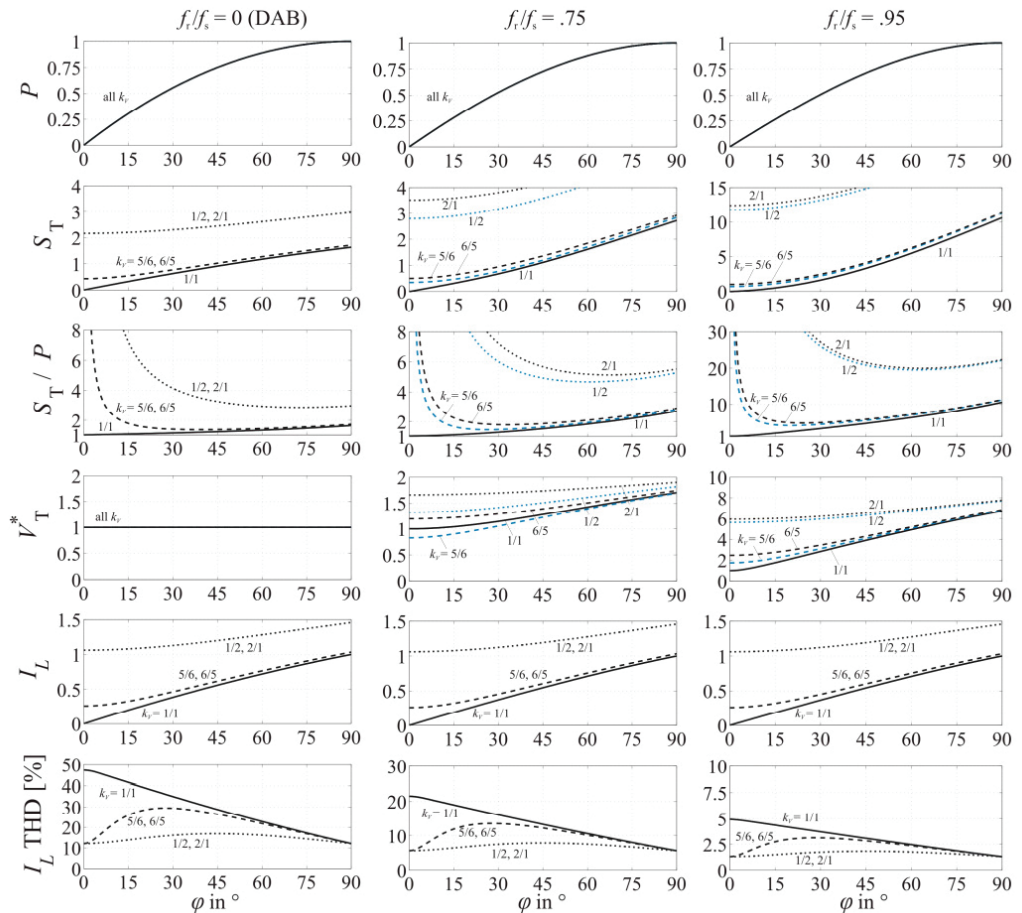R. Lenke, F. Mura and R. W. De Doncker, "Comparison of non-resonant and super-resonant dual-active ZVS-operated high-power DC-DC converters,"



R. Lenke, F. Mura and R. W. De Doncker, "Comparison of non-resonant and super-resonant dual-active ZVS-operated high-power DC-DC converters,"

DAB vs SRC: Conclusions

DAB



- + Smaller resonant tank
- + Smaller RMS currents
- + Wider Soft-switching range

SRC


- + Can be designed with larger XF inductance
- + Lower AC winding losses
- + Reduced device turn-off losses

R. Lenke, F. Mura and R. W. De Doncker, "Comparison of non-resonant and super-resonant dual-active ZVS-operated high-power DC-DC converters,"

Subinterval Equivalent Circuits

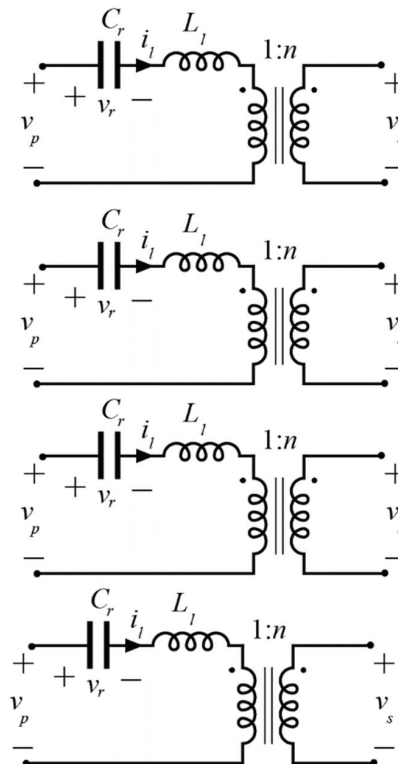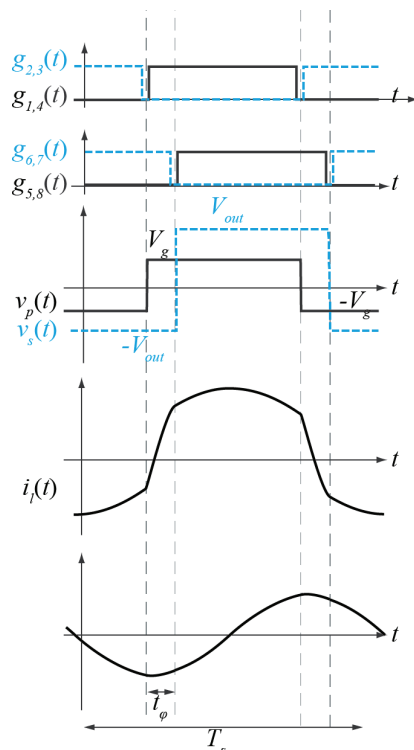

 Complete State Plane – Phase Shift Modulation



State Plane Solution

Averaging Step