
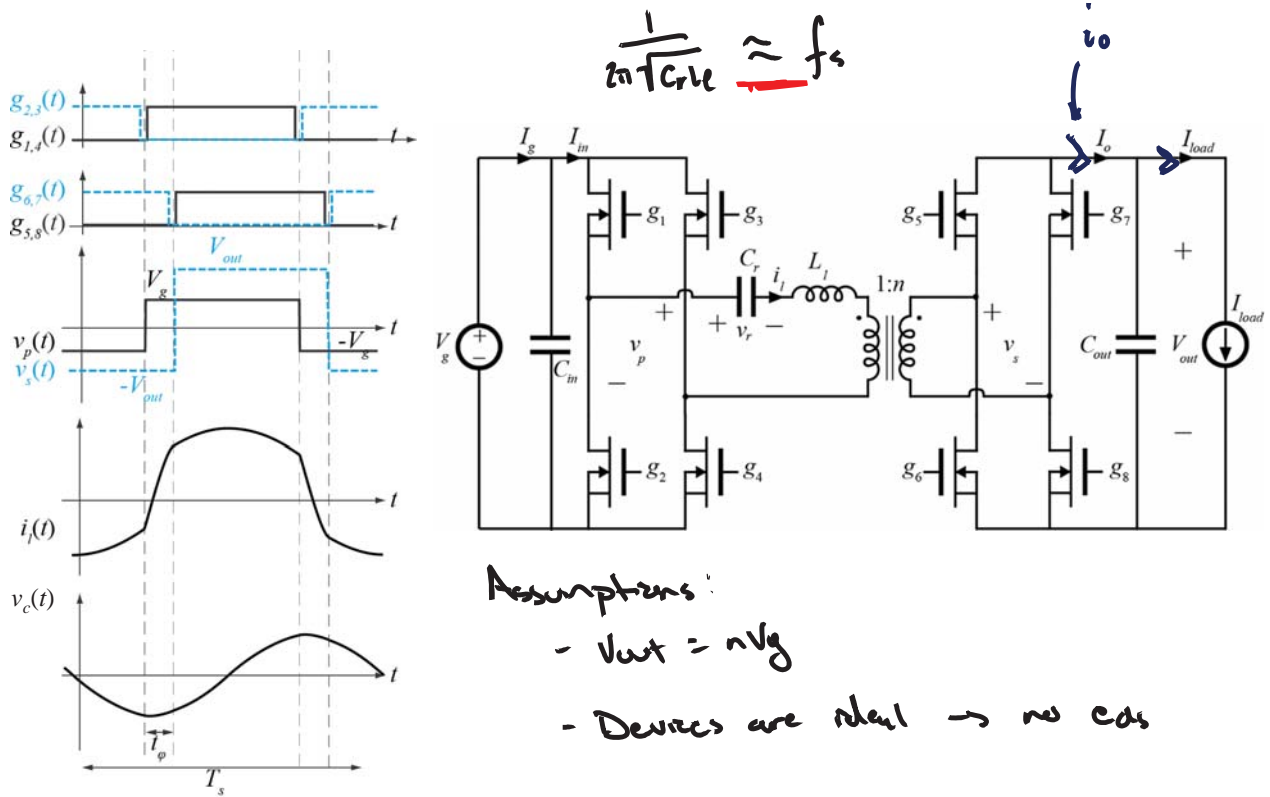


Series Resonant Converter

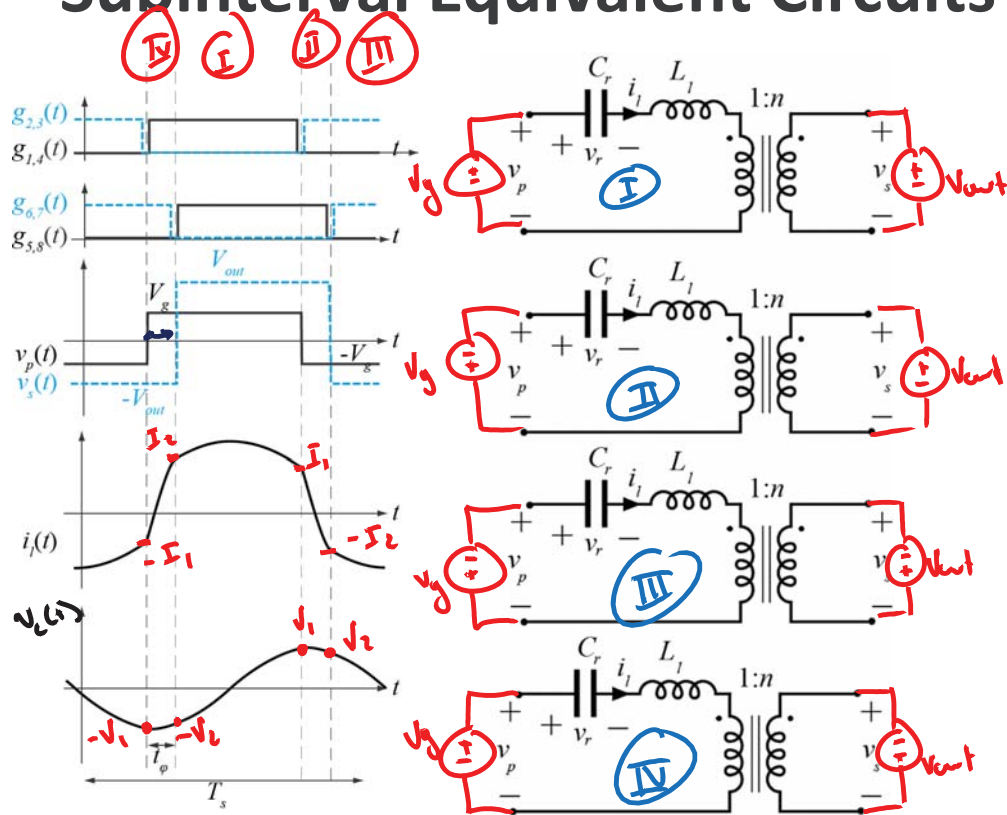

Subinterval Equivalent Circuits



$V_{insec} = V_g$

DC solution

$$M_{DC} = \frac{V_g - \frac{V_{out}}{n}}{V_{insec}} > 0$$

$$S_{DC} = \phi$$

$$M_{DC} = -V_g \frac{-V_{out}}{n} = -2$$

$$S_{DC} = \phi$$


$$M_{DC} = -V_g - \left(\frac{-V_{out}}{n}\right) = \phi$$

$$S_{DC} = \phi$$

$$M_{DC} = V_g - \left(\frac{-V_{out}}{n}\right) = 2$$

$$S_{DC} = \phi$$

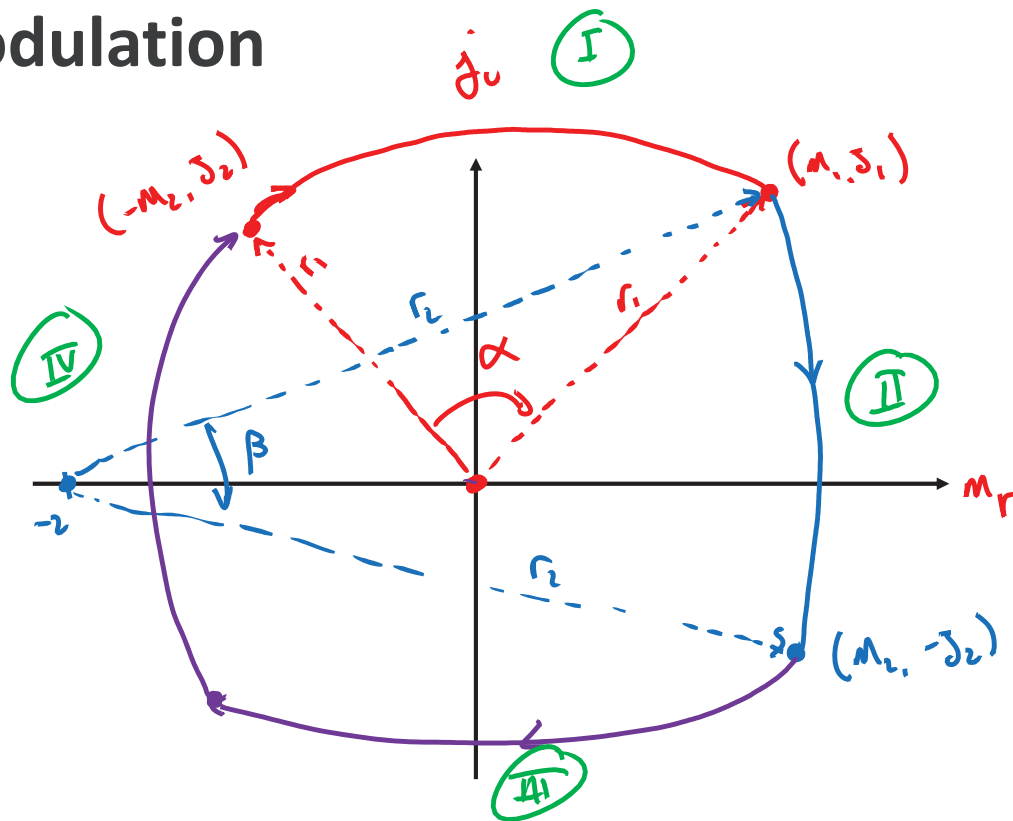Complete State Plane – Phase Shift Modulation



State Plane Solution

I $r_1^2 = m_2^2 + \omega_2^2 = m_1^2 + \omega_1^2$
 $\alpha = \tan^{-1}\left(\frac{m_2}{\omega_2}\right) + \tan^{-1}\left(\frac{m_1}{\omega_1}\right)$

II $r_2^2 = (2+m_1)^2 + \omega_1^2 = (2+m_2)^2 + \omega_2^2$
 $\beta = \tan^{-1}\left(\frac{\omega_1}{2+m_1}\right) + \tan^{-1}\left(\frac{\omega_2}{2+m_2}\right)$

$\frac{\pi}{F} = \alpha + \beta$

$$m_1^2 + \omega_1^2 = m_2^2 + \omega_2^2$$

$$-4 + m_1^2 + 4m_1 + \omega_1^2 = 4 + m_2^2 + 4m_2 + \omega_2^2$$

$$-4 - 4m_1 = -4 - 4m_2$$


$$\boxed{m_1 = m_2} \quad \& \quad \omega_1 = \omega_2$$

Averaging Step

$$n \langle i_{out} \rangle = \frac{2}{T_s} \int_0^{T_s/2} i_c(t) dt$$

$$= \frac{2}{T_s} [\theta_1 + \theta_2]$$
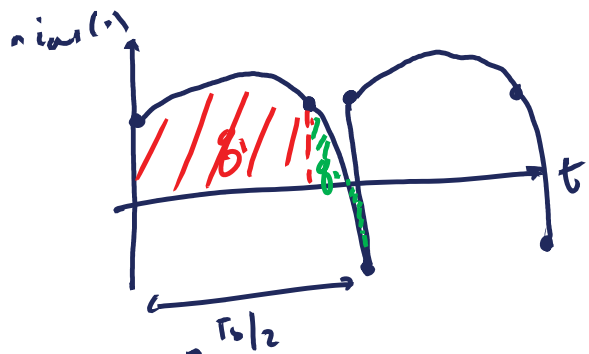
$$= \frac{2}{T_s} \left[C_r(V_1 + V_2) + C_r(V_1 - V_2) \right]$$



$$n \langle i_{out} \rangle = \frac{2}{T_s} 2 C_r V_1$$

$$\mathcal{J} = \frac{n \langle i_{out} \rangle}{E_{base}} = \frac{2}{T_s} \frac{2 C_r V_1}{V_g} \sqrt{\frac{L}{C_r}} = \boxed{\frac{F}{\pi} 2 M_1 = \mathcal{J}}$$

Complete Solution

$$\mathcal{J} = \frac{F}{\pi} 2 M_1 \rightarrow \frac{\pi}{F} = \alpha + \beta \rightarrow \alpha = 2 \tan^{-1} \left(\frac{M_1}{\mathcal{J}_1} \right)$$

$$\rightarrow \beta = 2 \tan^{-1} \left(\frac{\mathcal{J}_1}{2 + M_1} \right)$$

$$\tan \left(\frac{\alpha}{2} \right) = \frac{M_1}{\mathcal{J}_1}$$

$$\tan \left(\frac{\beta}{2} \right) = \frac{\mathcal{J}_1}{2 + M_1}$$


$$M_1 = \tan \left(\frac{\alpha}{2} \right) \tan \left(\frac{\beta}{2} \right) (2 + M_1)$$

$$M_1 = \frac{2 \tan \left(\frac{\alpha}{2} \right) \tan \left(\frac{\beta}{2} \right)}{1 - \tan \left(\frac{\alpha}{2} \right) \tan \left(\frac{\beta}{2} \right)}$$

$$\mathcal{J} = \frac{F}{\pi} 2 \left(\frac{2 \tan \left(\frac{\pi}{2F} - \frac{\beta}{2} \right) \tan \left(\frac{\beta}{2} \right)}{1 - \tan \left(\frac{\pi}{2F} - \frac{\beta}{2} \right) \tan \left(\frac{\beta}{2} \right)} \right)$$

$$\mathcal{J}_{ph} = r_1 = \sqrt{M_1^2 + \mathcal{J}_1^2}$$

SRC Control Trajectory

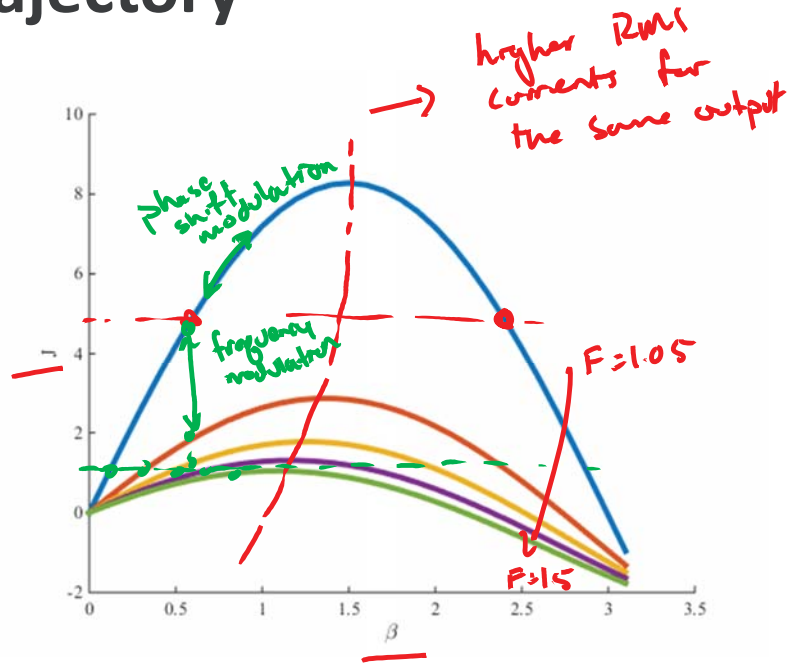

SRC Current Stress

