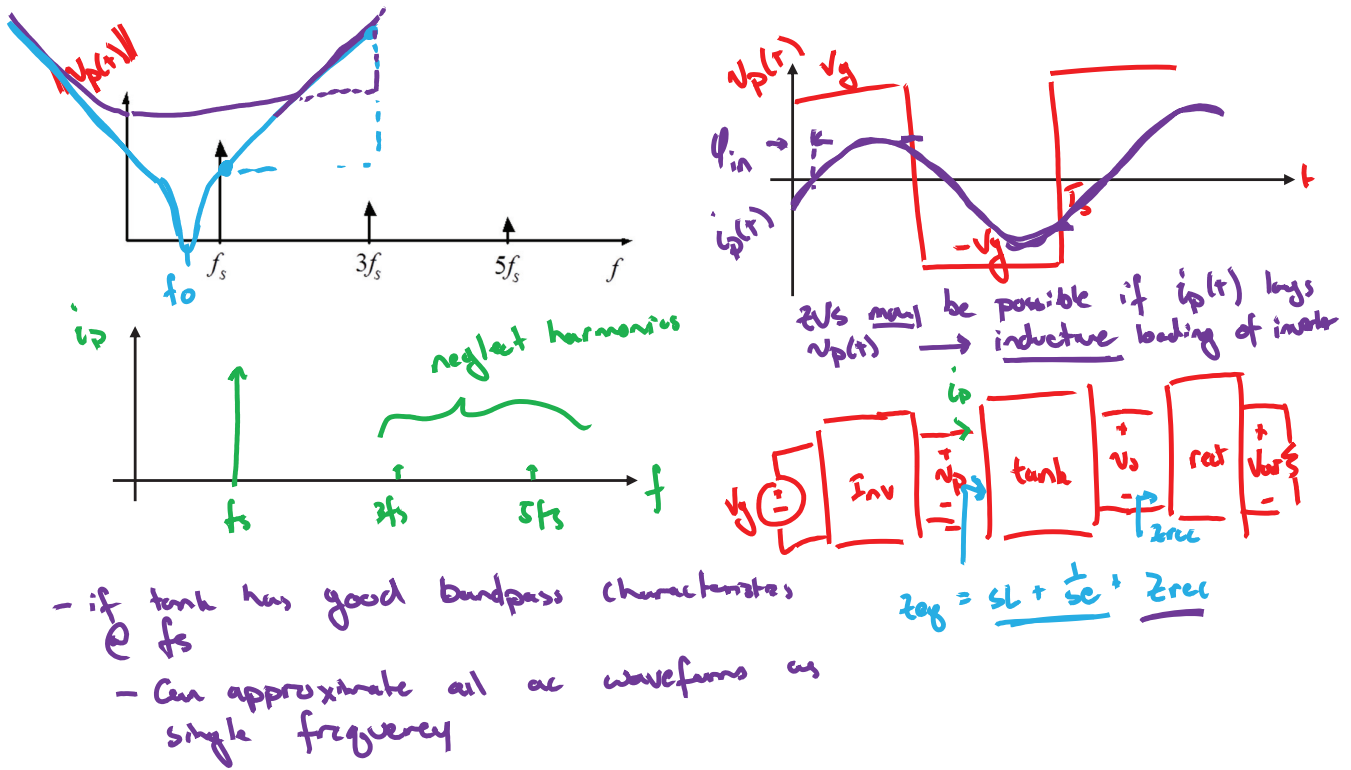


Sinusoidal Analysis (Ch 19)



Sinusoidal Analysis: Comments

- Generally most accurate when operating near resonance with a high Q
- Effective quality factor Q_e depends not only on resonant tank, but also on loading
- Analysis neglects switching intervals; can only predict where ZVS cannot be obtained

exact = state plane analysis
 approx = sinusoidal approx


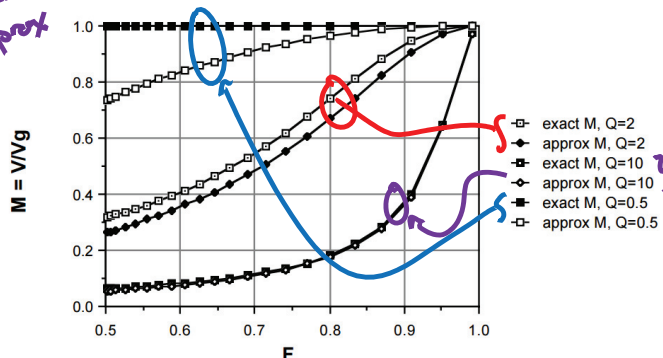


Fig. 2.14. Comparison of exact and approximate series resonant converter characteristics, below resonance.


diode rectifier full bridge

AC Link Waveforms

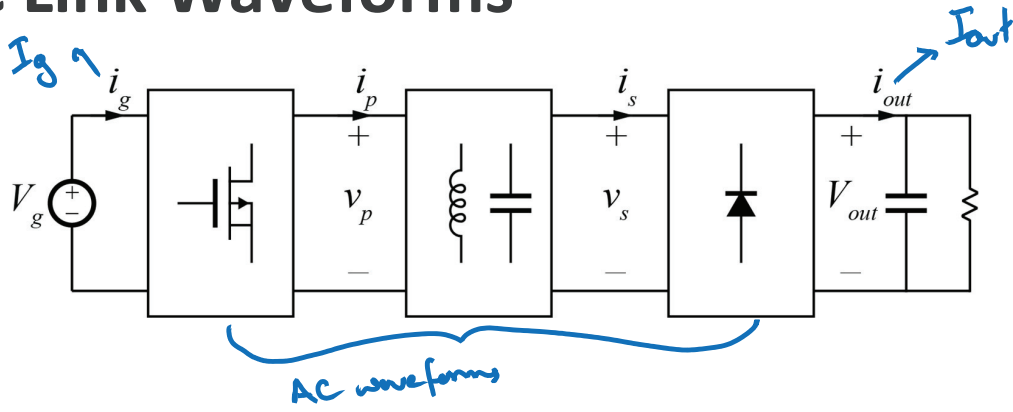

$v_p(t)$ = real signal
 $v_p(t)$ = sinusoidal approximation @ f_s

Switch Network Sinusoidal Analysis

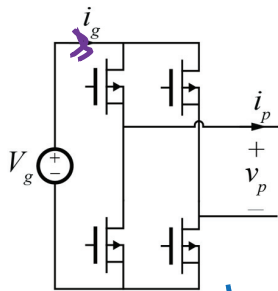

Fourier Series:

$$b_1 = \frac{1}{\pi} \int_{-\pi}^{\pi} f(x) \sin(x) dx$$

Apply to $v_p(t)$:


$$b_1 = \frac{2}{T_s} \int_0^{T_s} v_p(t) \sin(2\pi f_s t) dt$$

$$b_1 = \frac{2}{T_s} \cdot 2 \cdot \int_0^{T_s/2} V_g \sin(2\pi f_s t) dt$$

$$b_1 = \frac{4}{T_s} V_g \int_0^{\pi} \sin(u) \frac{du}{2\pi f_s}$$

$$b_1 = \frac{4}{T_s} V_g \frac{1}{2\pi f_s} [-\cos(u)]_0^{\pi} = \frac{4}{T_s} V_g \frac{1}{2\pi f_s} (2)$$

$$b_1 = \frac{4}{\pi} V_g$$

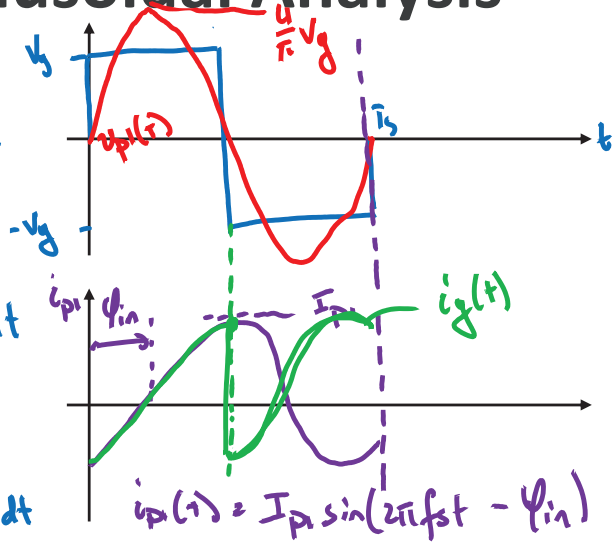

$$i_p(t) = I_p \sin(2\pi f_s t - \phi_{in})$$

Input Current

$$i_{p1}(t) = I_{p1} \sin(2\pi f_s t - \phi_{in})$$

$$\langle i_g \rangle = I_g = \frac{2}{T_s} \int_0^{T_s/2} i_{p1}(t) dt$$

$$= \frac{2}{T_s} \int_0^{T_s/2} I_{p1} \sin(2\pi f_s t - \phi_{in}) dt$$

$$= \frac{2}{T_s} I_{p1} \int_{-\phi_{in}}^{\pi - \phi_{in}} \sin(u) \frac{du}{2\pi f_s}$$


$$= \frac{2}{T_s} I_{p1} \frac{1}{2\pi f_s} \left[-\cos(u) \right]_{-\phi_{in}}^{\pi - \phi_{in}} = \frac{2}{T_s} I_{p1} \frac{1}{2\pi f_s} (\cos(\phi_{in}) + \cos(\phi_{in}))$$

$$u = 2\pi f_s t - \phi_{in}$$

$$du = 2\pi f_s dt$$


$$I_g = \frac{I_{p1}}{\pi} 2 \cos \phi_{in}$$

Switch Network Equivalent Circuit

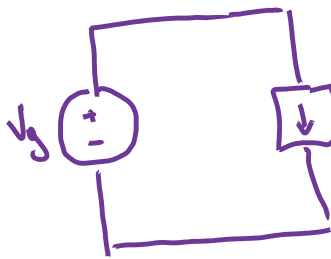

$$I_g = \frac{2}{\pi} I_{p1} \cos \phi_{in}$$

$$\omega_s = 2\pi f_s$$

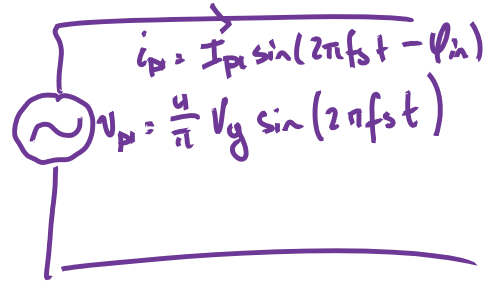

$$i_{p1} = I_{p1} \sin(2\pi f_s t - \phi_{in})$$

$$V_{p1} = \frac{4}{\pi} V_g \sin(2\pi f_s t)$$

$$P_g = V_g I_g = V_g \frac{2}{\pi} I_{p1} \cos \phi_{in} \checkmark$$

use identity

$$\sin(u) \sin(x) = \frac{1}{2} (\cos(u-x) - \cos(u+x))$$

$$\langle P_p \rangle = \frac{4}{\pi} V_g I_{p1} \frac{1}{T_s} \frac{1}{2} \int_0^{T_s} \cos(-\phi_{in}) - \cos(2\omega_s t - \phi_{in}) dt$$

$$= \frac{4}{\pi} V_g I_{p1} \frac{1}{T_s} \frac{1}{2} T_s \cos(\phi_{in}) = \frac{2}{\pi} V_g I_{p1} \cos \phi_{in} \checkmark$$

$$P_p = V_{p1} i_{p1} = \frac{4}{\pi} V_g I_{p1} \sin(\omega_s t) \sin(\omega_s t - \phi_{in})$$

$$\langle P_p \rangle = \frac{1}{T_s} \int_0^{T_s} P_p(t) dt$$