
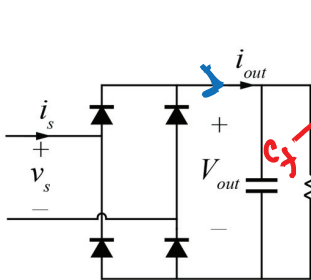


Diode Rectifier Sinusoidal Analysis

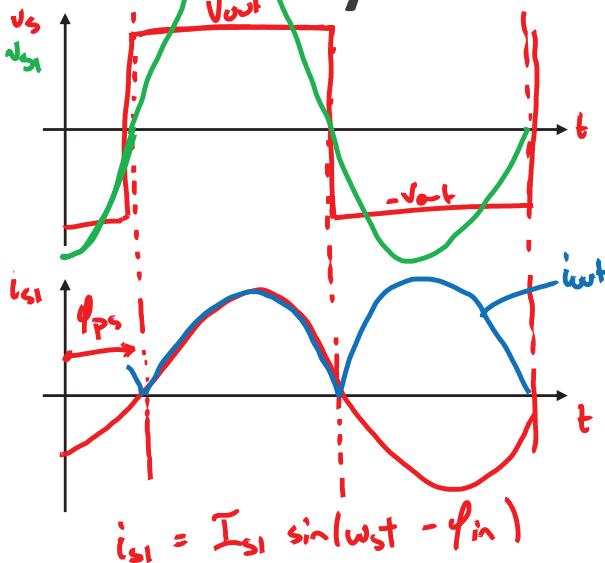

large filter element
 $V_{out} \approx V_{out}$
 Approx diodes as ideal



$$V_{s1} = \frac{4}{\pi} V_{out} \sin(\omega t - \phi_{ps})$$

(same derivation as inverter)



$$\langle i_{out} \rangle = I_{out} = \frac{1}{T} \int_0^T i_{out} dt$$

$$I_{out} = \frac{2}{\pi} I_{s1}$$


$$V_{out} = I_{out} R = \frac{2}{\pi} I_{s1} R \quad , \quad \text{by cap-Q balance on } C_f$$

Diode Rectifier Equivalent Circuit
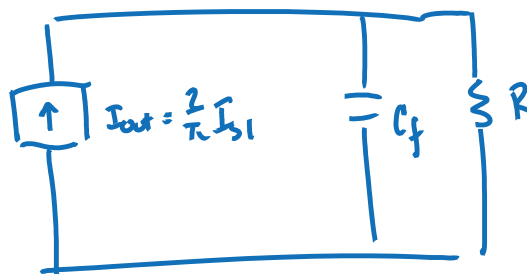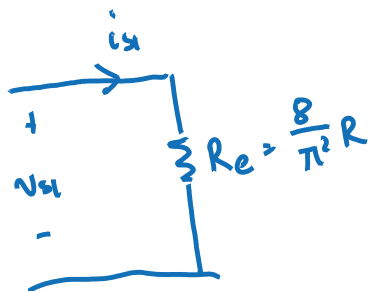
$$\frac{V_{s1}}{i_{s1}} = \frac{\frac{4}{\pi} V_{out} \sin(\omega t - \phi_{ps})}{I_{s1} \sin(\omega t - \phi_{ps})} = \frac{\frac{4}{\pi} (\frac{2}{\pi} I_{s1} R)}{I_{s1}} = \frac{8}{\pi^2} R = R_e$$




Other Implementations

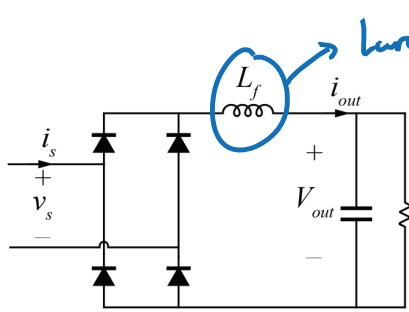


Large filter

Current is a square wave $\pm I_{L_f}$

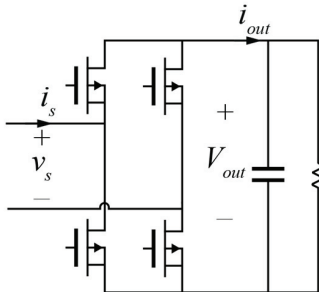

Z_e load \rightarrow can have reactive loading @ f_s

Complete Equivalent Circuit

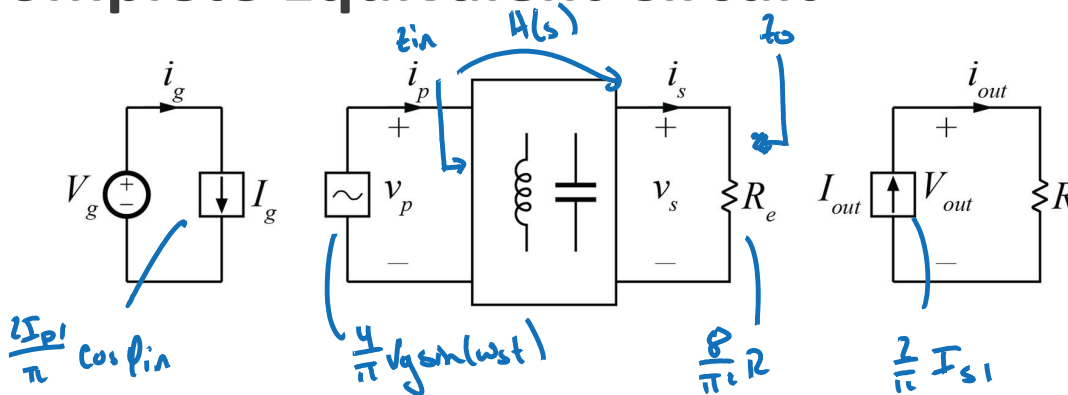

$\phi_{in}, I_{p1}, I_{s1}$ determined by complete circuit



$$M = \frac{V_{out}}{V_g} = \frac{V_{out}}{I_{out}} \cdot \frac{I_{out}}{I_{s1}} \cdot \frac{I_{s1}}{V_{s1}} \cdot \frac{V_{s1}}{V_{p1}} \cdot \frac{V_{p1}}{V_g}$$

$$M = \cancel{R} \cdot \cancel{\frac{2}{\pi}} \cdot \frac{1}{\cancel{\frac{8}{\pi} R}} \cdot \|H(j\omega_s)\| \cdot \cancel{\frac{4}{\pi}}$$

$$M = \frac{V_{out}}{V_g} = \|H(j\omega_s)\|$$


keep in mind $\phi_{in}, H(s), Z_o$ depend on R_e

Output Characteristic

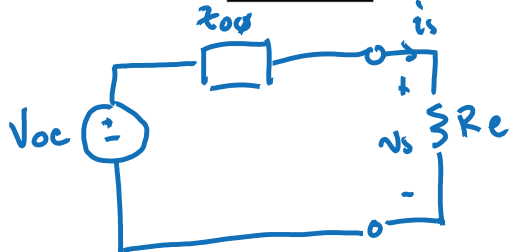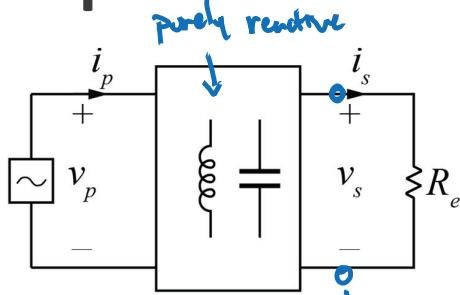

$$v_s = v_o \frac{R_e}{R_e + z_o\phi}$$

$$\|v_s\|^2 = \|v_o\|^2 \cdot \left\| \frac{R_e}{R_e + z_o\phi} \right\|^2$$

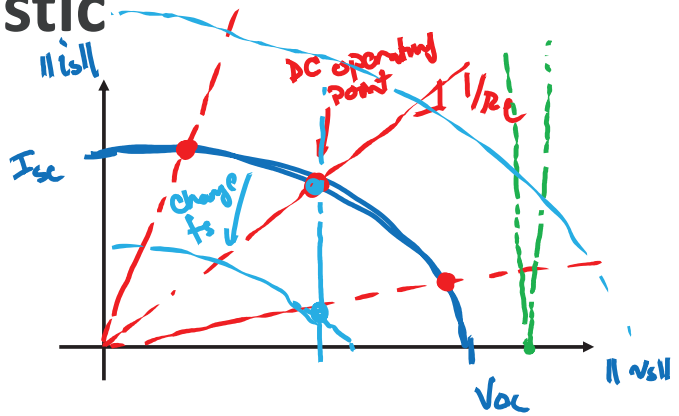

$$\|v_s\|^2 = v_o^2 \cdot \frac{R_e^2}{R_e^2 + \|z_o\phi\|^2}$$

$$\|v_s\|^2 R_e^2 + \|v_s\|^2 \|z_o\phi\|^2 = v_o^2 R_e^2$$

$$\frac{\|v_s\|^2}{v_o^2} + \frac{\|v_s\|^2 \|z_o\phi\|^2}{v_o^2 R_e^2} = 1$$

$$\boxed{\frac{\|v_s\|^2}{v_o^2} + \frac{\|i_s\|^2}{I_{sc}^2} = 1}$$