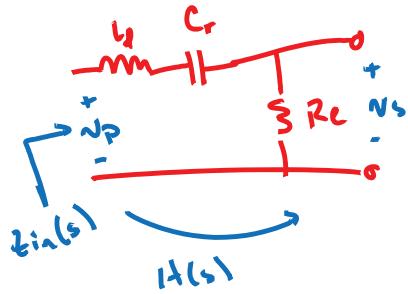


# Construction of Tank Transfer Function

SRC as an example (SRC w/ diode FB rectifier)



$$f_{in}(s) = sL + \frac{1}{sC} + R$$

$$H(s) = \frac{\frac{V_o}{V_p}}{s} = \frac{R_e}{sL_e + \frac{1}{sC_L} + R_e} = \frac{R_e}{Z_{in}(s)}$$

in standard form:

$$A(s) = \frac{s/Q_{ew0}}{\left(\frac{s}{w_0}\right)^2 + \frac{s}{Q_{ew0}} + 1}$$

$$\text{where } \omega_0 = \frac{1}{\sqrt{L_C C_R}}, \quad R_0 = \sqrt{\frac{L}{C}}, \quad Q_C = \frac{R_0}{R_C}$$

$Q_e$  = "effective" / loaded quality factor

$$M = \frac{V}{Q} = \|H(j\omega_s)\| = \frac{1}{\sqrt{1 + Q_e^2 \left(\frac{1}{F} - F\right)^2}}$$

# Tank Input Impedance

## src example

$$f_{in}(s) = sL_1 + \frac{1}{sC} + R_C$$

$$H(s) := \frac{Re}{2\pi i s + b}$$

$$\|\tau_{i,p}\| \rightarrow \|\tau_{i, \text{Re} \rightarrow \phi}\|$$

$$\|z_{i\omega}\| \rightarrow \|z_{\cdot, p_i \rightarrow \omega}\|$$

Sinusoidal approximation valid

- when

  - $\text{Re} \ll \omega$
  - $f_s \approx f_0$

