
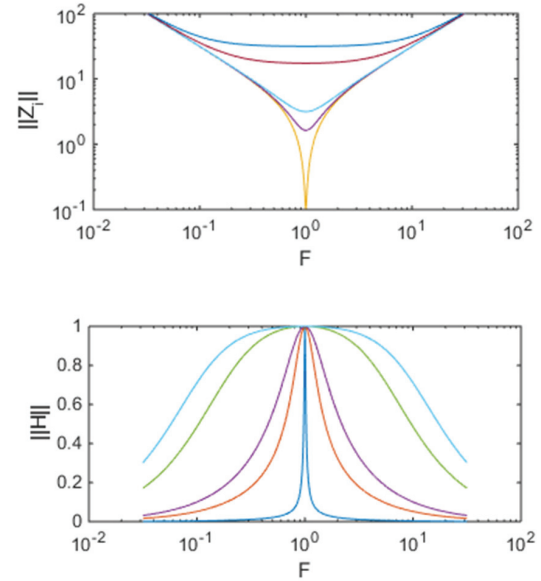


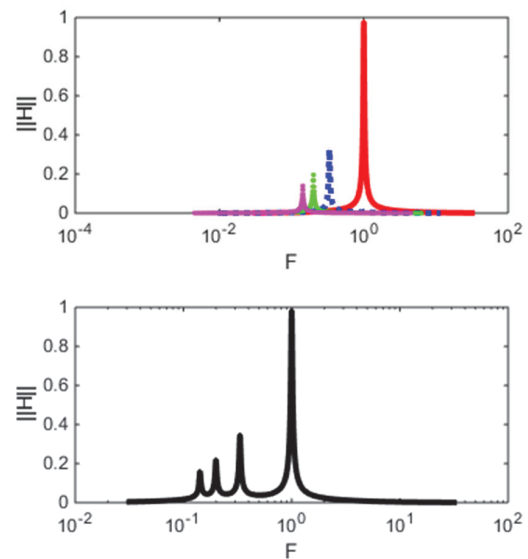
# Series Resonant Tank – Subharmonic Modes




## Subharmonic Modes - High Q




# Subharmonic Modes – Low Q

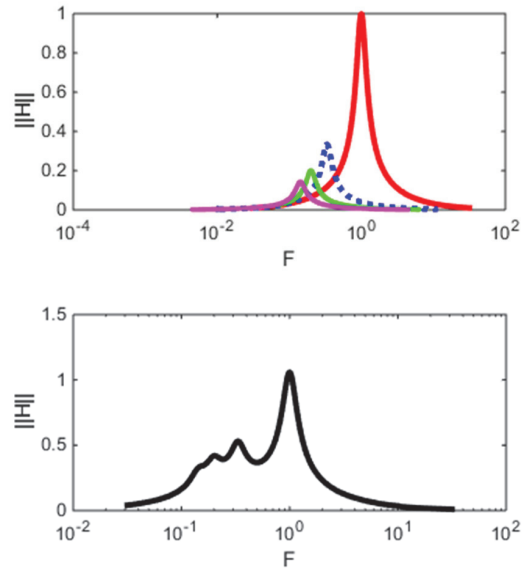


## SRC Control Plane

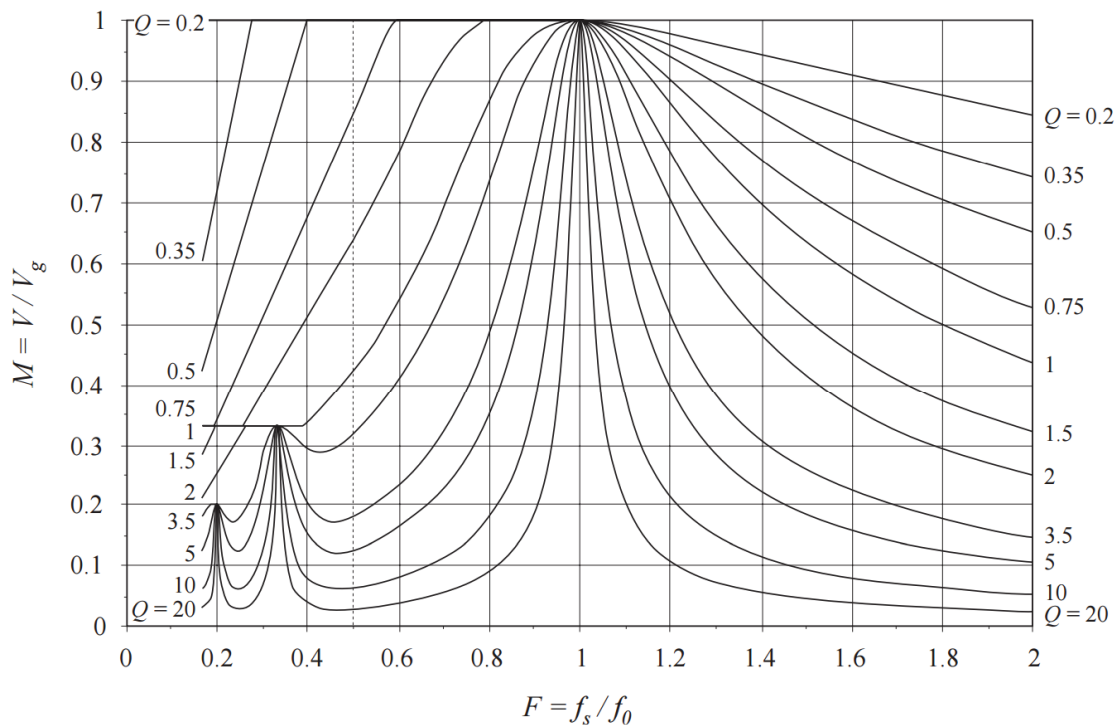






# SRC Mode Boundaries

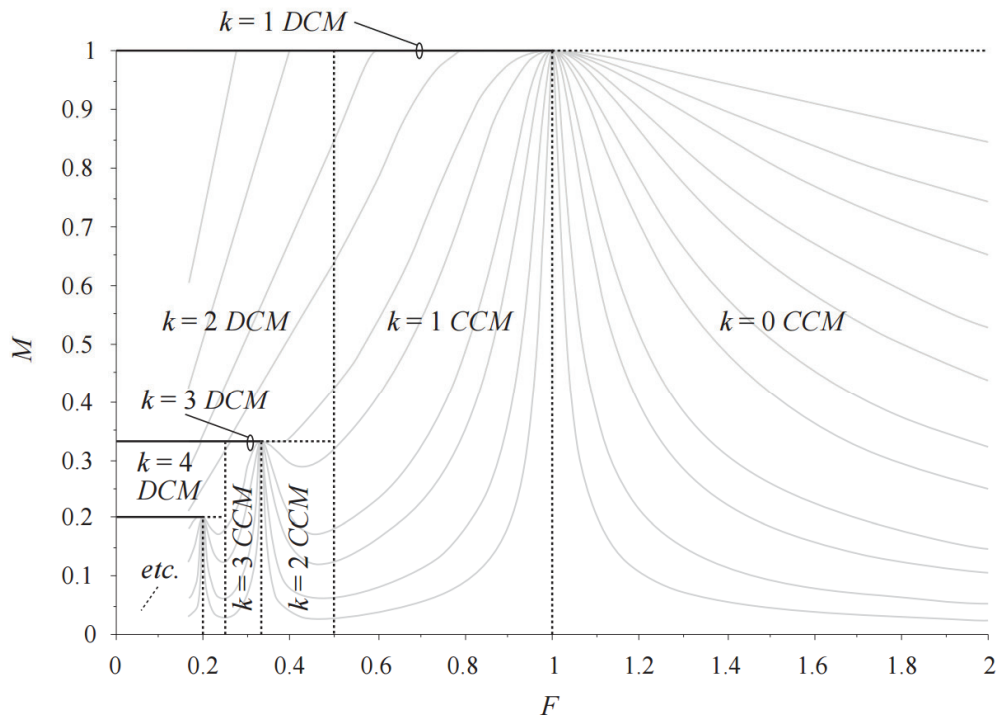


# ZVS Assist Circuits

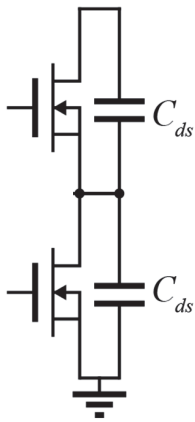


# ZVS Tank Examples

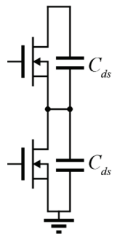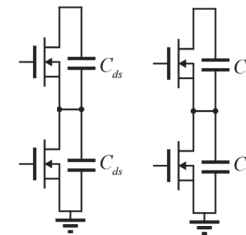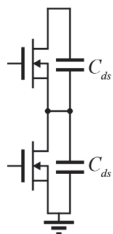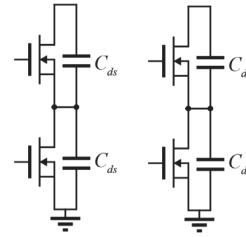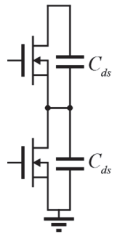

## Remaining Switching Losses

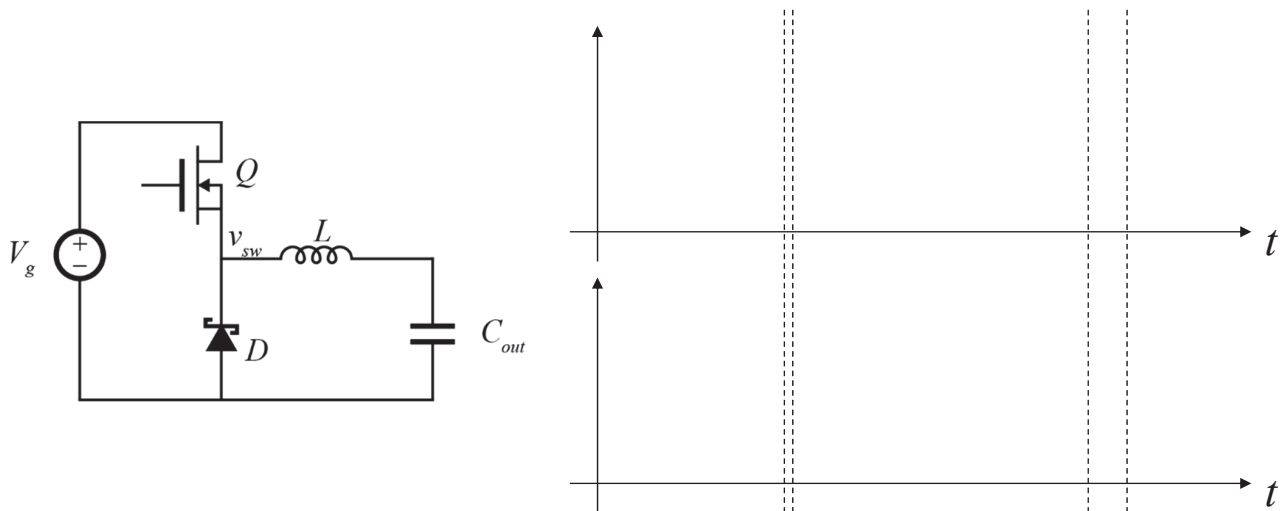

# Idealized Switching Waveforms

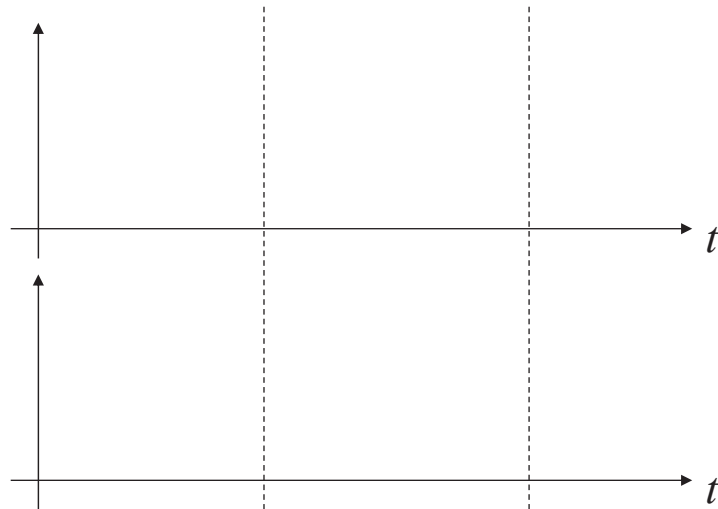

## Class-E Amplifier

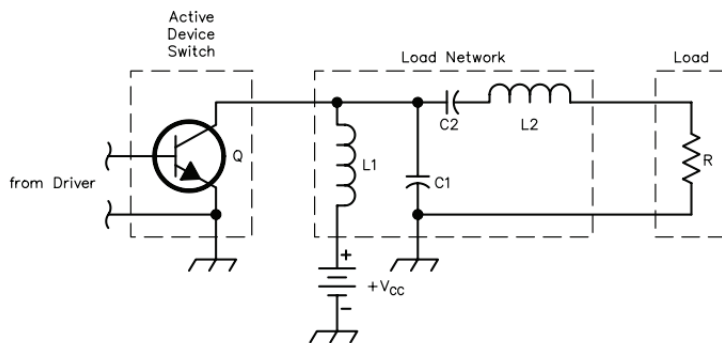


Fig 2—Schematic of a low-order Class-E amplifier.



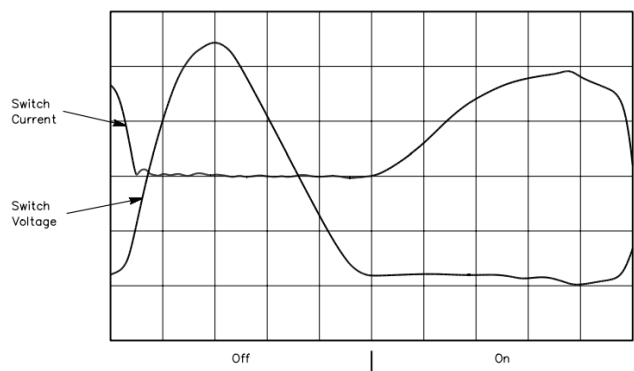
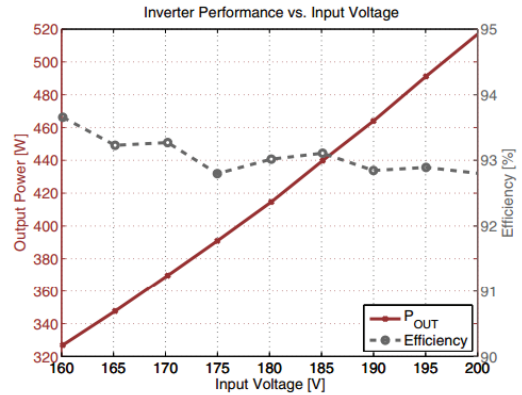


Fig 3—Actual transistor voltage and current waveforms in a low-order Class-E amplifier.


# Class $\Phi_2$ Inverter

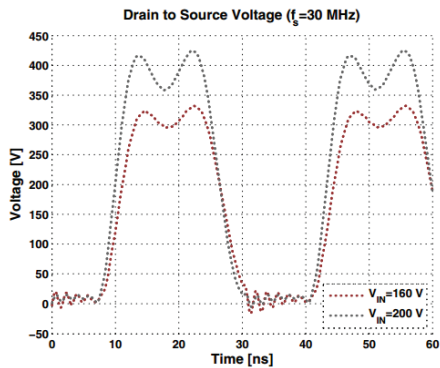

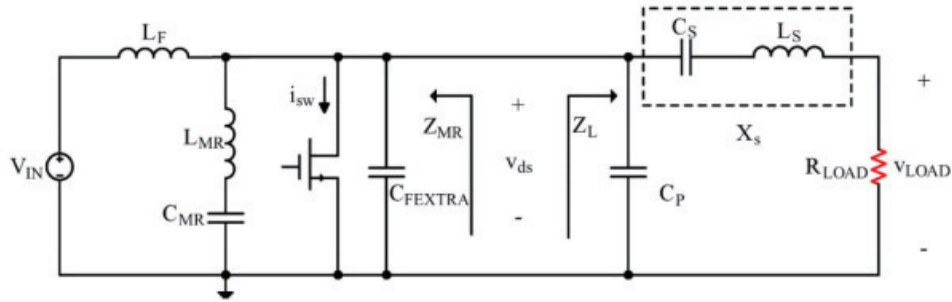J. M. Rivas, O. Leitemann, Y. Han, A. D. Sagneri, and D. J. Perreault, "A High-Frequency Resonant Inverter Topology With Low-Voltage Stress", 2008



# VHF DC-DC Converter

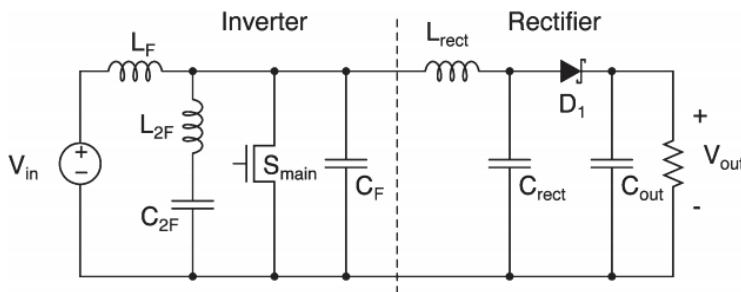

# $\Phi_2$ Boost Converter


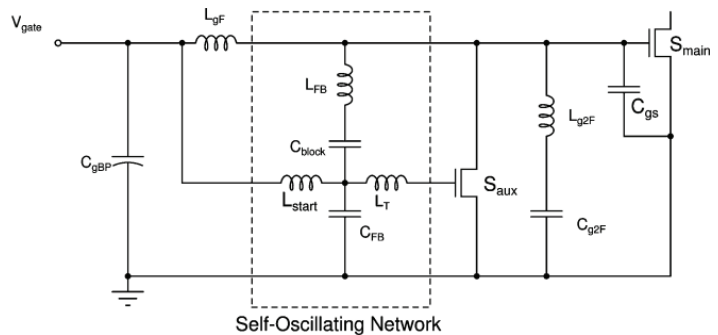


Fig. 5. Trapezoidal resonant gate drive circuit with self-oscillating network. The converter is enabled by applying the voltage  $V_{gate}$ , and disabled by setting  $V_{gate}$  to zero. This gate driver is employed in the 110-MHz converter (Fig. 9).

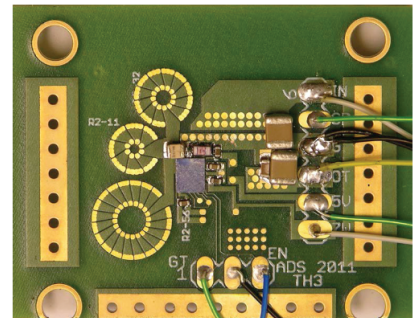R. C. N. Pilawa-Podgurski, A. D. Sagneri, J. M. Rivas, D. I. Anderson and D. J. Perreault, "Very-High-Frequency Resonant Boost Converters," 2009

