
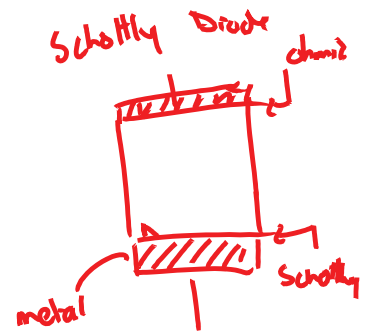
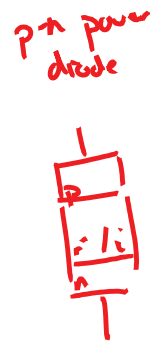



# Schottky Diode

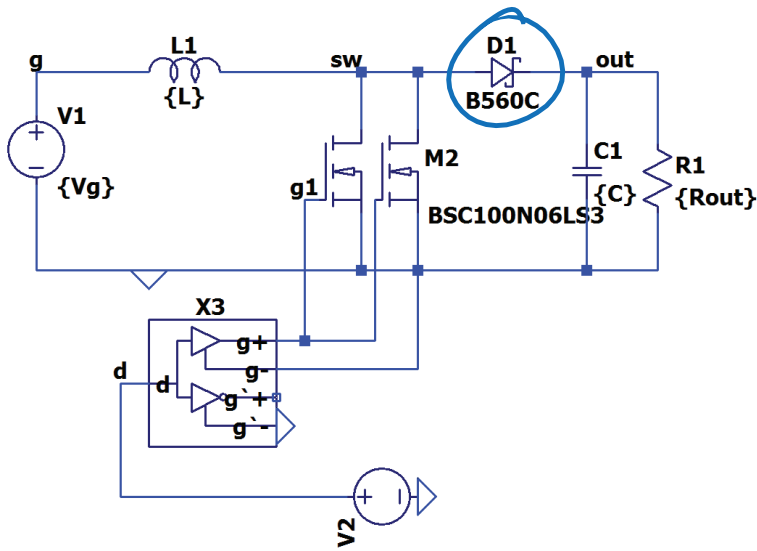


L	C <sub>out</sub>	f <sub>s</sub>	Diode	η (Sim)
22uH	22uF	202k	Si (FR)	93.9%
22uH	22uF	202k	Si Schottky	95.8%

only 2% increase!


## Simulation Waveforms

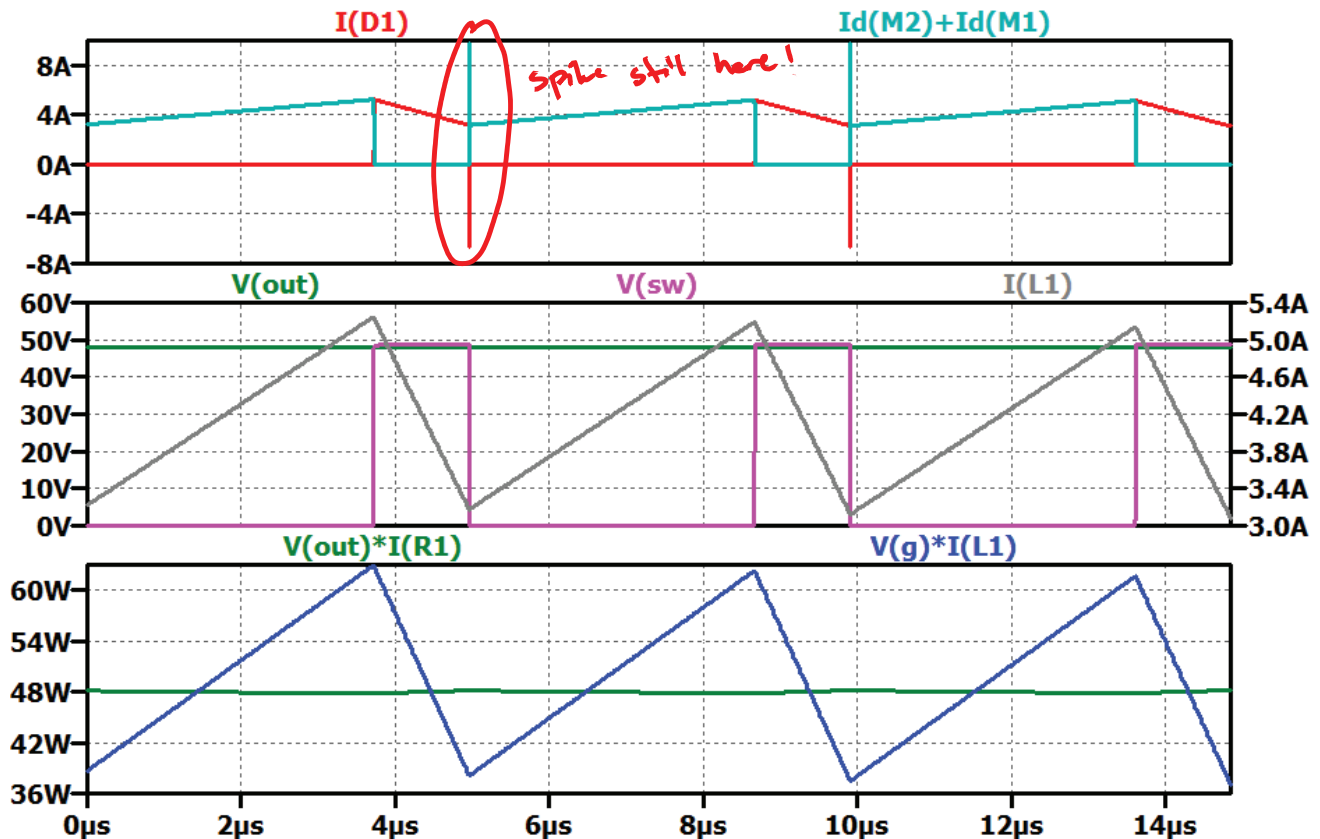

# Switching Transition – FET turn ON

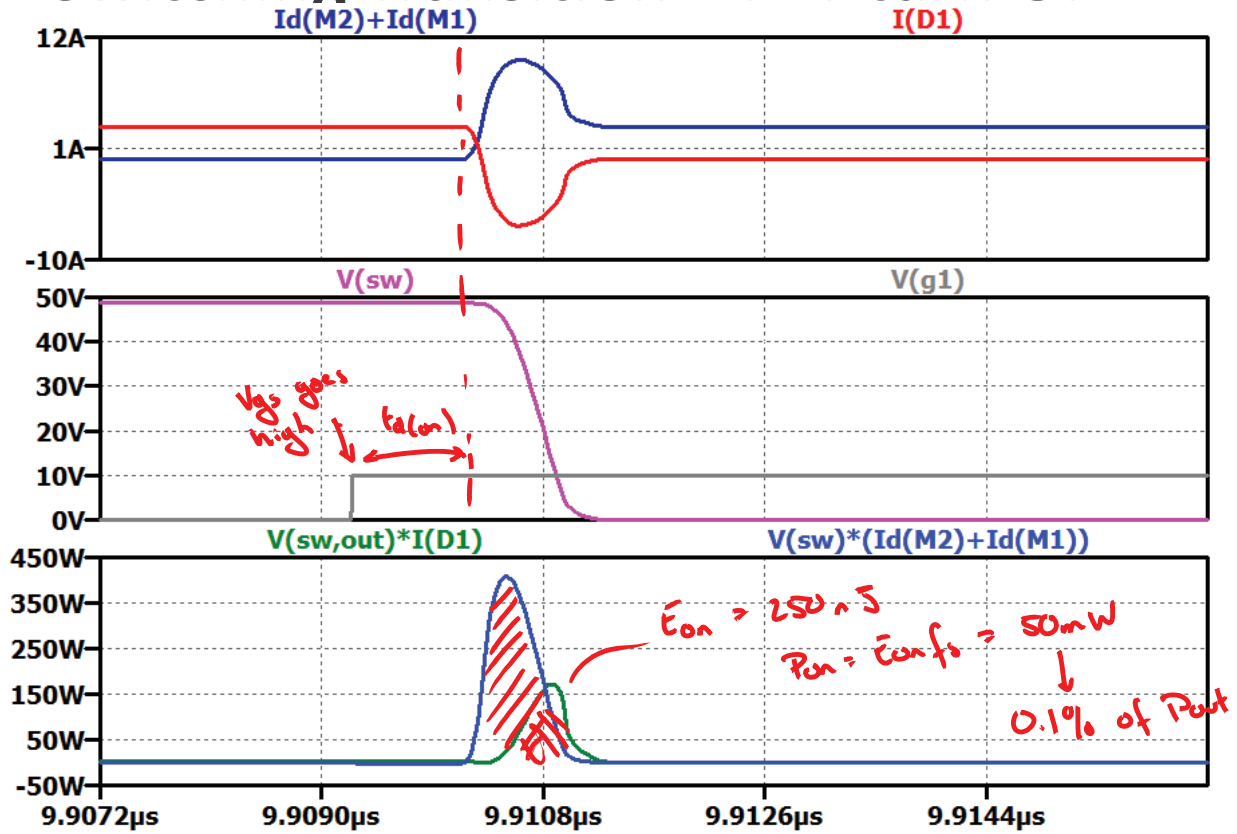

# Switching Transition – FET turn OFF

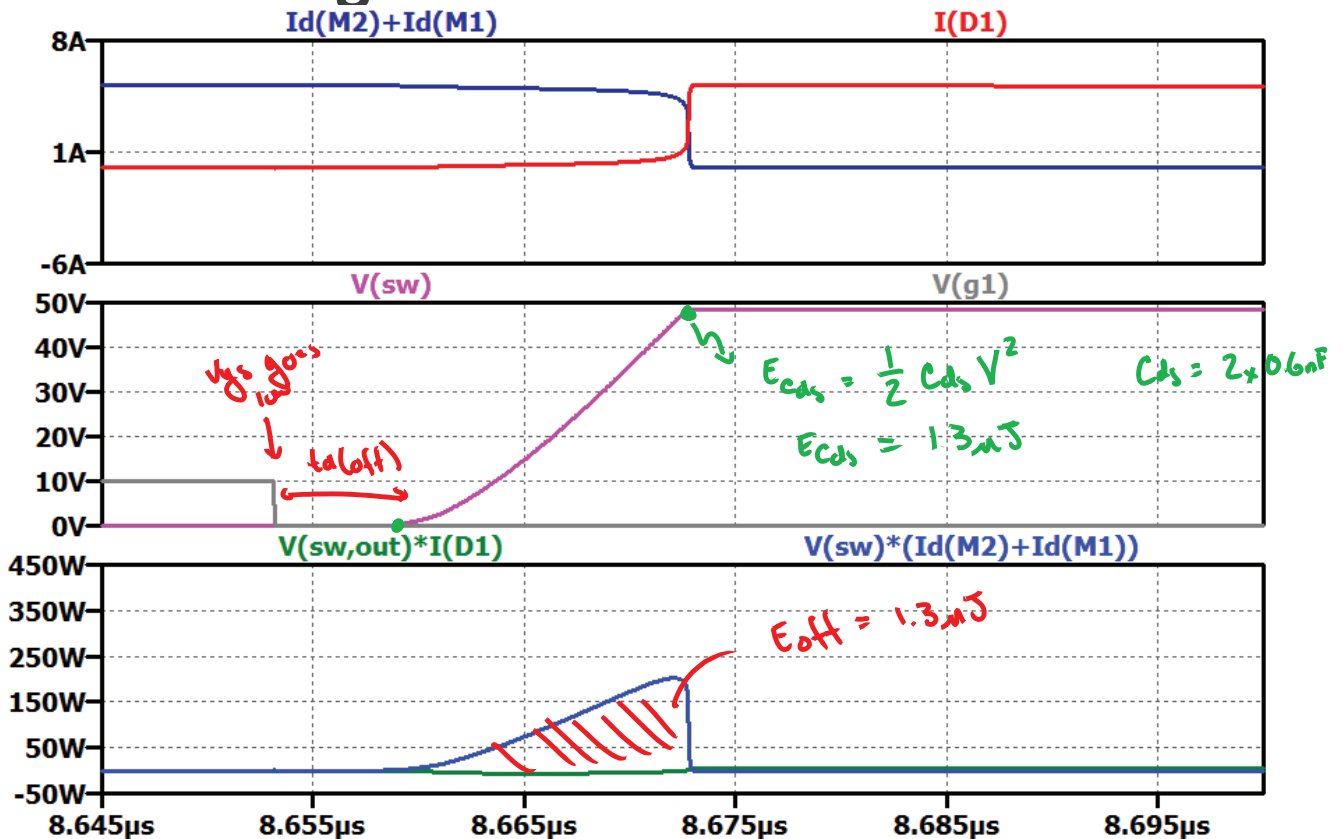


# MOSFET Switching Behaviors (1) - static

5 Typ. output characteristics

$I_D = f(V_{DS}); T_J = 25^\circ\text{C}$


parameter:  $V_{GS}$

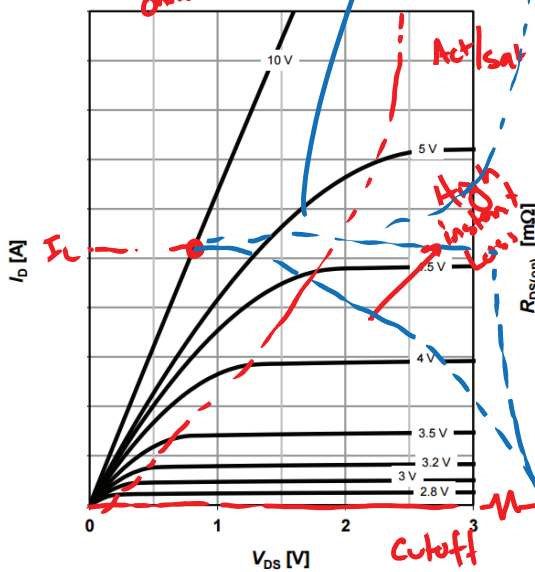





6 Typ. drain-source on resistance

$R_{DS(on)} = f(I_D); T_J = 25^\circ\text{C}$

parameter:  $V_{GS}$

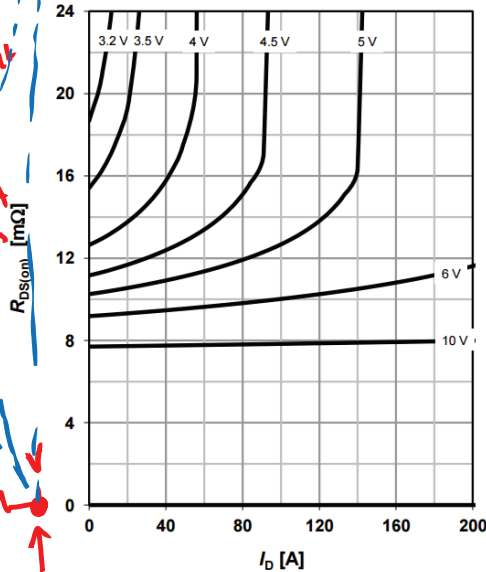

# MOSFET Stored Charge (2) - dynamic

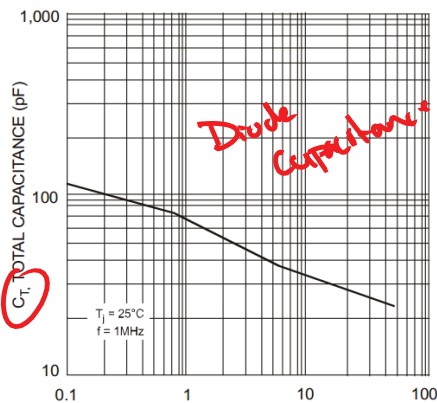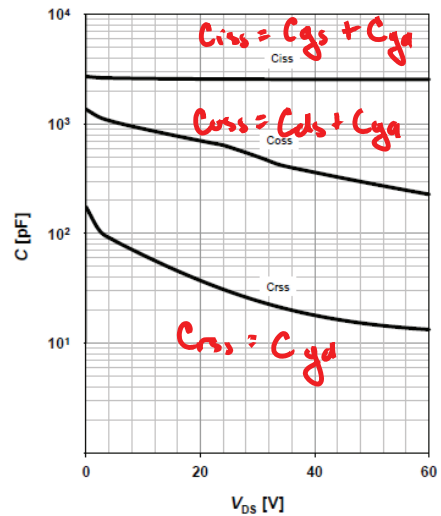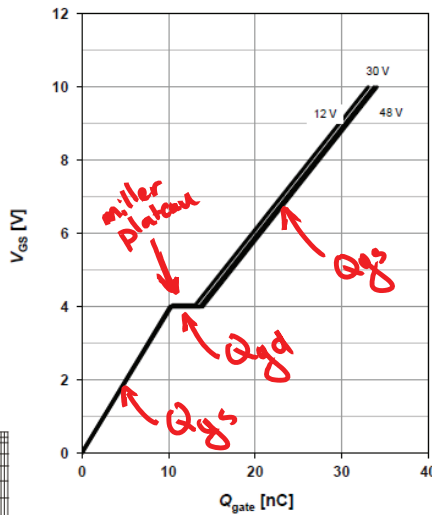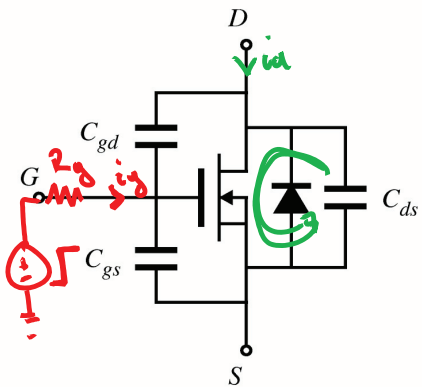


$Q_{gate} = Q_g = \int i_g dt$



$C_j = C_p$

# Device Capacitances – FET Turn Off

ECE 481

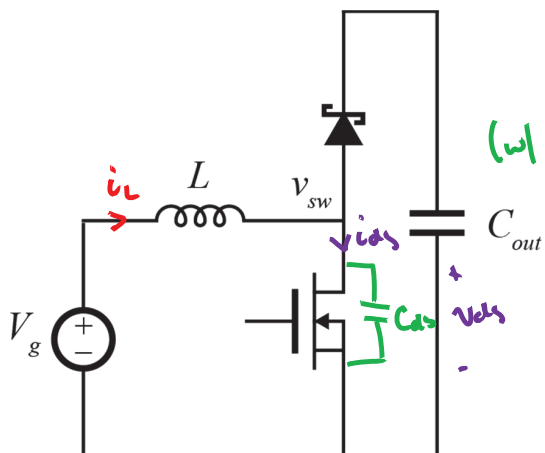

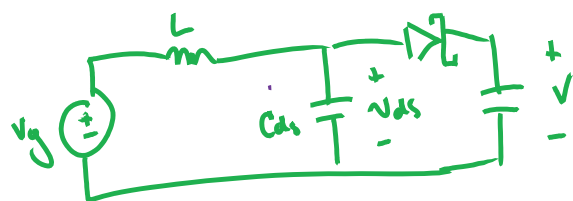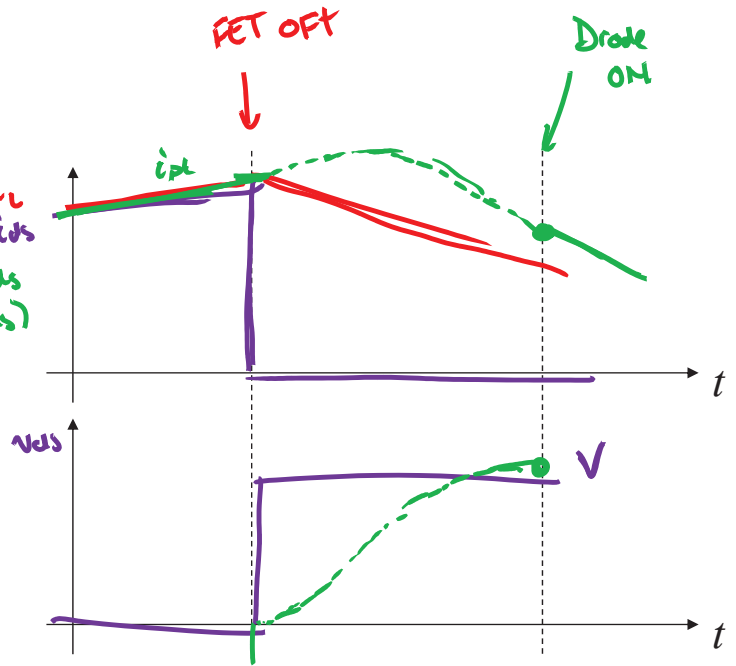$i_L$   
 $i_{ds}$   
 $i_{ds}$   
(w/  $C_{ds}$ )



$i_L(\phi) = i_{ph}$   
 $v_{ds}(\phi) = \phi$