

ZVS-QR State Plane

$$v_{Lr} = v_g \quad R_o = \sqrt{L_r/C_r}$$

$$\textcircled{I}: \frac{E_r}{C_r} t_1 = v_g \rightarrow \theta_1 = \frac{1}{\Delta_1}$$

$$\textcircled{II}: r_2^2 = \Delta_1^2 = \Delta_2^2 + 1$$

$$\Delta_2 = \sqrt{\Delta_1^2 - 1}$$


$$\beta = \pi + \sin^{-1}\left(\frac{1}{\Delta_1}\right)$$

$$\textcircled{III}: \frac{v_g}{L_r} t_3 = I_2 + I_L$$

$$\theta_3 = \Delta_2 + \Delta_1$$

$$\textcircled{IV}: X$$
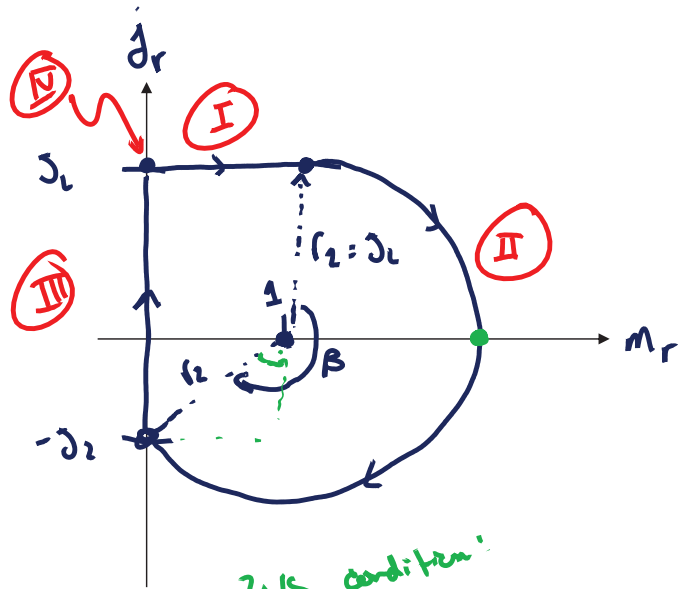
$$\theta_1 + \beta + \theta_3 + \theta_4 = \frac{2\pi}{F}$$



ZVS condition:
 $r_2 \geq 1$
 $\Delta_1 \geq 1$

Averaging

Apply volt-second balance on L_f

$$\langle v_{L_f} \rangle = \phi = \langle v_{sw} \rangle - V$$

$$\phi = v_g - \langle v_{cr} \rangle - \cancel{\langle v_{L_f} \rangle} - V$$


$$v = v_g - \langle v_{cr} \rangle$$

$$v = v_g - \frac{1}{T_s} \int_0^{T_s} v_{cr} dt = v_g - \frac{1}{T_s} [\lambda_1 + \lambda_2]$$

$$v = v_g - \frac{1}{T_s} \left[\frac{1}{2} v_g t_1 + v_g t_3 + L_r (I_2 + I_L) \right]$$

$$M = 1 - \frac{1}{T_s} \left[\frac{t_1}{2} + t_3 + \frac{L_r}{v_g} (I_2 + I_L) \right]$$
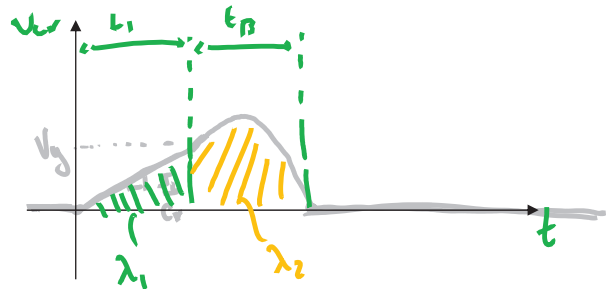
$$M = 1 - \frac{F}{2\pi} \left[\frac{\theta_1}{2} + \beta + \Delta_2 + \Delta_1 \right]$$



$$\lambda_1 + \lambda_2$$

$$\lambda_1 = \frac{1}{2} v_g t_1$$

$$\lambda_2 = \int_{t_3} v_{cr} dt = \int_{t_3} v_g - v_{cr} dt$$

$$= \int_{t_3} v_g - L_r \frac{di_{cr}}{dt} dt$$

$$\lambda_2 = v_g t_3 - L_r [-I_2 - I_L]$$

Complete Solution

$$M = 1 = \frac{F}{2\pi} \left[\frac{\theta_1}{2} + \beta + J_2 + J_4 \right]$$

$$M = 1 = \frac{F}{2\pi} \left[\frac{1}{2J_L} + \pi + \sin^{-1}\left(\frac{1}{J_L}\right) + \sqrt{J_L^2 - 1} + J_L \right]$$

F.P. $\left(\frac{1}{J_L}\right)$ in the textbook (20.61 & 20.16)



$$\theta_1 = \frac{1}{J_L}$$

$$J_2 = \sqrt{J_L^2 - 1}$$


$$\beta = \pi + \sin^{-1}\left(\frac{1}{J_L}\right)$$

$$\theta_3 = J_2 + J_L$$
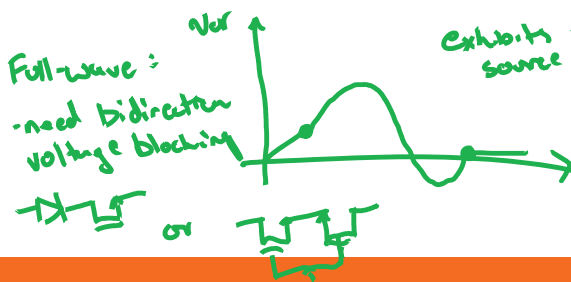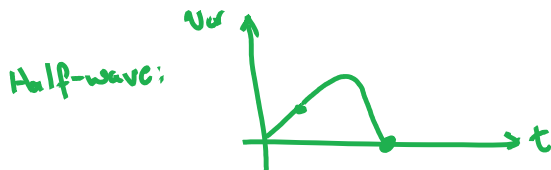
$$\frac{2\pi}{F} = \theta_1 + \beta + \theta_3 + \theta_4$$



exhibits voltage source behavior

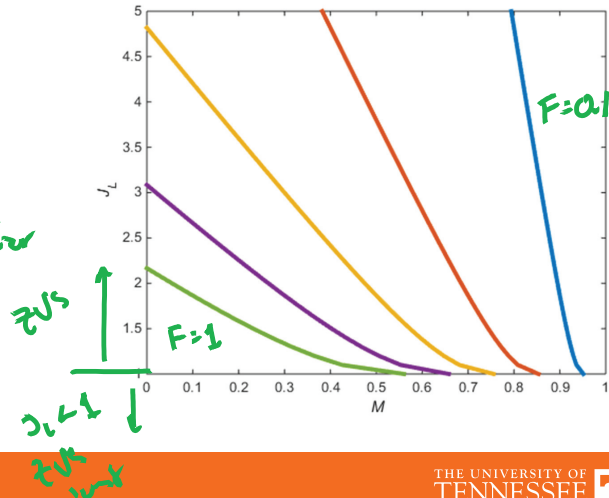

MOSFET Voltage Stresses

for ZVS $J_L \geq 1$

$$M_{cr,pt} = 1 + J_L$$

At minimum, when achieving ZVS, $J_L = 1$

$$M_{cr,pt} = 2 \rightarrow V_{cr,pt} = 2V_g$$


$$V_{cr,pt} = V_{as,pt}$$

For example if I want ZVS down to 20% Pout

At full load $J_L = 5$



$$M_{cr,pt} = 6 \rightarrow V_{cr,pt} = 6V_g$$

Test Circuit

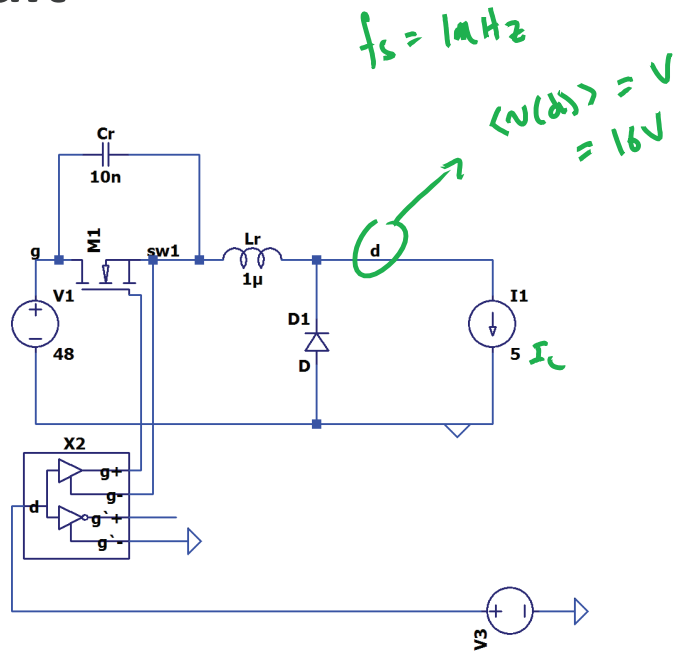


$$\zeta_L = \frac{5A}{48V} \sqrt{\frac{1\mu H}{10nF}} \approx 1 \rightarrow \text{operating close to ZVS boundary}$$


Simulation Results

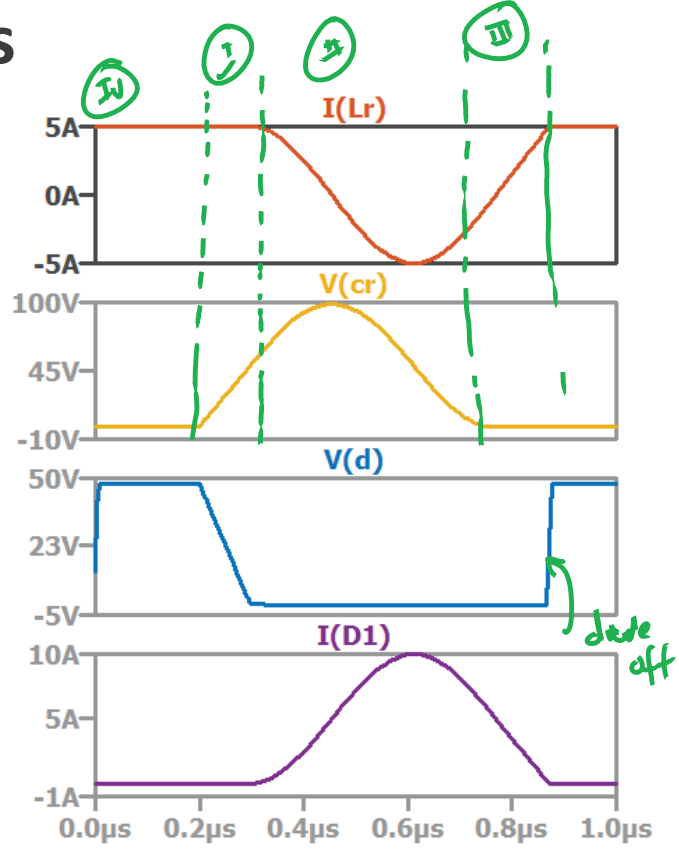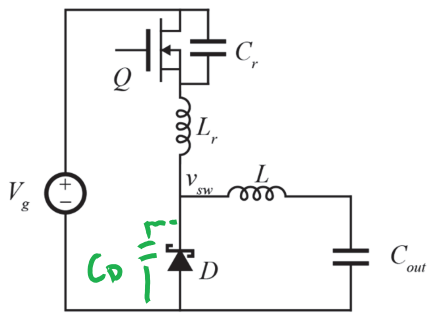


Diode Capacitance

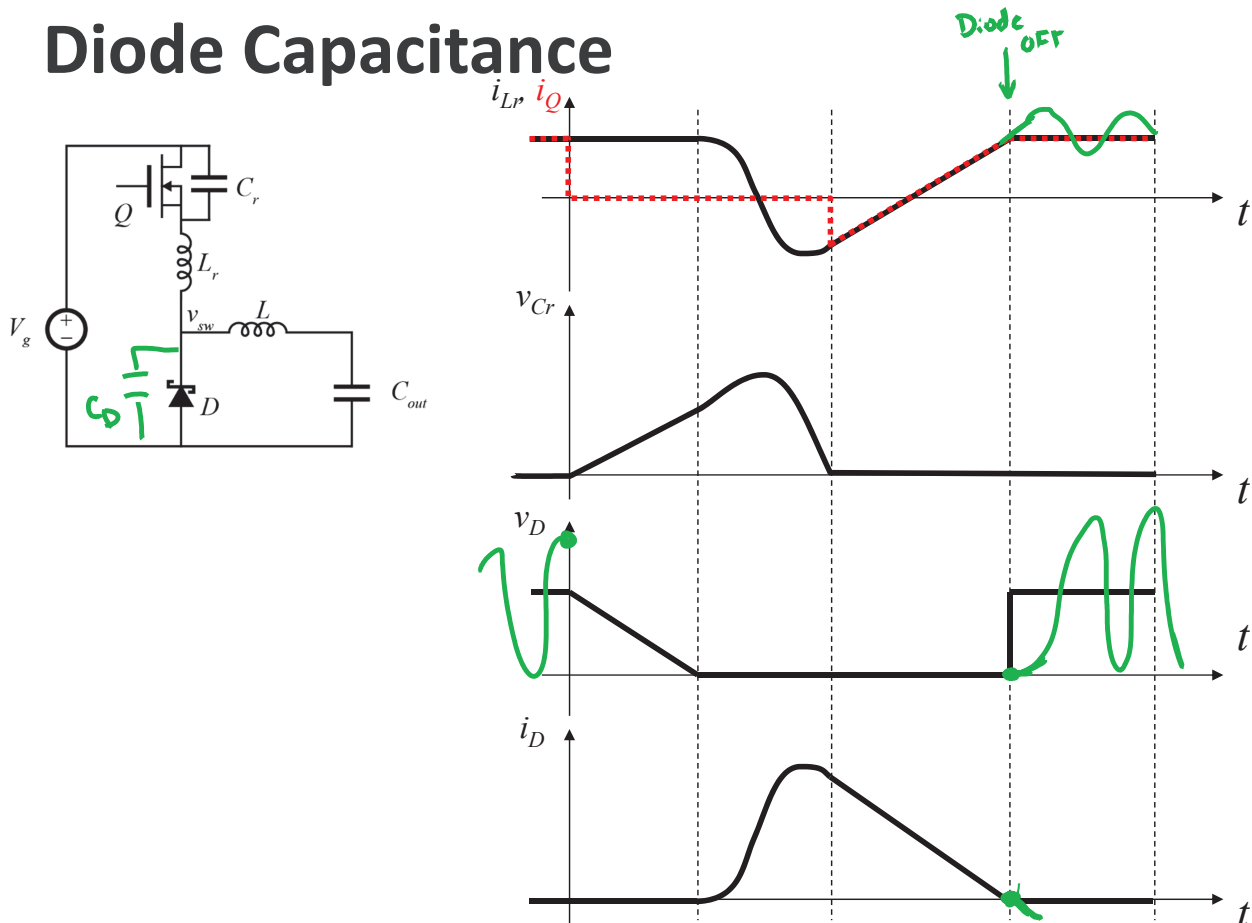


Simulation Results: Diode Capacitance

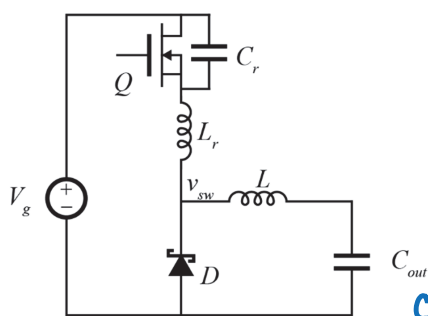

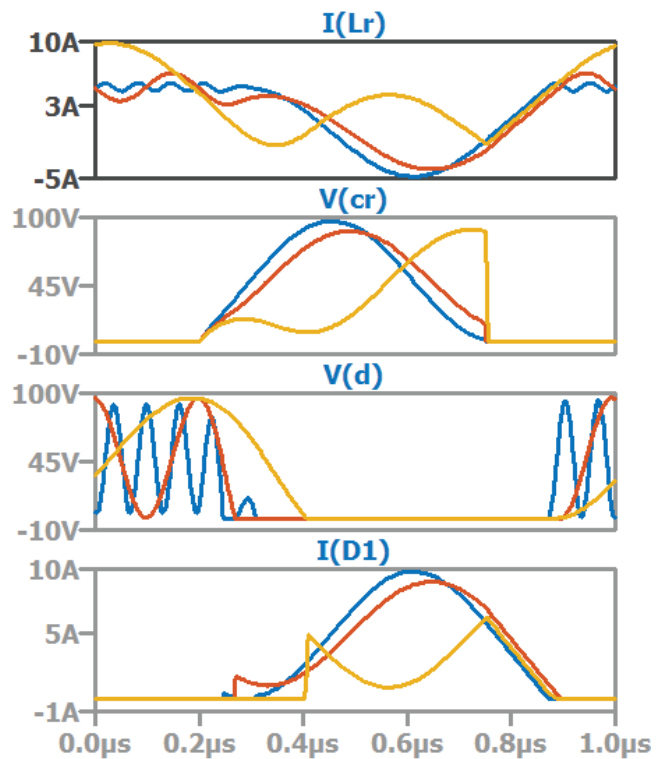
$C_a = 100\text{pF}$
 $C_a = 1\text{nF}$
 $C_a = 10\text{nF}$



Wishlist: Multi-Resonant

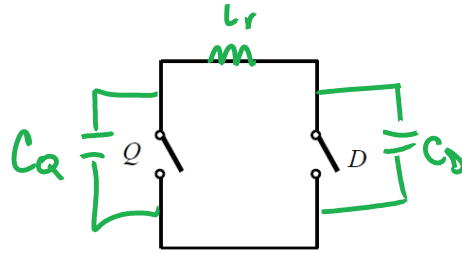

ZVS-MR Buck

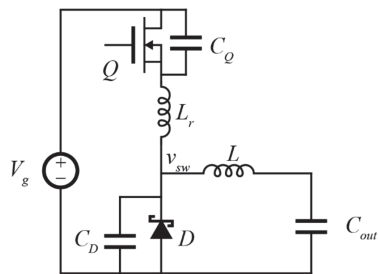

Operating Modes

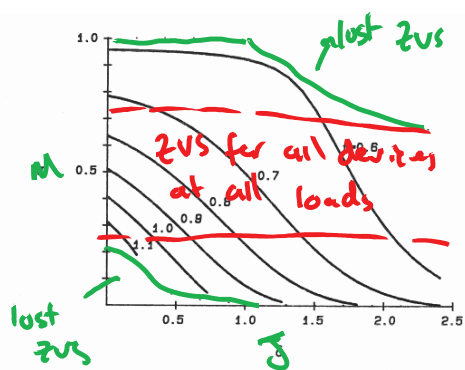


Figure 10.7: Load-to-output DC characteristics of a ZV-MR converter operating in modes (I, II)₁.

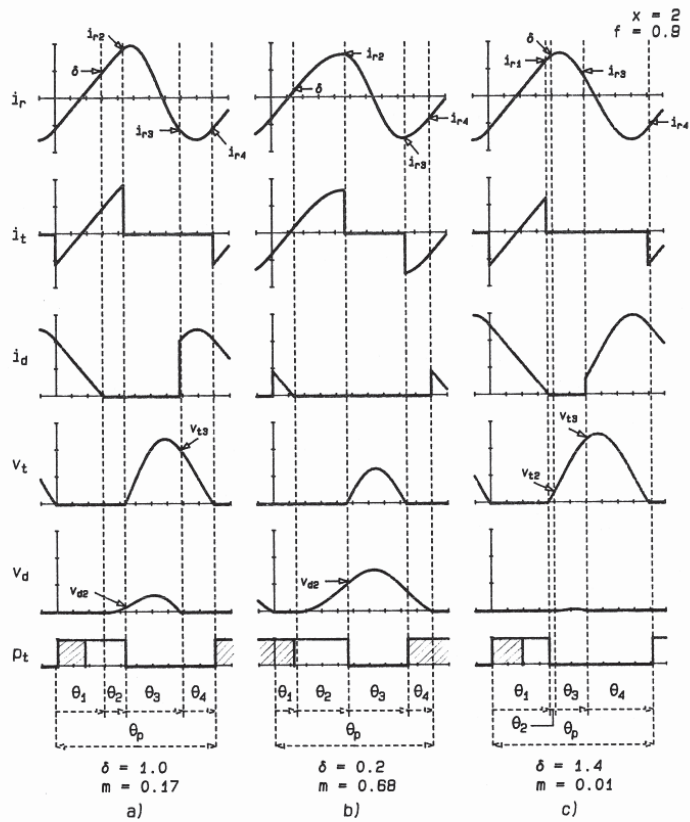
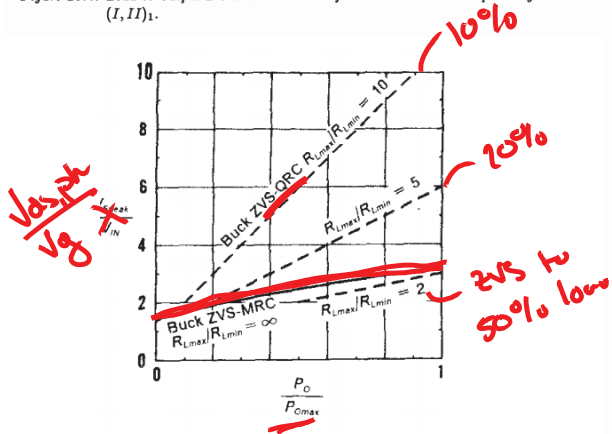


Figure 10.2: Typical waveforms for a ZV-MR converter operating in modes I₁ (a), II₁ (b) or III₁ (c).