


Averaging

Apply volt-second balance on L_f

$$\langle v_{Lf} \rangle = \phi = \langle v_{sw} \rangle - V$$

$$\phi = V_g - \langle N_{cr} \rangle - \cancel{\langle v_{Lf} \rangle} - V$$

$$V = V_g - \langle N_{cr} \rangle$$

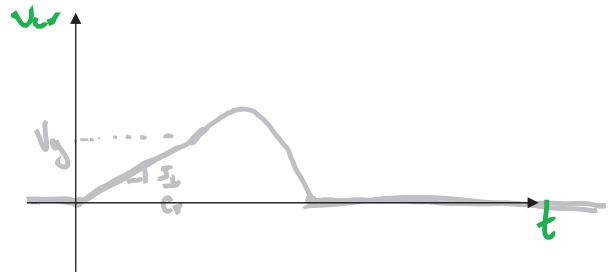

Complete Solution

$$\theta_1 = \frac{1}{J_L}$$

$$J_2 = \sqrt{J_L^2 - 1}$$


$$\beta = \pi + \sin^{-1}\left(\frac{1}{J_L}\right)$$

$$\theta_3 = J_2 + J_L$$



$$\frac{2\pi}{F} = \theta_1 + \beta + \theta_3 + \theta_4$$

MOSFET Voltage Stresses



Test Circuit

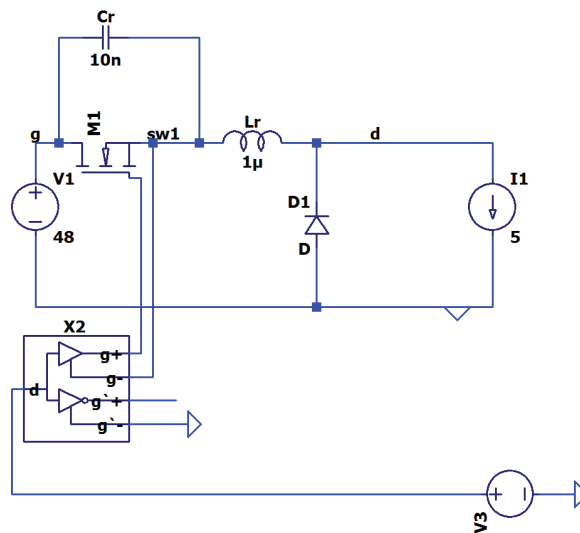



Simulation Results

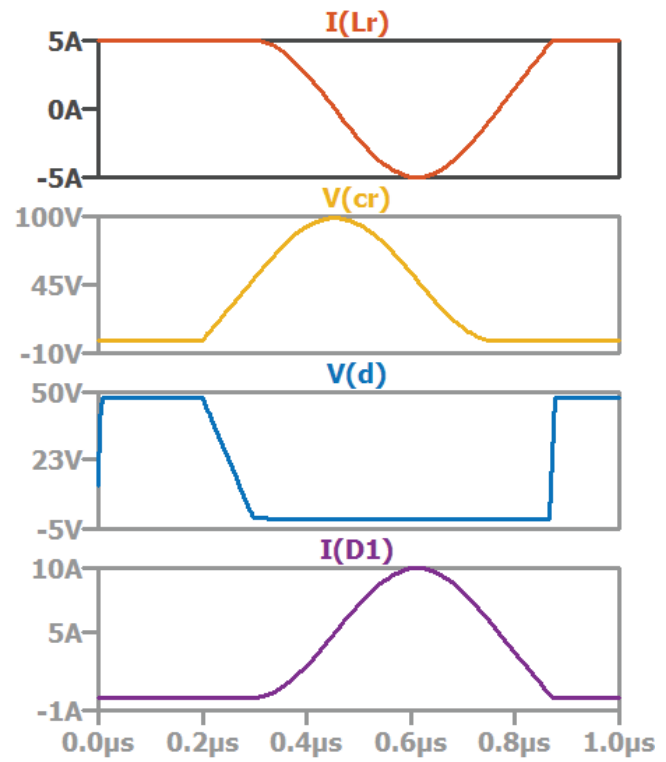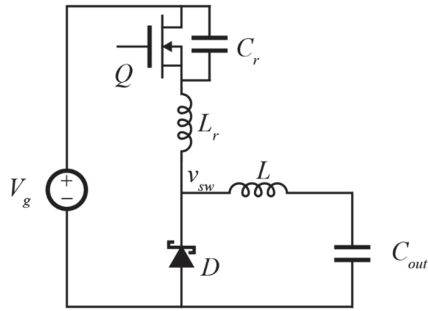


Diode Capacitance

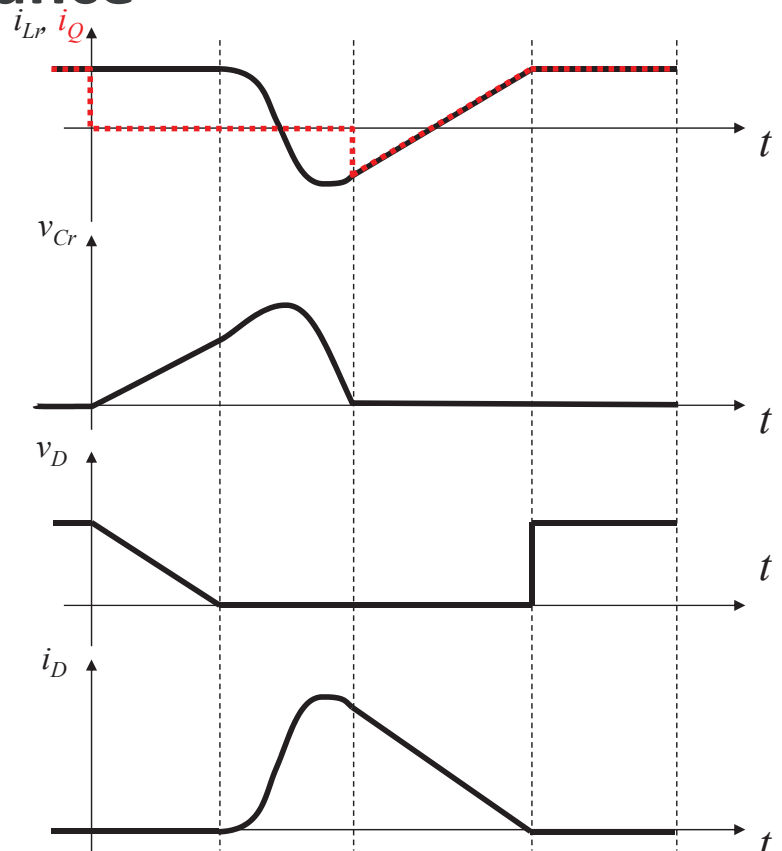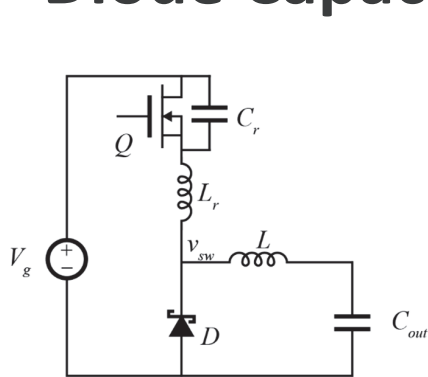


Simulation Results: Diode Capacitance

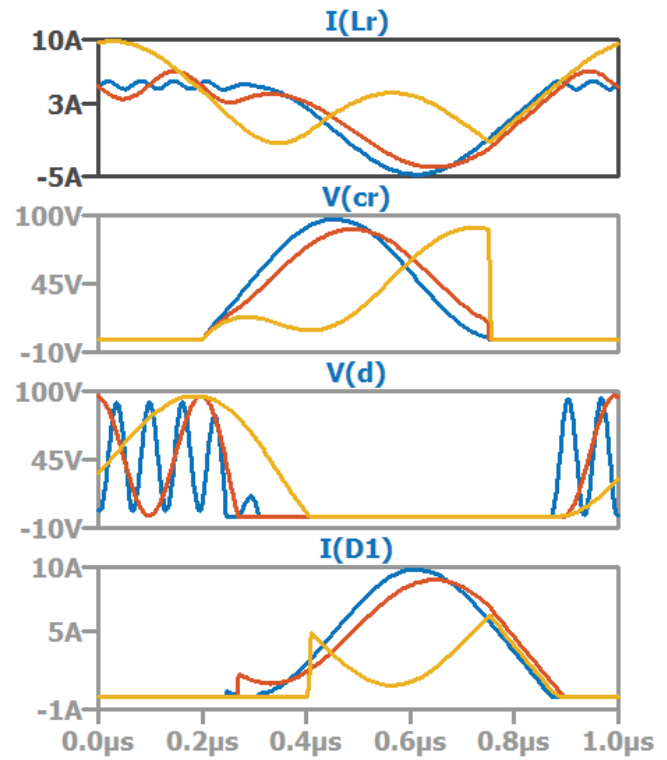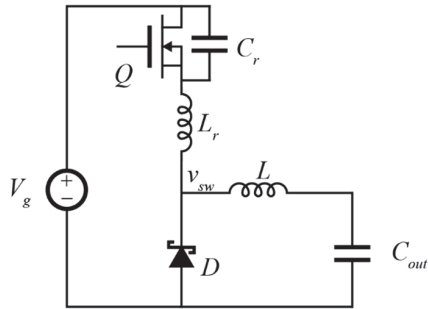

Wishlist: Multi-Resonant

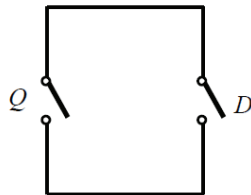

ZVS-MR Buck

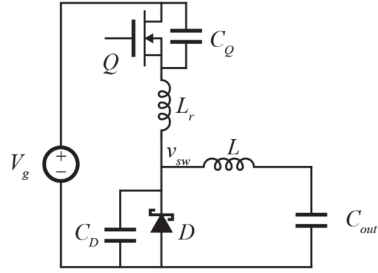

W. A. Tabisz and F. C. Lee, "Zero-voltage-switching multi-resonant technique-a novel approach to improve performance of high frequency quasi-resonant converters," *Power Electronics Specialists Conference*, 1988.

Operating Modes

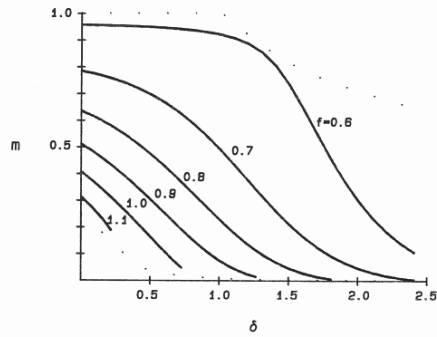


Figure 10.7: Load-to-output DC characteristics of a ZV-MR converter operating in modes (I, II)₁.

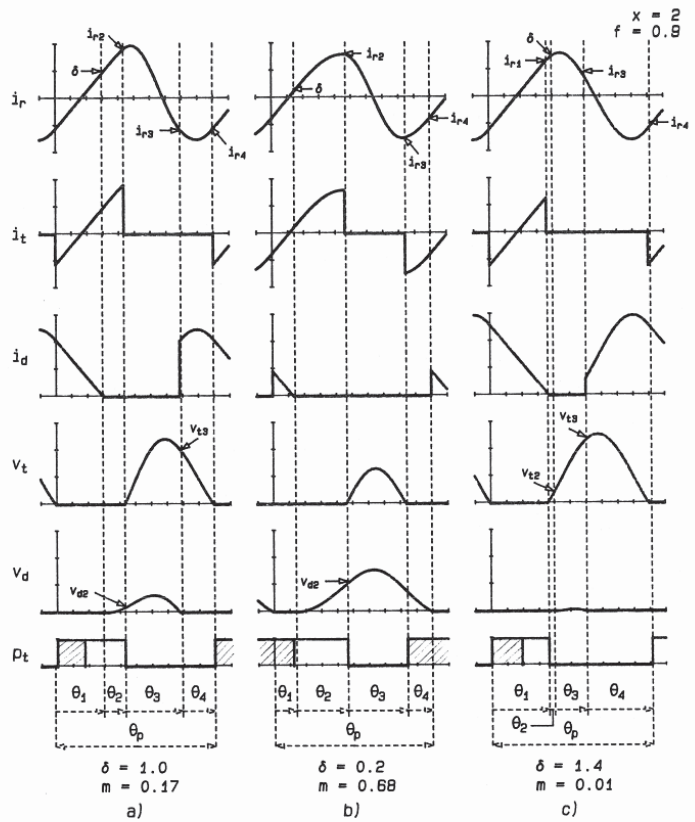
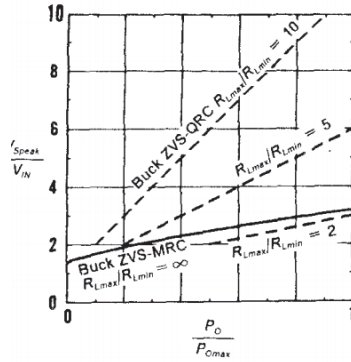


Figure 10.9: Typical waveforms for a ZV-MR converter operating in modes I₁ (a), II₁ (b) or III₁ (c).