

ZVS-QR Switch Cell SSM

$$M = 1 - F P_{1/2}(\frac{1}{2\alpha_c})$$

$$M = 1 - \frac{F}{2\pi} \left[\frac{1}{2\alpha_c} + \pi + \sin^{-1}\left(\frac{1}{2\alpha_c}\right) + \alpha_c + \sqrt{\alpha_c^2 - 1} \right]$$

$$F = \frac{f_s}{f_0} \quad \alpha_c = \frac{I_L}{V_g} R_0$$

M depends on f_s , i_L , and V_g

$$\hat{M} = k_i \hat{i}_L + k_f \hat{f}_s + k_v \hat{v}_g, \quad \begin{cases} k_i = \frac{\partial M}{\partial i_L} \Big|_{DC} = -F \frac{\partial P_{1/2}(\frac{1}{2\alpha_c})}{\partial \alpha_c} \frac{R_0}{V_g} \\ k_f = \frac{\partial M}{\partial f_s} \Big|_{DC} = -\frac{1}{f_0} P_{1/2}(\frac{1}{2\alpha_c}) \\ k_v = \frac{\partial M}{\partial V_g} \Big|_{DC} = -F \frac{\partial P_{1/2}(\frac{1}{2\alpha_c})}{\partial \alpha_c} \left(\frac{I_L^2}{V_g^2} \right) \end{cases}$$

$$P_{1/2}(\frac{1}{2\alpha_c}) = \frac{1}{2\pi} \left[\frac{1}{2\alpha_c} + \pi + \sin^{-1}\left(\frac{1}{2\alpha_c}\right) + \alpha_c + \sqrt{\alpha_c^2 - 1} \right]$$

$$\frac{\partial P_{1/2}(\frac{1}{2\alpha_c})}{\partial \alpha_c} = \frac{1}{2\pi} \left[\frac{-1}{2\alpha_c^2} + \frac{\frac{-1}{2\alpha_c^2}}{\sqrt{1 - (\frac{1}{2\alpha_c})^2}} + 1 + \frac{\alpha_c}{\sqrt{\alpha_c^2 - 1}} \right] \checkmark$$

this isn't right

Incorrect

$$\neq \frac{1}{2\pi} \left[\frac{-1}{2\alpha_c^2} + \frac{-\alpha_c^2}{\sqrt{\alpha_c^2 - 1}} + 1 + \frac{\alpha_c}{\sqrt{\alpha_c^2 - 1}} \right]$$

See next page for correct derivation

$$\neq \frac{1}{2\pi} \left[\frac{-1}{2\alpha_c^2} + \frac{\alpha_c^2 - 1}{\sqrt{\alpha_c^2 - 1}} + 1 \right] \quad \frac{-1}{2\alpha_c^2}$$

$$\neq \frac{1}{2\pi} \left[1 - \frac{1}{2\alpha_c^2} + \sqrt{\alpha_c^2 - 1} \right] \quad \frac{-1/\alpha_c}{\sqrt{1 - \frac{1}{\alpha_c^2}}}$$

Check


$$\frac{\partial P_{1/2}(\frac{1}{2\alpha_c})}{\partial \alpha_c} = f(\alpha_c) \quad \frac{-1/\alpha_c}{\sqrt{\alpha_c^2 - 1}} \neq \frac{-\alpha_c^2}{\sqrt{\alpha_c^2 - 1}}$$

Corrected Derivation from Previous Page


$$\begin{aligned} \frac{\partial P_{V_c}(\frac{1}{s_c})}{\partial s_c} &= \frac{1}{2\pi} \left[\frac{-1}{2s_c^2} + \frac{1}{\sqrt{1-(\frac{1}{s_c})^2}} \left(\frac{-1}{s_c^2} \right) + 1 + \frac{1/2}{\sqrt{s_c^2-1}} (2s_c) \right] \\ &= \frac{1}{2\pi} \left[\frac{-1}{2s_c^2} + \frac{-1/s_c}{\sqrt{s_c^2-1}} + 1 + \frac{s_c}{\sqrt{s_c^2-1}} \right] \\ &= \frac{1}{2\pi} \left[1 - \frac{1}{2s_c^2} + \frac{1/s_c(s_c^2-1)}{\sqrt{s_c^2-1}} \right] \end{aligned}$$

$$\frac{\partial P_{V_c}(\frac{1}{s_c})}{\partial s_c} = \frac{1}{2\pi} \left[1 - \frac{1}{2s_c^2} + \frac{\sqrt{s_c^2-1}}{s_c} \right]$$

SSM, Soft-Switching Buck

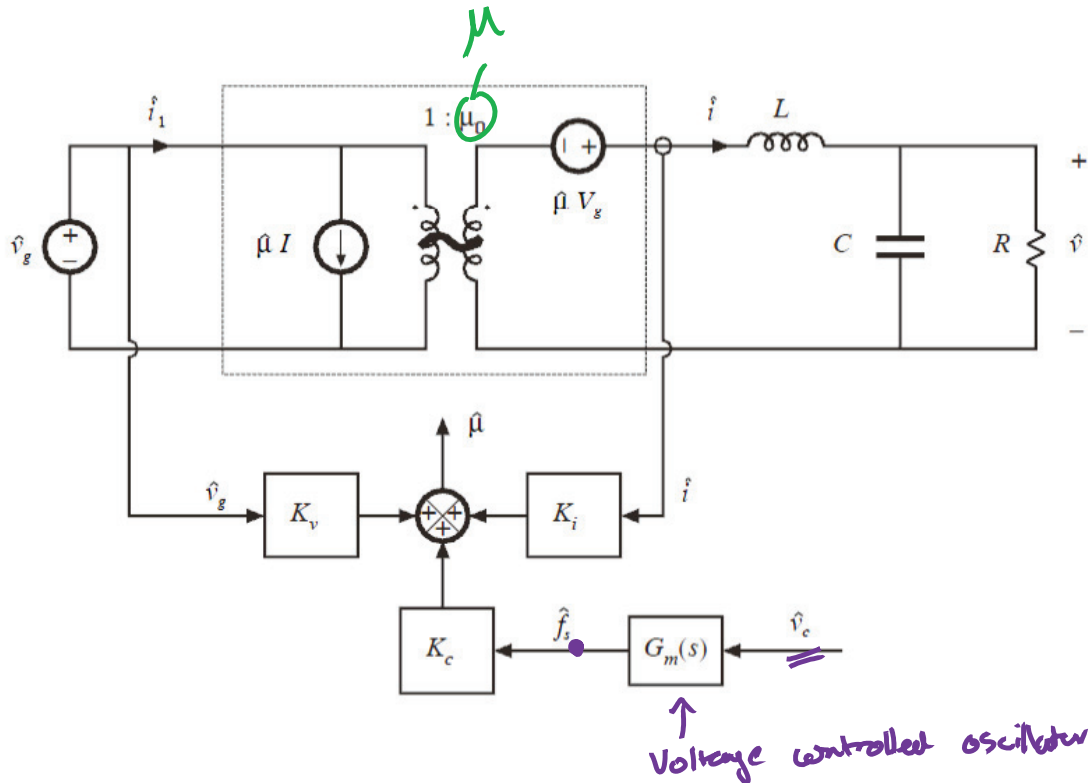


PWM Transfer Functions

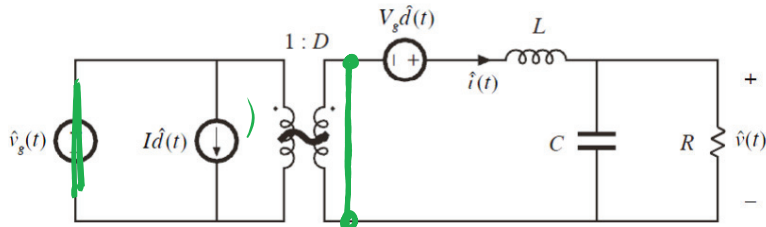


$$R \parallel \frac{1}{sC} = \frac{R}{1 + sCR}$$

$$G_{vd} = \left. \frac{\hat{v}}{\hat{d}} \right|_{\hat{v}_g=0} = V_g \frac{R \parallel \frac{1}{sC}}{sL + R \parallel \frac{1}{sC}} = V_g \frac{1}{s^2 LC + s \frac{L}{R} + 1}$$

$$G_{id} = \left. \frac{\hat{i}}{\hat{d}} \right|_{\hat{v}_g=0} = V_g \frac{1}{sL + R \parallel \frac{1}{sC}} = \frac{V_g}{R} \frac{1 + sCR}{s^2 LC + s \frac{L}{R} + 1}$$

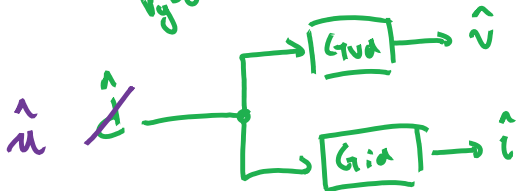


QR Transfer Functions

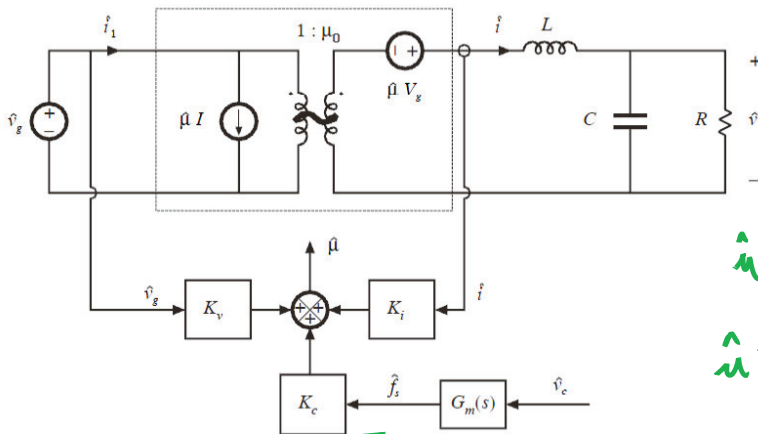

$$\hat{u} = \hat{v}_g k_v + \hat{f}_s k_c + K_i G_{id} \hat{u}$$
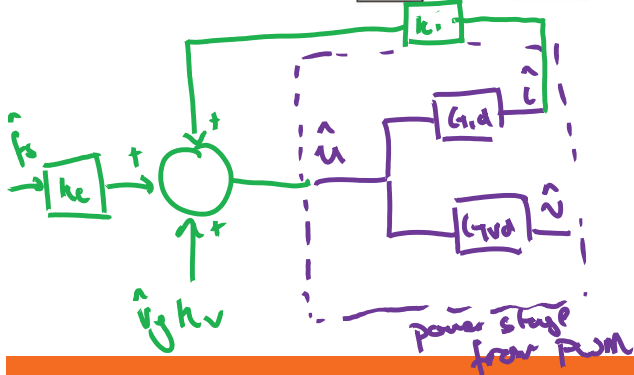
$$\hat{u} = \frac{\hat{v}_g k_v + \hat{f}_s k_c}{1 - k_i G_{id}}$$



$$G_{vc} = \left. \frac{\hat{v}}{\hat{f}_s} \right|_{\hat{v}_g=0} = \left(\frac{k_c}{1 - k_i G_{id}} \right) G_{vd}$$

$$G_{vc} = \frac{G_{vd} k_c}{1 - k_i G_{id}}$$

$$G_{vd} = \frac{V_g}{D(s)}$$

$$D(s) = s^2 LC + s \frac{L}{R} + 1$$

$$G_{id} = \frac{V_g}{R} \frac{(1+sCR)}{D(s)}$$

$$G_{vc} = \frac{\frac{V_g}{D(s)} k_c}{1 - k_i \frac{V_g}{R} \frac{(1+sCR)}{D(s)}} = \frac{V_g k_c}{s^2 LC + s \frac{L}{R} + 1 - k_i \frac{V_g}{R} (1+sCR)}$$

$$= \frac{V_g k_c}{s^2 LC + s \left(\frac{L}{R} - V_g C k_i \right) + \left(1 - k_i \frac{V_g}{R} \right)}$$


De gain changed

$$= \frac{\frac{V_g k_c}{1 - k_i \frac{V_g}{R}}}{s^2 LC + s \frac{L}{R} + 1 - \frac{V_g C k_i}{1 - k_i \frac{V_g}{R}} + 1}$$

ω_o changed

Q changed

Example

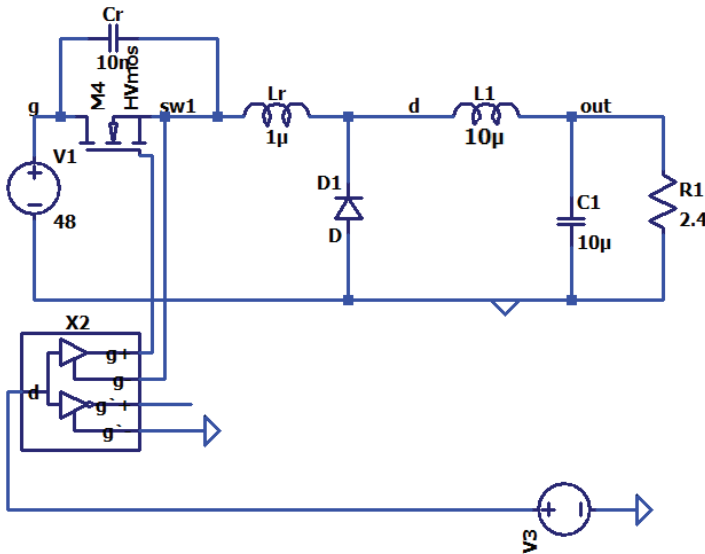

$$f_s = 1 \text{ MHz}$$

$$\zeta_c \approx 1$$

$$P_o = 60 \text{ W}$$

$$V = 12 \text{ V}$$


$$F = 0.6$$

$$k_c = 6.24 \times 10^{-2}$$

$$k_i = -0.005$$

$$k_v = 5.6 \times 10^{-4}$$

Control-to-Output Transfer Function

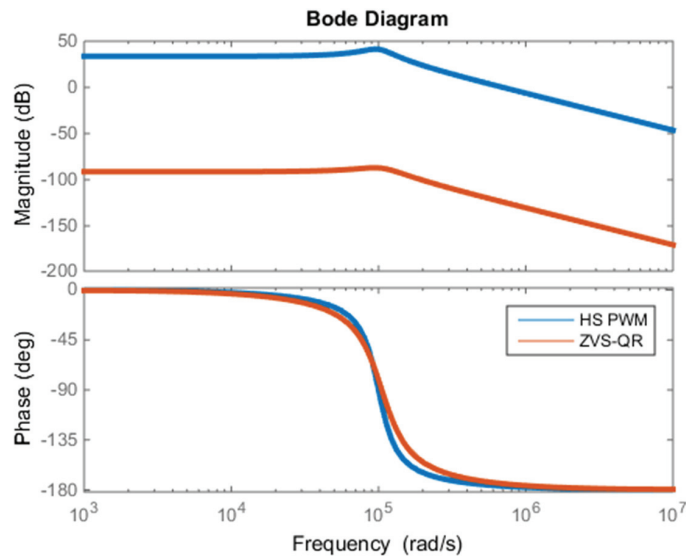

AC Link Converters?

