
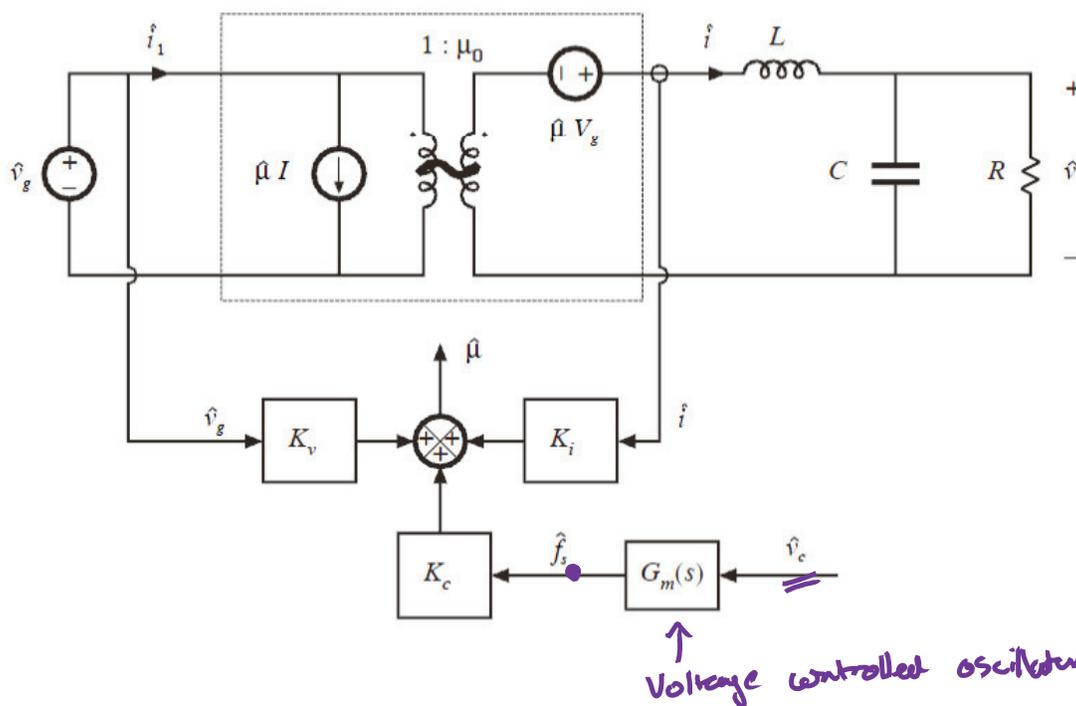



SSM, Soft-Switching Buck

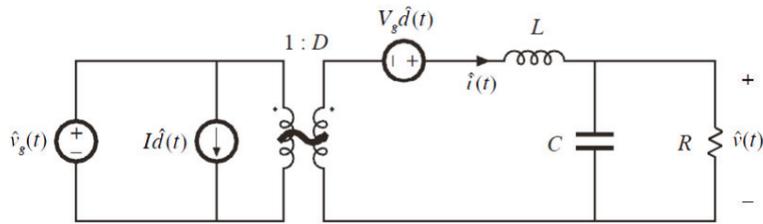


PWM Transfer Functions




QR Transfer Functions

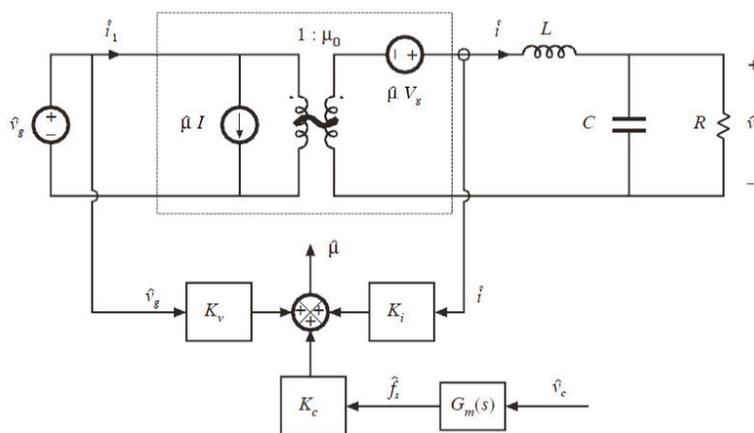


Example

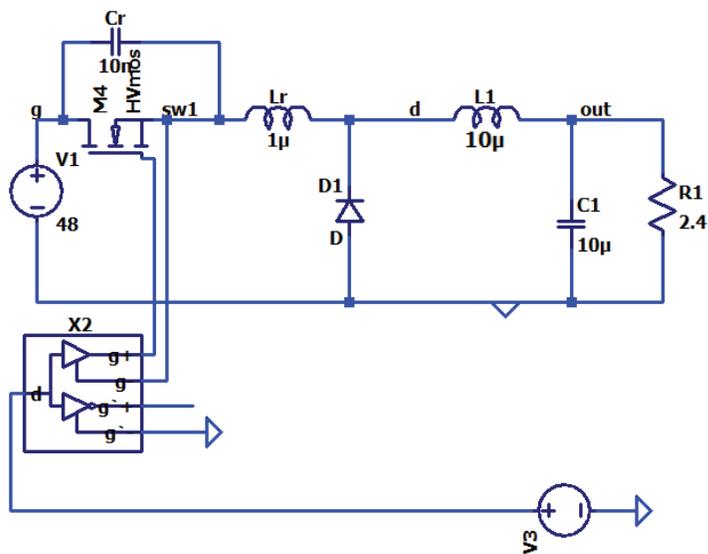

Control-to-Output Transfer Function

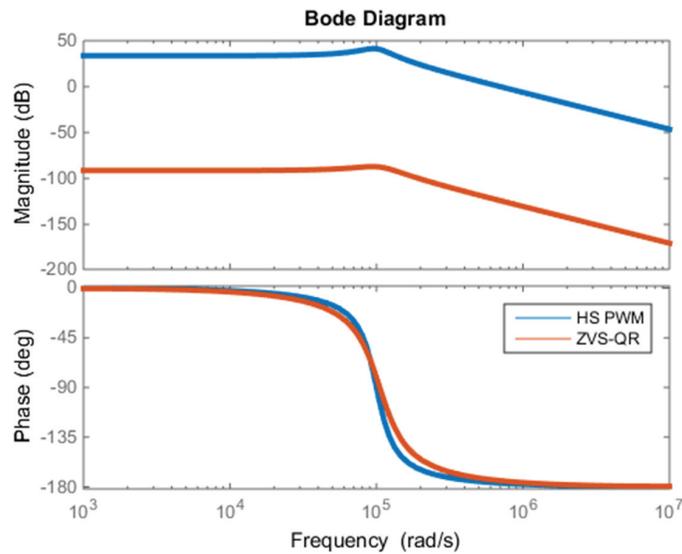

AC Link Converters?

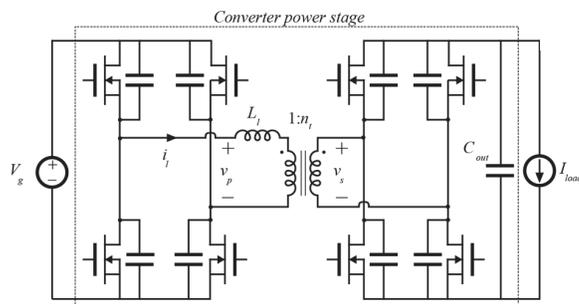

SUMMARY SO FAR

Converter Topologies

