
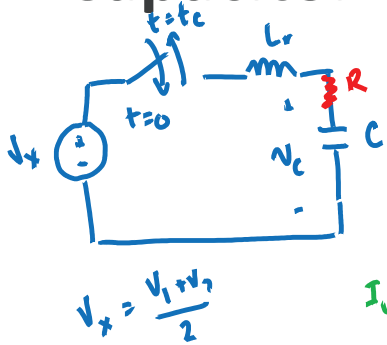


Capacitor Charging: Resonant

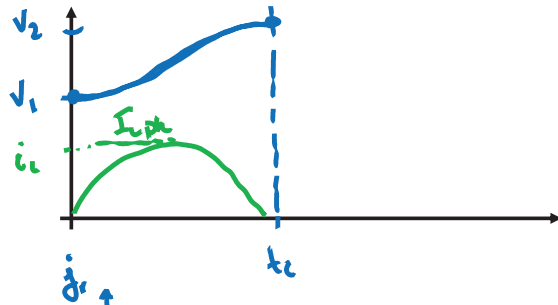

$$I_{c,pt} = \frac{V_s - V_1}{R_0} = \frac{V_2 - V_1}{2R_0}$$



$$\Delta E_c = \frac{1}{2} C (V_2^2 - V_1^2)$$


Assume i_c doesn't change when adding R

$$E_R = E_{loss} = \int_0^{t_c} i_c^2 R dt = i_{c,avg}^2 R t_c = \frac{I_{c,pt}^2}{2} R t_c$$

$$= \left(\frac{V_2 - V_1}{2R_0} \right)^2 \frac{R t_c}{2} = \frac{\pi R C}{2} \cdot \frac{(V_2 - V_1)^2}{4R_0}$$

$$t_c = \frac{1}{2f_0} = \frac{\pi}{\omega_0}$$
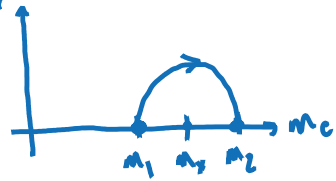
$$R_0 \omega_0 = \sqrt{\frac{L}{C}} \cdot \frac{1}{\sqrt{LC}} = \frac{1}{C}$$



$$E_R = \frac{\pi R C}{2} \frac{(V_2 - V_1)^2}{4R_0} = \underbrace{\frac{R\pi}{4R_0}}_{\text{scale factor}} \left[\underbrace{\frac{1}{2} C (V_2 - V_1)^2}_{E_{loss} \text{ in Voltage-source case}} \right]$$

$$\frac{R\pi}{4R_0} = \frac{R\pi}{4 \frac{1}{C\omega_0}} = \frac{RC\pi}{4} \left(\frac{\pi}{t_c} \right) = \frac{\pi^2}{4} \frac{RC}{t_c}$$

$$\bar{E}_R = \frac{\pi^2}{4} \frac{RC}{t_c} \left[\frac{1}{2} C (V_2 - V_1)^2 \right]$$

$$\frac{\pi^2}{4} \approx 2.5$$

Comparison of Capacitor Charging

Cap charged from V_1 to V_2 in time t_c

Voltage $E_{ev} = \frac{E_{loss}}{2} = \frac{1}{2} C (V_2 - V_1)^2$

Assumptions
 $t_c \gg RC = \tau$

Current $2 \frac{RC}{t_c} E_{ev}$




X

Resonant $\frac{\pi^2}{4} \frac{RC}{t_c} E_{ev}$

High-Q resonance

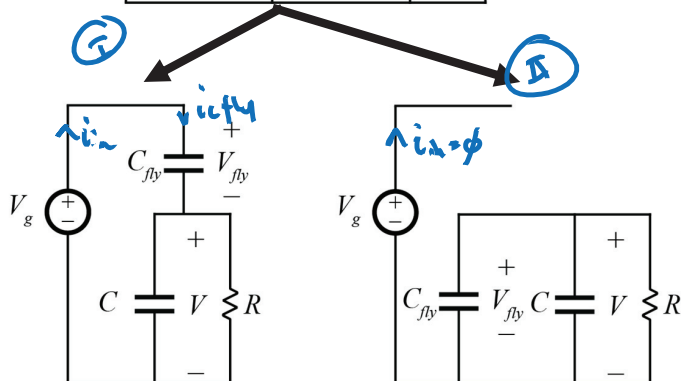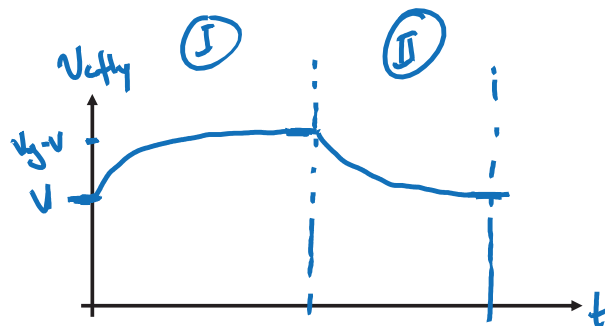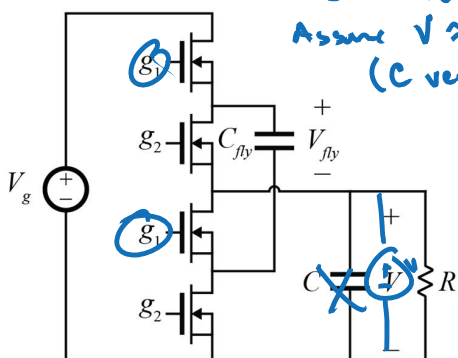2:1 SC Revisited

Assume $t_c \gg RC$
 Assume $V \approx \text{constant}$
 (C very large)



Energy loss

- I $\frac{1}{2} C_{fly} (2V - V_g)^2$
- II $\frac{1}{2} C_{fly} (V_g - 2V)^2$

$P_{loss} = C_{fly} (V_g - 2V)^2 f_s$


$P_{in} = V_g \Delta Q_{ch,5} f_s$
 $= V_g C_{fly} (V_g - 2V) f_s$

Equivalent Circuit Model


$$P_{\text{loss}} = \frac{C_f f_s}{4} (V_g - 2V)^2$$

$$P_{\text{in}} = V_g \frac{C_f f_s}{4} (V_g - 2V)$$

$$R_{\text{eq}} = \frac{1}{C_f f_s}$$

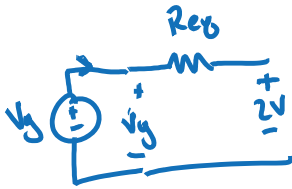

\Rightarrow

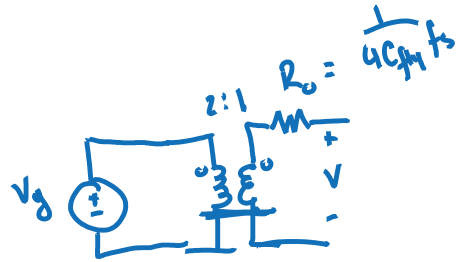

for high η , want small R_o
 \rightarrow Large C_f , Large f_s