
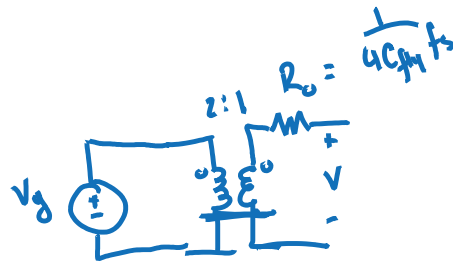


Equivalent Circuit Model


$$P_{loss} = C_{fly} f_s (V_g - 2V)^2$$

$$P_{in} = V_g C_{fly} f_s (V_g - 2V)$$

$$R_{eq} = \frac{1}{C_{fly} f_s}$$

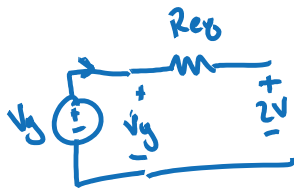


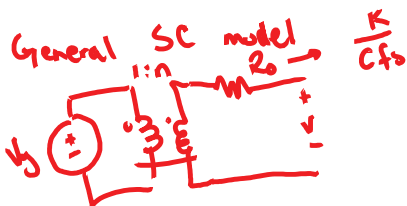for high η , want small R_o
 \rightarrow Large C_{fly} , Large f_s



Limit: $t_c \gg \tau$
 $\frac{1}{2} \frac{1}{f_s} \gg R C_{fly}$

2:1 – Current Loaded

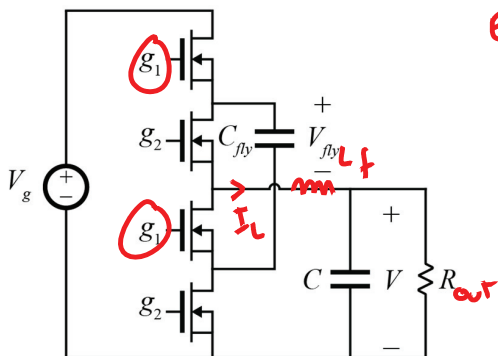

$$E_{loss} = E_{C,i}^I + E_{C,i}^{II}$$

$$= \frac{1}{2} C [2I_L R (V_1 - V_1)] + \frac{1}{2} C [2(-I_L) R (V_1 - V_2)]$$

$$= 2I_L R (V_2 - V_1) C$$

$$\Delta Q = I_L \frac{T_s}{2}$$

$$E_{loss} = 2I_L R \left(I_L \frac{T_s}{2} \right) = I_L^2 R T_s$$


$$R = 2r_{on} + R_L + C S R_C$$

This topology no longer has any charge-sharing


3-level Buck

- PWM regulation possible


2:1 – Resonant Implementation

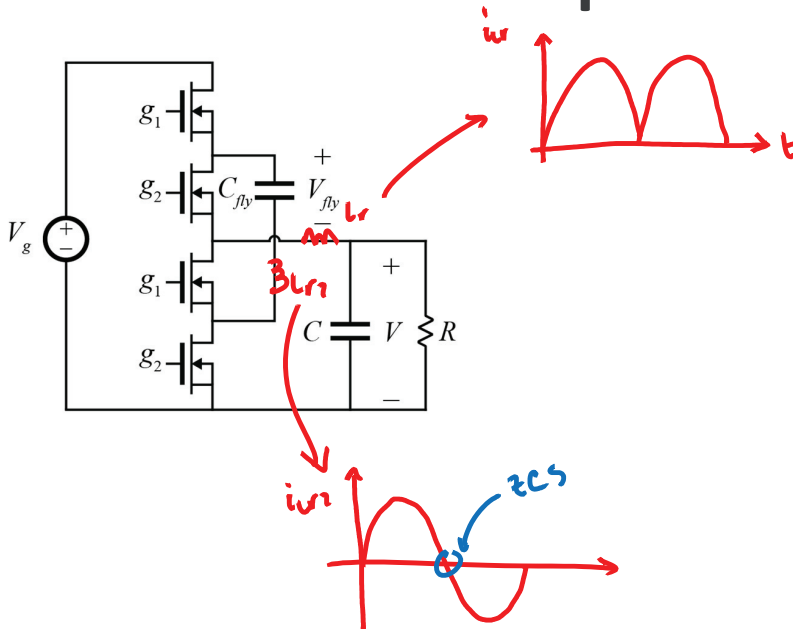

Slow and Fast Switching Limits

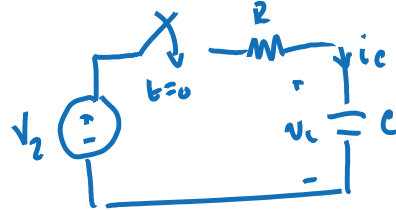

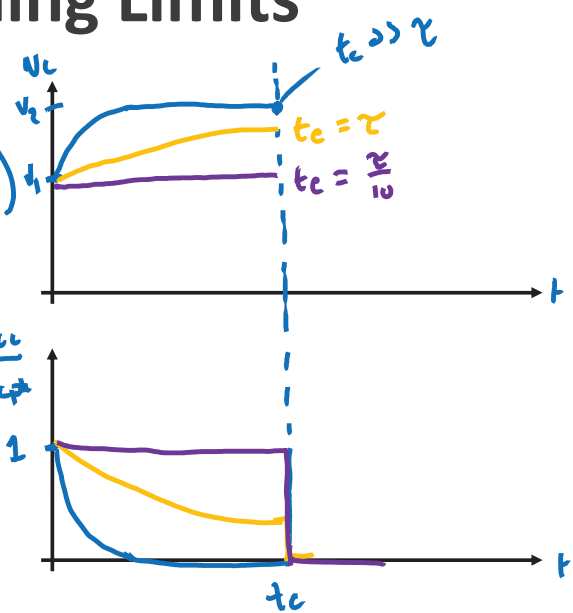$v_c(t=0) = v_1$
 $v_c(t > 0) = v_1 + (v_2 - v_1)(1 - e^{-\frac{t}{RC}})$



$\frac{t_c}{\tau}$	$\frac{v_c(t_c)}{v_2 - v_1}$
1/10	9.5%
1/2	39%
1	63%
3	95%
∞	100%

SSL $\rightarrow t_c \gg \tau$
 Slow switching limit
 FSL $\rightarrow t_c \ll \tau$
 Fast switching limit

2:1 SC – FSL Model



$$P_{out} = V \left[\frac{V_g - V_{cft1} - V}{R} \cdot \frac{t_1}{T_s} + \frac{V_{cft1} - V}{R} \cdot \frac{t_2}{T_s} \right]$$

$$t_1 = t_2 = \frac{T_s}{2}$$

$$P_{out} = \frac{V}{R} \left[\frac{V_g}{2} - V \right]$$

$$= V \frac{\left(\frac{V_g}{2} - V \right)}{R}$$

$$R = R_o$$

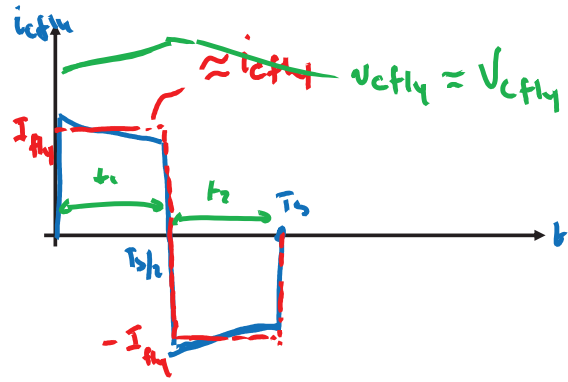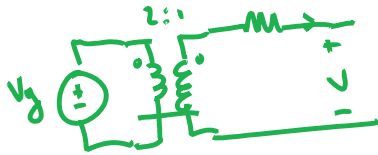

SSL and FSL

