


# 2:1 SC – FSL Model

$$P_{out} = V \left[ \frac{V_g - V_{cft1} - V}{R} \cdot \frac{t_1}{T_s} + \frac{V_{cft1} - V}{R} \cdot \frac{t_2}{T_s} \right]$$


$$t_1 = t_2 = \frac{T_s}{2}$$

$$P_{out} = \frac{V}{R} \left[ \frac{V_g}{2} - V \right]$$

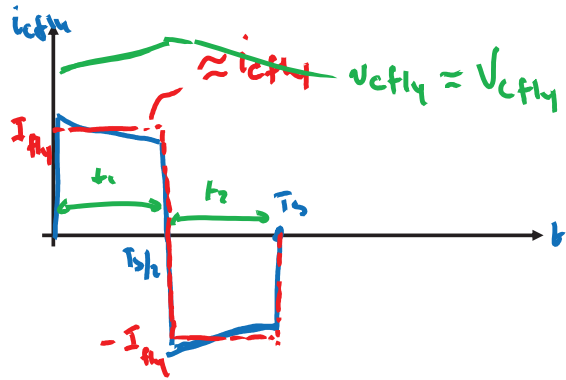
$$= V \frac{\left( \frac{V_g}{2} - V \right)}{R}$$



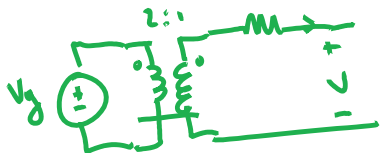$R = R_0$  whatever resistance is in the charging path



# SSL and FSL

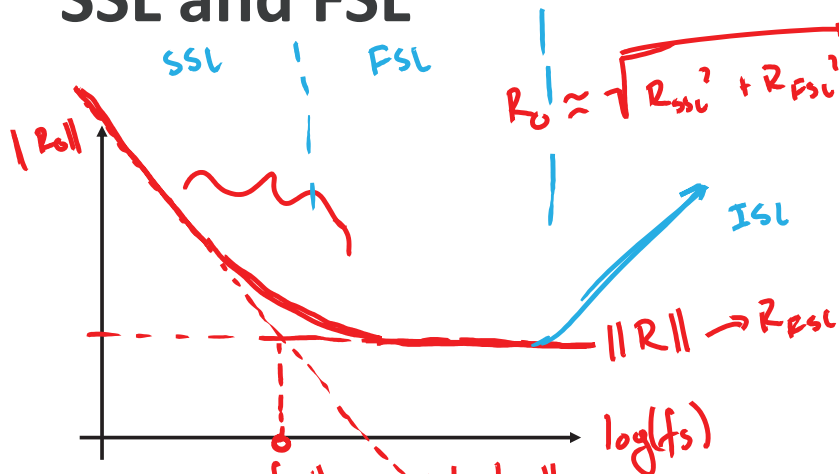


$$R > \frac{1}{4Cf_{crit}} R$$

$$f_s = \frac{1}{4Cf_{crit} R}$$

$$\frac{1}{T_s} = \frac{1}{2t_c} = \frac{1}{4Cf_{crit} R}$$

$$t_c = 2Cf_{crit} R = 2\tau @ f_{crit}$$


# SC Converter Topologies

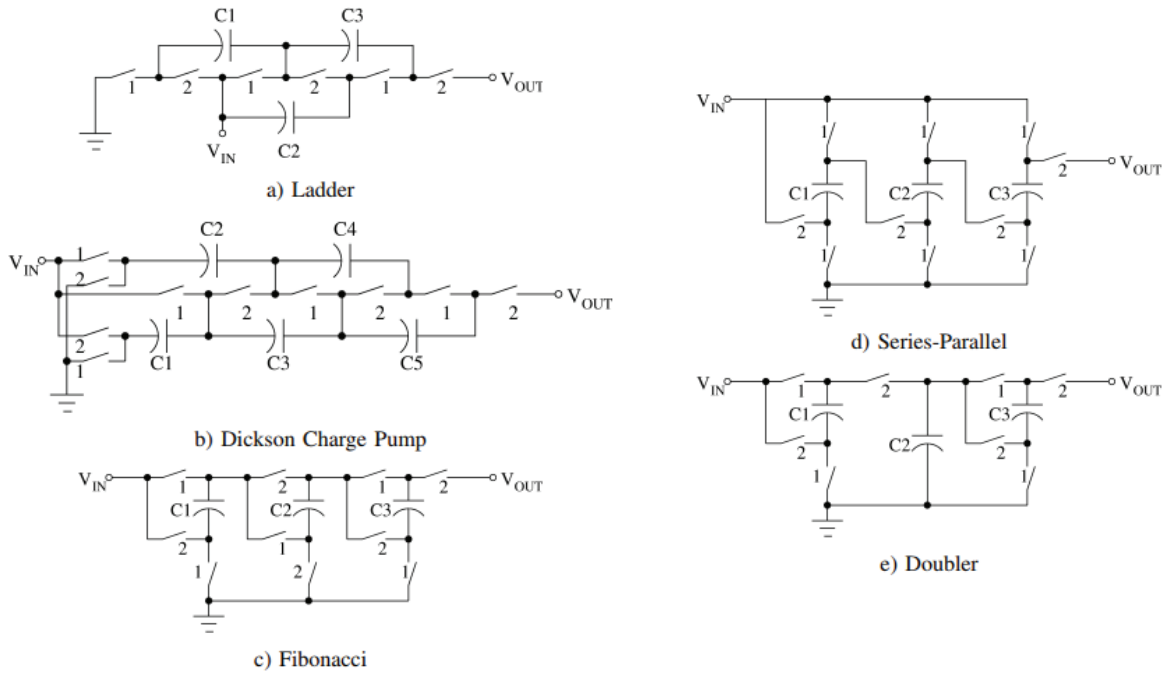

M Seeman and S. Sanders, "Analysis and Optimization of Switched-Capacitor DC-DC Converters"



## Dickson Converter

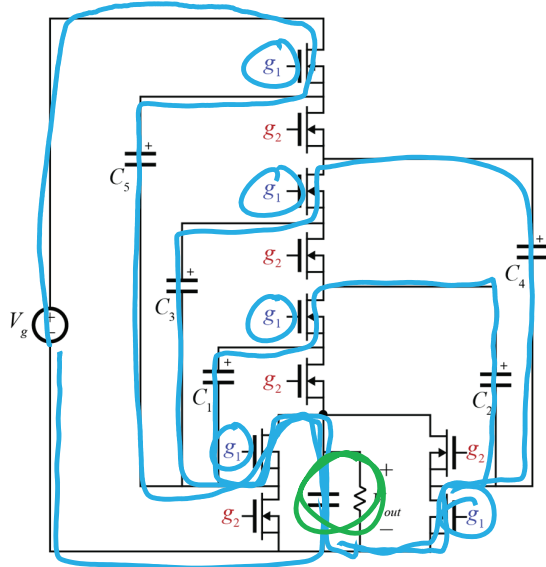


Y. Lei, R. May, and R. Pilawa-Podgurski, "Split-Phase Control: Achieving Complete Soft-Charging Operation of a Dickson Switched-Capacitor Converter," 2016


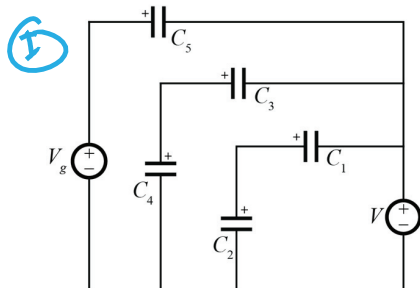
# Dickson Subintervals

Approximate: all caps have very small ripple





$$V_g = 6V$$

$$V_{C1} = 4V$$

$$V_{C2} = V + V_{C1} = 2V$$

→ This is a 6:1 SC converter

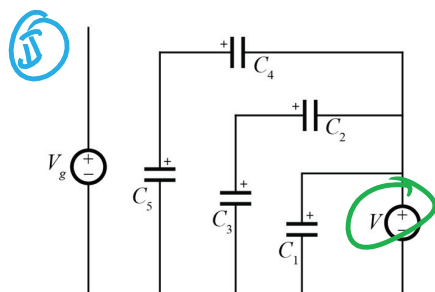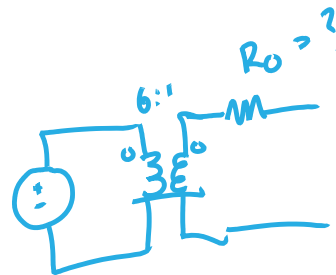

$$V_{C5} = 5V$$

$$V_{C3} = 3V$$

$$V_{C1} = V$$

## Charge Vector Analysis: Notation

$q_x^I$  = charge in/out of element  $x$  during subinterval  $I$

$a_x^I = \frac{q_x^I}{q_{out}^I}$ , normalized with respect to  $q_{out}^I = q_{out}^I + q_{out}^{II} + \dots$

$$\bar{a}^I = [a_{in}^I, \overbrace{a_{C1}^I, a_{C2}^I, \dots, a_{CN}^I}^{\bar{a}_C^I}, a_{out}^I]$$

$$\bar{v}^I = [V_g, V_{C1}^I, V_{C2}^I, \dots, V_{CN}^I, V_{out}]$$

$V_{C1}^I$  = Voltage on  $C_1$  at the end of the subinterval when operated in SSL

# Charge Vector Analysis: Rules


- KVL & KCL must be satisfied
  - for all caps  $\langle i_{c_i} \rangle_{T_0} = \phi$  in steady state
- $$\int_0^{T_0} i_{c_i} dt = \phi = \beta_{c_i}^I + \beta_{c_i}^{II} + \dots + \beta_{c_i}^N = \phi$$

↳ looking @ our vectors

$$a_{c_i}^I + a_{c_i}^{II} + \dots = \phi$$

for two switching subintervals,  $a_{c_i}^I = -a_{c_i}^{II}$

To find output resistance

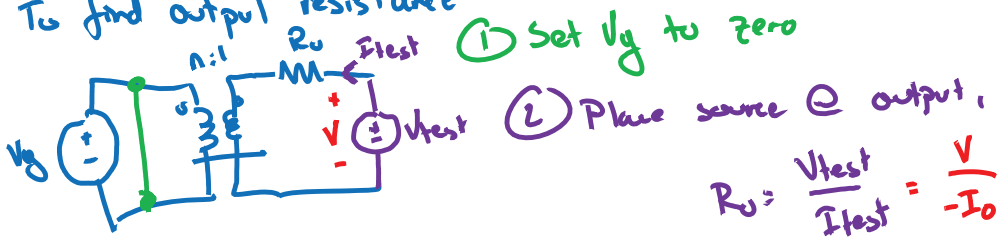

# Tellegen's Theorem

For any circuit which satisfies KVL & KCL

$$\sum_i V_i I_i = \phi \quad (\text{energy conservation})$$

*i = elements*  
*Voltage across*  
*Current through*

Now, for our SC converter:

$$\bar{a}^I \bar{v}^I = \phi \quad \& \quad \bar{a}^{II} \bar{v}^{II} = \phi$$

$$\bar{a}^I \bar{v}^I + \bar{a}^{II} \bar{v}^{II} = \phi$$

*by normalization*

$$V_{out} (a_{c_1}^I + a_{c_2}^{II}) + V_{in} (a_{L_1}^I + a_{L_2}^{II}) + \bar{a}_c^I \bar{v}_c^I + \bar{a}_c^{II} \bar{v}_c^{II} = \phi$$

*when finding Ro*

$$V_{out} + \bar{a}_c^I (\bar{v}_c^I - \bar{v}_c^{II}) = \phi$$

$$V_{out} + \bar{a}_c^I (\Delta \bar{v}_c) = \phi$$

# Tellegen's Theorem

$$V_{out} + \bar{a}_c^T (\Delta \bar{V}_c) = 0$$

$$\Delta V_{ci} = \frac{q_i}{C_i}$$

$$V_{out} + \bar{a}_c^T \cdot \left( \frac{\bar{q}_c^T}{\bar{C}} \right) = 0$$

$$\perp_{\bar{q}_c^T f_s} \left( V_{out} + \sum_{\text{caps}} \frac{q_i}{f_{out}} \frac{q_{ci}}{C_i} \right) = 0$$

$$\frac{V_{out}}{\bar{q}_c^T f_s} = \frac{V_{out}}{I_{out}} = -R_o = - \sum_{\text{caps}} \left( \frac{q_{ci}}{f_{out}} \right)^2 \perp_{C_i f_s}$$

$$R_{o,eq} = \sum_{\text{caps}} \frac{(a_{ci})^2}{C_i f_s}$$