

# Steady-State Large-Signal Analysis


$$\mathbf{x}(T_s) = \left( \prod_{i=n_{sw}}^1 e^{A_i t_i} \right) \mathbf{x}(0) + \sum_{i=1}^{n_{sw}} \left\{ \left( \prod_{k=n_{sw}}^{i+1} e^{A_k t_k} \right) A_i^{-1} (e^{A_i t_i} - I) \mathbf{B}_i \right\} U$$

In steady-state,  $\mathbf{x}(T_s) = \mathbf{x}(0)$


$$\mathbf{x}(T_s) = \left( I - \prod_{i=n_{sw}}^1 e^{A_i t_i} \right)^{-1} \sum_{i=1}^{n_{sw}} \left\{ \left( \prod_{k=n_{sw}}^{i+1} e^{A_k t_k} \right) A_i^{-1} (e^{A_i t_i} - I) \mathbf{B}_i \right\} U$$

Gives explicit solution for steady-state operation of any switching circuit


## Small Signal Modeling

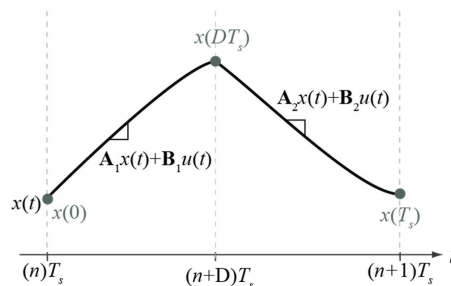

# Small Signal Modeling

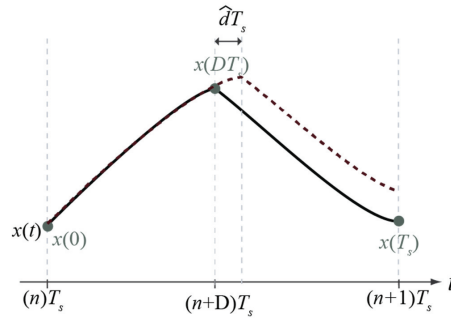

# Small Signal Modeling

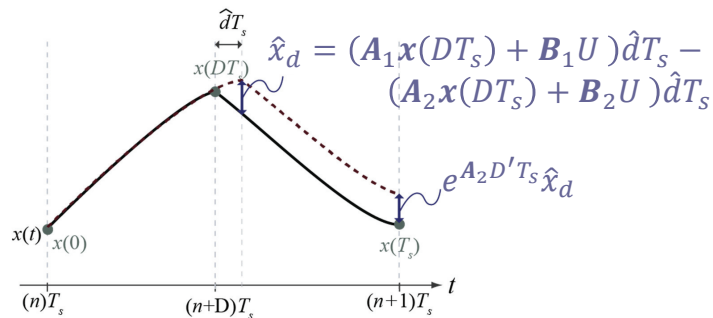

# Complete Small Signal Model

This completes the small-signal model


$$\hat{\mathbf{x}}[n + 1] = \mathbf{\Phi}\hat{\mathbf{x}}[n] + \mathbf{\Psi}\hat{u}[n] + \mathbf{\Gamma}\hat{d}[n]$$

where


$$\mathbf{\Gamma} = e^{A_2 D' T_s} \left( (\mathbf{A}_1 - \mathbf{A}_2) \mathbf{X}_D + (\mathbf{B}_1 - \mathbf{B}_2) U \right) T_s$$

with  $\mathbf{X}_D = \mathbf{x}(DT_s)$  in steady-state

## Example Results

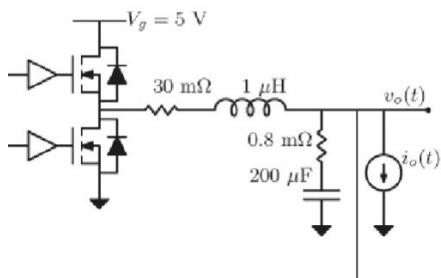


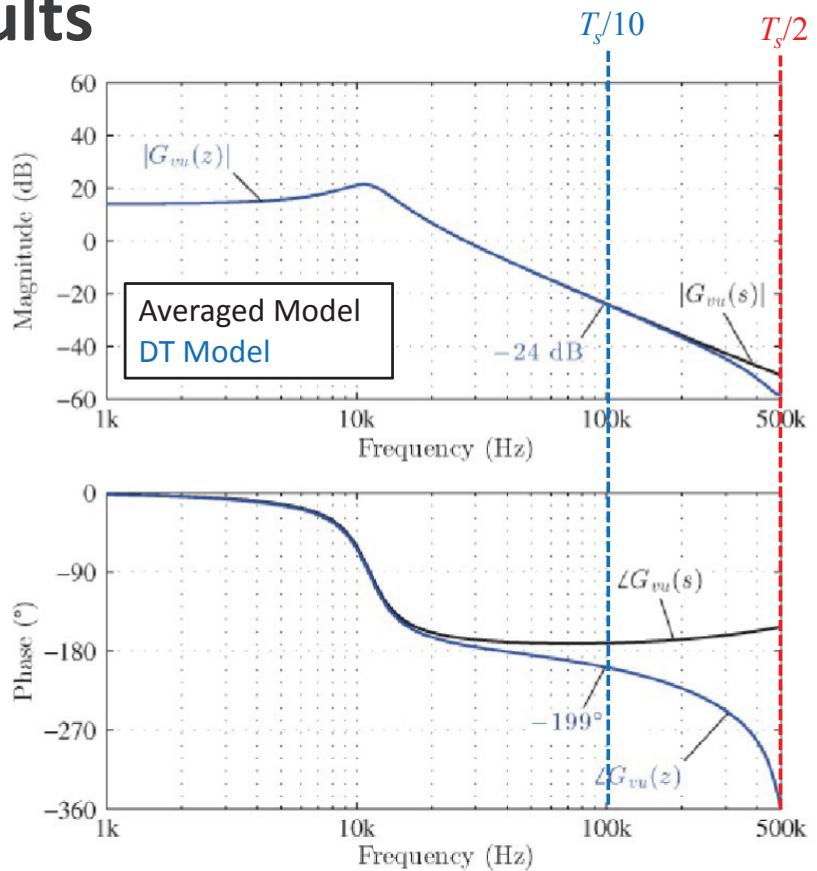\* Includes  $t_d=760$ ns of delay in feedback loop



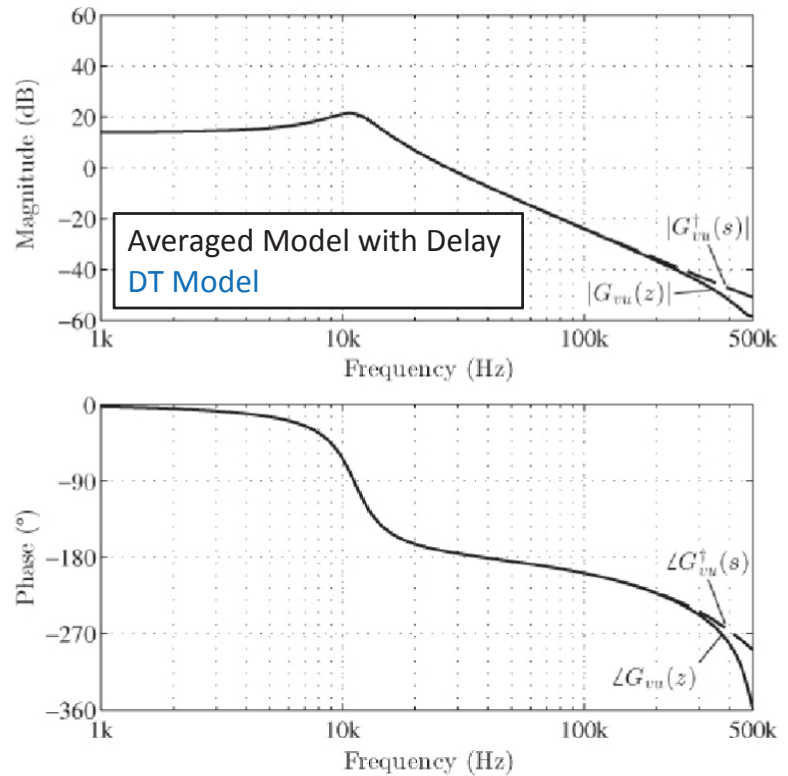
# Inclusion of Delay

$$G_{vu}^{\dagger}(s) = G_{vu}(s)e^{-st_d}$$



# Current Control


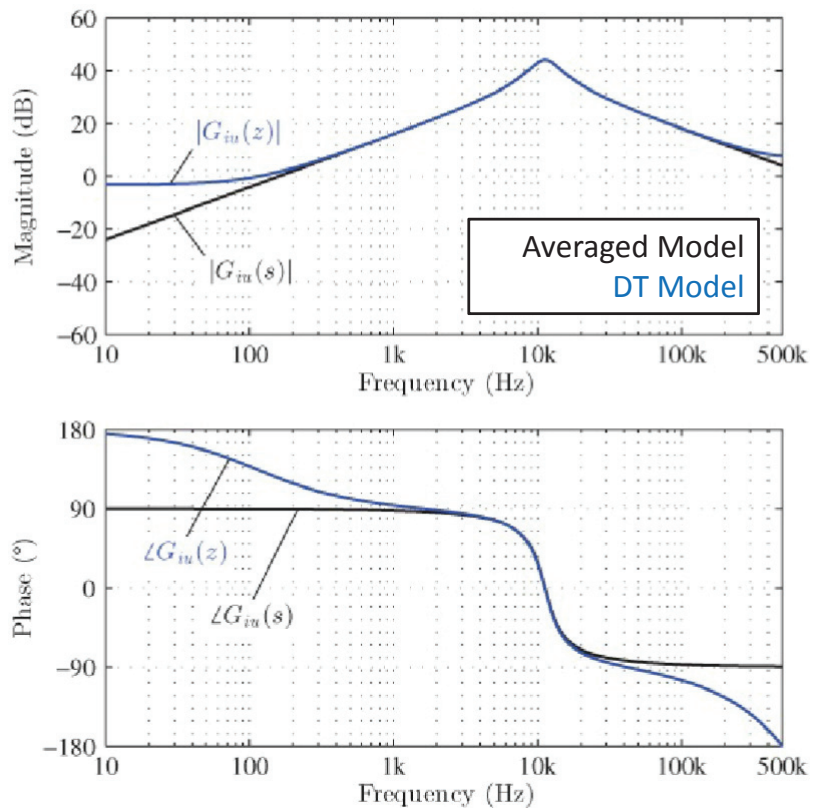


# Discrete Time Analysis: Results

$$X_{ss} = \left( I - \prod_{i=n_{sw}}^1 e^{A_i t_i} \right)^{-1} \sum_{i=1}^{n_{sw}} \left\{ \left( \prod_{k=n_{sw}}^{i+1} e^{A_k t_k} \right) A_i^{-1} (e^{A_i t_i} - I) B_i \right\} U$$



- Valid for any switched circuit, as long as
  1. Inputs,  $U$ , are constant or slowly varying
  2. All times  $t_i$  are known
  3. Every subinterval can be described by a linear circuit
- Requires no dedicated analysis other than finding  $A_i$  and  $B_i$
- Decisively **not** a design-oriented equation
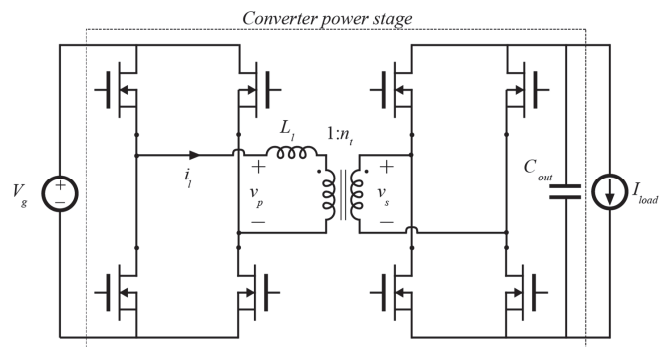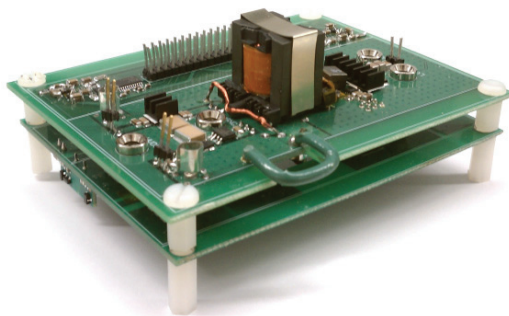
## Example: DAB Design Using Dedicated Analysis





- Design of a high step-down DAB for Data Centers
- 150-to-12V, 120 W, 1MHz, design
- Prototype achieved 98.4% peak efficiency

# DAB Topology

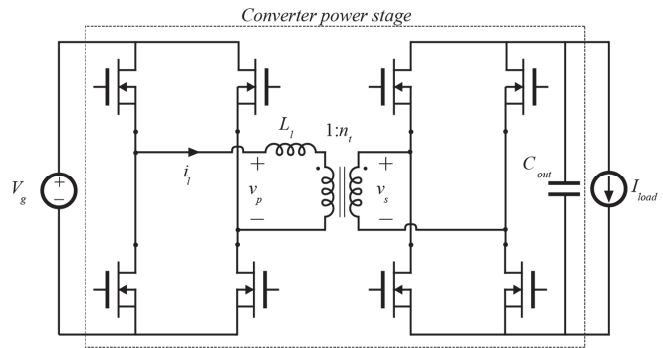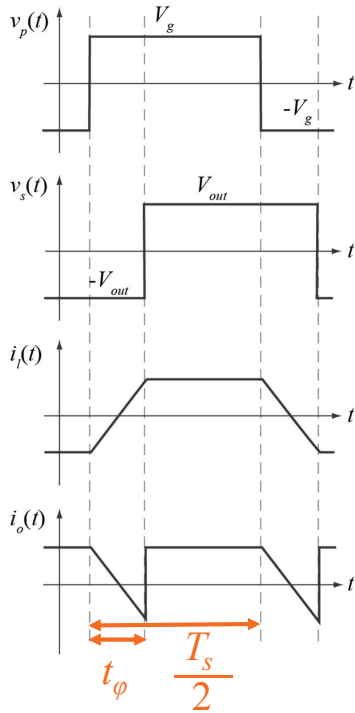

- Near-DCX Operation
- Phase-shift modulation to control power flow
- Zero-voltage switching of all devices at high power



## Linear Averaged Modeling of DAB

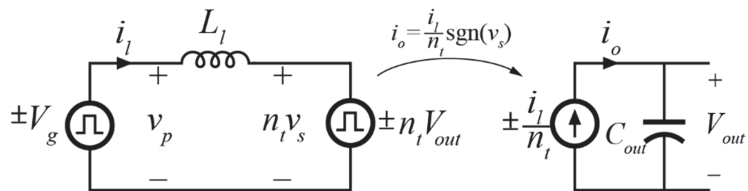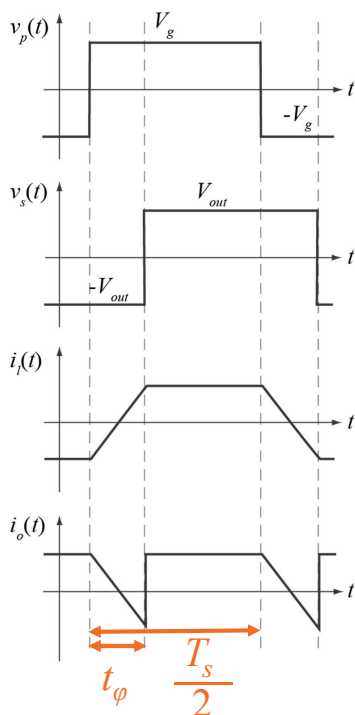

- Modeling  $\dot{x}_i$  as constant within any subinterval, waveforms are PWL
- Can solve low-frequency behavior from waveforms


$$\langle i_o \rangle |_{T_s} \approx \int_0^{T_s} \frac{i_o(t) dt}{T_s} = \frac{v_g(t)}{n_t L_l T_s} (T_s t_\phi - 2t_\phi^2)$$

# DAB Operated at High Frequency

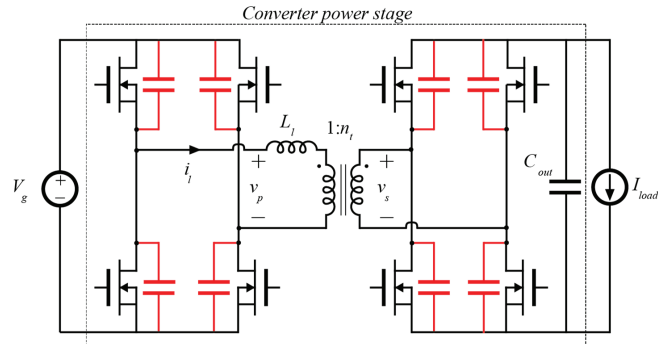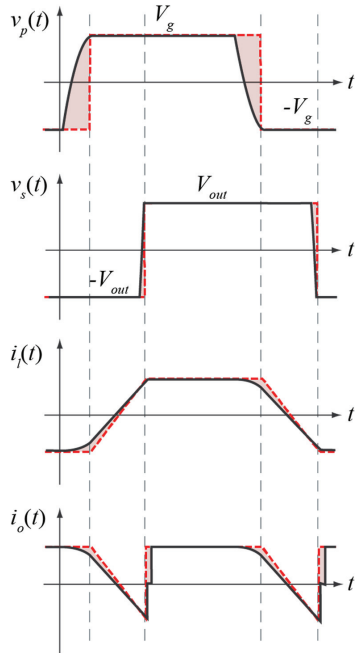


- Resonance between  $L_l$  and transistor capacitance distorts waveforms
- Resonance *may* need to be modeled when operating at high frequency


## DAB Waveforms

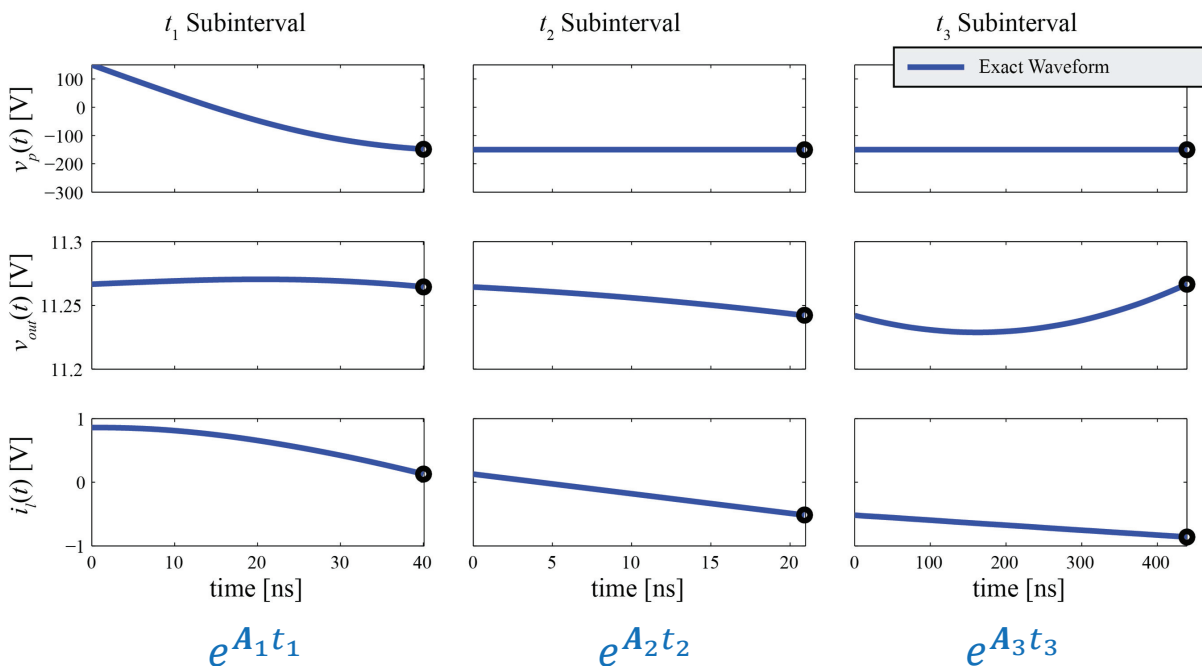

# Linear Waveform Approximation

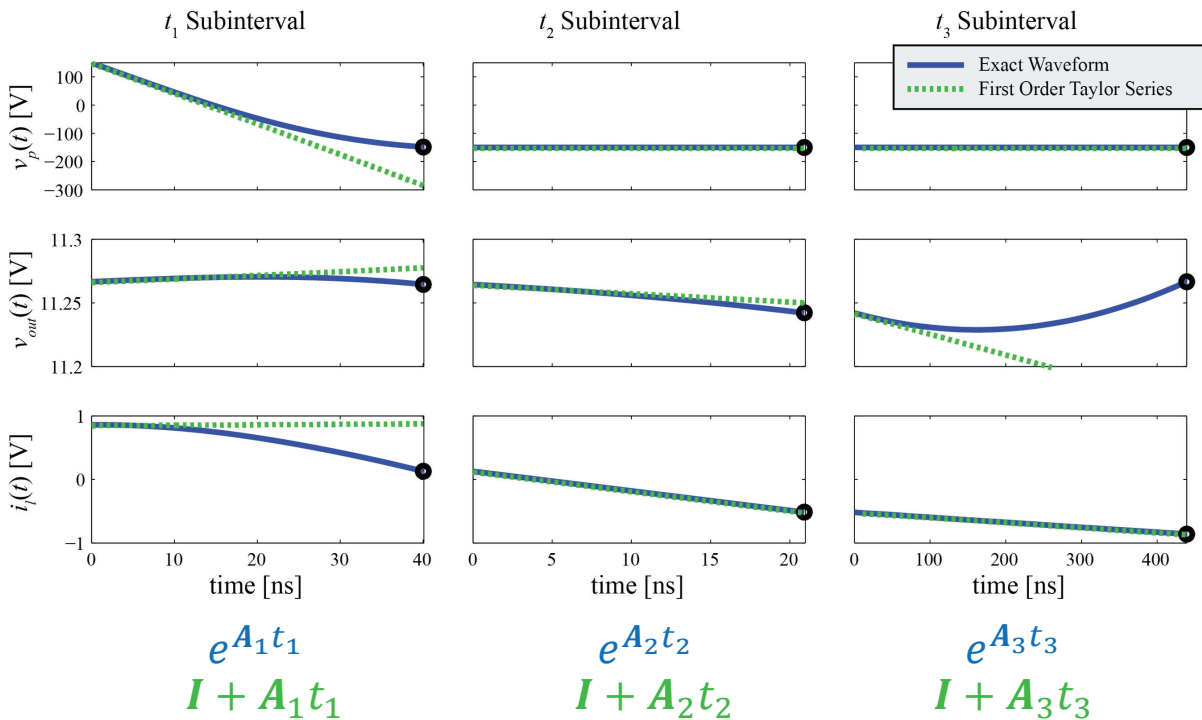


# Linear Waveform Approximation

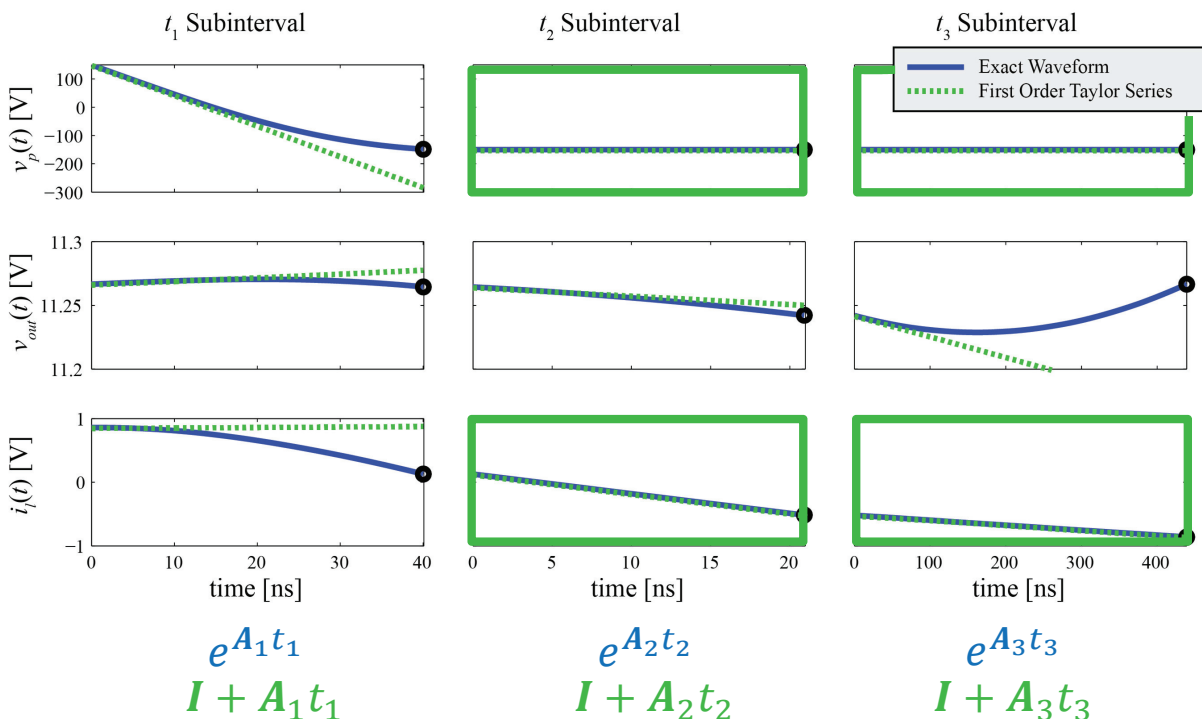






# Second Order Approximation

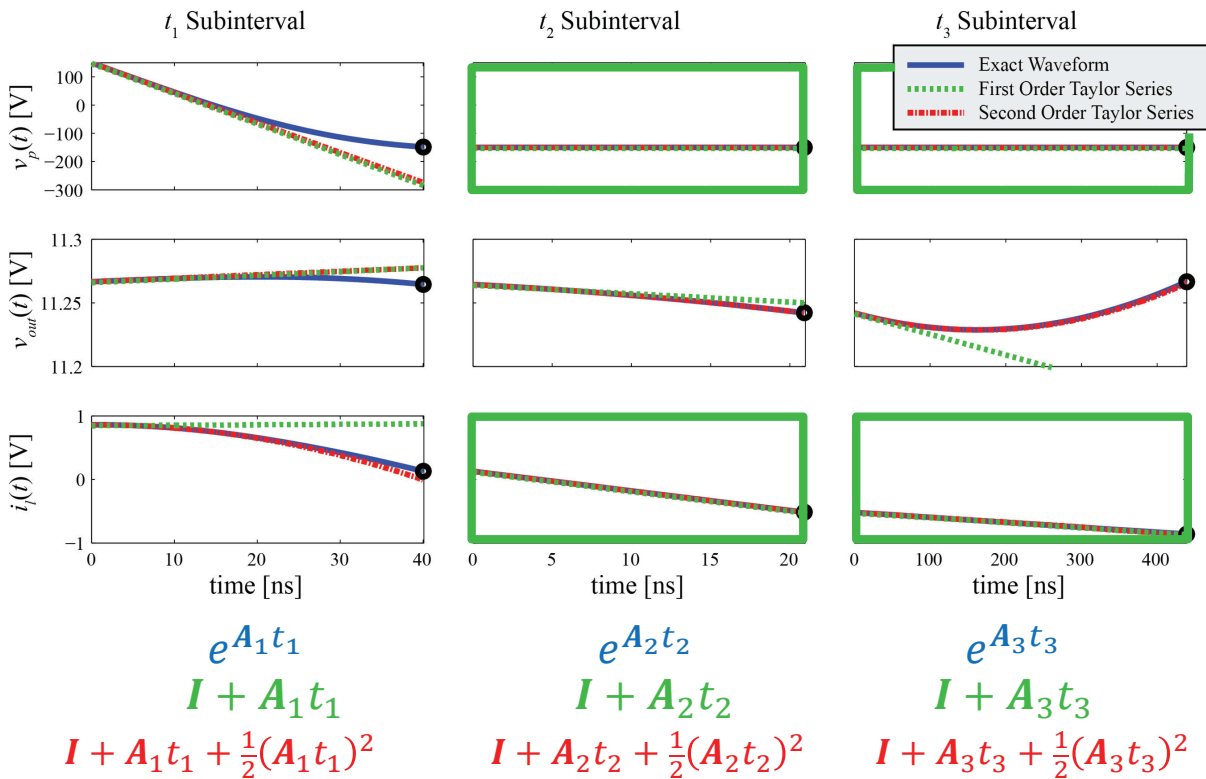

# Second Order Approximation

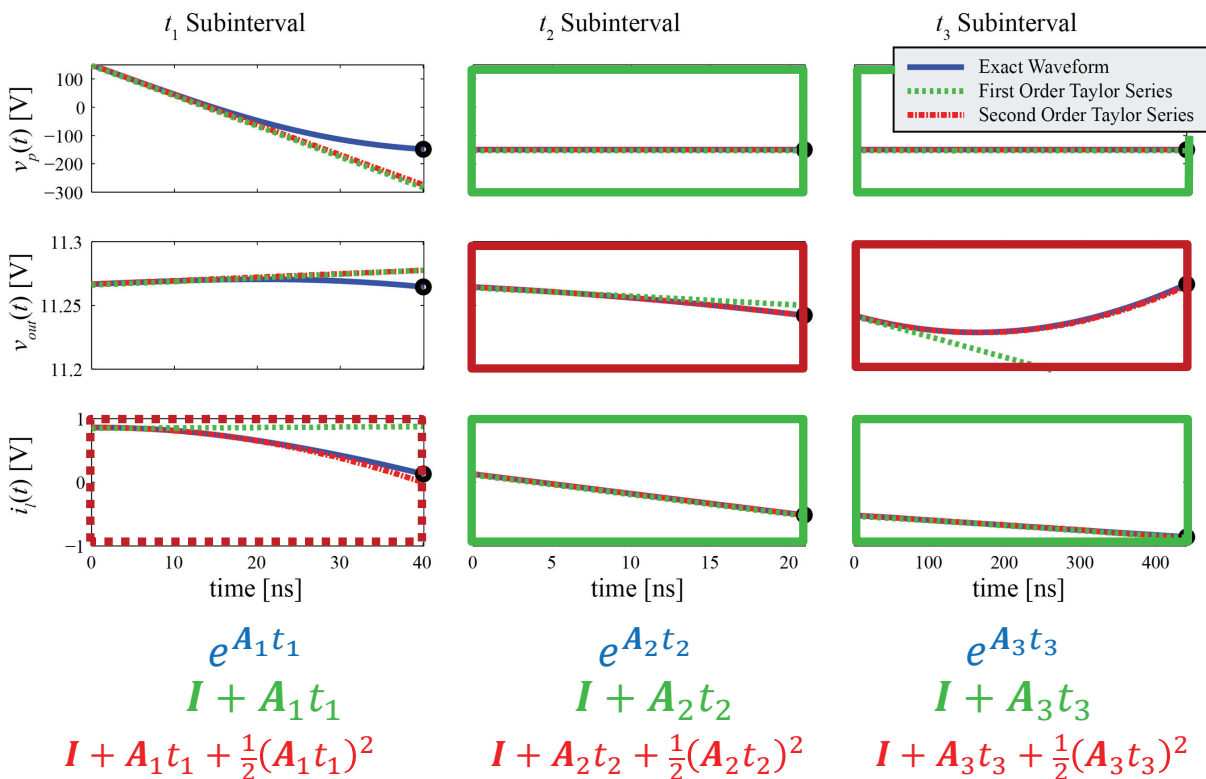

# State Plane Analysis of DAB Converter

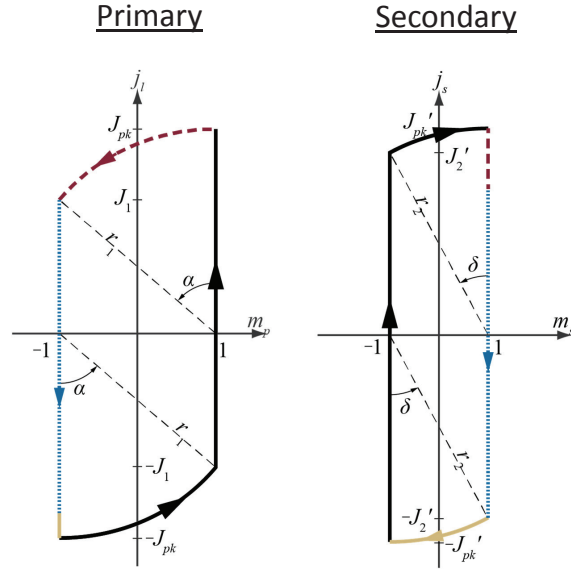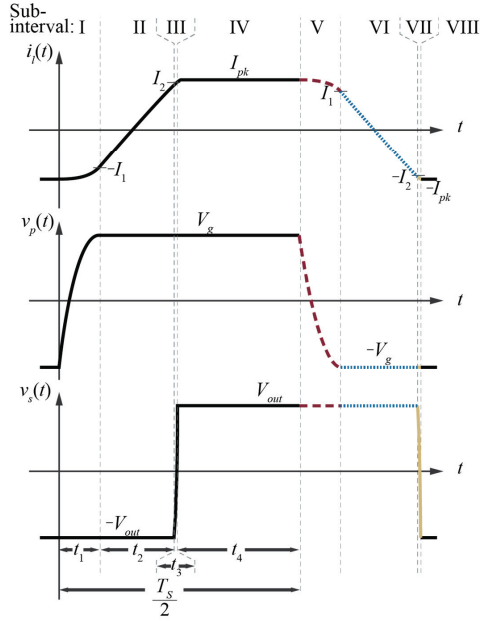

$$I_{base} = V_g \sqrt{\frac{C_p}{L_l}}$$

$$I_{base} = V_g \sqrt{\frac{C_s}{n_t^2 L_l}}$$

## State Plane Solution

Solution "Read off" state plane

$$\alpha = \sin^{-1} \frac{2}{J_p}$$

Primary Dead Time

$$\beta = \frac{1}{2}(J_2 + J_1)$$

Phase Shift

$$\delta = n_t \sin^{-1} \frac{2n_t}{R_0' J_p} \sqrt{\frac{C_s}{C_p}}$$


Secondary Dead Time

$$\zeta = \frac{F}{\pi} - \alpha - \beta - \delta$$


$$J_1 = \sqrt{J_p^2 - 4}$$

$$J_2 = \frac{R_0}{R_0'} \sqrt{\left( J_p \frac{R_0'}{R_0} \right)^2 - (2n_t)^2}$$
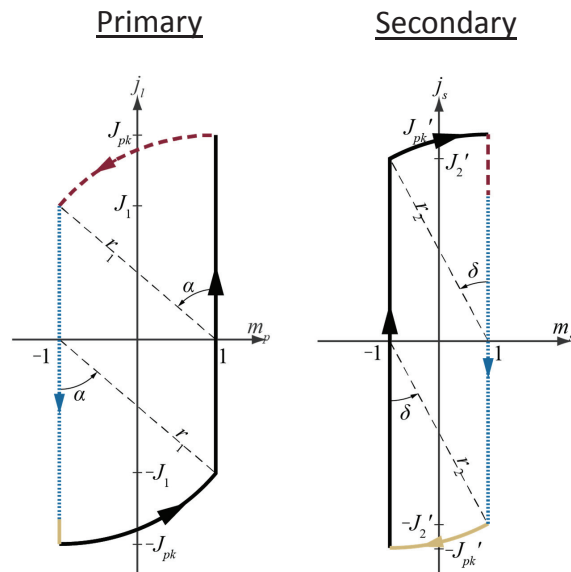
$$J = \frac{F}{\pi} \left[ 2 + \frac{1}{4}(J_1^2 - J_2^2) + J_p \left( \frac{\pi}{F} - \alpha - \beta - \delta \right) \right]$$




# Different Operating Modes

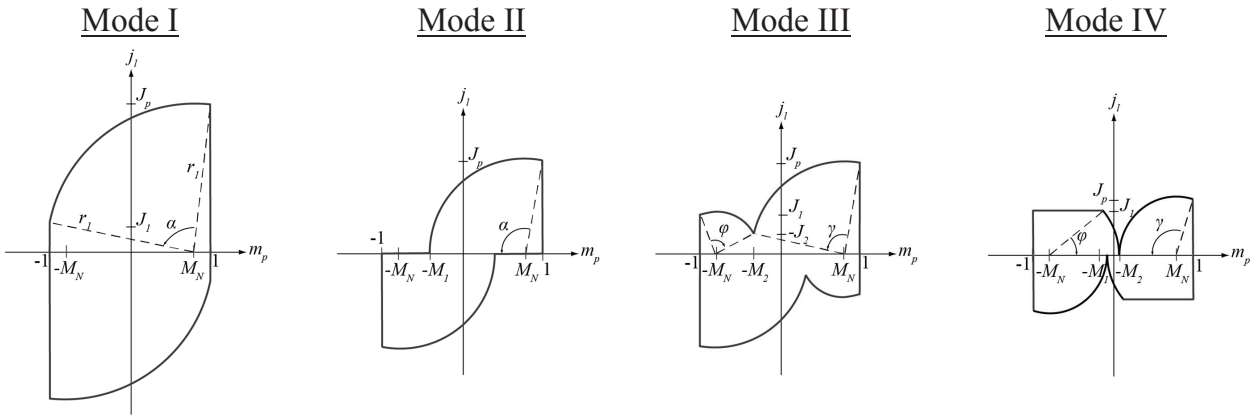





- As control, input and load vary, operating mode changes
- In each mode, solution is a set of transcendental equations

# Different Operating Modes

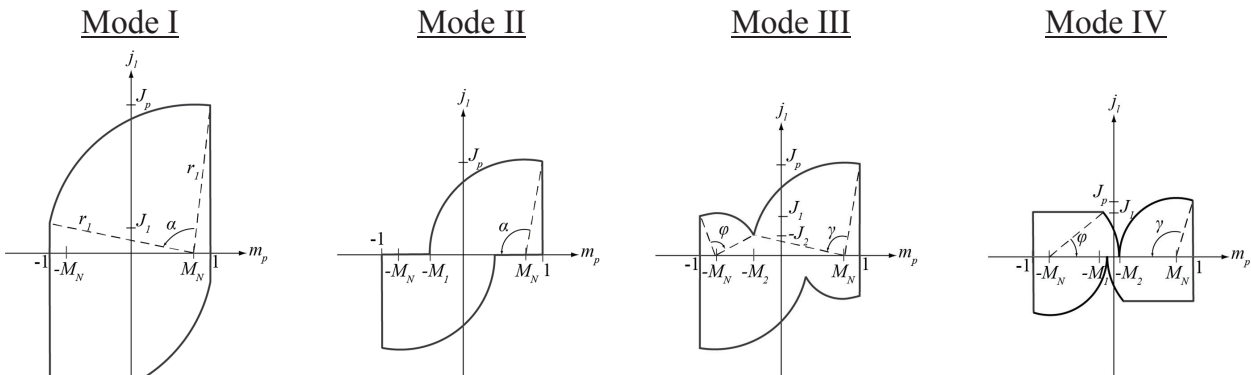

$J_1 = \sqrt{J_p^2 - 4M_N}$ $\alpha = \cos^{-1} \left( 1 - \frac{(J_p - J_1)^2 + 4}{2J_p^2 + 2(1 - M_N)^2} \right)$ $\beta = \frac{J_1 + J_2}{1 + M_N}$ $\zeta = \frac{J_p - J_2}{1 - M_N}$ $\frac{\pi}{F} = \alpha + \beta + \delta$ $J = \frac{\langle i_o \rangle}{I_{base}} = \frac{F}{n_t \pi} \left( 2 + \frac{J_p + J_2}{2} \zeta + \frac{J_1 - J_2}{2} \beta \right)$	$M_1 = \sqrt{J_p^2 + (1 - M_N)^2} - M_N$ $\alpha = \cos^{-1} \left( 1 - \frac{J_p^2 + (1 + M_1)^2}{2(M_1 - M_N)^2} \right)$ $J = \frac{\langle i_o \rangle}{I_{base}} = \frac{F}{n_t \pi} \left( 1 + M_1 + \frac{J_p + J_2}{2} \zeta - \frac{J_2}{2} \beta \right)$ $\beta = \frac{J_1 + J_2}{1 + M_N}$ $\zeta = \frac{J_p - J_2}{1 - M_N}$ $\frac{\pi}{F} = \alpha + \beta + \delta$	$\gamma = \cos^{-1} \left( 1 - \frac{(J_p + J_2)^2 + (1 + M_2)^2}{2(1 - M_N)^2 + 2J_p^2} \right)$ $\phi = \cos^{-1} \left( 1 - \frac{(J_1 + J_2)^2 + (1 - M_2)^2}{2(M_N - M_2)^2 + 2J_2^2} \right)$ $J_2^2 = (1 - M_N)^2 + J_p^2 - (M_2 + M_N)^2$ $J_1^2 = -(1 - M_N)^2 + J_2^2 + (M_N - M_2)^2$ $\zeta = \frac{J_p + J_1}{1 - M_N}$ $\frac{\pi}{F} = \gamma + \phi + \zeta = \alpha + \zeta$ $J = \frac{\langle i_o \rangle}{I_{base}} = \frac{F}{n_t \pi} \left( 2M_2 + \frac{J_p - J_1}{2} \zeta \right)$	$\phi = \cos^{-1} \left( 1 - \frac{J_1^2 + (M_1 - M_2)^2}{2(M_N - M_2)^2} \right)$ $J = \frac{\langle i_o \rangle}{I_{base}} = \frac{F}{n_t \pi} \left( 2M_2 + 1 - M_1 + \frac{J_p - J_1}{2} \zeta \right)$ $J_2^2 = (1 - M_N)^2 + J_p^2 - (M_2 + M_N)^2$ $J_1^2 = -(1 - M_N)^2 + J_2^2 + (M_N - M_2)^2$ $\zeta = \frac{J_p + J_1}{1 - M_N}$ $\frac{\pi}{F} = \gamma + \phi + \zeta = \alpha + \zeta$
---	---	--	---


# Model Validation

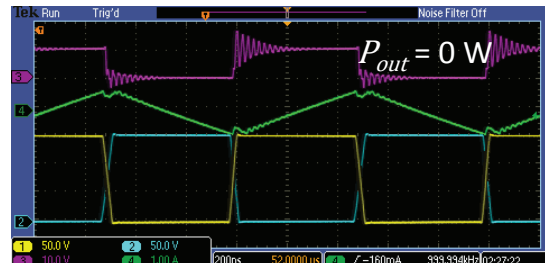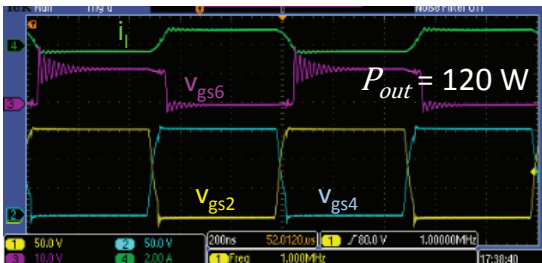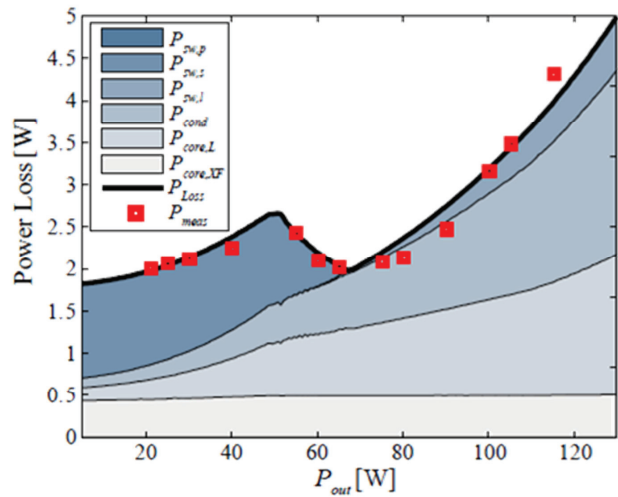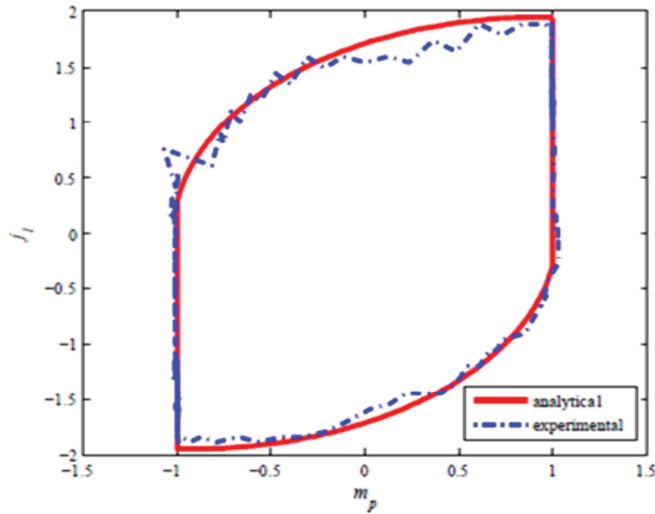

D Costinett, D. Maksimovic, and R Zane, "Design and Control for High Efficiency in High Step-Down Dual Active Bridge Converters Operating at High Switching Frequency," *IEEE Trans. On Pwr. Elec.*, 2013



# State Plane Analysis Characteristics

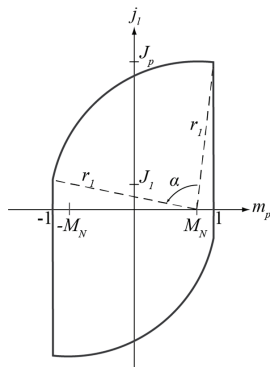

$$J_1 = \sqrt{J_p^2 - 4M_N}$$

$$\alpha = \cos^{-1} \left( 1 - \frac{(J_p - J_1)^2 + 4}{2J_p^2 + 2(1 - M_N)^2} \right)$$

$$\beta = \frac{J_1 + J_2}{1 + M_N}$$

$$\zeta = \frac{J_p - J_2}{1 - M_N}$$

$$\frac{\pi}{F} = \alpha + \beta + \delta$$

$$J = \frac{\langle i_o \rangle}{I_{base}} = \frac{F}{n_t \pi} \left( 2 + \frac{J_p + J_2}{2} \zeta + \frac{J_1 - J_2}{2} \beta \right)$$


## For analysis

- State plane analysis is simple and intuitive
- Plots give insight into converter operation
- Easy to write equations for single parameter of interest

## For Design


- Complete solution is not solvable in closed-form
- No loss mechanisms included inherently
- Can only be computed, inverted numerically
- Design intuition comes only from repeated numerical evaluation

# Different Operating Modes

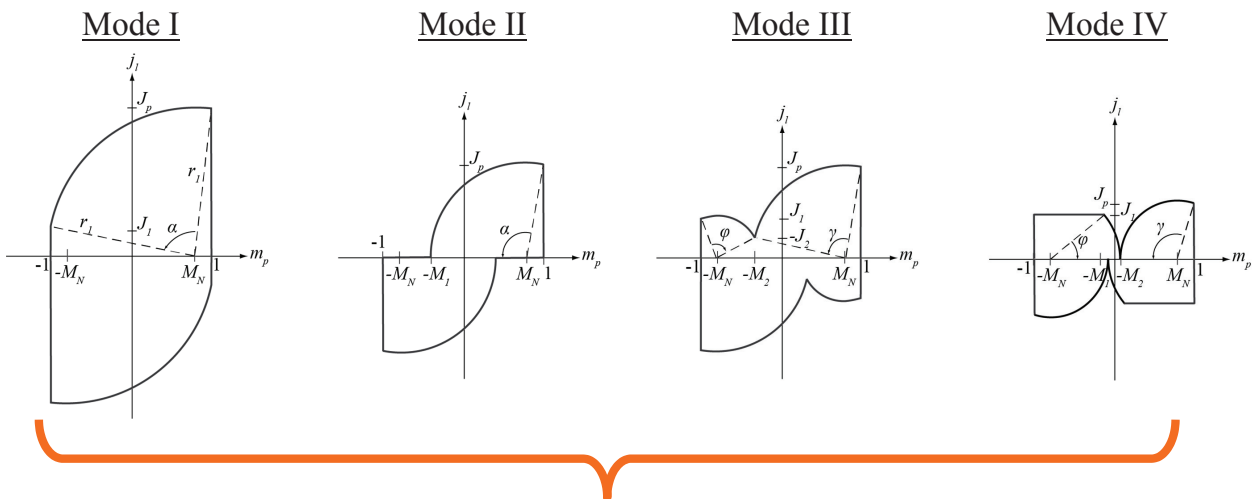


$$X_{ss} = \left( I - \prod_{i=n_{sw}}^1 e^{A_i t_i} \right)^{-1} \sum_{i=1}^{n_{sw}} \left\{ \left( \prod_{k=n_{sw}}^{i+1} e^{A_k t_k} \right) A_i^{-1} (e^{A_i t_i} - I) B_i \right\} U$$

## Discrete Time Model Validation

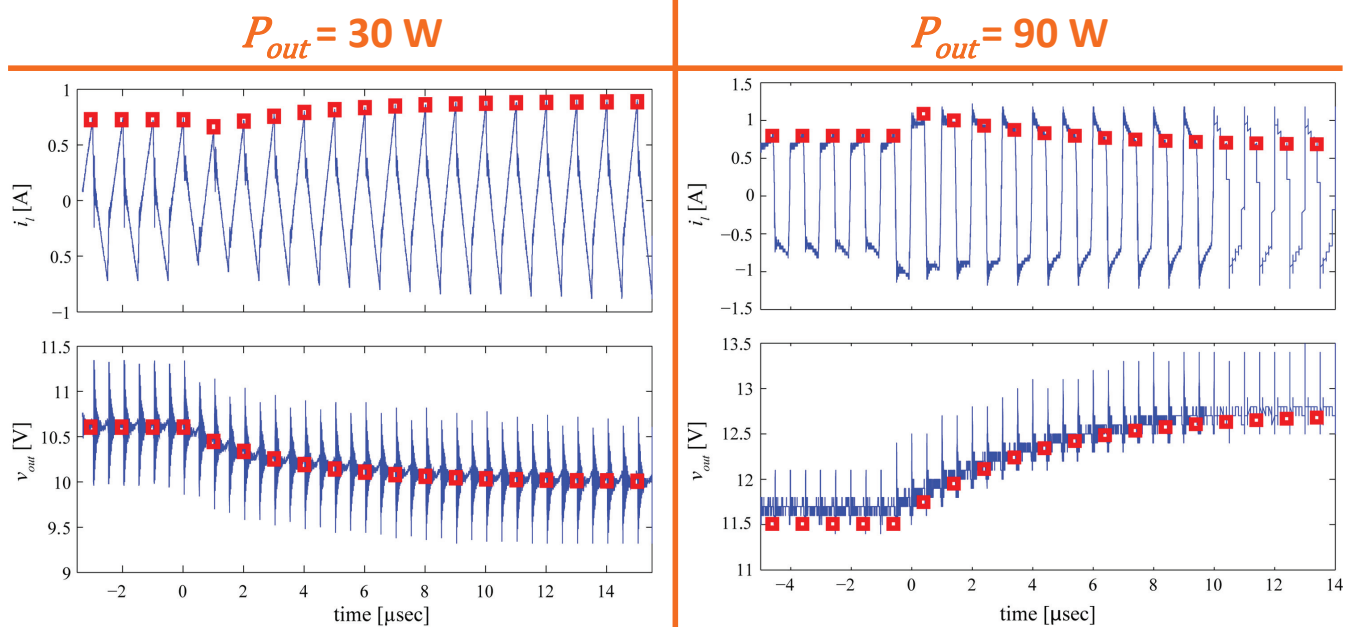


# Discrete Time Dynamic Model Validation

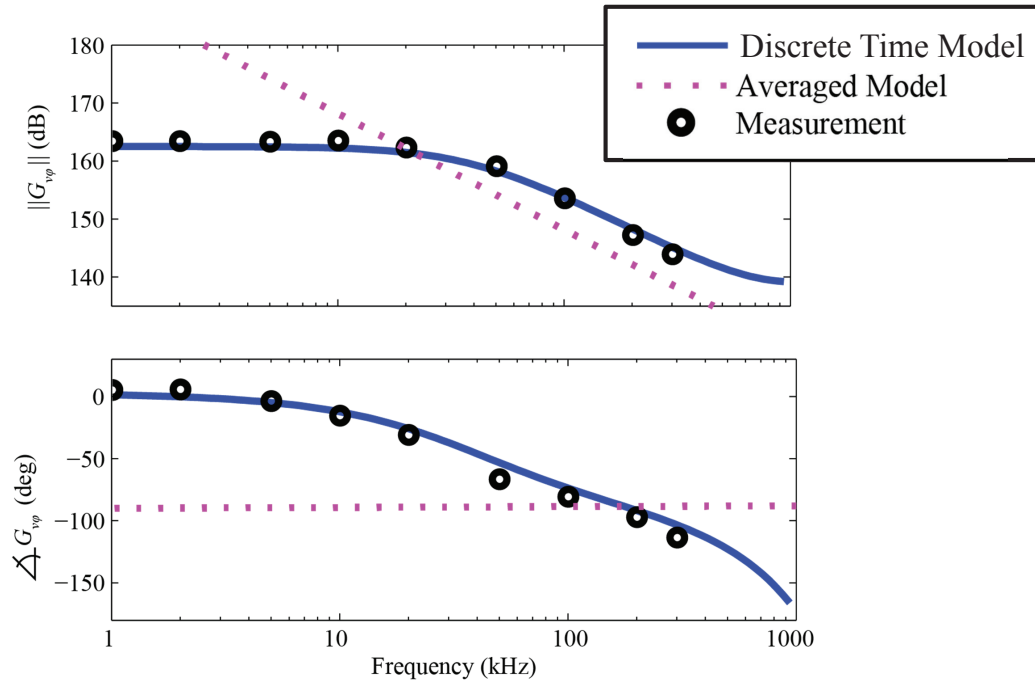


D. Costinett, R. Zane, and D. Maksimovic, "Discrete-time small-signal modeling of a 1 MHz efficiency-optimized dual active bridge converter with varying load," in Proc. IEEE Workshop Contr. Modl. (COMPEL), June 2012, pp. 1–7.

## Different Operating Modes

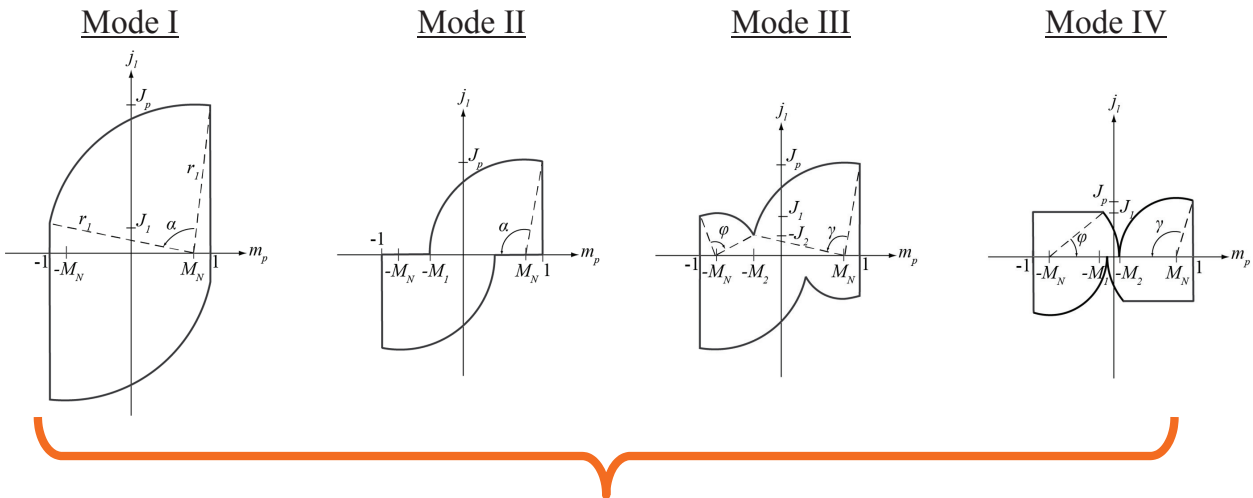

$$\mathbf{X}_{ss} = \left( \mathbf{I} - \prod_{i=n_{sw}}^1 e^{\mathbf{A}_i t_i} \right)^{-1} \sum_{i=1}^{n_{sw}} \left\{ \left( \prod_{k=n_{sw}}^{i+1} e^{\mathbf{A}_k t_k} \right) \mathbf{A}_i^{-1} (e^{\mathbf{A}_i t_i} - \mathbf{I}) \mathbf{B}_i \right\} \mathbf{U}$$

# Different Topologies

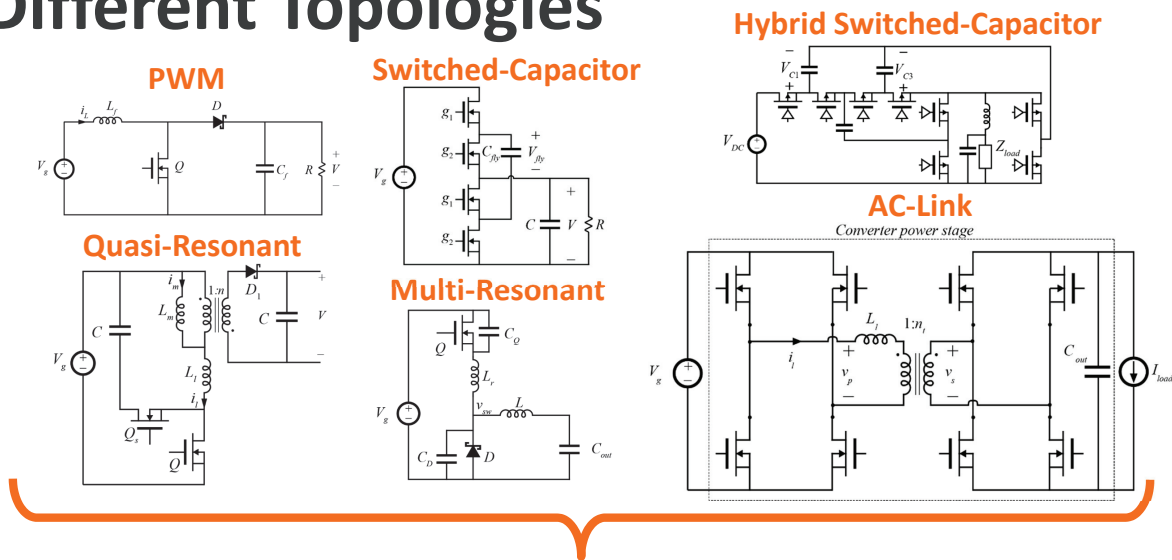


$$X_{SS} = \left( I - \prod_{i=n_{sw}}^1 e^{A_i t_i} \right)^{-1} \sum_{i=1}^{n_{sw}} \left\{ \left( \prod_{k=n_{sw}}^{i+1} e^{A_k t_k} \right) A_i^{-1} (e^{A_i t_i} - I) B_i \right\} U$$

## Applications of Analysis

- Dedicated analysis (e.g. State Plane) useful to obtain detailed knowledge of circuit operation
  - Effort required precludes consideration of broad range of vastly different designs
  - In complex, high-performance circuits, result is often still not “invertible”
- Discrete time analysis is general, and requires no dedicated analysis
  - Can we get the same level of **design intuition**
    - By supplementing with dedicated analysis
    - By using computational design
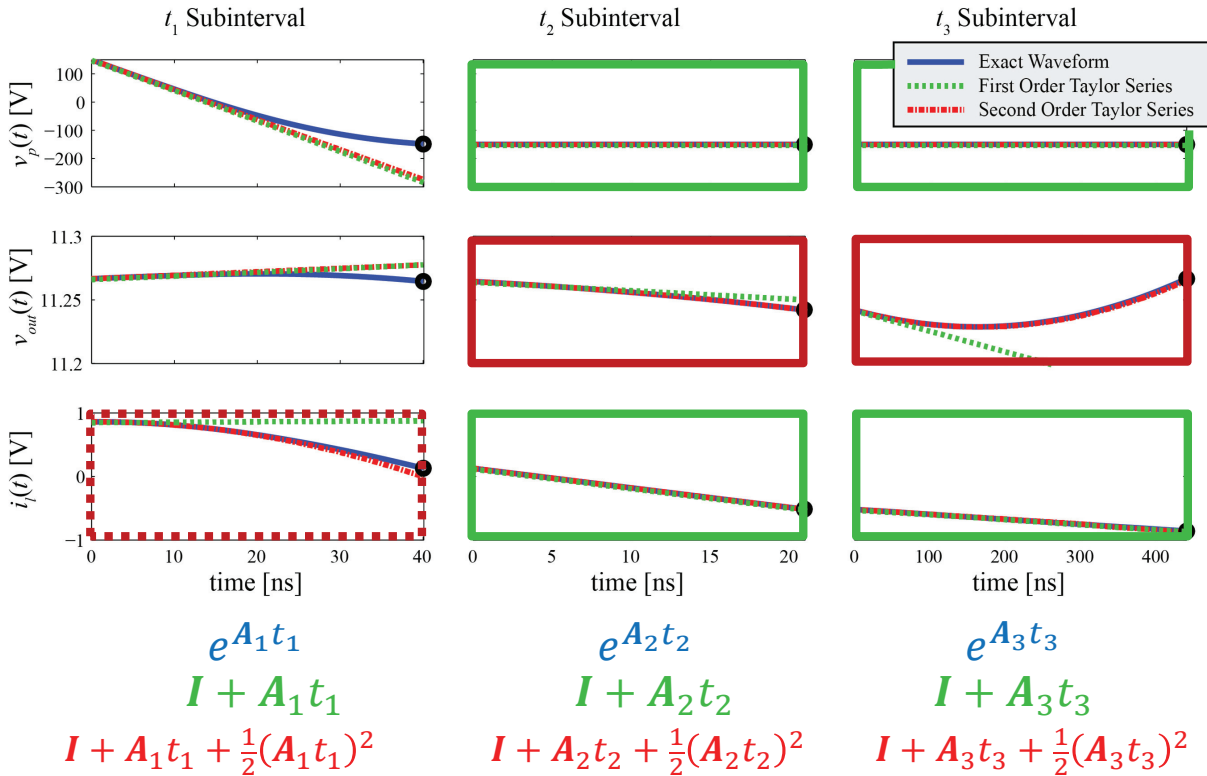
# Analytical Approach: Selective Linearization



## Model ZVS as Disturbance

Consider how model takes transition into account:


$$\Phi = e^{A_3 t_3} e^{A_2 t_2} e^{A_1 t_1} I_{HC}$$

where

$$\hat{x}(t_1) = e^{A_1 t_1} \hat{x}(t_0)$$

with  $A_1 \in \mathbb{R}^{3 \times 3}$

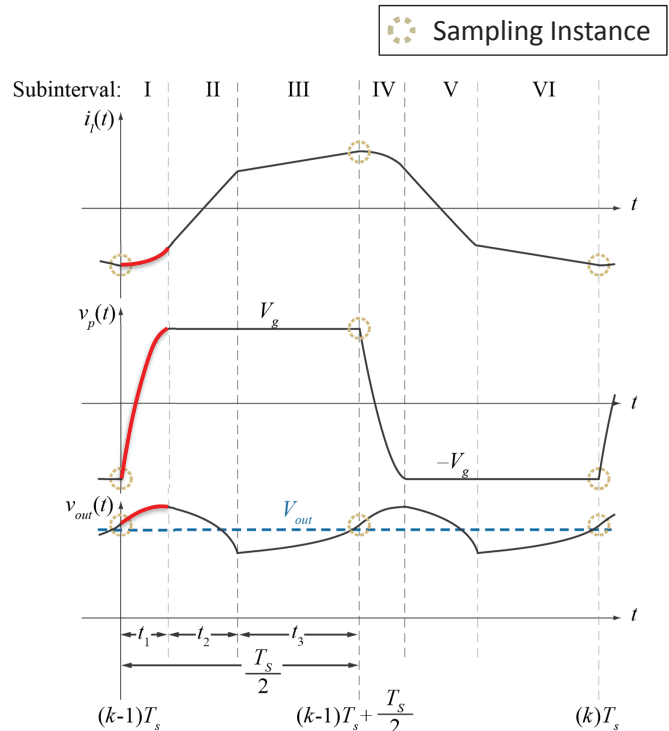Using dedicated analysis, solve new matrix  $A_{res} \in \mathbb{R}^{2 \times 2}$  which models how ZVS transition affects states at  $t=t_1$





# Resonant Transition Matrix


Eliminating resonant interval reduces system to second order,  $\mathbf{x} = [i_l \ v_{out}]^T$

New matrix takes the form

$$\mathbf{A}_{res} = \begin{bmatrix} \frac{\partial v_{out}(t_1)}{\partial v_{out}(0)} & \frac{\partial v_{out}(t_1)}{\partial i_l(0)} \\ \frac{\partial i_l(t_1)}{\partial v_{out}(0)} & \frac{\partial i_l(t_1)}{\partial i_l(0)} \end{bmatrix}$$

Linearized with respect to  $\mathbf{x}(0)$ , rather than time

## Resonant Interval Solution

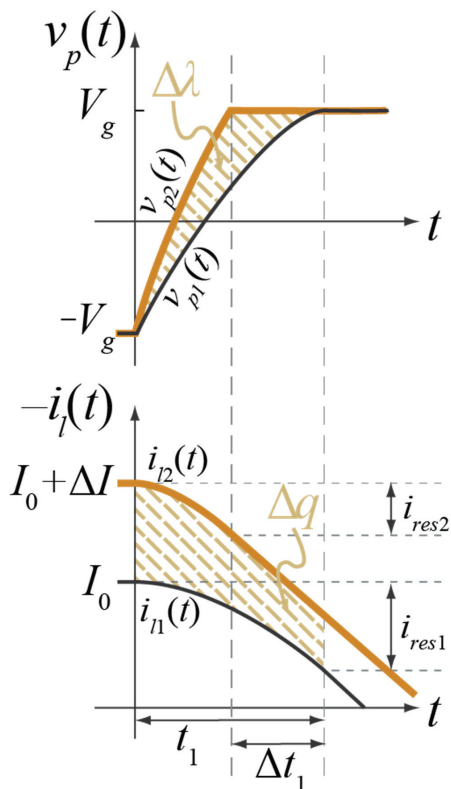

Linearized relations solved using circuit analysis

$$\frac{\Delta\lambda}{\Delta I} = L_l - L_l \sqrt{1 - \left(\frac{2V_g}{R_0 I_0}\right)^2},$$

$$\frac{\Delta Q}{\Delta I} = \frac{2V_g C_p}{I_0},$$

Relationships vary depending on operating mode

# Linearized Result

Assuming small ripple on  $V_{out}$

$$\mathbf{A}_{res} = \begin{bmatrix} \frac{\partial v_{out}(t_1)}{\partial v_{out}(0)} & \frac{\partial v_{out}(t_1)}{\partial i_l(0)} \\ \frac{\partial i_l(t_1)}{\partial v_{out}(0)} & \frac{\partial i_l(t_1)}{\partial i_l(0)} \end{bmatrix} = \begin{bmatrix} 1 & \frac{\Delta Q}{\Delta I} \frac{1}{C_{out}} \\ 0 & 1 - \frac{\Delta \lambda}{\Delta I} \frac{1}{L_l} \end{bmatrix}$$

Resulting model is now

$$\Phi = e^{\mathbf{A}_3 t_3} e^{\mathbf{A}_2 t_2} \mathbf{A}_{res} \mathbf{I}_{HC}$$

$$\Gamma = e^{\mathbf{A}_3 t_3} (\mathbf{A}_2 - \mathbf{A}_3) \mathbf{X}_0$$

where  $\Phi \in \mathbb{R}^{2 \times 2}$  and  $\Gamma \in \mathbb{R}^{2 \times 1}$



## Resulting Model

$$\Phi = \begin{bmatrix} 1 - \frac{\omega_f^2 t_\zeta^2}{2n_t^2} & \frac{\frac{\Delta Q}{\Delta I} (L_l n_t - \frac{t_\zeta^2}{2C_{out} n_t}) + t_\zeta (\frac{\Delta \lambda}{\Delta I} - L_l)}{\frac{n_t}{\omega_f^2}} \\ \frac{t_\zeta}{L_l n_t} & -1 + \frac{\frac{\Delta \lambda}{\Delta I} (C_{out} n_t - \frac{t_\zeta^2}{2L_l n_t}) - t_\zeta \frac{\Delta Q}{\Delta I} + \frac{t_\zeta^2}{2n_t}}{\frac{n_t}{\omega_f^2}} \end{bmatrix}$$

Previously, an accurate, closed-form expression for  $\Phi$  was intractable


Model now of suitable complexity for design-oriented analysis

# Model Accuracy

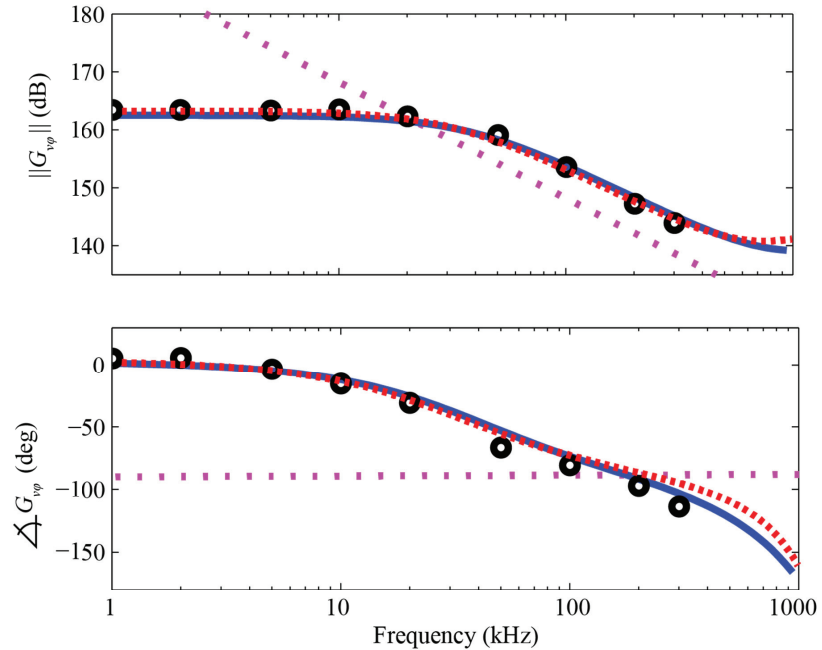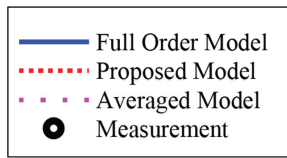


## Numerical Approach: HDSC Example

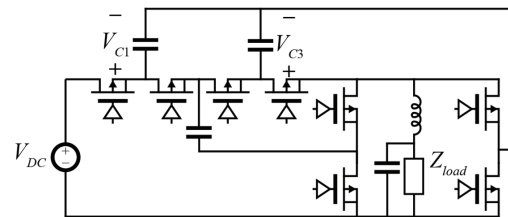- 4:1 Hybrid Dickson Switched-Capacitor Converter
- 48-to-5 V, 0-100 A output
- Including  $C_{OSS}$ , 13 states, 3 subintervals



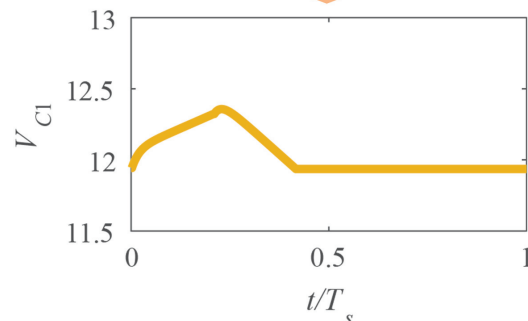
$$X_{ss} = \left( I - \prod_{i=n_{sw}}^1 e^{A_i t_i} \right)^{-1} \sum_{i=1}^{n_{sw}} \left\{ \left( \prod_{k=n_{sw}}^{i+1} e^{A_k t_k} \right) A_i^{-1} (e^{A_i t_i} - I) B_i \right\} U$$




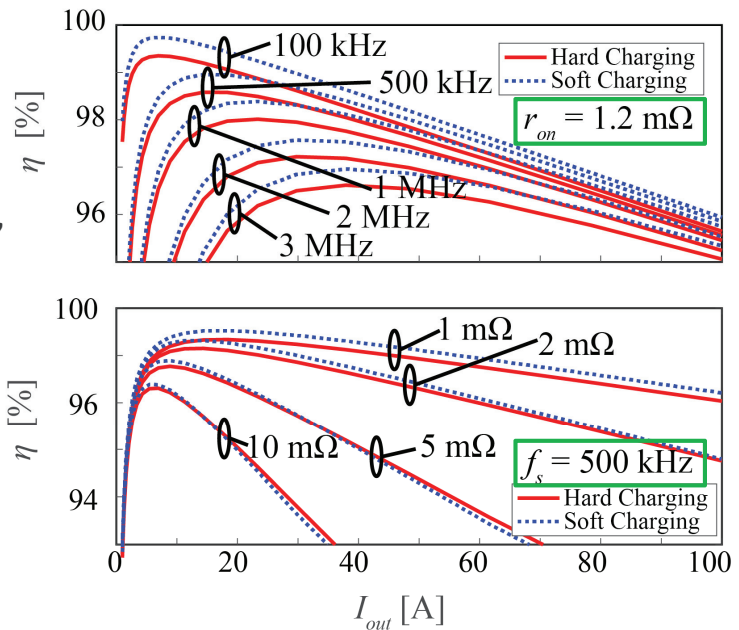
# HDSC: Predicted Efficiency

- Inherent efficiency prediction
  - Full, large-signal models
  - No “ideal waveform” assumption
- Total computation time  $\sim 10\text{ms}$  per operating point
- No converter-specific derivation


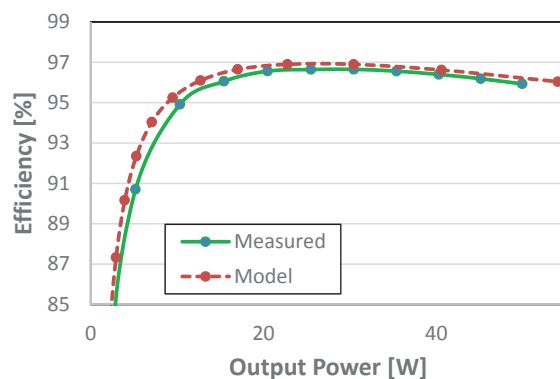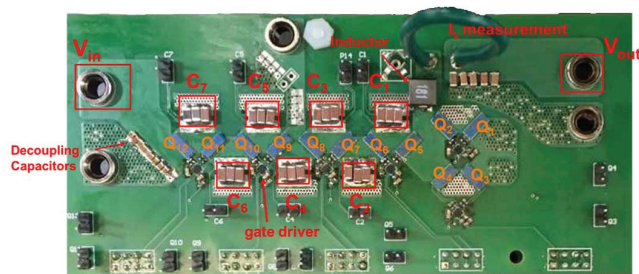
## Model Validation

- Constructed 8:1 HDSC converter
  - Measured 96.7% peak efficiency at 30W
  - Model predicts 96.9% at 30.4W
- Model includes capacitor ESR




# Limiting Assumptions of the Approach

1. Inputs are DC or slowly varying
2. All subinterval times are known
3. In each subinterval, converter reduces to a linear equivalent circuit


# Limiting Assumptions of the Approach

- ~~1. Inputs are DC or slowly varying~~
2. All subinterval times are known
3. In each subinterval, converter reduces to a linear equivalent circuit


# Non-Controlled Switching Times

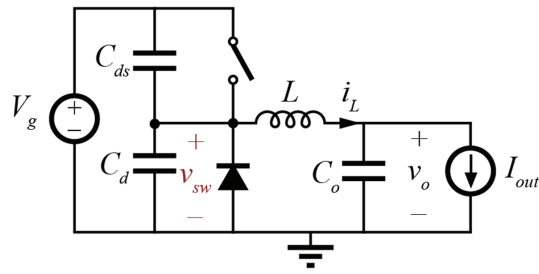


# Non-Controlled Switching Times

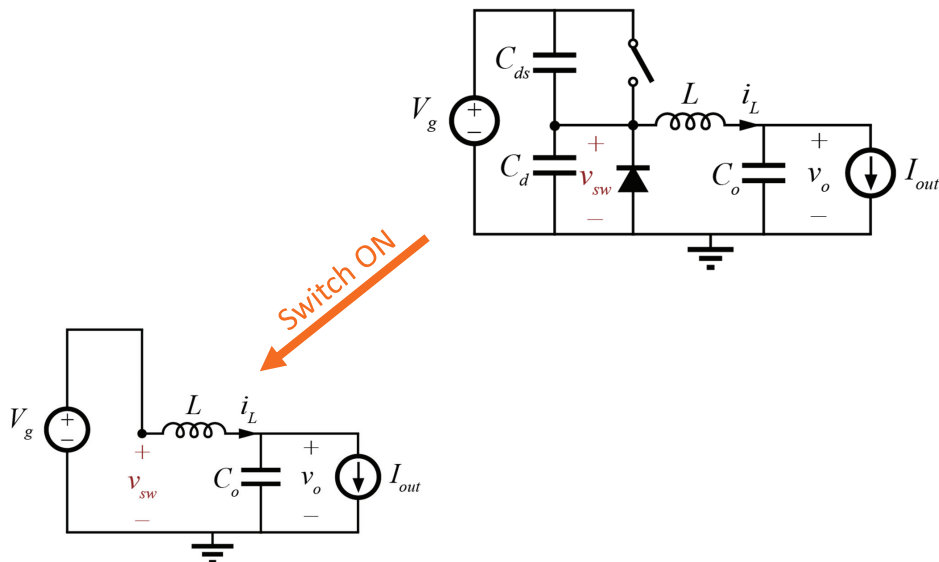



# Non-Controlled Switching Times

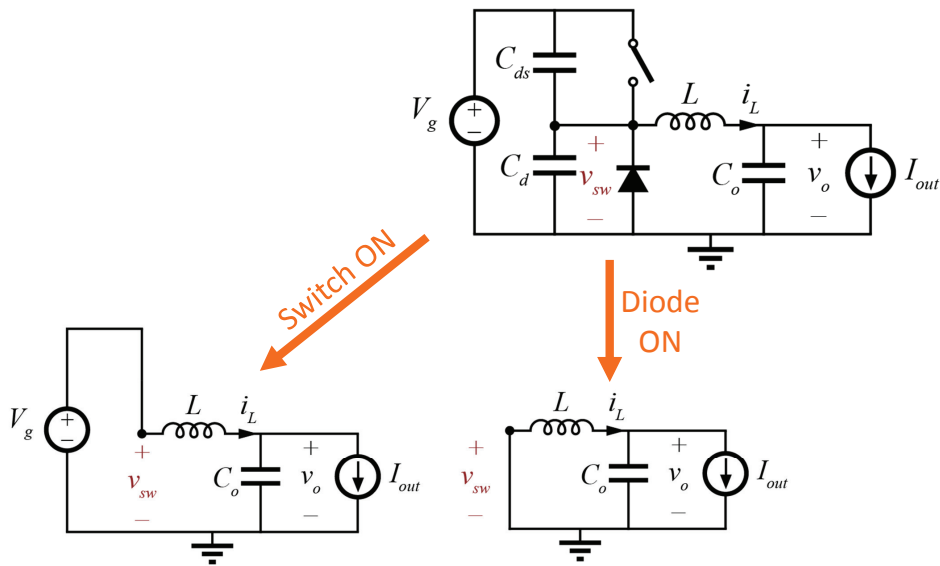




# Non-Controlled Switching Times

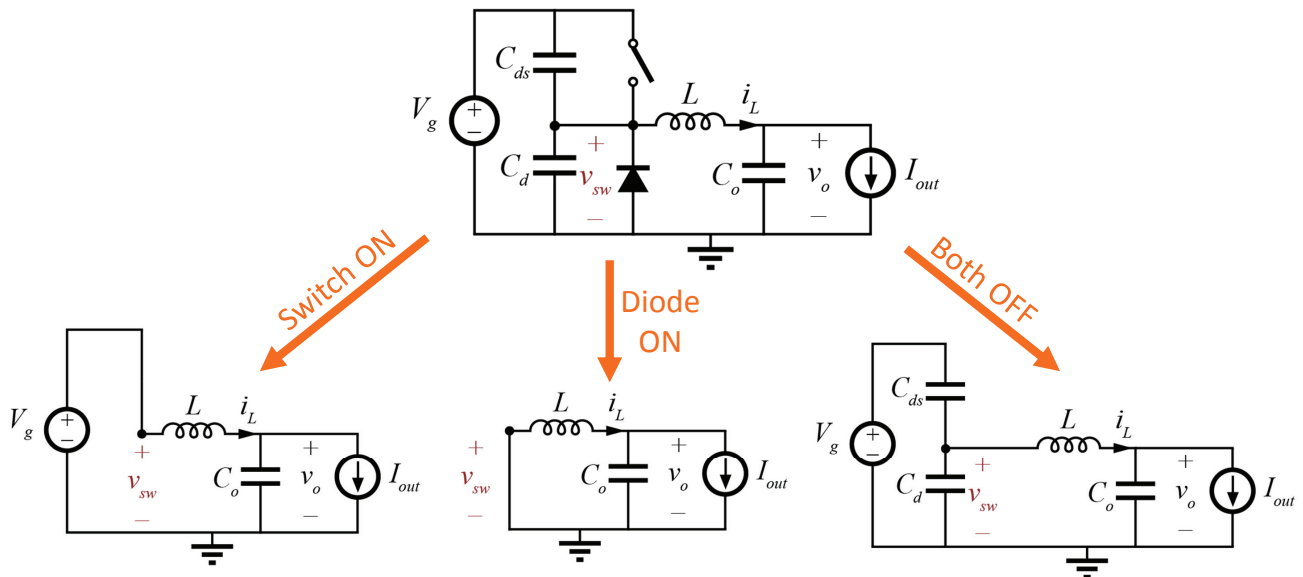

# Non-Controlled Switching Times

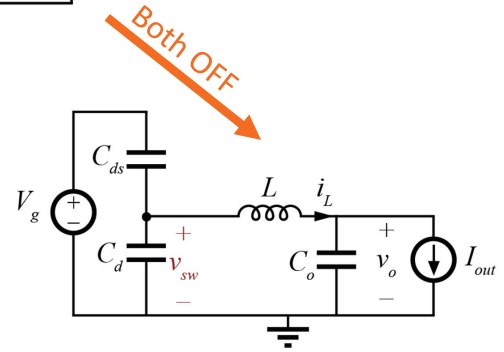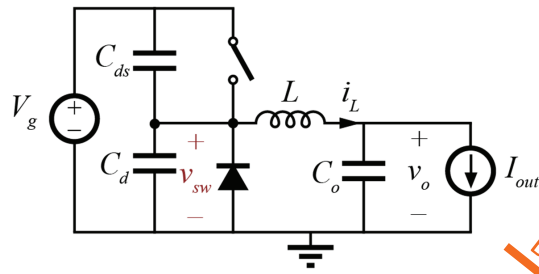


# Non-Controlled Switching Times

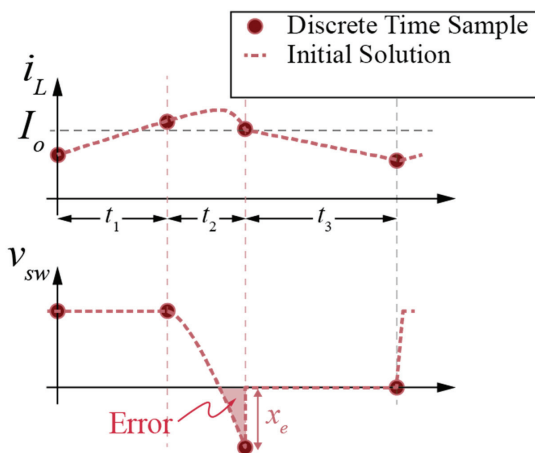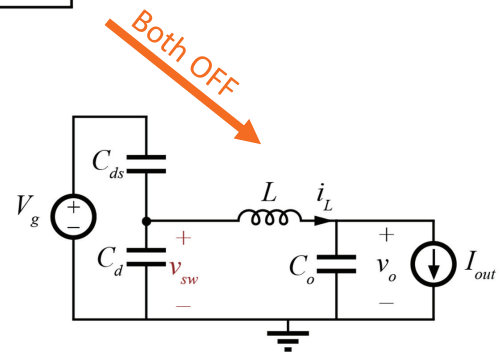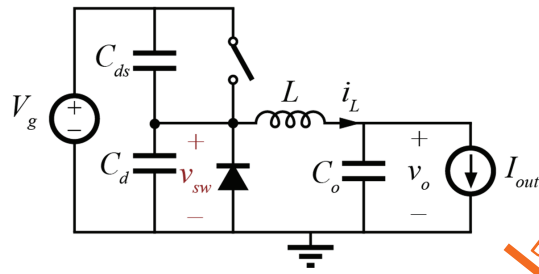




# Non-Controlled Switching Times

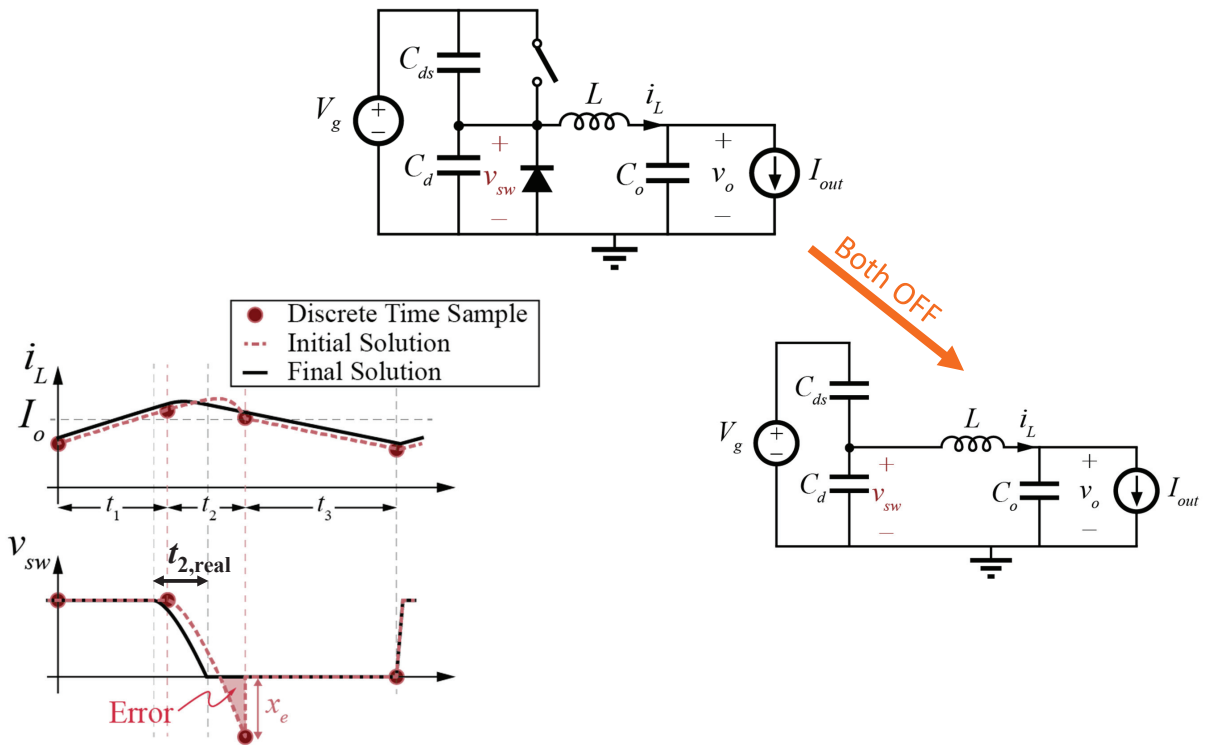


# Non-Controlled Switching Times

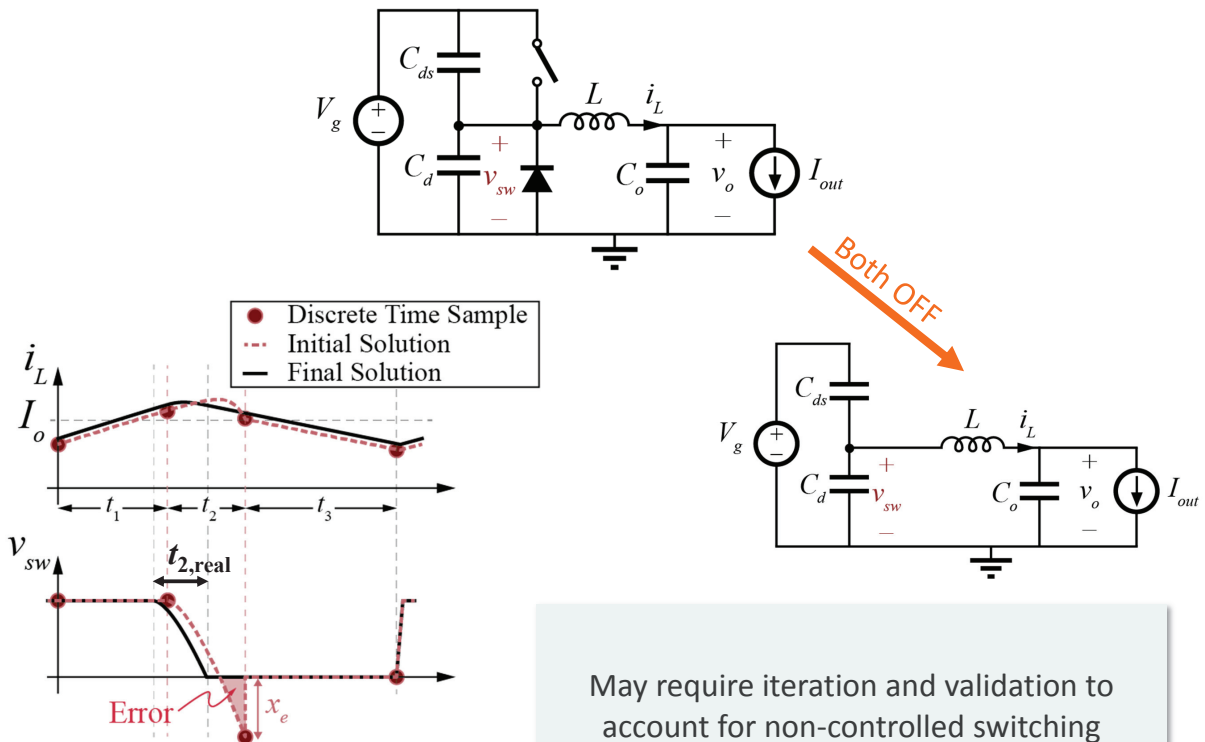

May require iteration and validation to account for non-controlled switching


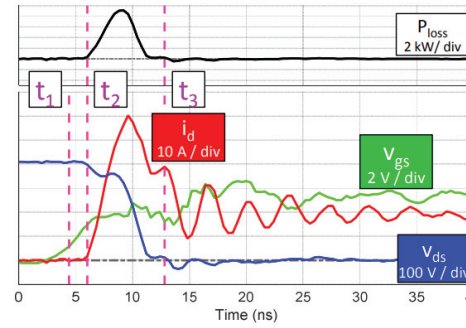
# Nonlinear Losses: Switching Loss

- High frequency switching behaviors highly nonlinear



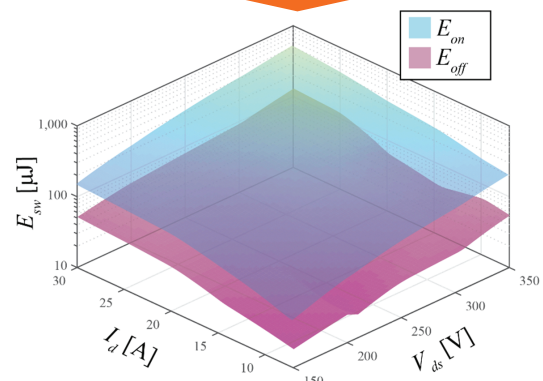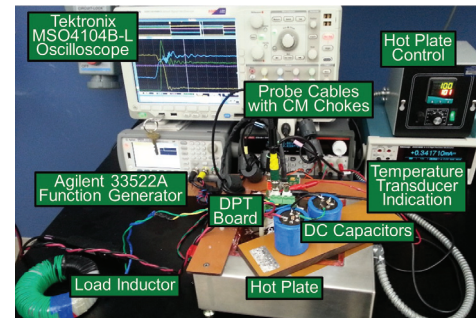
## Switching Loss Modeling

- High frequency switching behaviors highly nonlinear
- Common approach: Empirical characterization
- Still reverts to “high- $\eta$ ” approximation




## COURSE CONCLUSIONS

## HF Power Electronics – When and Why

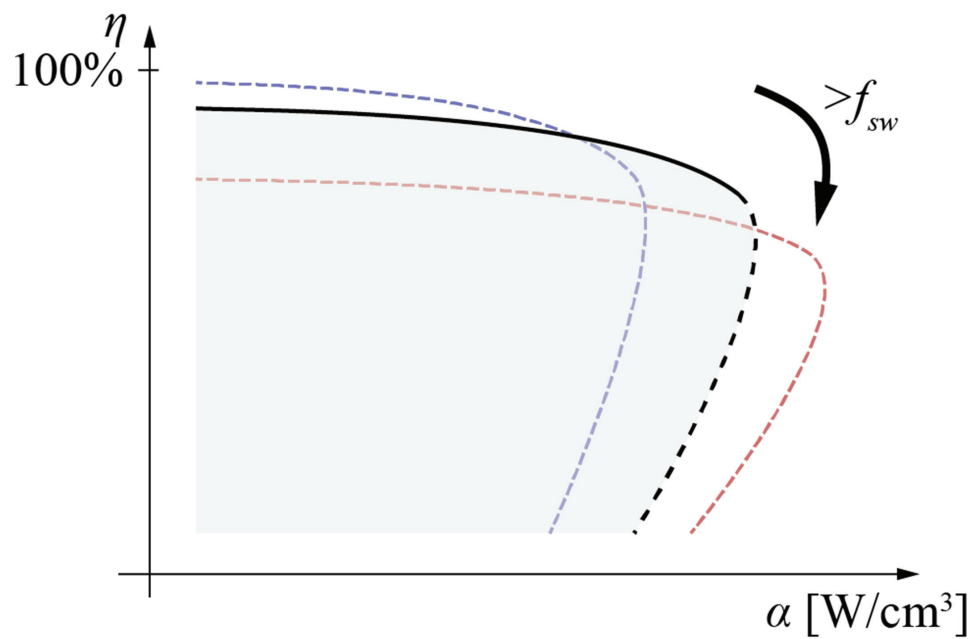

# HF Power Electronics – When and Why

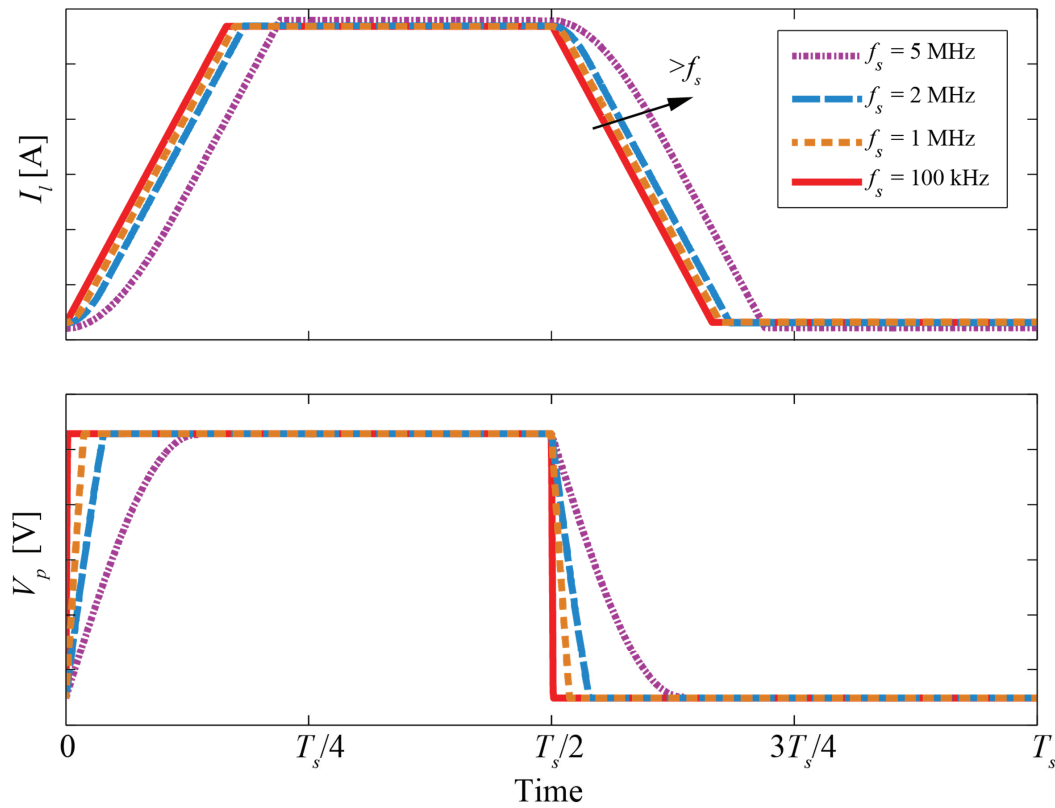

Thank you for all your hard work, and good luck with finals!