
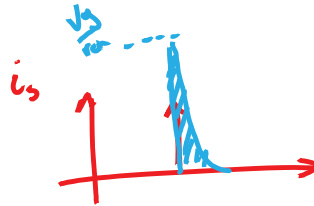

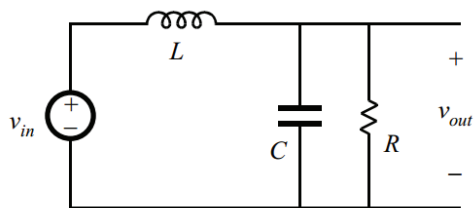
# Announcements

- Homework #1 due prior to class today
- More information on power device design
  - <http://potential.eecs.utk.edu/About.php?topic=PowerSemiconductors>



## Resonant Circuit Analysis





$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{s^2 LC + s \frac{L}{R} + 1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

$$Q = \frac{R}{R_0}$$

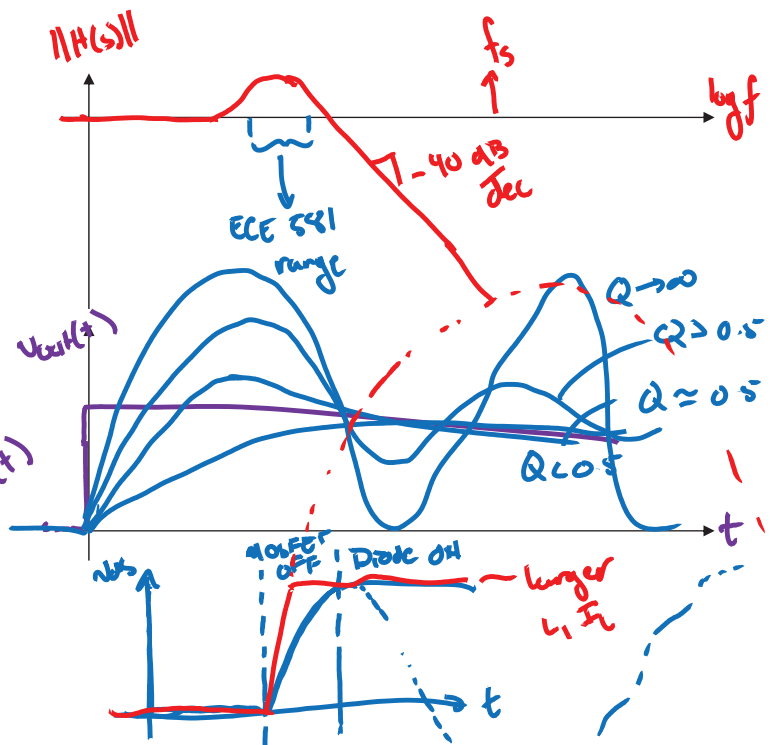
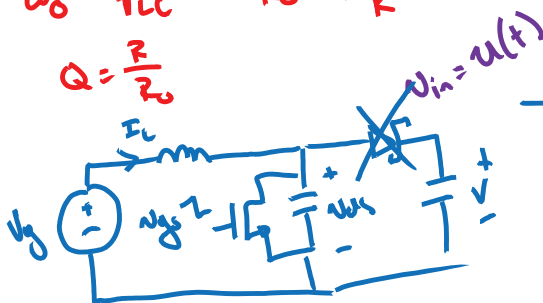


# Soft Switching


- Advantages
  - Reduced switching loss
  - Possible operation at higher switching frequency
  - Lower EMI
- Disadvantages
  - Increased current and/or voltage stresses due to circulating current
  - Higher peak and rms current values
  - ~~Complexity of analysis and modeling~~

*integration of parasitics into operation*


## Limitations: Gate Drive

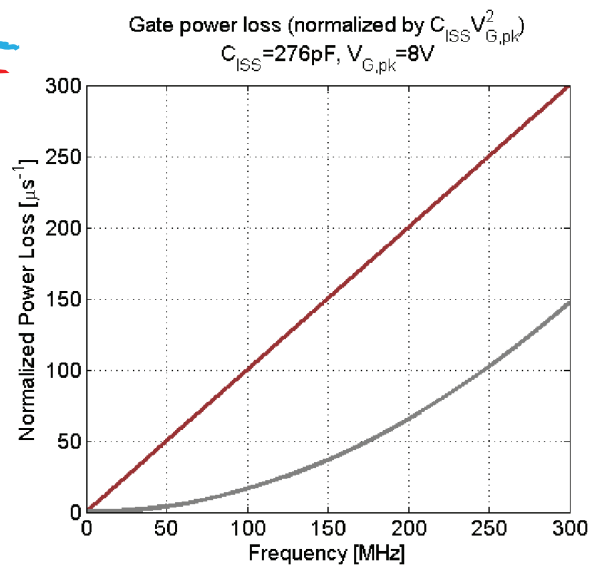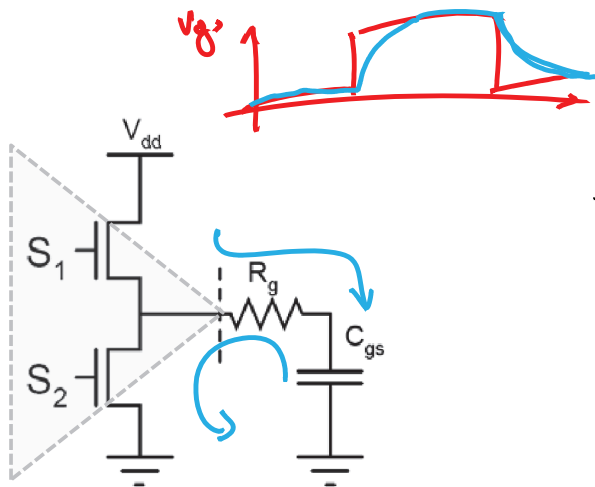


# Limitations: $t_d/T_s$

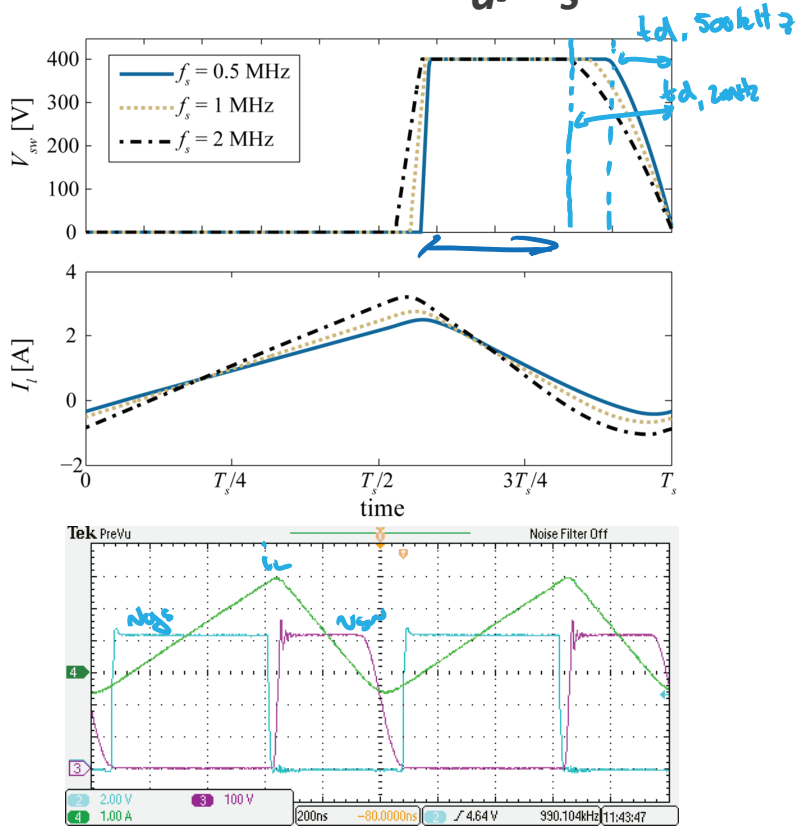

# Limitations: Thermal

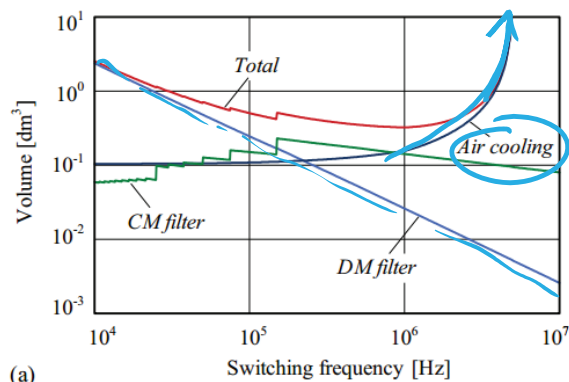


(a)

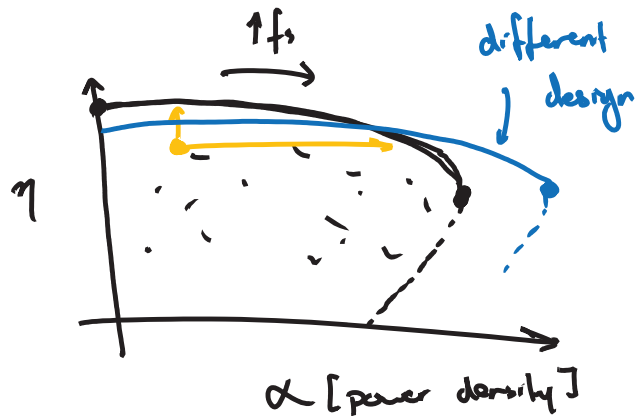


Pareto Optimal: any increase in one parameter comes at the cost of another.



# Limitations: Magnetics Design

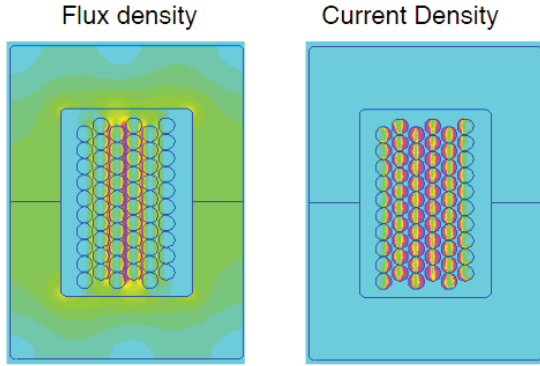

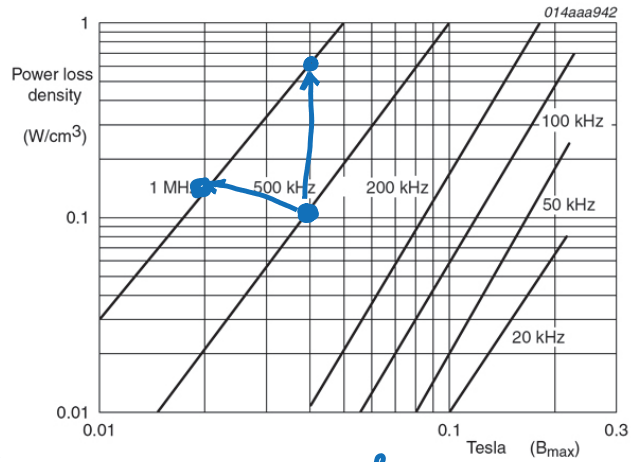Skin, Proximity, Fringe, Gap, etc. worse at HF




$$P_{core} = k_{fe} (\Delta B)^\beta f_s^\alpha V_c$$


$$\alpha \sim 2-3+$$

$\beta, \alpha$  are nonlinear functions  $f_s$  at sufficiently high  $f_s$   $\alpha > \beta$

# Limitations: Circuit Modeling

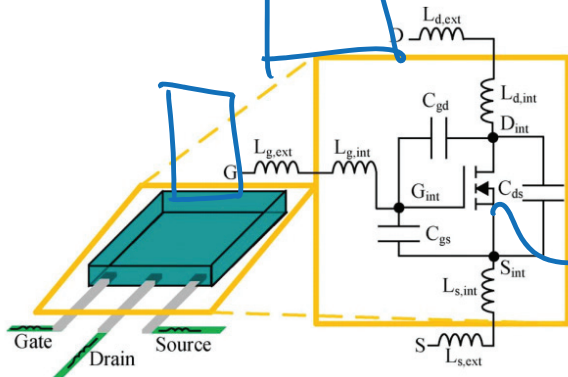



transfer characteristics

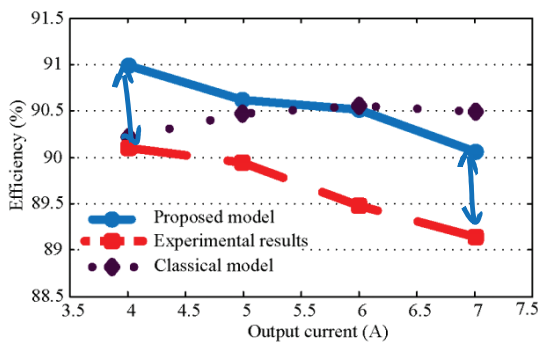

150-to-400V, 150W Boost


## EXPERIMENTAL EXAMPLE

### ZVS with Si diode

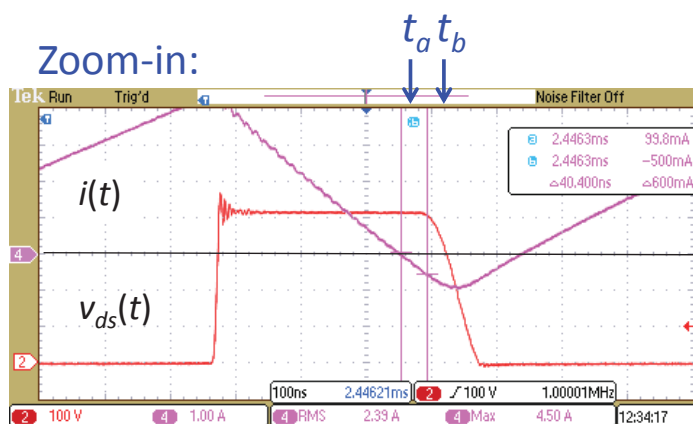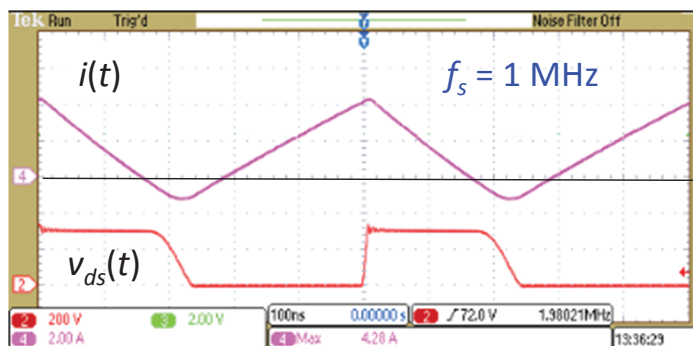


- ZVS turn-ON
  - Eliminated losses due to  $C_{sw}$  discharge during turn-ON transient
  - Eliminated losses due to MOSFET  $di_F/dt$  during turn-ON transient
- Diode reverse recovery still impacts the waveforms and losses
- Increased current ripple
  - Increased conduction losses ( $bv > 30\%$ )
  - Increased  $dv_{ds}/dt$  upon turn-OFF, MOSFET turn-OFF speed is more important


# Loss Breakdown: Soft-Switched Si Boost

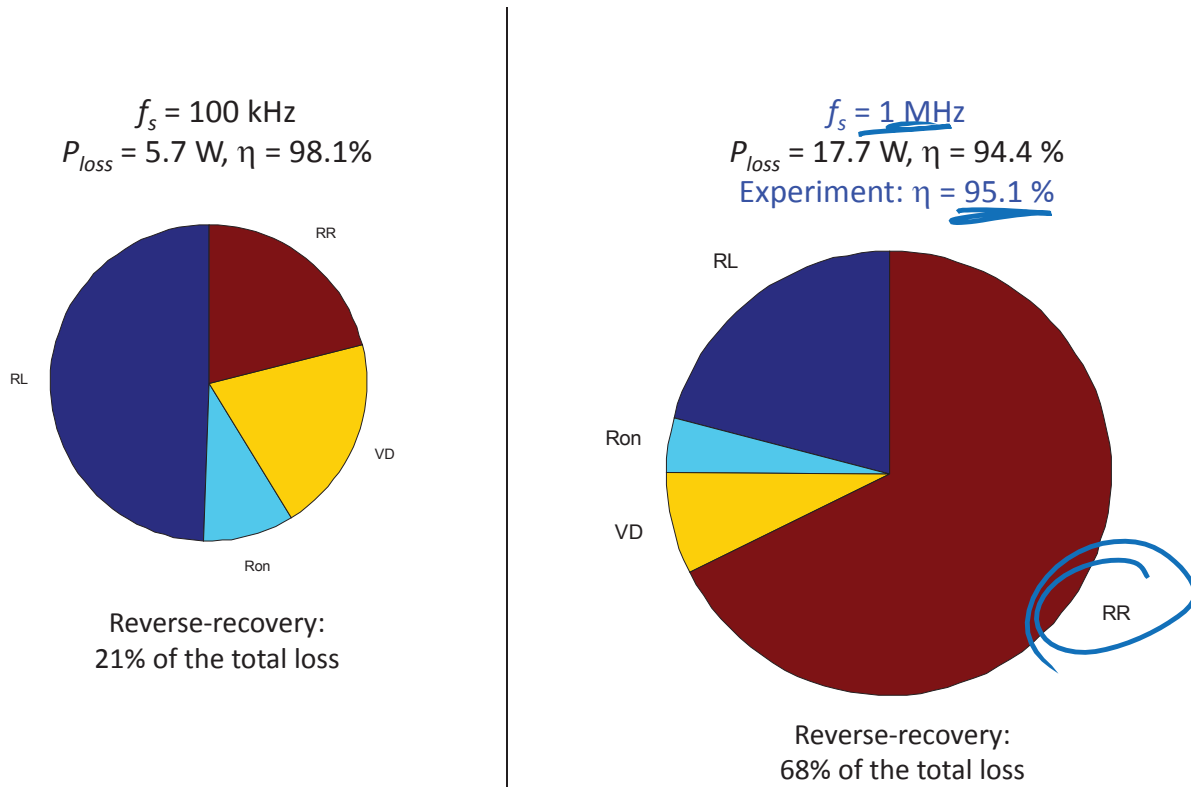

## Soft-switched SiC diode

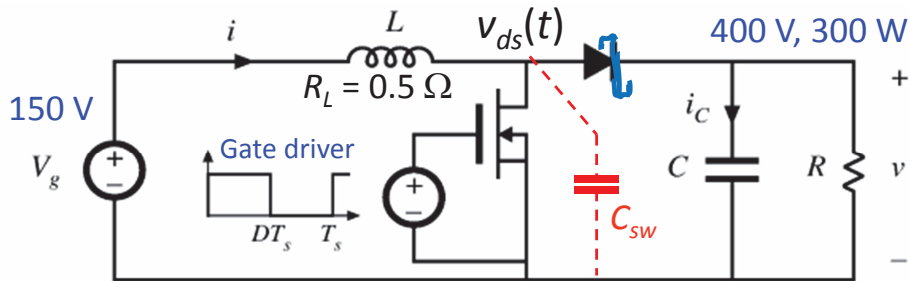

SiC diode, "soft-switched" operation

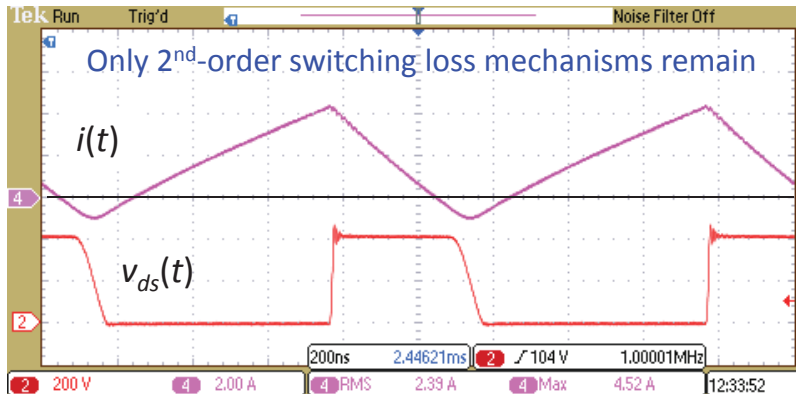

$f_s = 1 \text{ MHz}$

### MOSFET


- $di_f/dt = 200 \text{ A}/\mu\text{s}$
- $C_{ds,eq} = 45 \text{ pF}$
- $R_{on} = 0.15 \Omega$

### SiC diode

- $t_{rr} = 0, Q_{rr} = 0$
- $2C_{d,Req} - C_{d,eq} = 64 \text{ pF}$
- $V_D = 1.8 \text{ V}$
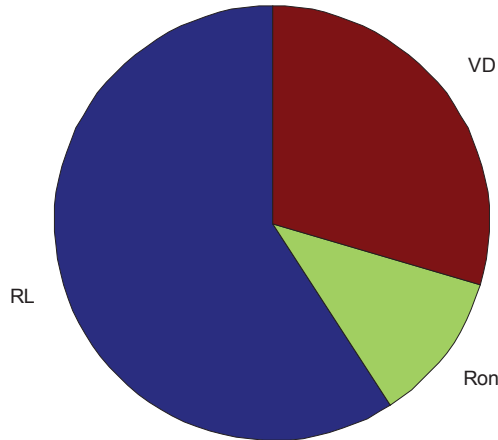
# Soft-switched Boost with SiC diode

Conduction losses only, 2<sup>nd</sup>-order switching losses not included in the model



VD 100 kHz or 1 MHz  
98.5% efficiency  
 $P_{loss} = 4.5 \text{ W}$


Experiments:

98.7% at 1 MHz  
98.0% at 2 MHz

Power supply technology limits become dominated by:

- Magnetics
- 2<sup>nd</sup>-order switching loss mechanisms, e.g. gate-drive losses, parasitic inductances (layout and packaging)
- Gate-drive circuitry and controllers to support high-frequency operation

## Speed Limitations with WBG Devices

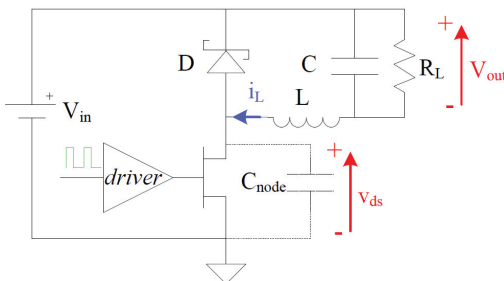


Standard hard-switched PWM operation at 50 MHz  
 $dv_{ds}/dt$  dominated by probe (4 pF) capacitance

TriQuint TGF2023-02  
12W, DC-to-18 GHz  
RF/microwave HEMT

FOM for switching applications

$$C_{ds}R_{on} \approx 1 \Omega\text{pF}$$

$$Q_gR_{on} \approx 10 \Omega\text{pC}$$

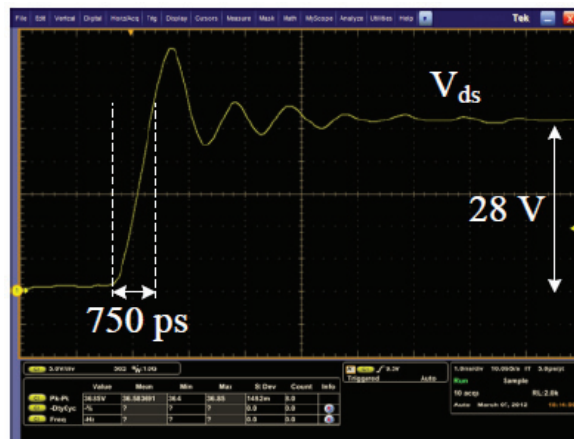

Emerging GaN HEMT devices may enable completely new RF-based design approaches in power electronics

# VHF power electronics [11]

Resonant Design		
Component	Value	Type
$L_F$	33 nH	Coilcraft 1812SMS
$L_{2F}$	12.5 nH	Coilcraft A04TG
$L_{rect}$	22 nH	1812SMS
$C_{2F}$	39 pF	ATC100A
$C_{out}$	10 $\mu$ F	ATC100A
$C_{in}$	75 $\mu$ F	Multilayer Ceramics
$S_{main}$	22 $\mu$ F	Multilayer Ceramics
$D$		Freescale MRF6S9060 Fairchild S310

Conventional Design		
Component	Value	Type
$L_{boost}$	10 $\mu$ H	Coilcraft D03316T-103ML
$C_{out}$	75 $\mu$ F	Multilayer Ceramics
$C_{in}$	22 $\mu$ F	Multilayer Ceramics
$S_{main}$		LT1371HV
$D$		Fairchild S310


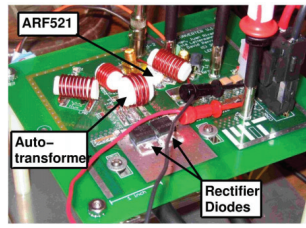
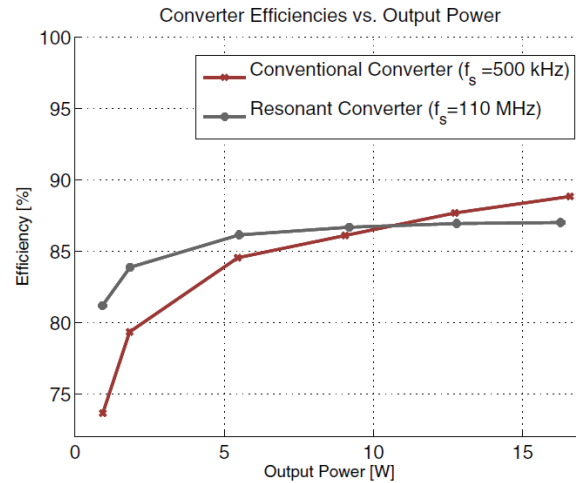


Fig. 8. Prototype  $\Phi_2$  de-dc Converter.

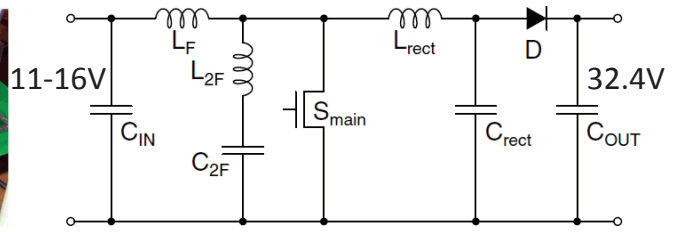

[11] D.J. Perreault, et..al. "Opportunities and challenges in very high frequency power conversion," IEEE APEC 2009.

## Topics Covered

- **Course Topics**
  - High Frequency Power Conversion
    - Switching losses and device selection
    - Resonance in power electronics
    - Soft switching (ZVS and ZCS)
    - Magnetics design
  - Non-resonant soft switching converters
    - Constant frequency control
    - State-plane analysis
    - Resonant switches
    - Modeling and Simulation
    - Discrete time models
  - Resonant Converters
    - Resonant converter topologies
    - Sinusoidal analysis
    - AC-modeling and frequency modulation
    - State-plane analysis
  - Applications and practical issues of high frequency converters