

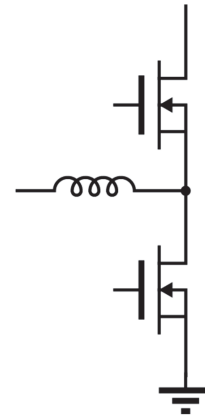



Synchronous Switching

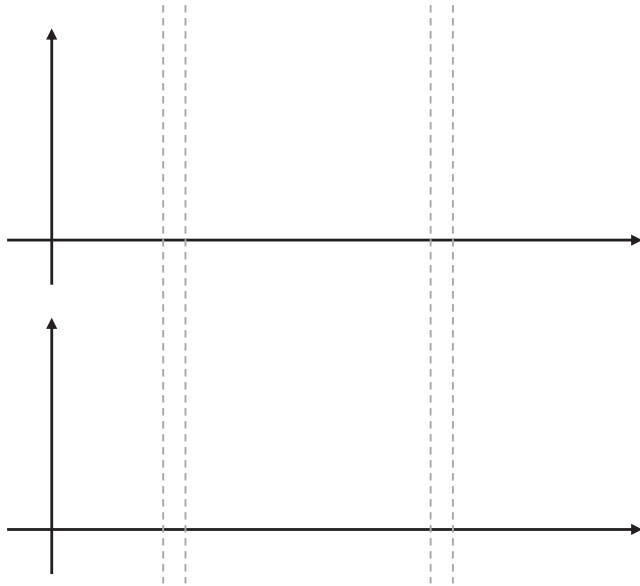

MOSFET Cross Section

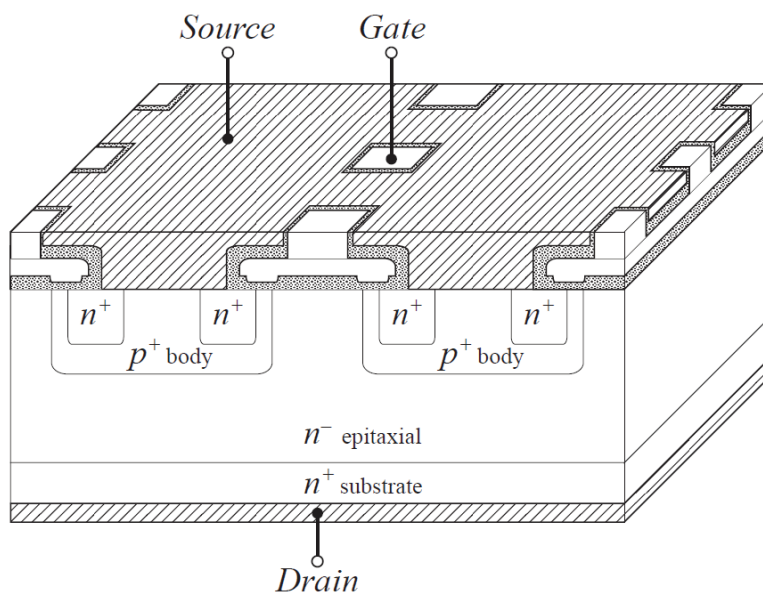

MOSFET Depletion Capacitance

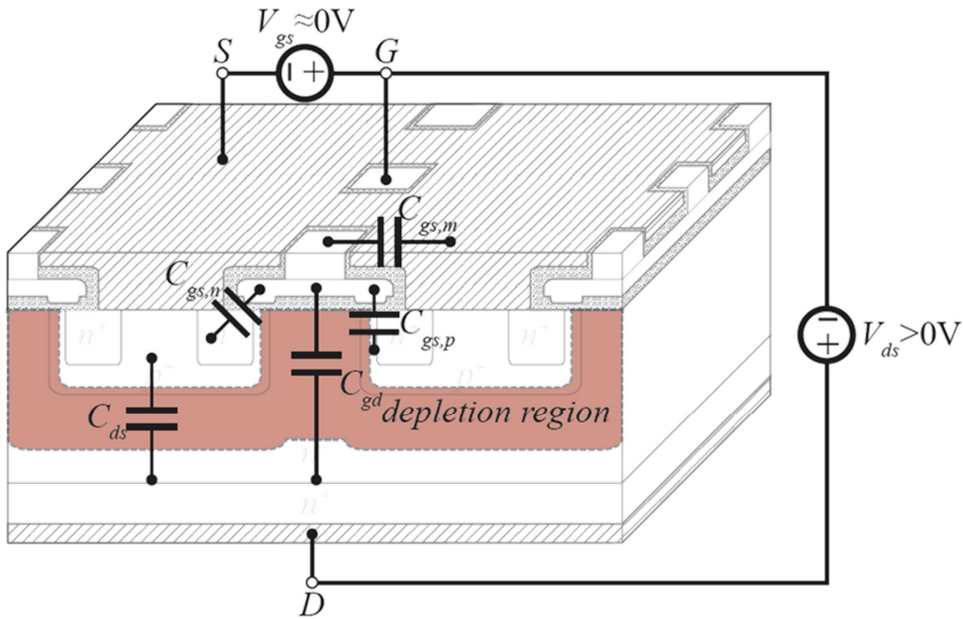


Gate Charge

9 Typ. gate charge

$V_{GS} = f(Q_{gate}); I_D = 5.2 \text{ A pulsed}$

parameter: V_{DD}

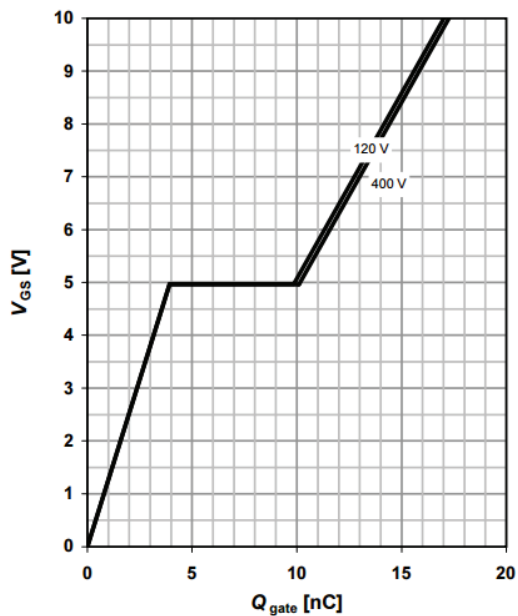



Overlap Time

9 Typ. gate charge




$V_{GS} = f(Q_{gate}); I_D = 5.2 \text{ A pulsed}$

parameter: V_{DD}


Gate threshold voltage	$V_{GS(th)}$	$V_{DS} = V_{GS}, I_D = 0.34 \text{ mA}$	2.5	3	3.5	
Gate resistance	R_G	$f = 1 \text{ MHz, open drain}$	-	1.8	-	Ω

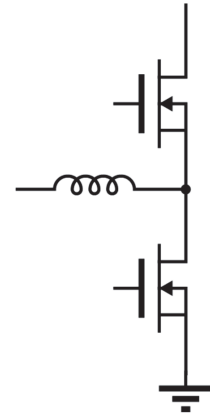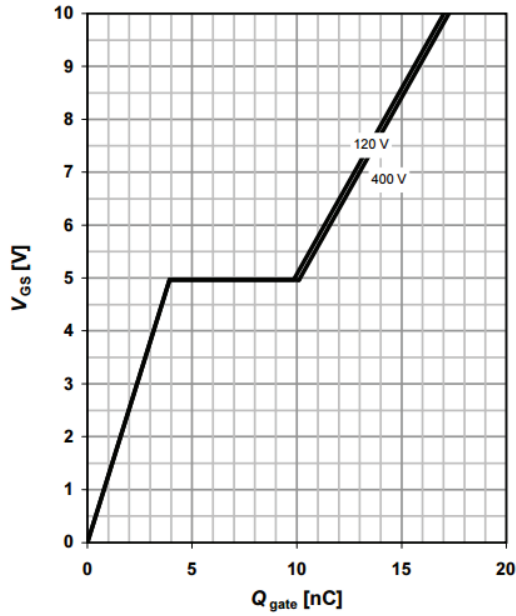


FET Turn-On

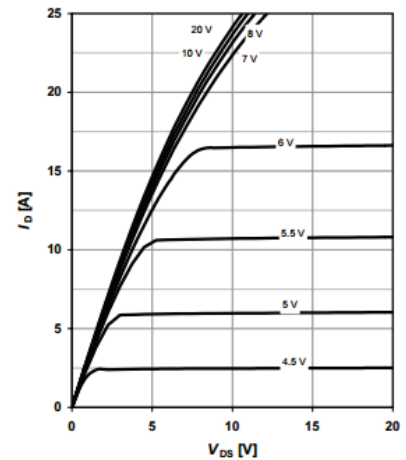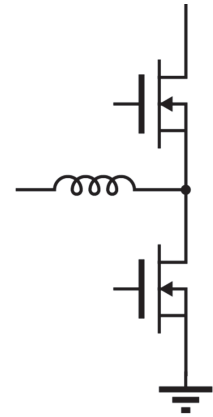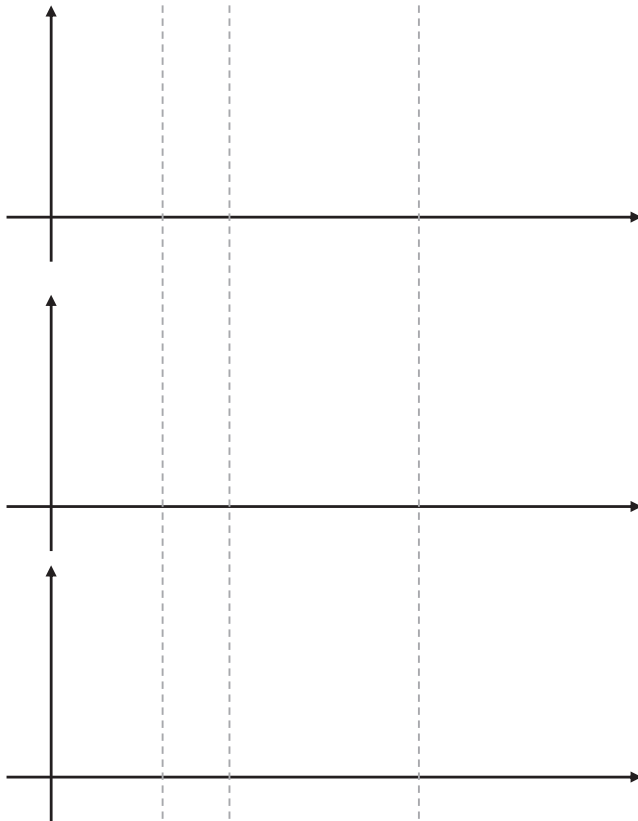

Device Transconductance

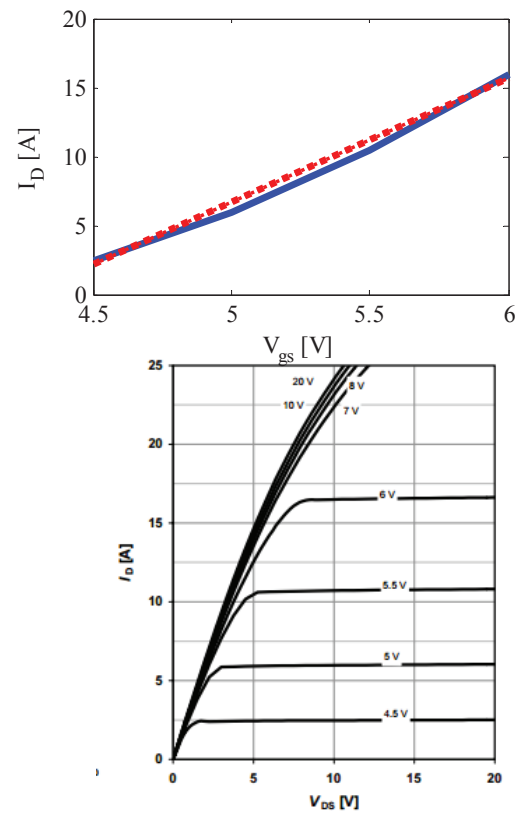

Example Simulation

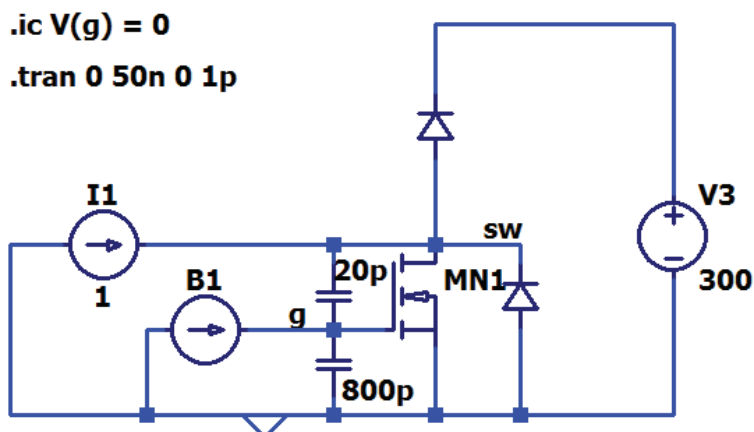

I=IF(V(g)<10,1,0)

.model myD D(n=.01)

.model testFET VDMOS(Rg=.1 Rd=0 Rs=0 Vto=3 Kp=9 Cgdmax=0p
+ Cgdmin=0p Cgs=0p Cjo=1.5f Is=26p Rb=0m Vds=600 Ron=385m Qg=0n)

Simulation Waveforms – Turn On

