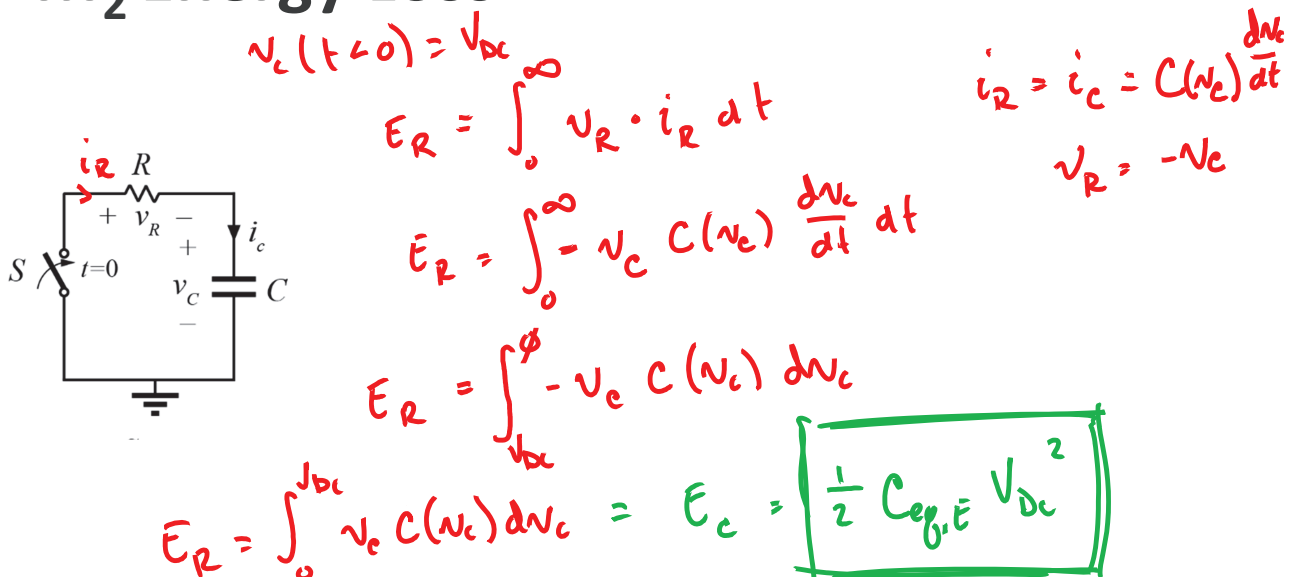



C_{oss} Losses in a Half Bridge



M_2 Energy Loss



M₁ Energy Loss

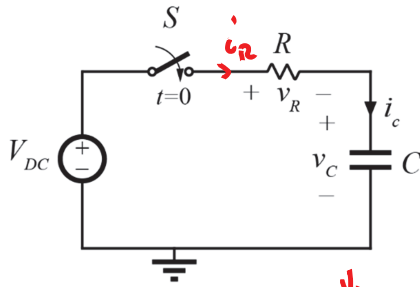

$$v_C(t=0) = \phi \quad \begin{cases} i_R = i_C = C(v_C) \frac{dv_C}{dt} \\ v_R = V_{DC} - v_C \end{cases}$$

$$E_R = \int_0^{\infty} v_R i_R dt = \int_0^{\infty} (V_{DC} - v_C) C(v_C) \frac{dv_C}{dt} dt$$

$$E_R = \int_0^{V_{DC}} (V_{DC} - v_C) C(v_C) dv_C$$

$$E_R = V_{DC} \underbrace{\int_0^{V_{DC}} C(v_C) dv_C}_{Q_C} - \underbrace{\int_0^{V_{DC}} C(v_C) v_C dv_C}_{E_C}$$

$$E_R = V_{DC} (V_{DC} C_{G,Q}) - \frac{1}{2} C_{G,E} V_{DC}^2$$



Total Half Bridge C_{OSS} Loss

$$E_{C,tot} = E_{R1} + E_{R2} = \frac{1}{2} C_{G,E} V_{DC}^2 + \underbrace{\left(V_{DC}^2 C_{G,Q} - \frac{1}{2} C_{G,E} V_{DC}^2 \right)}_{\text{from } m_1}$$

$$E_{C,tot} = V_{DC}^2 C_{G,Q} !$$

only applies if $C_{ds1} = C_{ds2}$

Energy Equivalent

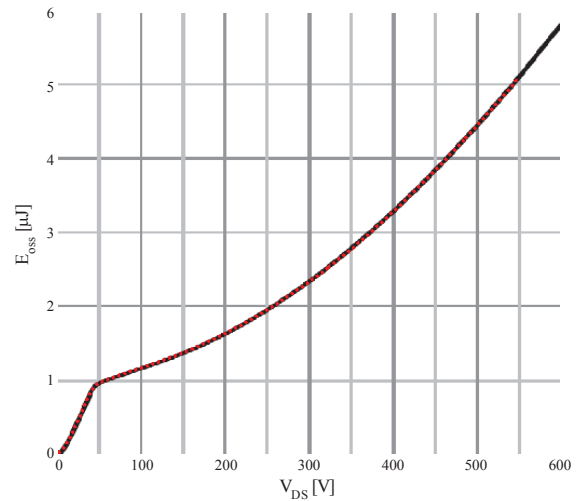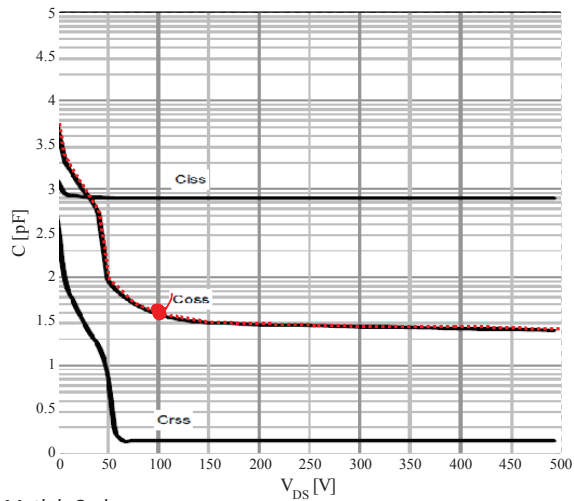

Matlab Code:

```
Vdc = 550;
```

```
Vds = [0 5 10 40 50 75 100 150 200 300 400 500 600];  
Coss = [5500 2500 1900 550 95 50 38 30 29 27 27 25 24]*1e-12;
```

```
vx = 0.01:.01:Vdc;  
Cx = 10.^interp1(Vdc,log10(Coss),vx,'linear');
```

```
E = cumtrapz(vx, Cx.*vx);  
Ceq_e = 2*(E)./vx.^2;
```

Nonlinear Capacitance Extraction

- <http://web.eecs.utk.edu/~dcostine/personal/PowerDeviceLib/DigiTest/index.html>

Datasheet Reported Capacitance


Dynamic characteristics

Input capacitance	C_{iss}	$V_{GS}=0\text{ V}, V_{DS}=100\text{ V},$	-	790	-	pF
Output capacitance	C_{oss}	$f=1\text{ MHz}$	-	38	-	
Effective output capacitance, energy related ⁶⁾	$C_{o(er)}$	$V_{GS}=0\text{ V}, V_{DS}=0\text{ V}$ to 480 V	-	36	-	
Effective output capacitance, time related ⁷⁾	$C_{o(tr)}$		-	96	-	
Turn-on delay time	$t_{d(on)}$	$V_{DD}=400\text{ V},$ $V_{GS}=10\text{ V}, I_D=5.2\text{ A},$ $R_G=3.3\ \Omega$	-	10	-	ns
Rise time	t_r		-	5	-	
Turn-off delay time	$t_{d(off)}$		-	40	-	
Fall time	t_f		-	5	-	

⁶⁾ $C_{o(er)}$ is a fixed capacitance that gives the same stored energy as C_{oss} while V_{DS} is rising from 0 to 80% V_{DSS} .

⁷⁾ $C_{o(tr)}$ is a fixed capacitance that gives the same charging time as C_{oss} while V_{DS} is rising from 0 to 80% V_{DSS} .

Example Simulation

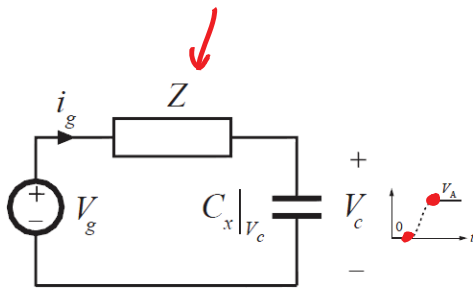


$C_{eq,Q} = 70.5\text{ pF}$

$C_{eq,E} = 56.4\text{ pF}$

$C_{eq,tzvs} = 64.1\text{ pF}$

$C_{eq,Z} = 84.5\text{ pF}$

t_{zvs}

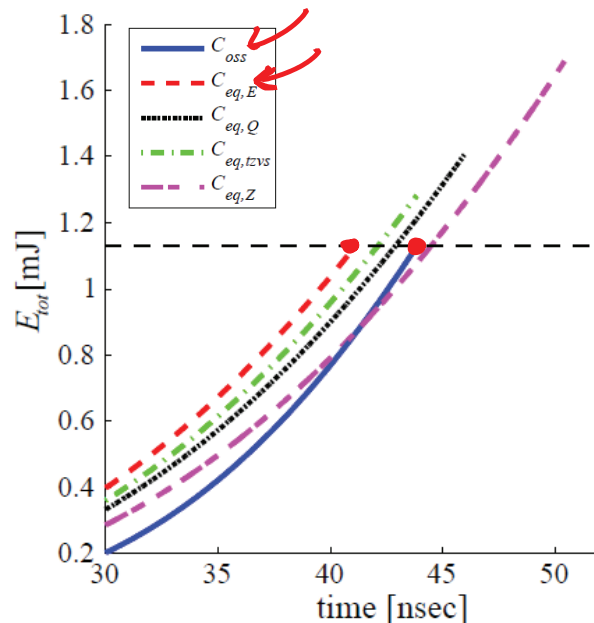

Further Simulation

