
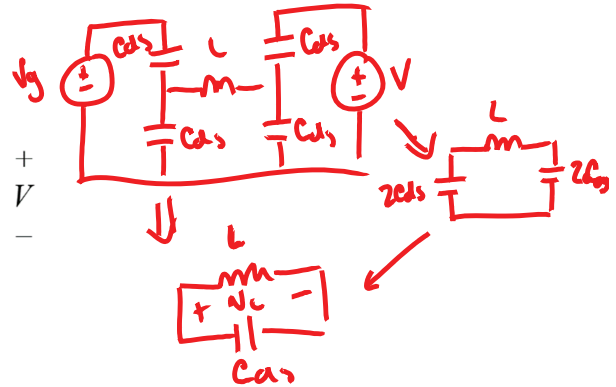
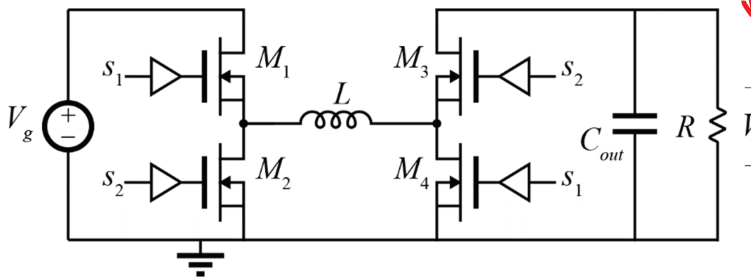
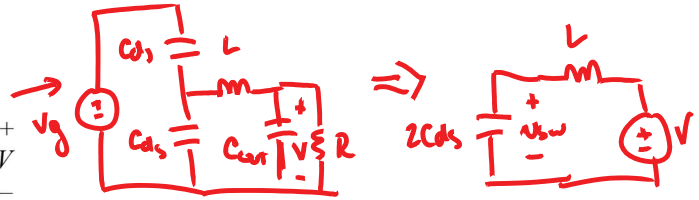



# Time-Domain Analysis of Switching Transitions

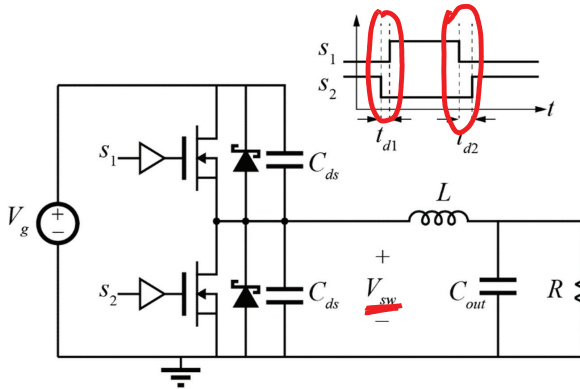- (1) Assume  $C_{ds}$  is linear (e.g. by equivalent)
- (2) Assume  $C_{out} \gg C_{ds}$



## Resonant Circuit Solution

General L-C resonant circuit w/ bias

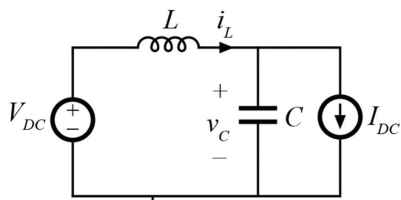

Initial conditions:

$$\begin{aligned} v_C(t=0) &= V_0 \\ i_L(t=0) &= I_0 \end{aligned}$$

$$(1) C \frac{dv_C}{dt} = i_L - I_{DC}$$

$$(2) L \frac{di_L}{dt} = V_{DC} - v_C$$

$$V_{DC} - v_C = L \frac{d}{dt} \left( C \frac{dv_C}{dt} + I_{DC} \right)$$

$$\begin{aligned} V_{DC} - v_C &= LC \frac{d^2 v_C}{dt^2} \\ LC \frac{d^2 v_C}{dt^2} + v_C - V_{DC} &= 0 \end{aligned}$$

$$\begin{cases} v_C = \sqrt{\frac{L}{C}} (I_0 - I_{DC}) \sin\left(\frac{t}{\sqrt{LC}}\right) + (V_0 - V_{DC}) \cos\left(\frac{t}{\sqrt{LC}}\right) + V_{DC} \\ i_L = \sqrt{\frac{C}{L}} (V_{DC} - V_0) \sin\left(\frac{t}{\sqrt{LC}}\right) + (I_0 - I_{DC}) \cos\left(\frac{t}{\sqrt{LC}}\right) + I_{DC} \end{cases}$$

# Normalization and Notation

Define  $\omega_0 = \frac{1}{\sqrt{LC}} = 2\pi f_0$ ,  $R_0 = \sqrt{\frac{L}{C}}$

$$V_c = R_0(I_0 - I_{DC}) \sin(\omega_0 t) + (V_0 - V_{DC}) \cos(\omega_0 t) + V_{DC}$$

$$i_L = -\frac{1}{R_0} (V_0 - V_{DC}) \sin(\omega_0 t) + (I_0 - I_{DC}) \cos(\omega_0 t) + I_{DC}$$

Normalize:

$$m_c = \frac{V_c}{V_{base}}$$

$$j_L = \frac{i_L}{I_{base}}$$

$V_{base}$  is arbitrary DC voltage

$$I_{base} = \frac{V_{base}}{R_0}$$

$$t_x = \omega_0 t$$



pick  $V_{base} = V_{DC}$

$I_{base} = \frac{V_{DC}}{R_0}$

$$v_c(t) = V_{DC} + (V_0 - V_{DC}) \cos\left(\frac{t}{\sqrt{LC}}\right) + (I_0 - I_{DC}) \sqrt{\frac{L}{C}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_L(t) = I_{DC} + (I_0 - I_{DC}) \cos\left(\frac{t}{\sqrt{LC}}\right) + (V_{DC} - V_0) \sqrt{\frac{C}{L}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$$\begin{cases} m_c = \frac{V_c}{V_{DC}} = 1 + \left(\frac{V_0}{V_{DC}} - 1\right) \cos(\omega_0 t) + \frac{I_0 - I_{DC}}{V_{DC}} R_0 \sin(\omega_0 t) \\ j_L = \frac{I_{DC} R_0}{V_{DC}} + \frac{R_0}{V_{DC}} (I_0 - I_{DC}) \cos(\omega_0 t) + \frac{R_0}{R_0} \left(1 - \frac{V_0}{V_{DC}}\right) \sin(\omega_0 t) \end{cases}$$

$$\begin{cases} m_c = 1 + A \cos \omega_0 t + B \sin \omega_0 t \\ j_L = \frac{I_{DC} R_0}{V_{DC}} + B \cos \omega_0 t - A \sin \omega_0 t \end{cases}$$

Try looking at

$$(m_c - 1)^2 + \left(j_L - \frac{I_{DC} R_0}{V_{DC}}\right)^2 =$$

$$A^2 \cos^2 \omega_0 t + B^2 \sin^2 \omega_0 t + 2AB \cos \omega_0 t \sin \omega_0 t + B^2 \cos^2 \omega_0 t + A^2 \sin^2 \omega_0 t$$

$$A^2 (\cos^2 \omega_0 t + \sin^2 \omega_0 t) + B^2 (\cos^2 \omega_0 t + \sin^2 \omega_0 t) - 2AB \cos \omega_0 t \sin \omega_0 t + 2AB \cos \omega_0 t \sin \omega_0 t$$

$$= A^2 + B^2 = \left(\frac{V_0}{V_{DC}} - 1\right)^2 + \left(\frac{R_0}{V_{DC}} (I_0 - I_{DC})\right)^2$$



$$(m_c(t) - 1)^2 + (j_c(t) - \frac{I_{DC} R_o}{V_{DC}})^2 = (\frac{V_o}{V_{DC}} - 1)^2 + (\frac{R_o(I_o - I_{DC})}{V_{DC}})^2$$


This is the equation for a circle!

- center at  $m_c = 1$ ,  $j_c = \frac{I_{DC} R_o}{V_{DC}}$


- radius is  $r^2 = (\frac{V_o}{V_{DC}} - 1)^2 + (\frac{R_o(I_o - I_{DC})}{V_{DC}})^2$

$$J_{DC} = \frac{I_{DC} R_o}{V_{DC}} = \frac{I_{DC}}{I_{base}}$$

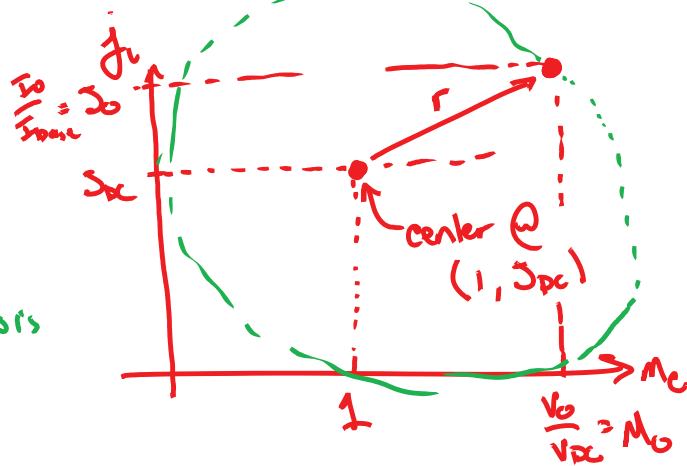Take Diff EQs →  
Geometric / trig analysis



## State Plane Analysis

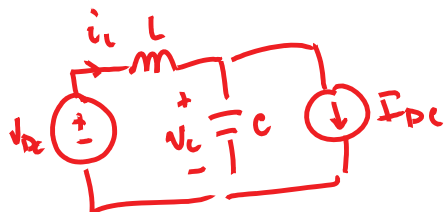


$$m_c = \frac{v_c}{V_{base}} \quad V_{base} = \dots$$

$$j_c = \frac{i_c}{I_{base}} \quad I_{base} = \frac{V_{base}}{R_o}$$

Circle center = DC solution  
 $v_c = V_{DC}$        $m_c = M_{DC}$   
 $i_c = I_{DC}$        $j_c = J_{DC}$

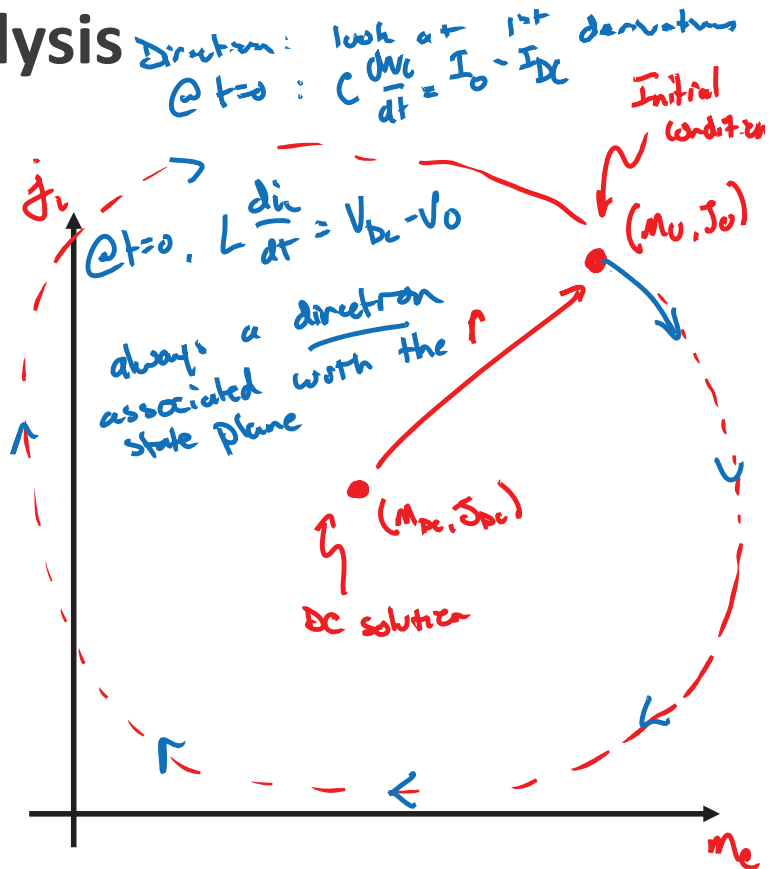Initial Condition:  
 $v_c(t=0) = V_o \rightarrow M_o$   
 $i_c(t=0) = I_o \rightarrow J_o$



[1] R. Oruganti and F. C. Lee, "Resonant Power Processors, Part I - State Plane Analysis", Industry Applications, IEEE Tran. on, vol. 21, no. 6, nov 1985.

[2] D. P. Atherton, Nonlinear Control Engineering. London: Van Nostrand Reinhold, 1982, Ch. 2.