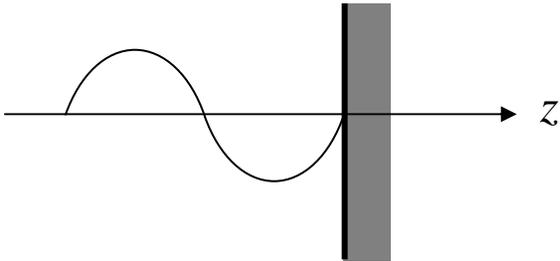


## Standing Wave

Interference between the incident & reflected waves  $\rightarrow$  Standing wave

A string with one end fixed on a wall



$$\text{Incident: } y_1(z, t) = Y_0^+ \cos(\omega t - \beta z)$$

$$\tilde{Y}_1(z) = Y_0^+ e^{-j\beta z}$$

(Set the incident wave's phase to be 0, i.e.,  $Y_0^+$  real & positive.)

$$\text{Reflected: } y_2(z, t) = |Y_0^-| \cos(\omega t + \beta z + \phi)$$

$$\tilde{Y}_2(z) = Y_0^- e^{j\beta z}, \text{ where } Y_0^- = |Y_0^-| e^{j\phi} = |Y_0^-| \angle \phi$$

The total displacement

$$\tilde{Y}(z) = \tilde{Y}_1(z) + \tilde{Y}_2(z) = Y_0^+ e^{-j\beta z} + Y_0^- e^{j\beta z}$$

$$\text{We must have } \tilde{Y}(0) = 0 \quad \Rightarrow \quad Y_0^+ + Y_0^- = 0 \quad \text{i.e.} \quad Y_0^- = -Y_0^+$$



$$\tilde{Y}(z) = Y_0^+ (e^{-j\beta z} - e^{j\beta z})$$

$$\tilde{Y}(z) = Y_0^+ (e^{-j\beta z} - e^{j\beta z})$$

Recall that  $e^{j\theta} - e^{-j\theta} = 2j \sin \theta \quad \Rightarrow \quad \tilde{Y}(z) = -2jY_0^+ \sin(\beta z)$

$$y(z, t) = \text{Re}[-2jY_0^+ \sin(\beta z)] = 2Y_0^+ \sin(\beta z) \sin(\omega t) \quad \text{Why sin?}$$

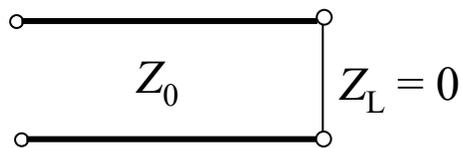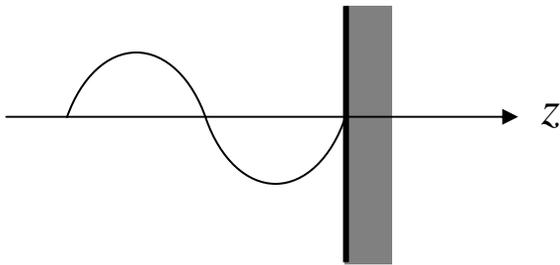See Wikipedia Standing Wave animation to get visual picture:  
[Harmonic oscillation at each  \$z\$ , with amplitude following  \$\sin\(\beta z\)\$](#)



$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = -1$$

Similarly, shorted transmission line:

By definition of “short circuit,  $\tilde{V}(0) = 0 \Rightarrow V_0^+ + V_0^- = 0$

$$V_0^- = -V_0^+ \quad \Gamma = -1$$

$$\tilde{V}(z) = -2jV_0^+ \sin(\beta z)$$

$$v(z, t) = \text{Re}[-2jV_0^+ \sin(\beta z)] = 2V_0^+ \sin(\beta z) \sin(\omega t)$$

Like a mirror. [What property of a mirror makes it a mirror?](#)

But,  $I_0^- = I_0^+ \quad \frac{I_0^+}{I_0^-} = -\Gamma = 1$

Find  $\tilde{I}(z)$  and  $i(z, t)$  on your own.

What if the transmission line is terminated in open circuit?

Note: open ended  $\neq$  open circuit for high frequencies!

(You will see how to make an open circuit later.)



$$V_0^- = V_0^+ \quad \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = 1$$

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + e^{j\beta z}) = 2V_0^+ \cos(\beta z)$$

Find  $v(z, t)$  on your own.

$$I_0^- = -I_0^+ \quad (\text{since total current is 0, by definition of open circuit})$$

Find  $\tilde{I}(z)$  and  $i(z, t)$  on your own.

In all the above examples,  $\Gamma = \pm 1$ . Completely reflected.

At very high frequencies, we often can only measure the amplitude or power ( $\propto$  amplitude squared), but not the instantaneous values or the waveform.


The following example is for the short circuit. The open circuit is similar (just with a shift of origin).

The amplitude of the voltage wave  $v(z, t)$  at position  $z$  is

$$|\tilde{V}(z)| = \sqrt{\tilde{V}(z)\tilde{V}^*(z)}$$

The “complex amplitude” containing the phase

$$\begin{aligned} |\tilde{V}(z)| &= \sqrt{\tilde{V}(z)\tilde{V}^*(z)} \\ &= |-2jV_0^+ \sin(\beta z)| \\ &= 2|V_0^+| |\sin(\beta z)| \end{aligned}$$

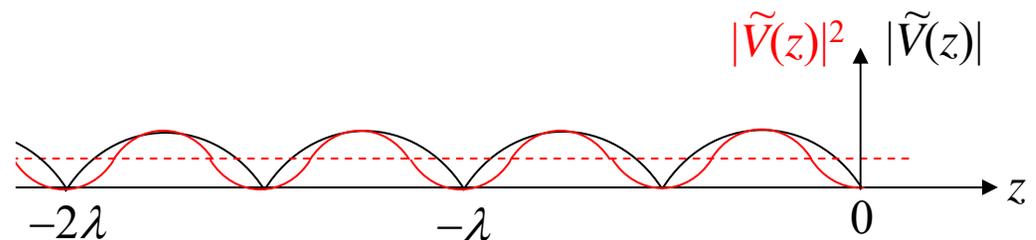


$$|\tilde{V}(z)|^2 = 4|V_0^+|^2 \sin^2(\beta z) = 2|V_0^+|^2 [1 - 2\cos(2\beta z)]$$

Question: What's the spatial period of the standing wave?

The open circuit: Just a shift of the origin

$$\begin{aligned} |\tilde{V}(z)| &= 2|V_0^+| |\cos(\beta z)| \\ |\tilde{V}(z)|^2 &= 4|V_0^+|^2 \cos^2(\beta z) \\ &= 2|V_0^+|^2 [1 + 2\cos(2\beta z)] \end{aligned}$$

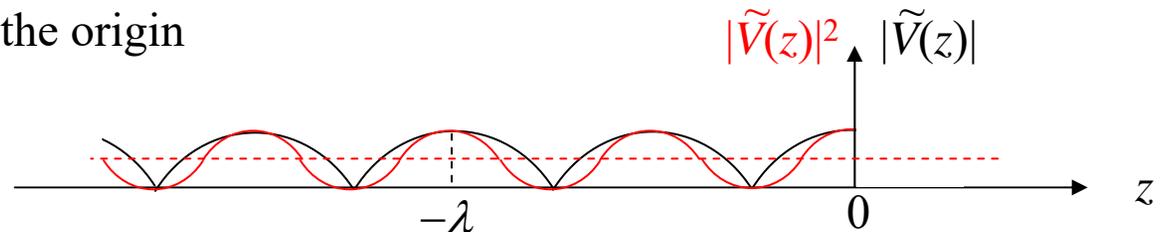

For both the short circuit (SC) and open circuit (OC),

$$|\tilde{V}(z)|_{\max} = 2|V_0^+|$$

Constructive

$$|\tilde{V}(z)|_{\min} = 0$$

Destructive

$$|\Gamma| = 1$$

Complete reflection. Completely a standing wave.

There are cases where  $|\Gamma| = 1$  but  $\Gamma \neq \pm 1$ .

Also complete reflection. We'll talk about those cases later.

What if  $|\Gamma| \neq 1$  ?

Partially standing, partially traveling.

Now, let's look at the maxima and minima of this combination of a standing wave and a traveling wave.

Recall that, in general,  $\Gamma$  is a complex number:

$$\Gamma = |\Gamma|e^{j\theta_r}$$

$$\tilde{V}(z) = \underbrace{V_0^+ e^{-j\beta z}}_{\text{Incident}} + \underbrace{V_0^- e^{j\beta z}}_{\text{Reflected}} = V_0^+ e^{-j\beta z} + \Gamma V_0^+ e^{j\beta z} = V_0^+ e^{-j\beta z} + |\Gamma| e^{j\theta_r} V_0^+ e^{j\beta z}$$

$$|\tilde{V}(z)| = \sqrt{\tilde{V}(z) \tilde{V}^*(z)}$$

$$= \sqrt{V_0^+ (e^{-j\beta z} + |\Gamma| e^{j\theta_r} e^{j\beta z}) (V_0^+)^* (e^{j\beta z} + |\Gamma| e^{-j\theta_r} e^{-j\beta z})}$$

Notice that  $V_0^+ (V_0^+)^* = |V_0^+|^2$   $V_0^+$  is a complex amplitude

$$\therefore |\tilde{V}(z)| = |V_0^+| \sqrt{(\dots)(\dots)}$$


$$= |V_0^+| \sqrt{1 + |\Gamma|^2 + \underbrace{2|\Gamma| \cos(2\beta z + \theta_r)}_{\text{Interference term}}}$$

Similarly,  $|\tilde{I}(z)| = |I_0^+| \sqrt{1 + |\Gamma|^2 - 2|\Gamma| \cos(2\beta z + \theta_r)}$

It's more convenient to plot  $|\tilde{V}(z)|^2$  and  $|\tilde{I}(z)|^2$  than the amplitudes.


$$2\beta z = 2\pi$$
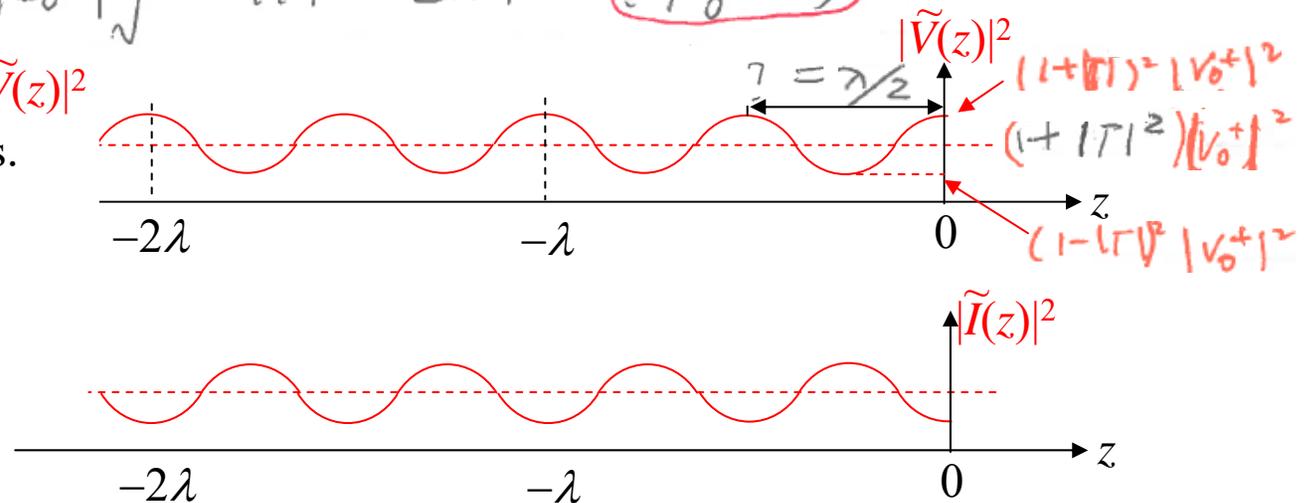
$$\therefore z = \frac{2\pi}{2\beta} = \frac{1}{2} \lambda$$



$$|\tilde{V}(z)| = |V_0^+| \sqrt{(\dots)(\dots)}$$

$$= |V_0^+| \sqrt{1 + |\Gamma|^2 + \underbrace{2|\Gamma| \cos(2\beta z + \theta_r)}_{\text{Interference term}}}$$

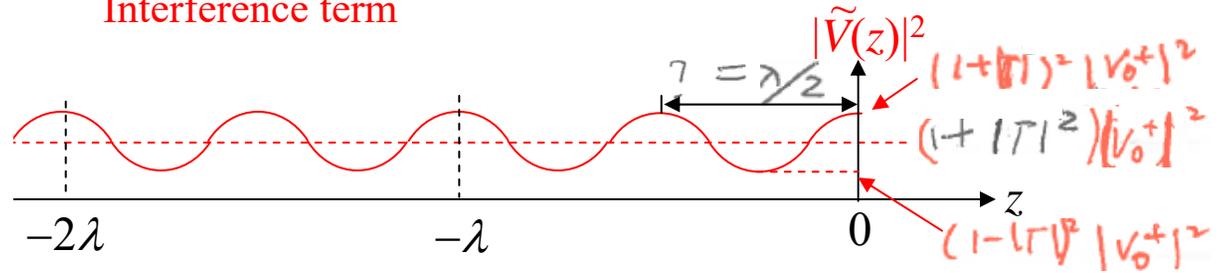

Constructive interference

$$|\tilde{V}|_{max} = |V_0^+| \sqrt{1 + |\Gamma|^2 + 2|\Gamma|}$$

$$= |V_0^+| (1 + |\Gamma|)$$

Pay attention to the max, min, and average values

Destructive interference

$$|\tilde{V}|_{min} = |V_0^+| \sqrt{1 + |\Gamma|^2 - 2|\Gamma|}$$


$$= |V_0^+| (1 - |\Gamma|)$$

In this plot, we have assumed a special case  $\theta_r = 0$ .  
 Can you think of a kind of load that leads to  $\theta_r = 0$ ?  
 Question: In general, what's the condition for  $\theta_r = 0$ ?

We stated that it's more convenient to plot the amplitudes squared than the amplitudes themselves.


But how does the plot of  $|\tilde{V}(z)|$  look?

It looks like this:

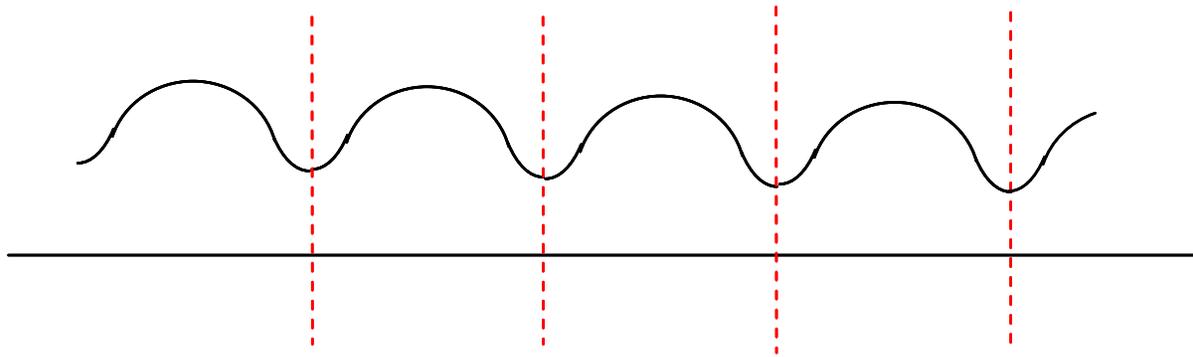

Work out the max and min values.

Notice the important difference between its shape and that of  $|\tilde{V}(z)|$

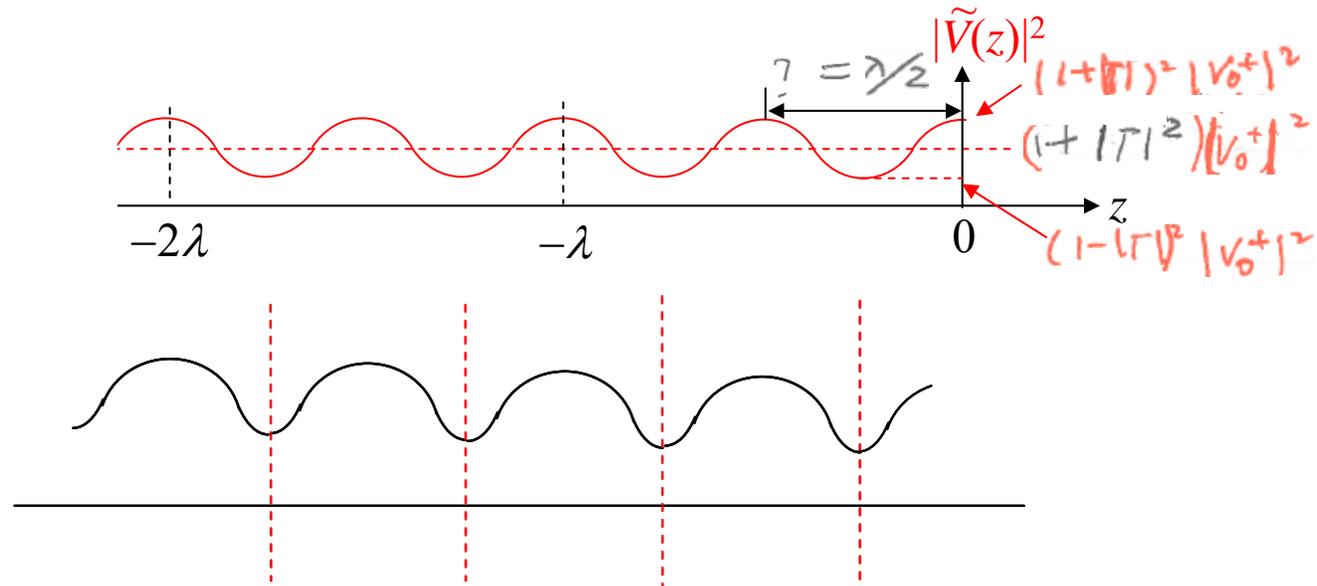

$$|\tilde{V}|_{\max} = |V_0^+| \sqrt{1 + |\Gamma|^2 + 2|\Gamma|} = |V_0^+| (1 + |\Gamma|)$$

$$|\tilde{V}|_{\min} = |V_0^+| \sqrt{1 + |\Gamma|^2 - 2|\Gamma|} = |V_0^+| (1 - |\Gamma|)$$

Now we define the voltage standing wave ratio (VSWR), or simply standing wave ratio (SWR)

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

Special (extreme) cases:

$$|\Gamma| = 1, \quad S = \infty \Rightarrow \text{All standing wave. } |\tilde{V}|_{\min} = 0$$

(Recall short & open. Other such cases to be discussed)

$$|\Gamma| = 0, \quad S = 1 \Rightarrow \text{All traveling wave. No reflection.}$$

(What's the condition for this? How does the plot look?)

## Slotted line

A tool to measure impedance. See in the textbook, Fig. 2-16 (pp. 74 in 7/E, pp. 73 in 6/E, or pp. 60 in 5/E). Based on the one-to-one mapping between  $z_L$  and  $\Gamma$ .

The detector measures the local field (proportional to voltage) as a function of longitudinal position  $z$ .

Sliding the detector, you find the voltage maxima and minima.

The distance between adjacent minima is \_\_\_\_\_


You also get the max/min ratio

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

(You only care about the ratio, not the actual values.)

Solving  $S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$ , you get  $|\Gamma|$ . **But this is not  $\Gamma$  yet!**

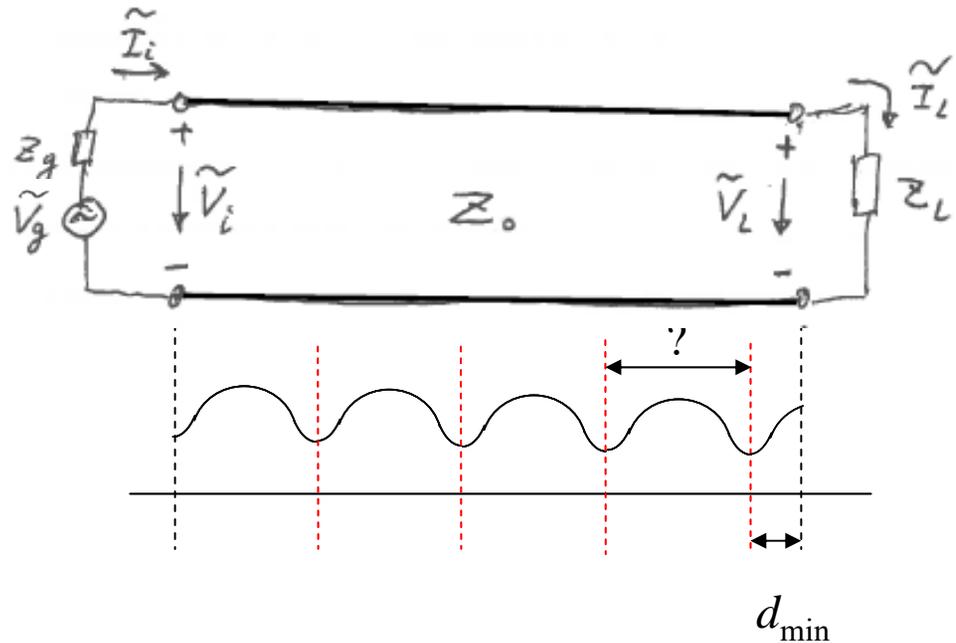The hope is: If you know  $\Gamma$ , you get  $z_L$  using the one-to-one mapping between the two. (Recall that.) You know  $Z_0$ , thus you can find  $Z_L$ .



The hope is: If you know  $\Gamma$ , you get  $z_L$  using the one-to-one mapping between the two. (Recall that.) You know  $Z_0$ , thus you can find  $Z_L$ .

$\Gamma = |\Gamma|e^{j\theta_r}$       We already know  $|\Gamma|$ . Just need to find  $\theta_r$ .

We know  $\frac{\lambda}{2} \xrightarrow{\beta = \frac{2\pi}{\lambda}}$   $\beta$

We know  $z_{\min} = -d_{\min}$


$2\beta z_{\min} + \theta_r = -\pi$

$-2\beta d_{\min} + \theta_r = -\pi$

$2\beta d_{\min} - \theta_r = \pi$

So you find  $\theta_r$ .

$\Gamma = |\Gamma|e^{j\theta_r} \implies z_L \implies Z_L$

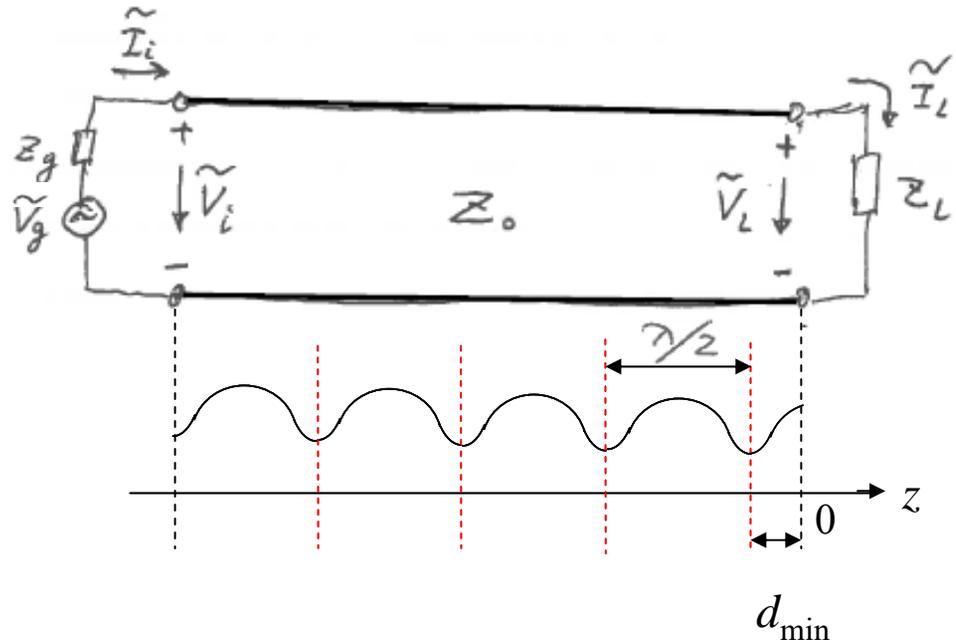

$|\tilde{V}(z)| = |V_0^+| \sqrt{1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta z + \theta_r)}$

Question:


In principle, we can also obtain the result by measuring positions of maxima.

But we prefer minima. Why?

We have so far always dealt with negative  $z$ , because we draw the transmission line to the left of the load.

We don't like to always carry the negative sign.

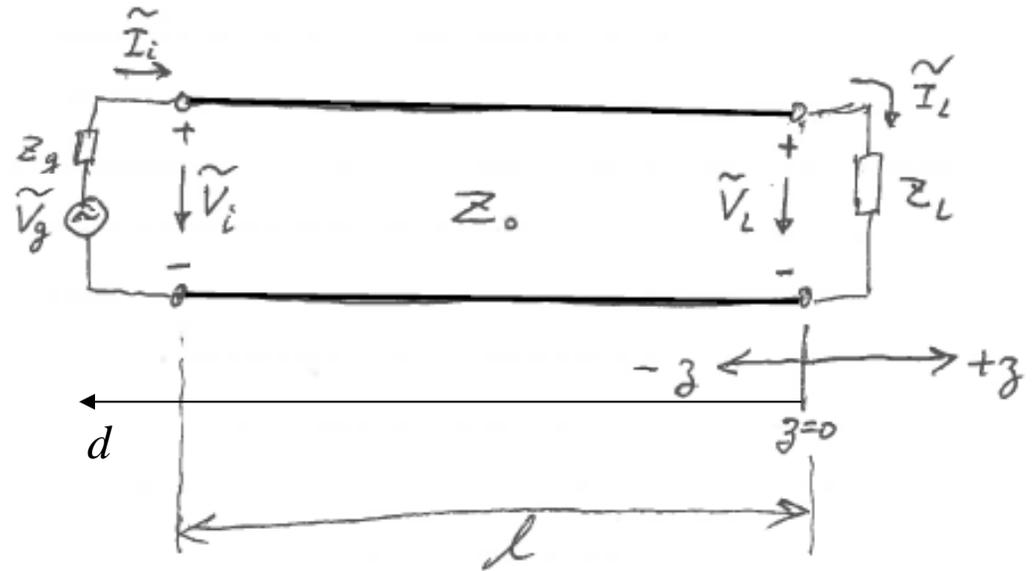So we define  $d = -z$ , the distance from the load.



$$\tilde{V}(z) = \underbrace{V_0^+ e^{-j\beta z}}_{\text{Incident}} + \underbrace{\Gamma V_0^+ e^{j\beta z}}_{\text{Reflected}}$$

$$\tilde{V}(z) = V_0^+ e^{-j\beta z} + \Gamma V_0^+ e^{j\beta z}$$

$$\Rightarrow \tilde{V}(d) = V_0^+ e^{j\beta d} + \Gamma V_0^+ e^{-j\beta d}$$

$$\tilde{I}(z) = I_0^+ e^{-j\beta z} - \Gamma I_0^+ e^{j\beta z}$$


$$\Rightarrow \tilde{I}(d) = I_0^+ e^{j\beta d} - \Gamma I_0^+ e^{-j\beta d}$$

Pay attention to signs.

$$\tilde{V}(d) = V_0^+ e^{j\beta d} + \Gamma V_0^+ e^{-j\beta d}$$

$$\tilde{I}(d) = I_0^+ e^{j\beta d} - \Gamma I_0^+ e^{-j\beta d}$$
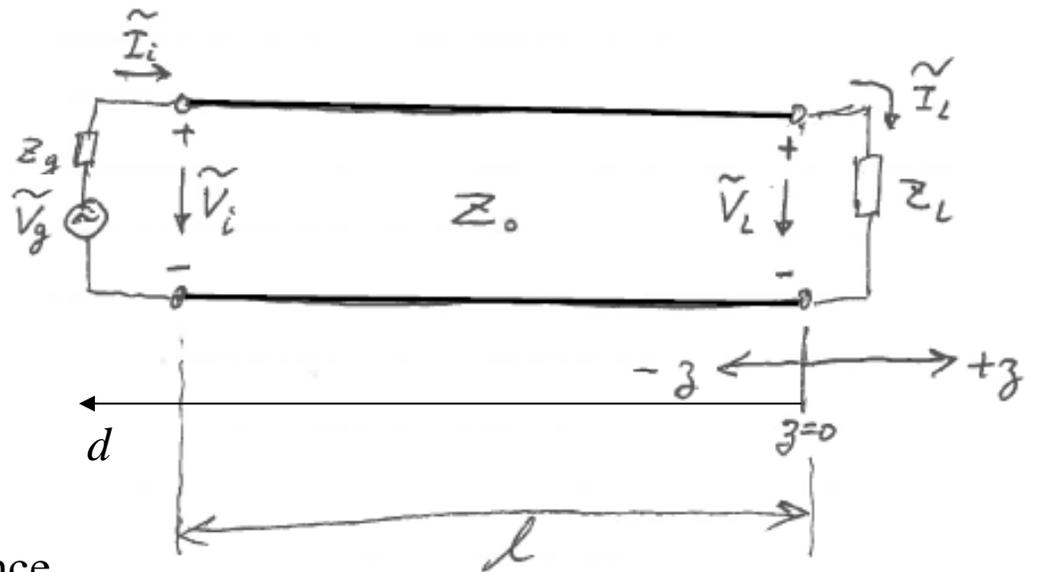
$$\frac{\tilde{V}^+(d)}{\tilde{I}^+(d)} = \frac{V_0^+}{I_0^+} = Z_0$$



Now let's consider the equivalent impedance looking into the transmission line at a distance  $d$  from the load:

$$\begin{aligned} Z(d) &= \frac{\tilde{V}(d)}{\tilde{I}(d)} = \frac{V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d})}{V_0^+ (e^{j\beta d} - \Gamma e^{-j\beta d})} Z_0 \\ &= Z_0 \cdot \frac{1 + \Gamma e^{-2j\beta d}}{1 - \Gamma e^{-2j\beta d}} \equiv Z_0 \cdot \frac{1 + \Gamma_d}{1 - \Gamma_d} \end{aligned}$$

Compare to  $\frac{Z_L}{Z_0} = \frac{1 + \Gamma}{1 - \Gamma}$ , thus the definition.  $\Gamma_d = \Gamma e^{-2j\beta d}$

$$Z(d) = Z_0 \cdot \frac{1 + \Gamma_d}{1 - \Gamma_d}, \quad \Gamma_d = \Gamma e^{-2j\beta d} \quad (\text{equivalent reflection coefficient at } d)$$

How to interpret this?

Say, the incident wave voltage is  $\tilde{V}(d)$  at  $d$ .

When it arrives at the load, it becomes  $\tilde{V}(d)e^{-j\beta d}$   
 -- just a phase shift.

At the load, the reflection wave is  $\tilde{V}(d)\Gamma e^{-j\beta d}$

This reflection wave travels a distance  $d$  to back.

At distance  $d$ , it becomes

$$\tilde{V}(d)\Gamma e^{-j\beta d} e^{-j\beta d} = \tilde{V}(d)\Gamma e^{-2j\beta d}$$


-- just another phase shift.

Thus the equivalent reflection coefficient at  $d$  is

$$\Gamma_d = \Gamma e^{-2j\beta d}$$

-- just imagine the interface is at  $d$ .

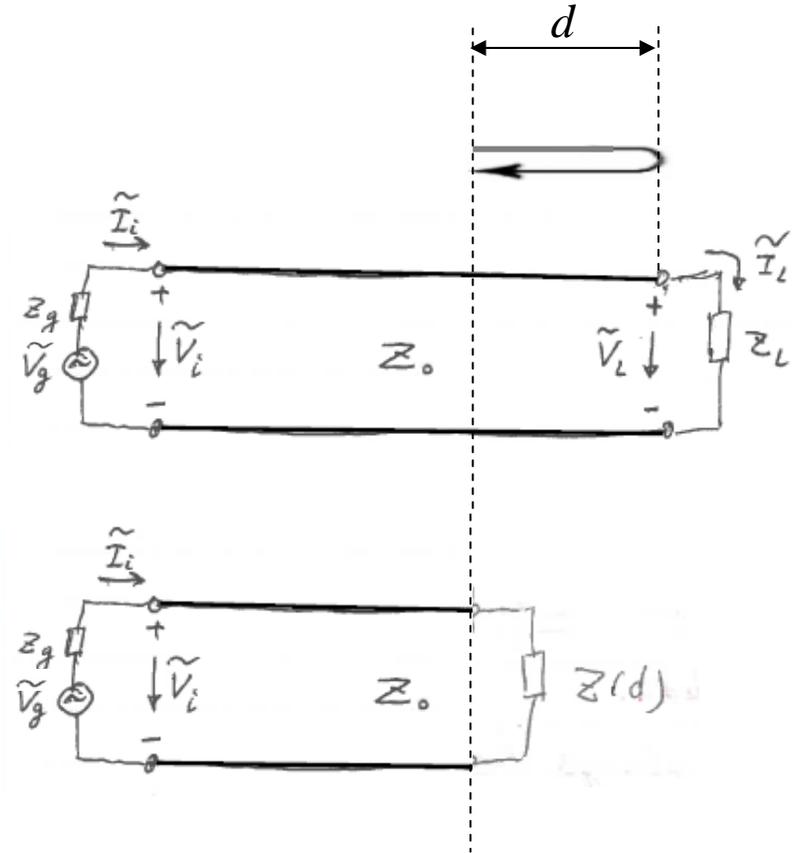$Z(d)$  corresponds to  $\Gamma_d$  in exactly the same manner as any  $Z_L$  to  $\Gamma$ .






Therefore the equivalent circuit.

$Z(d)$  corresponds to  $\Gamma_d$  in exactly the same manner as any  $Z_L$  to  $\Gamma$ .

Therefore the equivalent circuit.

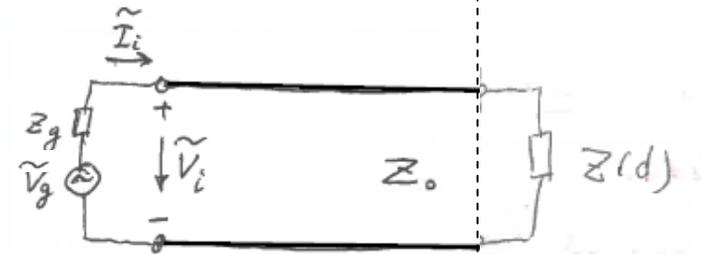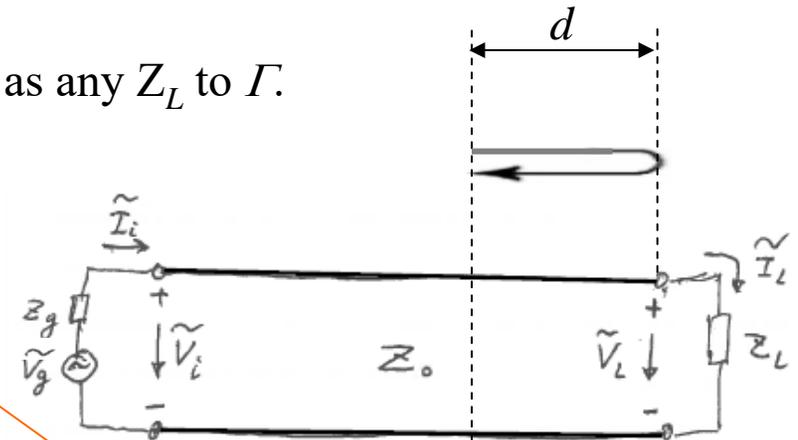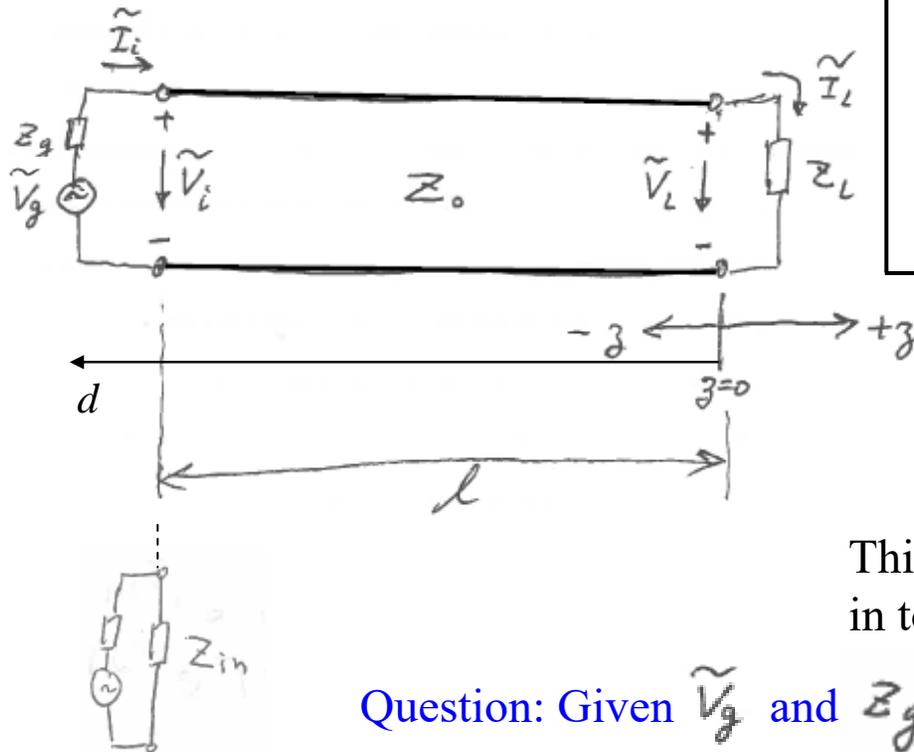You can have such an equivalent circuit at any  $d$ , all the way up to  $l$  for the entire transmission line:



At the input end of the transmission line,

$$Z_{in} = Z(l) = Z_0 \frac{1 + \Gamma_l}{1 - \Gamma_l}$$

This way, you turn the transmission line problem in to a simple circuit problem.

Question: Given  $\tilde{V}_g$  and  $Z_g$ , how do you find  $\tilde{V}_i$ ?



$$Z_{sc}(d) = \frac{\tilde{V}_{sc}(d)}{\tilde{I}_{sc}(d)}$$

$$= j Z_0 \tan \beta d$$

Understand this from a physics point of view:

Reactive loads don't dissipate power.  
Thus complete reflection.  
The difference is just in the phase.

Equivalent impedance


For  $\tan \beta d > 0$

$$j\omega L_{eq} = j Z_0 \tan \beta d \Rightarrow L_{eq} = \frac{Z_0}{\omega} \tan \beta d$$

For  $\tan \beta d < 0$


$$\frac{1}{j\omega C_{eq}} = j Z_0 \tan \beta d \Rightarrow C_{eq} = -\frac{1}{\omega Z_0 \tan \beta d}$$

Notice frequency dependence.

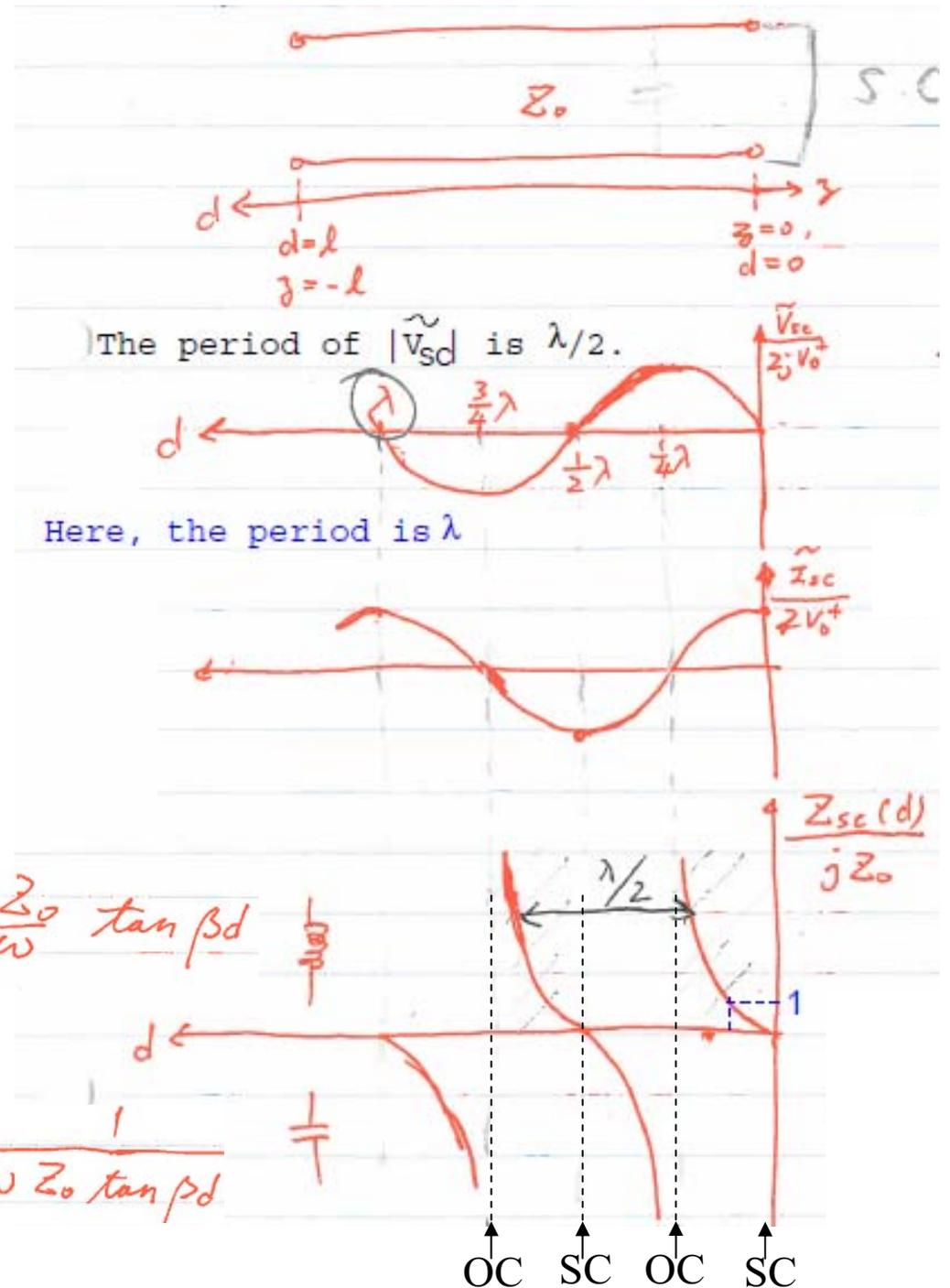
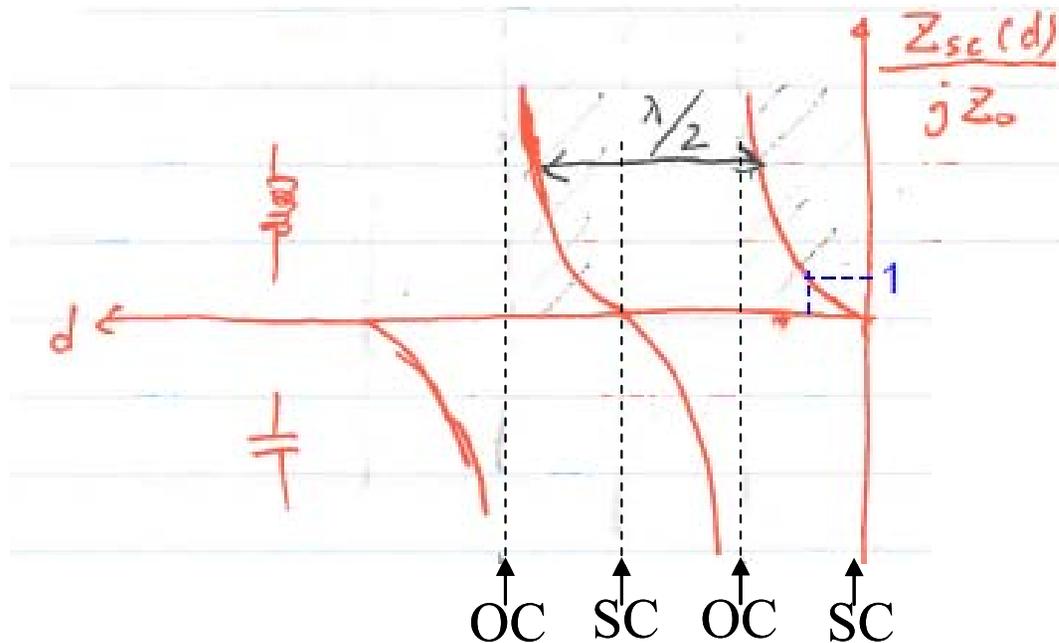
## The case of open circuit termination

Now that we already know the case of short circuit termination, what's the easiest way to work out the open circuit termination case?



With a short circuit, you can make an open circuit.

(For complete solution, see Fig. 2-21 in textbook, pp. 81 in 7/E or pp. 82 in 6/E)

Now let's go back to the general case and look at the equivalent input impedance.

$$Z_{in} = Z(d=l) = Z_0 \frac{e^{j\beta l} + \Gamma e^{-j\beta l}}{e^{j\beta l} - \Gamma e^{-j\beta l}}$$

(make sure you understand how this is arrived at)

Insert

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$e^{j\beta l} = \cos \beta l + j \sin \beta l$$

$$e^{-j\beta l} = \cos \beta l - j \sin \beta l$$

and you get


$$Z_{in} = \frac{Z_L \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_L \sin \beta l} Z_0$$

or in the normalized form:

$$z_{in} = \frac{z_L \cos \beta l + j \sin \beta l}{\cos \beta l + j z_L \sin \beta l}$$

Recall that  $z_L = \frac{Z_L}{Z_0}$

Question: What is the unit of  $z_L$ ?

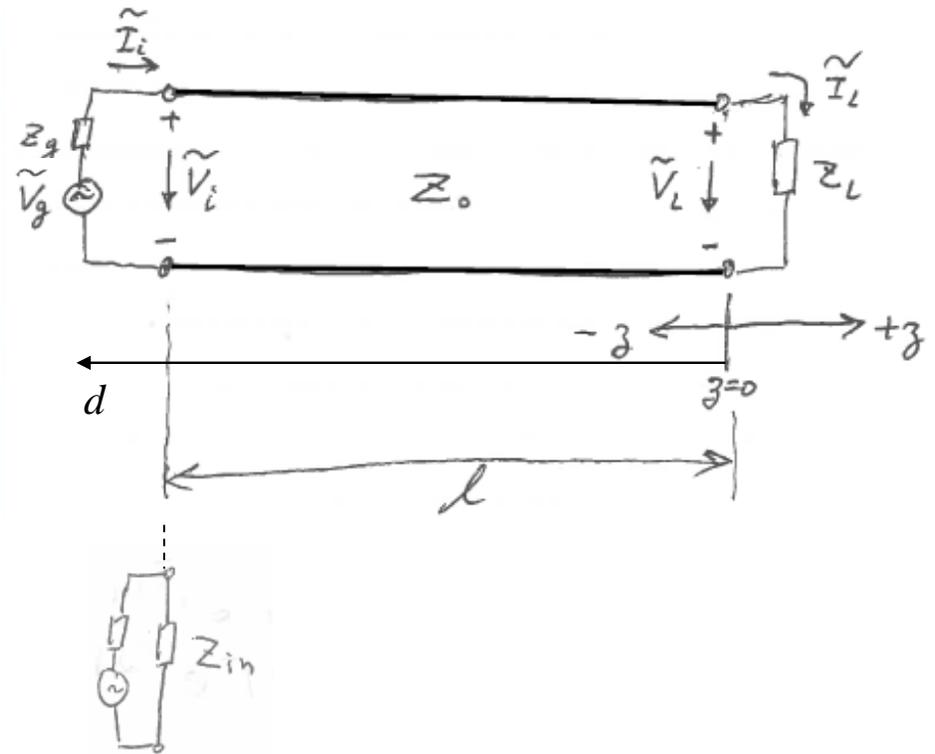

Do not confuse “input” with “incident”


$\tilde{V}_i$  or  $\tilde{V}_{in}$  is the voltage at the input end. It is the sum of incident and reflected waves **there**.

$$\tilde{V}_{in} = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} = V_0^+ (e^{j\beta l} + \Gamma e^{-j\beta l})$$

incident                      reflected

The incident wave voltage at the input end is
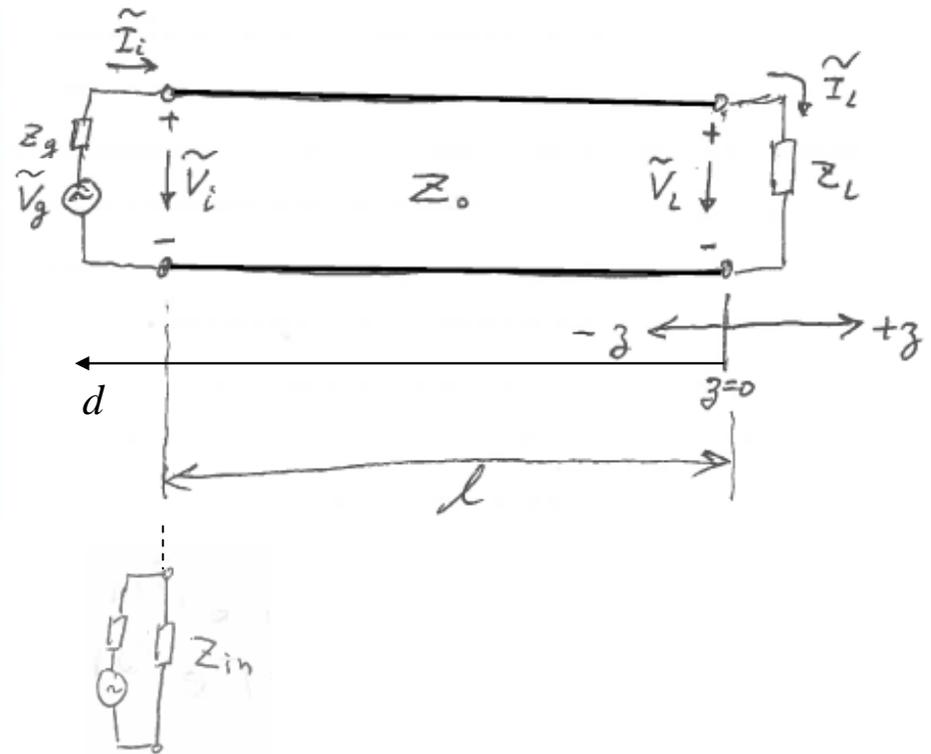
$$\tilde{V}_{in(inc)} = V_0^+ e^{j\beta l}$$



The quarter wavelength magic

$$Z_{in} = \frac{Z_L \cos \beta l + jZ_0 \sin \beta l}{Z_0 \cos \beta l + jZ_L \sin \beta l} Z_0$$

For  $\beta l = n\pi$ ,

i.e.  $l = n \cdot \frac{\lambda}{2}$


$$Z_{in} = Z_L$$

Periodic. This is for generic  $Z_L$ .  
For the special case of purely reactive loads, see slide 17.

For  $\begin{cases} \cos \beta l = 0 \\ \sin \beta l = \pm 1 \end{cases}$  i.e.  $\beta l = n\pi + \frac{1}{2}\pi$ ,

i.e.  $l = n \cdot \frac{\lambda}{2} + \frac{\lambda}{4}$ ,

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

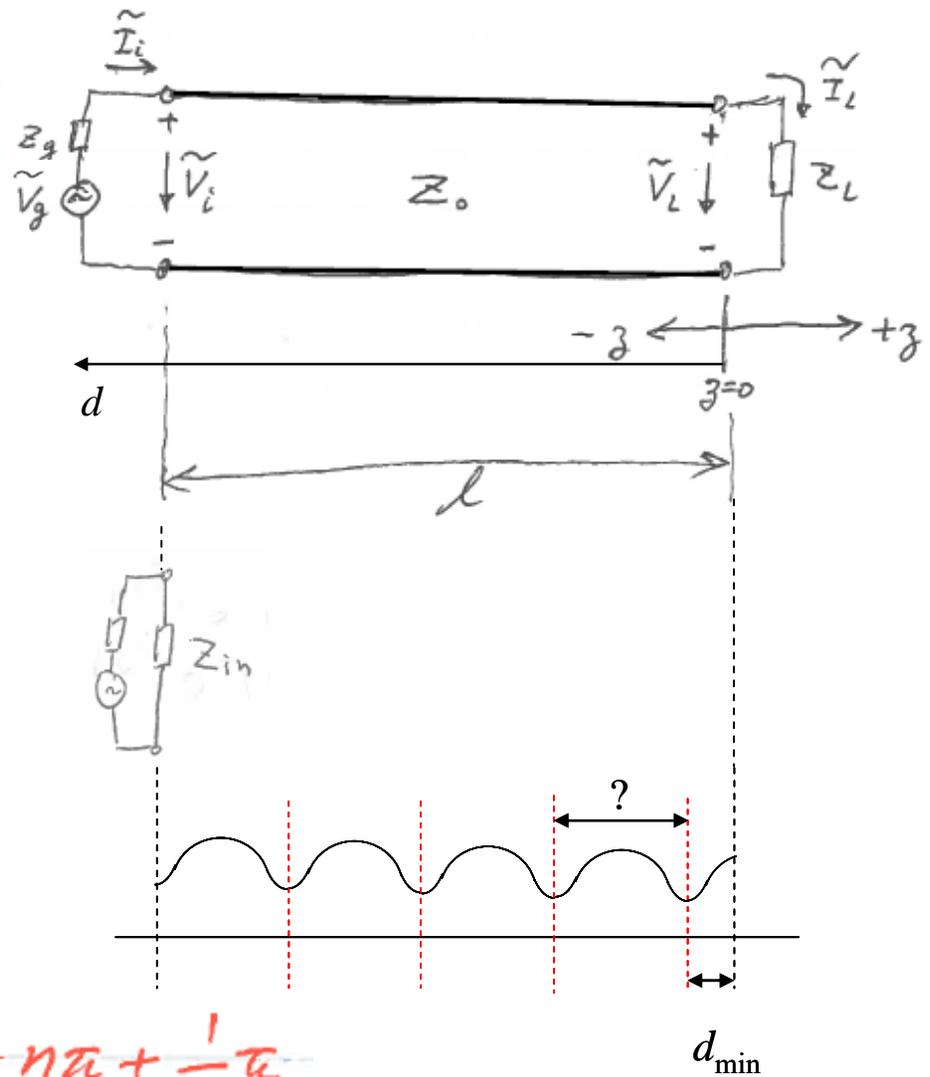

For  $l = n \cdot \frac{\lambda}{2} + \frac{\lambda}{4}$ ,

$$Z_{in} = \frac{Z_0^2}{Z_L}$$



or

$$Z_0 = \sqrt{Z_{in} \cdot Z_L}$$

Question: What are the equivalent “normalized” forms?

The quarter wavelength transformer

-- a method for impedance matching

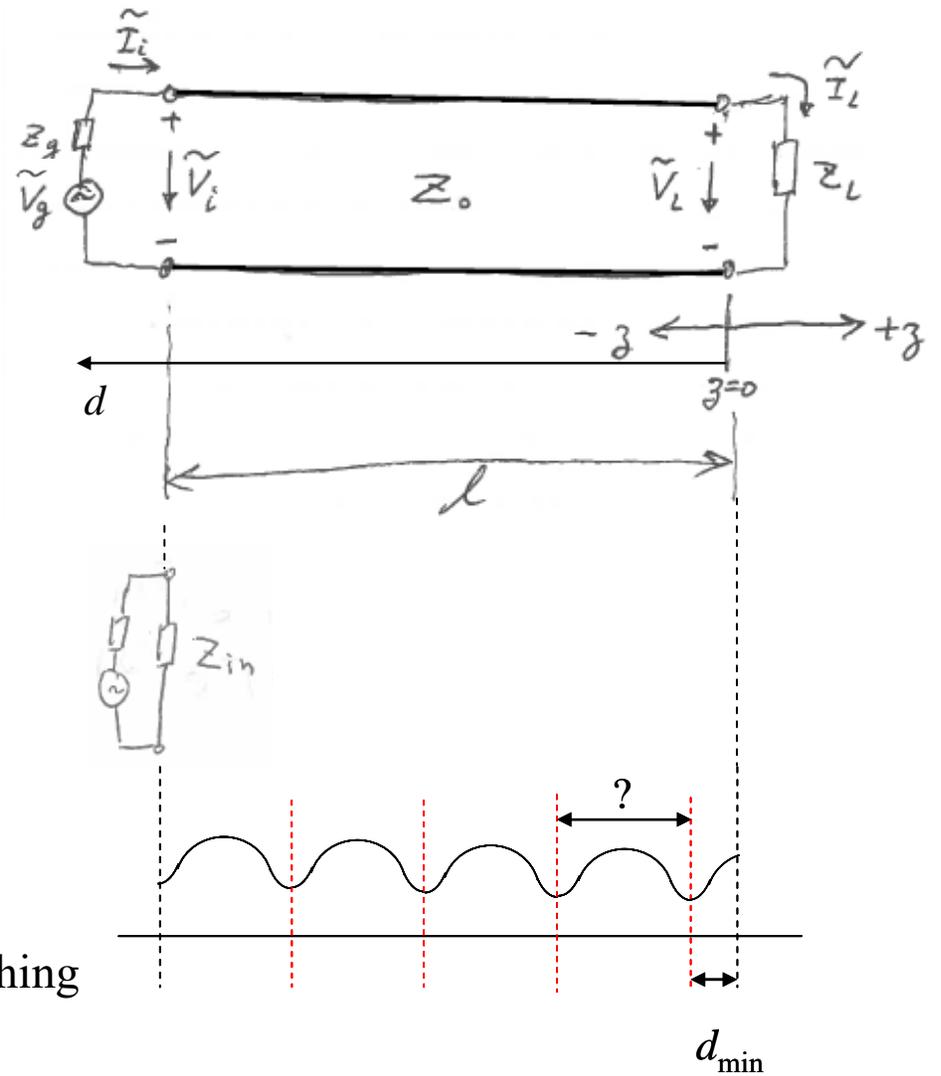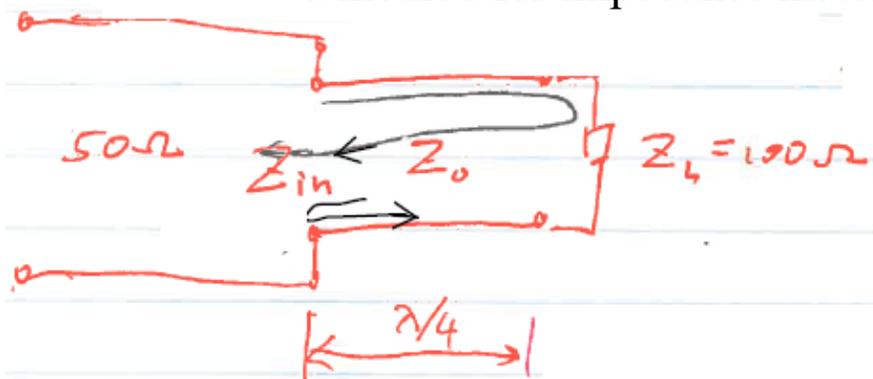


# The quarter wavelength transformer

To better understand why it works, let's look at its optical analog.




WITHOUT ANTI-REFLECTIVE

WITH ANTI-REFLECTIVE

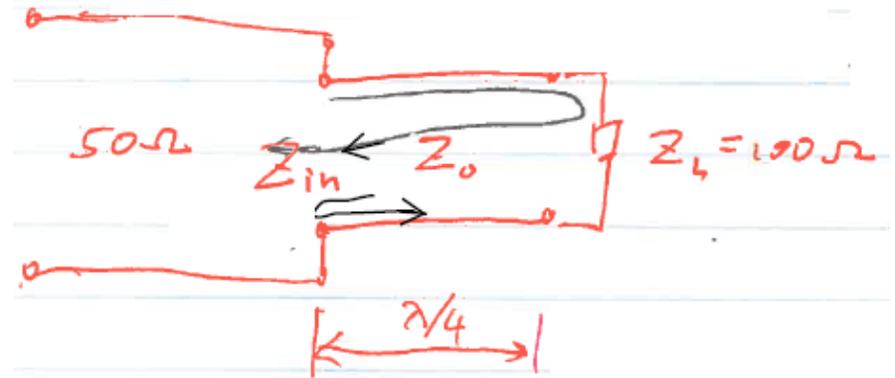


## Anti-reflection coating

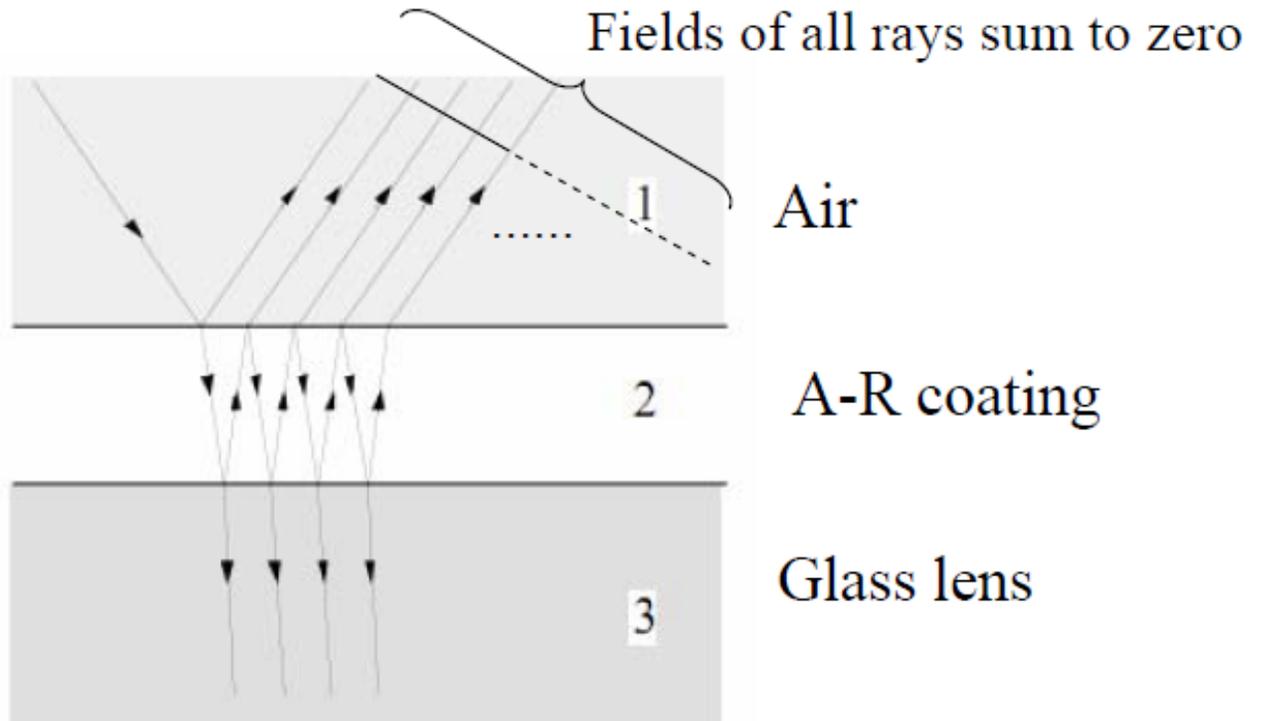

The quarter wavelength magic explained in the multiple reflection point of view

Optical analog: the AR coating

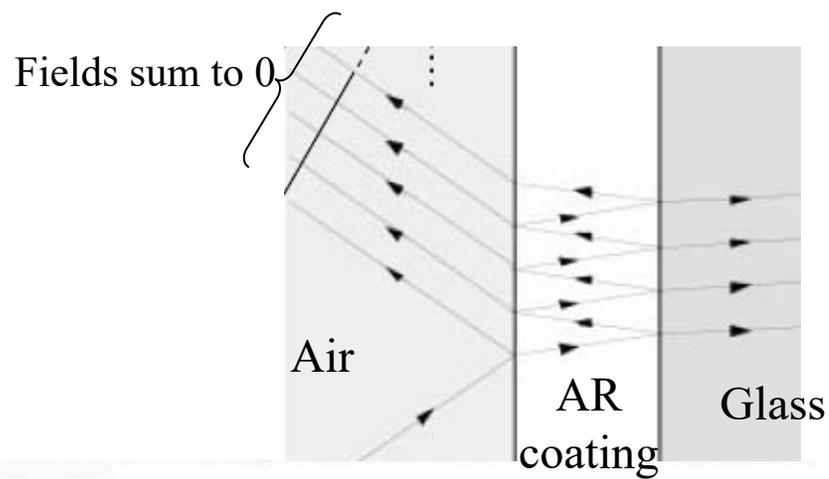


$$\Gamma_1 = \frac{Z_1 - Z_0}{Z_1 + Z_0}$$

$$\Gamma_2 = \frac{Z_0 - Z_1}{Z_0 + Z_1}$$


$$\Gamma_3 = \frac{R_L - Z_1}{R_L + Z_1}$$

$$T_1 = \frac{2Z_1}{Z_1 + Z_0}$$

$$T_2 = \frac{2Z_0}{Z_1 + Z_0}$$

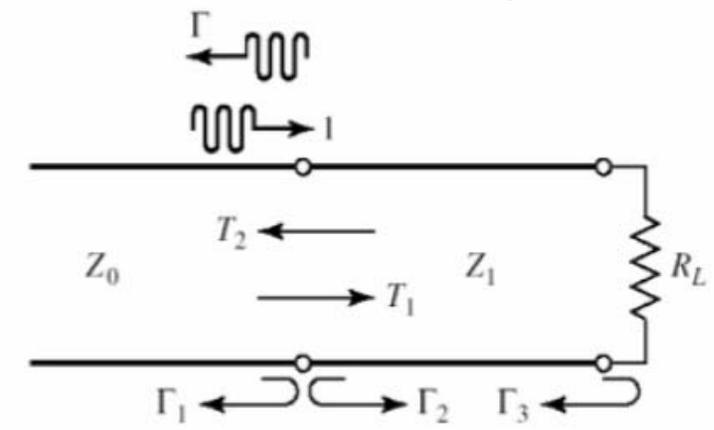

Voltages (or fields) sum to 0

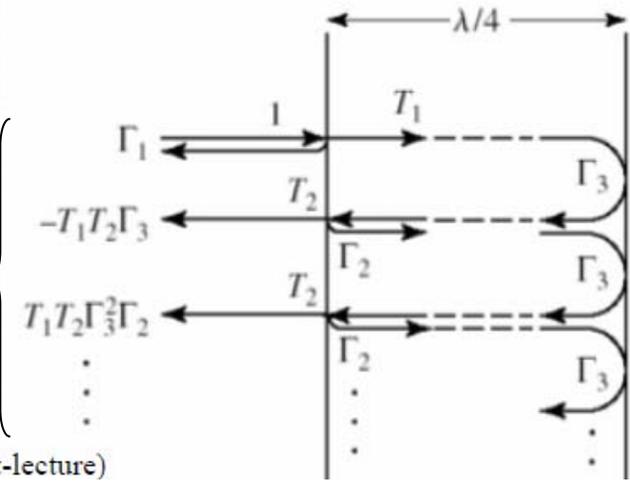

(Adapted from: Naveed Ramzan, <http://www.slideshare.net/nramzan19/smith-chart-lecture>)

## Take-home messages

- Standing waves are simply due to **interference** between incident & reflected waves.
- The variations of real positive amplitudes (of voltage & current) and modulus squares of amplitudes ( $|\tilde{V}(d)|^2$  and  $|\tilde{I}(d)|^2$ ) with position (i.e. distance from load) are **periodic**, analogous to interference stripes in optics and are indeed one-dimensional interference patterns.
- The period of the patterns are **half wavelength**.
- The reflection wave amplitude is a fraction ( $\leq 1$ ) of the incident, and its **phase is shifted** relative to the incident, right upon reflection. Thus the reflection coefficient is complex.
- In general voltage and current of a transmission line are combinations of a traveling wave and a standing wave.
- When the load is **purely reactive** (including short and open) **complete reflection**. These are the same in terms of absence of energy dissipation. Thus the you can obtain any desired reactance value by terminating a transmission line in any reactive component; you only need to have the right distance from the load.
- At any distance  $d$  from the load, you have an equivalent impedance  $Z(d)$ , such that you feel as if the transmission line is terminated in  $Z(d)$  right there.
- $Z(\lambda/4)$  and  $Z_L$  [or more generally  $Z(d + \lambda/4)$  and  $Z(d)$ ] have a special relation, which is used as **a method for impedance matching**. This method eliminates reflection because multiple reflections sum up to 0.