
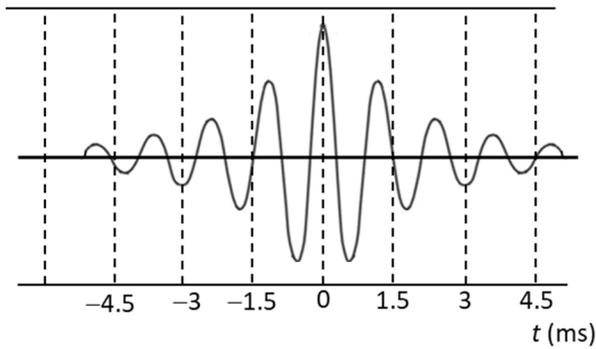
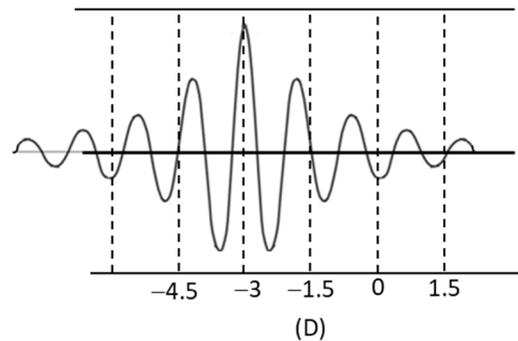
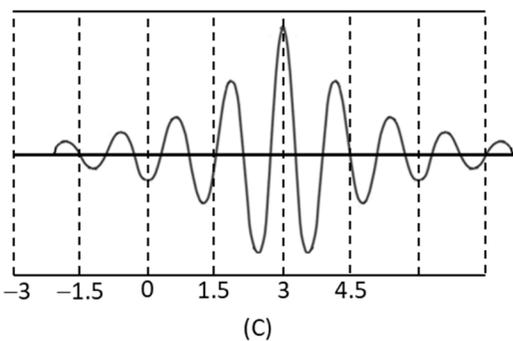
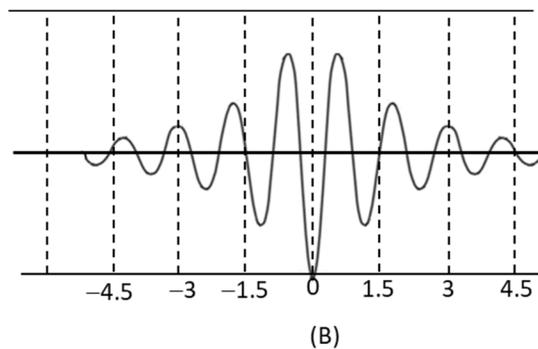


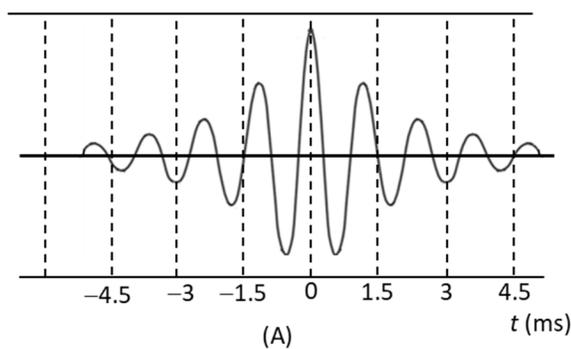**Problem 1** Total 9 points

An audio signal, consisting of a periodic train of wave packets, is fed to a speaker and one channel of an oscilloscope. The oscilloscope is adjusted to display one wave packet of this signal, as sketched in the figure below. A microphone is 1 m away from the speaker, and its output is fed to another channel of the oscilloscope. Both signals are fed to oscilloscope channels via coaxial cables. The speed of sound is  $(1000/3)$  m/s.



(1) Which of the following sketches best depicts the waveform of the microphone output? Explain your choice.

**Solution:**

4 The microphone output is delayed with regard to the speaker signal by the time it takes for the sound wave to propagate from the speaker to the microphone,  $\Delta t = 1 \text{ m} / (1000/3 \text{ m/s}) = 3 \text{ ms}$ . Therefore, (C) is the correct waveform.

(2) A train of wave packets in the above contains frequency components within a bandwidth. Each single frequency component of the input signal  $V_i \cos \omega t$  to the speaker,  $t$  being time, corresponds to the Fourier component of the same frequency,  $V_o \cos(\omega t - \phi)$ , of the output of the microphone. Find the function  $\phi(\omega)$ .

**Solution:**

5

The microphone output is delayed with regard to the speaker signal by  $\Delta t$ , therefore its Fourier component corresponding to  $V_i \cos \omega t$  is

$$V_o \cos[\omega(t - \Delta t)] = V_o \cos(\omega t - \omega \Delta t) = V_o \cos(\omega t - \phi).$$

Therefore  $\phi(\omega) = \omega \Delta t = \omega(0.003 \text{ s})$ .


Notice that  $\phi$  depends on  $\omega$ , and is proportional to  $\omega$ .

**Problem 2 Total 46 points**

(1) A transmission line of characteristic impedance  $Z_0 = 50 \Omega$  is terminated in a purely resistive load  $25 \Omega$ . For frequency  $f = 300 \text{ MHz}$ , find the equivalent impedance  $Z_1(d)$  at distance  $d = 25 \text{ cm}$  from the load towards the generator.

(2) A transmission line of characteristic impedance  $Z_0 = 50 \Omega$  is terminated in a short circuit. For frequency  $f = 300 \text{ MHz}$ , find the equivalent impedance  $Z_2(d)$  at distance  $d = 25 \text{ cm}$  from the short-circuit termination towards the generator.

(3) The figure below shows a transmission line system with the same characteristic impedance  $Z_0 = 50 \Omega$  for the main line and both branches, operating at frequency  $f = 300 \text{ MHz}$ . What is the total impedance at the junction of the two branches? What is the magnitude of the voltage reflection coefficient  $|\Gamma_1|$  of the branch terminated in the  $25 \Omega$  load? What is the magnitude of the voltage reflection coefficient  $|\Gamma_2|$  of the branch terminated in a short circuit? What is the magnitude of the voltage reflection coefficient  $|\Gamma|$  of the main line before the junction? The generator (not shown in figure) sends out an incident power  $P_{\text{inc}} = 9 \text{ mW}$ . What is the power  $P_{\text{ref}}$  reflected back to the generator? What are the incident and reflected power, respectively, on the branch terminated in the  $25 \Omega$  load? What is the power dissipated by the load?

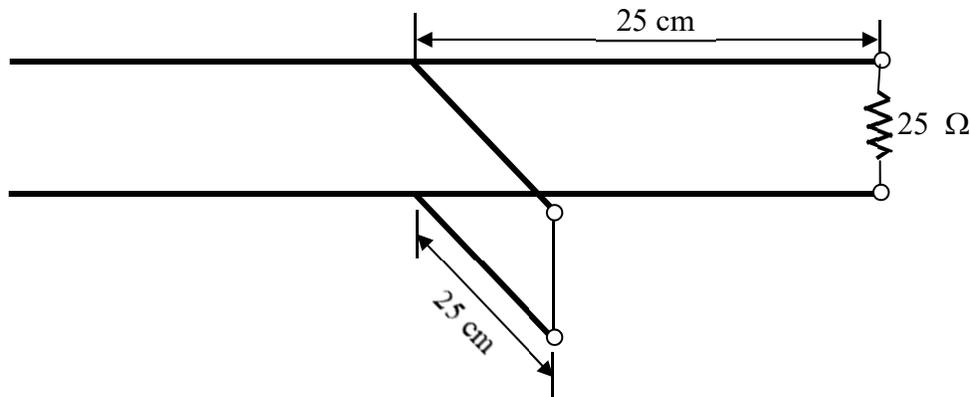**Solution:**

$f = 300 \text{ MHz} \rightarrow \lambda = c/f = (3 \times 10^8 \text{ m/s}) / (3 \times 10^8 / \text{s}) = 1 \text{ m}$ . ← 2 points (student automatically receive these

$d = 25 \text{ cm} = \lambda/4$ .

points if answers the following correctly)

(1) The normalized load is 0.5. The normalized equivalent impedance  $\lambda/4$  away is 2. Therefore,  $Z_1(d) = 100 \Omega$ . 4

(2) The equivalent impedance  $\lambda/4$  away from a short circuit is an open circuit. Therefore,  $Z_2(d) = \infty$ . 4

(3) The total impedance of  $100 \Omega$  in parallel with an open circuit is  $100 \Omega$ . 2

$|\Gamma_1| = 1/3$ .  $|\Gamma_2| = 1$ .  $|\Gamma| = 1/3$ . 3 3 2

$P_{\text{ref}} = |\Gamma|^2 P_{\text{inc}} = (1/9) \times 9 \text{ mW} = 1 \text{ mW}$  on the main line. 3

On the branch of the  $25 \Omega$  load, the incident and reflected power are 9 mW and 1 mW, respectively. The power dissipated by the load is therefore 8 mW.

1

1

2

### Problem 2 cont'd

(4) For frequency  $f = 600$  MHz, repeat (1).

(5) For frequency  $f = 600$  MHz, repeat (2).

(6) For the transmission line system shown in the above figure with frequency  $f = 600$  MHz, what is the total impedance at the junction of the two branches? What is the magnitude of the voltage reflection coefficient  $|\Gamma|$  of the main line before the junction? The generator (not shown in figure) sends out an incident power  $P_{\text{inc}} = 9$  mW. What is the power  $P_{\text{ref}}$  reflected back to the generator? What is the power dissipated by the load?

### Solution:

$$f = 600 \text{ MHz} \rightarrow \lambda = c/f = (3 \times 10^8 \text{ m/s}) / (6 \times 10^8 / \text{s}) = 0.5 \text{ m.}$$

← 2 points (student automatically receive these points if answers the following correctly)

$$d = 25 \text{ cm} = \lambda/2.$$

(4) The equivalent impedance  $\lambda/2$  away is the same as the load. Therefore,  $Z_1(d) = 25 \Omega$ . 4

(5) The equivalent impedance  $\lambda/2$  away from a short circuit is also a short circuit. Therefore,  $Z_2(d) = 0$ . 4

(6) The total impedance of  $25 \Omega$  in parallel with a short circuit is 0. 2

$$|\Gamma| = 1. 3$$

$$P_{\text{ref}} = |\Gamma|^2 P_{\text{inc}} = 9 \text{ mW. } 2$$

The power dissipated by the load is 0. 2

**Problem 3 total 31 + 14 points (14 bonus points for the 2nd solution)**

A load  $Z_L = (90.5 + 25j) \Omega$  is to be matched to a  $Z_0 = 50 \Omega$  lossless transmission line by using a shorted stub. Determine

- (1) How far should the stub be away from the load in terms of the wavelength ( $d/\lambda$ );
- (2) The required stub **admittance and impedance** (give actual values in S and  $\Omega$ , respectively), and whether it is inductive or capacitive;
- (3) The length of the stub in terms of the wavelength ( $l_s/\lambda$ ), and
- (4) The standing wave ratios of the transmission line between the stub and the load, that of the stub, and that of the transmission line between the generator and the stub.

**Caution:** you need to find 3 SWRs for 3 segments.

- (5) What is the voltage reflection coefficient  $\Gamma_L$  at the load? What is the voltage reflection coefficient  $\Gamma_S$  at the short-circuit termination of the stub?

Note: There are two independent solutions to each single-stub matching problem. You only need to get one to get full points for (1) through (3). If you get both solutions right, **you will receive bonus points**. In other words, you may get > 100 points on this test. If you mix up the  $d$  or  $l_s$  values for the two solutions, however, you lose both the bonus and basic points.

**Solution:**

$$z_L = (90.5 + 25j)/50 = 1.81 + 0.5j$$

2 points (student automatically receive these points if answers the following correctly)

Using the Smith chart or simple calculation for this resistive load, we find  $y_L = 0.51 - 0.14j$ . 3

(1) Solution 1:  $d/\lambda = 0.181$ , where  $y(d) = 1 + 0.71j$  3

Solution 2:  $d/\lambda = 0.377$ , where  $y(d) = 1 - 0.71j$  ← 2nd solutions earns 3+3=6 bonus points

(2) Solution 1: To cancel  $y(d)$ , we need  $y_{\text{stub}} = -0.71j$ . ← 1: automatically received if below right

$$Y_{\text{stub}} = -0.71j / (50 \Omega) = -j14 \text{ mS} \quad 1$$

$$Z_{\text{stub}} = j71 \Omega \quad 1$$

The required stub impedance is inductive. 1

Solution 2: To cancel  $y(d)$ , we need  $y_{\text{stub}} = +0.71j$ .

$$Y_{\text{stub}} = +0.71j / (50 \Omega) = +j14 \text{ mS}$$

$$Z_{\text{stub}} = -j71 \Omega$$

The required stub impedance is capacitive.

2nd solutions earns 1+1+1+1=4 bonus points

(3) Solution 1:  $y_{\text{stub}} = -0.71j$  2  
 $l_s/\lambda = 0.152$  2

Solution 2:  $y_{\text{stub}} = +0.71j$  } 2nd solutions earns 2+2=4 bonus points  
 $l_s/\lambda = 0.348$  }

(4) For both solutions,  $|\Gamma| = 1/3$  and  $S = 2$  between the load and the stub. 2

$S = 1$  between the stub and the generator. Impedance matched! 4


$S = \infty$  for the stub. Short! 4

(5) The voltage reflection coefficient at the load  $\Gamma_L = (1/3)\angle 21.9^\circ$ . 4

The voltage reflection coefficient at the short-circuit termination of the stub  $\Gamma_S = -1$ . 2

# The Complete Smith Chart

Black Magic Design

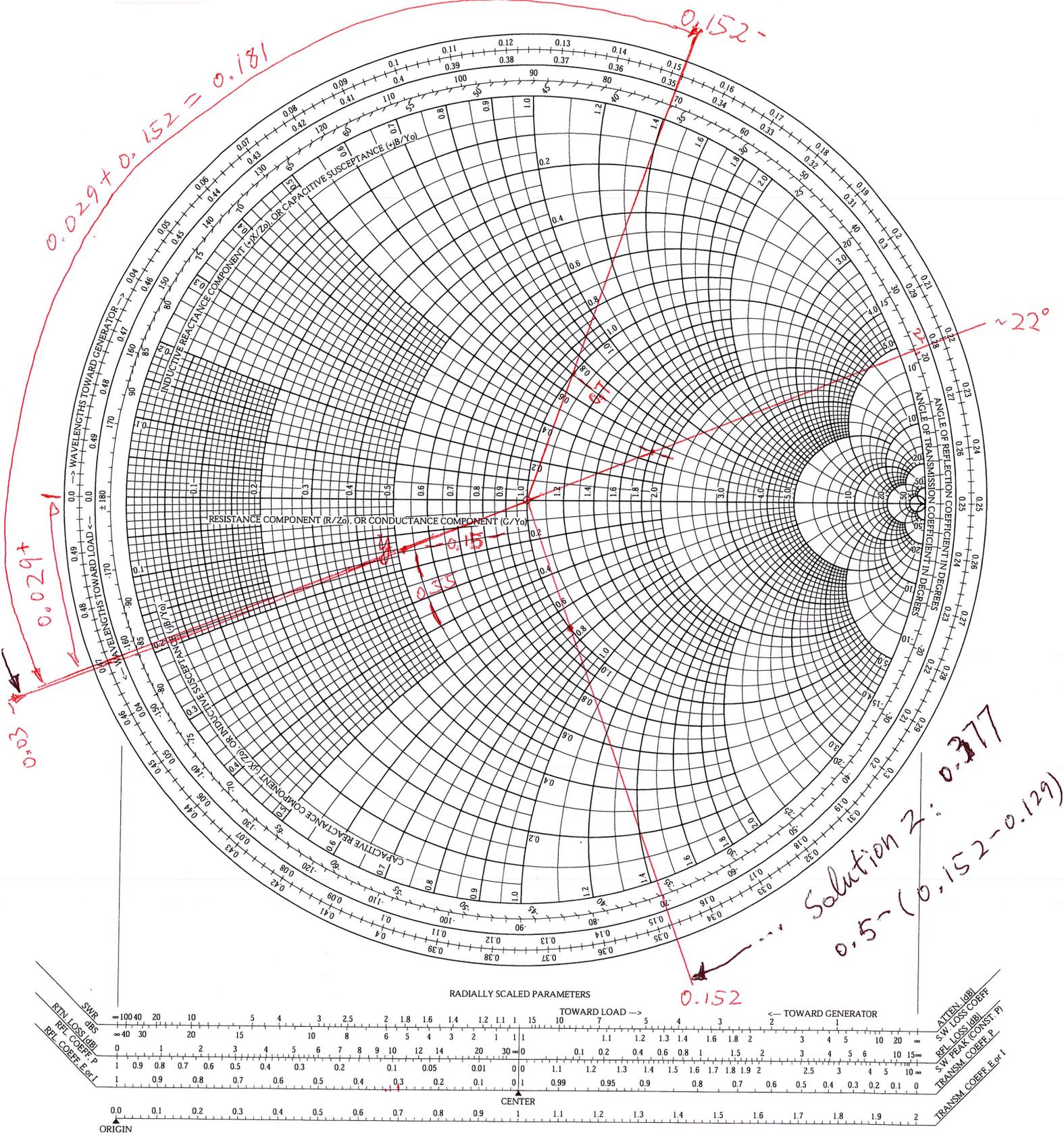

$0.029 + 0.152 = 0.181$

0.152


0.029 +

0.15  
0.55

0.152

Solution 2: 0.377  
 $0.5 - (0.152 - 0.129)$

22°

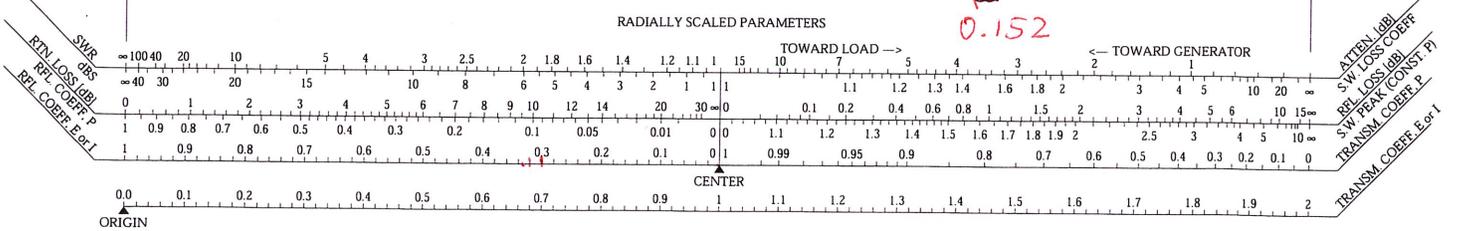


Solution 2

# The Complete Smith Chart
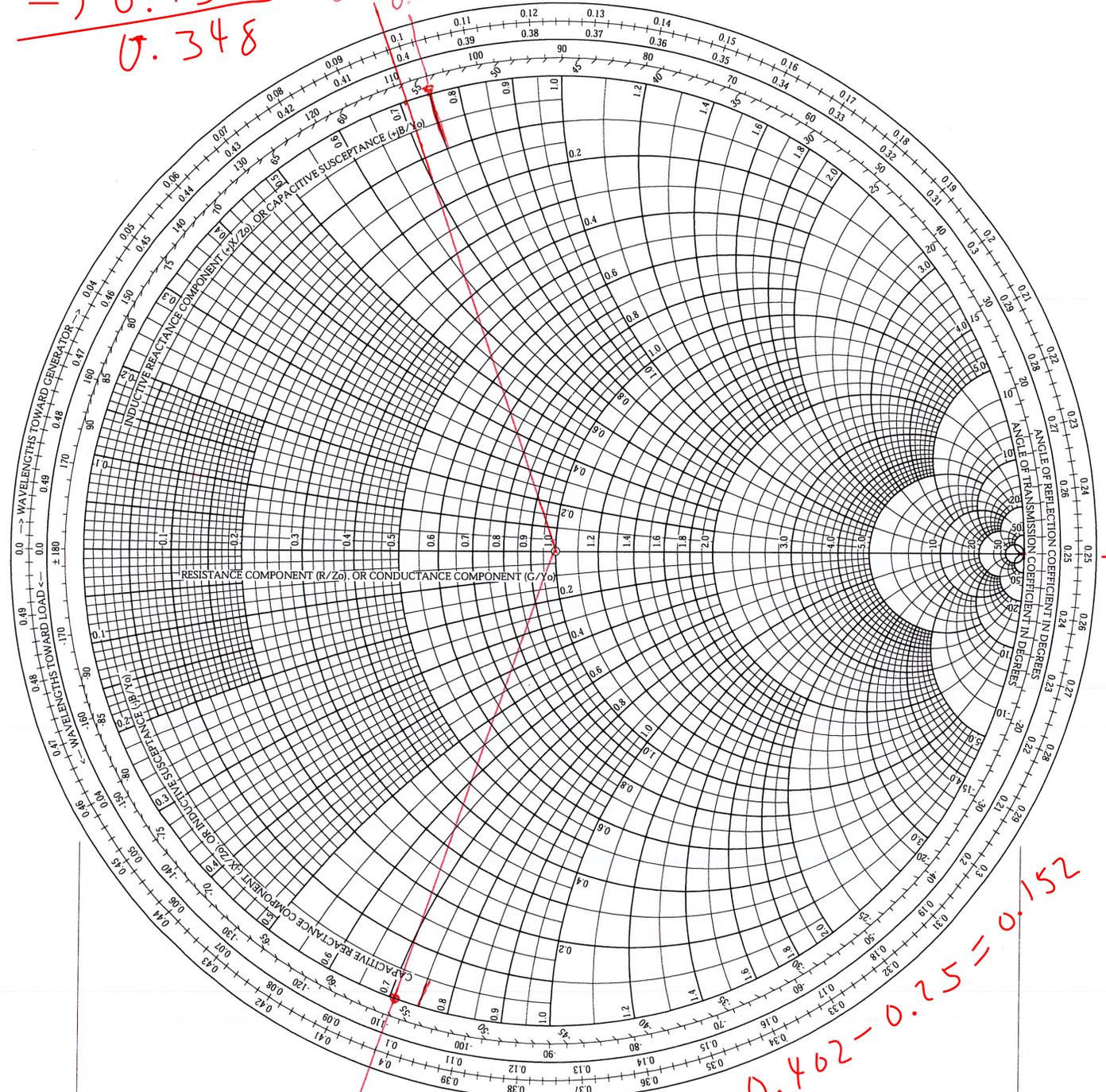
## Black Magic Design


$$\begin{array}{r} 0.5 \\ -) 0.152 \\ \hline 0.348 \end{array}$$

$$\begin{array}{r} 0.098 \\ +) 0.75 \\ \hline \end{array}$$



$$0.402 - 0.75 = 0.152$$

0.402

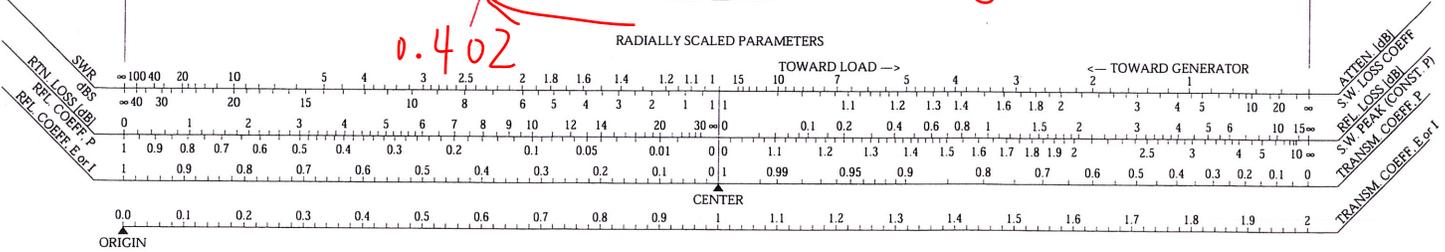

**Problem 4** Total 14 points

Generate the voltage bounce diagram for a 2-m long lossless transmission line of characteristic impedance  $Z_0 = 75 \Omega$  and phase velocity  $v_p = 2c/3$  (where  $c$  is the speed of light), assuming that the line is fed by a voltage pulse, with a width  $\tau = 5$  ns and a height  $V_g = 1$  V, applied at time  $t = 0$  by a generator circuit with  $R_g = 25 \Omega$ . The line is terminated in a load  $R_L = 225 \Omega$ . Use the bounce diagram to plot  $v(t)$  at the load.

Find the steady state voltage and current.

**Solution:**

The single trip time

$$T = \frac{l}{v_p} = \frac{2 \text{ m}}{2 \times 10^8 \text{ m/s}} = 10^{-8} \text{ s} = 10 \text{ ns}$$

The incident voltage of the first single trip

$$V_i^+ = \frac{Z_0}{Z_0 + R_g} V_g = \frac{75}{75 + 25} \times 1 \text{ V} = 0.75 \text{ V}$$

The reflection coefficient at the load

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0} = \frac{225 - 75}{225 + 75} = \frac{150}{300} = \frac{1}{2}$$

The reflection coefficient at the generator


$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0} = \frac{25 - 75}{25 + 75} = -\frac{50}{100} = -\frac{1}{2}$$

See next page for the bounce diagram and the waveform.

At the steady state,  $v(\infty) = 0$ ,  $i(\infty) = 0$ , since the input is a pulse. 2

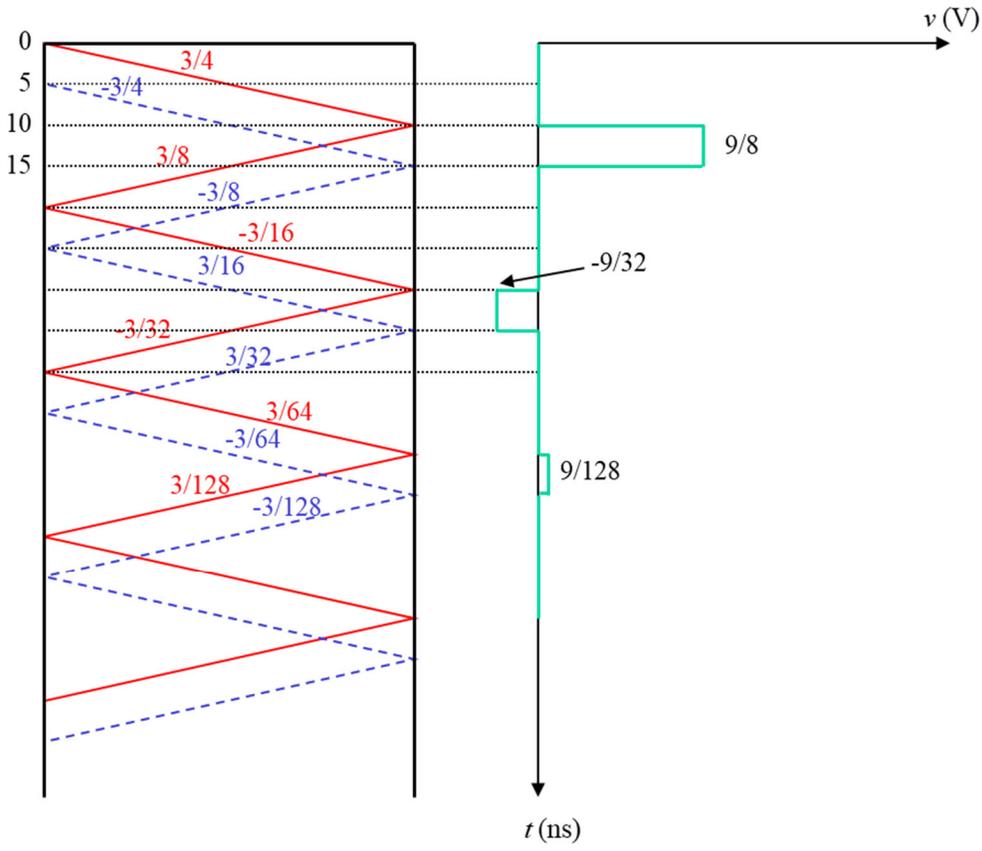Automatically received if bounce chart  
& waveform right





4 points for chart & waveform. Three pulses sufficient. Must indicate time and level for each pulse; any understandable means is acceptable.