

ECE 202  
Spring Semester, 2002  
HW Set #10  
Revised

Due: April 15, 2002

wlg (wlg@utk.edu)

course home page: <http://web.utk.edu/~green/home.htm>

Name \_\_\_\_\_  
print( last, first)

Work the following problems from the text. Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. Do neat work. **Underline your answers. Show how you got your equations.** Each problem counts 10 points. **Be sure to show how you got your answers.**

$$15.2 \quad y_{11} = \frac{1}{6} S, \quad y_{12} = y_{21} = \frac{-1}{12} S, \quad y_{22} = y_{11}$$

$$15.5 \quad y_{11} = \frac{1}{Z_1} S, \quad y_{12} = 0, \quad y_{21} = \frac{\gamma}{Z_2}, \quad y_{22} = \frac{1}{Z_2} S$$

$$15.7 \quad y_{11} = j\omega(C_1 + C_2) S, \quad y_{12} = -j\omega C_2 S, \quad y_{21} = g - j\omega C_2 S, \quad y_{22} = \frac{1}{R} + j\omega(C_2 + C_3) S$$

$$15EF-1 \quad V_1 = 36 V$$

15.12 In addition to the Z parameters, also find the H parameters.

$$z_{11} = 400 \text{ ohms}, \quad z_{12} = 15 \text{ ohms}, \quad z_{21} = -2e^{-6} \text{ ohms}, \quad z_{22} = 50 \text{ kohms}$$

$$h_{11} = 1 \text{ k } \Omega, \quad h_{12} = 3e^{-4}, \quad h_{21} = 40, \quad h_{22} = 20 \mu S; \quad \Delta H = 8e^{-3}$$

$$15.18 \quad \frac{V_2}{V_s} = \frac{h_{21} R_L}{h_{12} h_{21} R_L - (1 + h_{22} R_L)(R_L + h_{11})}$$

$$15.24 \quad A = \frac{-1}{\gamma}, \quad B = \frac{-Z_2}{\gamma}, \quad C = \frac{-1}{\gamma Z_1}, \quad D = \frac{-Z_2}{\gamma Z_1}$$

$$15.39 \quad A = 3, \quad B = j8, \quad C = 3 - j1, \quad D = 3 + j8$$