

Desk Copy

ECE 300  
Spring Semester, 2004  
HW Set #10

April 20, 2004

wlg

Name Green  
Print (last, first)

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 10 points except problem 15.12 counts 20 points.

$$15.2 \quad y_{11} = (1/6) \text{ S}, \quad y_{12} = -(1/12) \text{ S}, \quad y_{21} = -(1/12) \text{ S}, \quad y_{22} = (1/6) \text{ S}$$

$$15.5 \quad y_{11} = (1/Z_1) \text{ S}, \quad y_{22} = 0, \quad y_{21} = (\gamma/Z_2) \text{ S}, \quad y_{12} = (1/Z_2) \text{ S}$$

$$15.7 \quad y_{11} = j\omega(C_1 + C_2) \text{ S}, \quad y_{12} = -j\omega C_2 \text{ S}, \quad y_{21} = g - j\omega C_2 \text{ S}, \quad y_{22} = \frac{1}{R} + j\omega(C_2 + C_3) \text{ S}$$

$$15\text{EF-1} \quad V_1 = 36 \text{ V}$$

15.12 In addition to the Z parameters, also find the H parameters.

$$z_{11} = 400 \text{ ohms}, \quad z_{12} = 15 \text{ ohms}, \quad z_{21} = -2 \times 10^{-6} \text{ ohms}, \quad z_{22} = 50 \text{ ohms}$$

$$h_{11} = 1 \text{ k}\Omega, \quad h_{12} = 3e^{-4}, \quad h_{21} = 40, \quad h_{22} = 20 \mu \text{ S}; \quad \Delta H = 8e^{-3}$$

$$15.18 \quad \frac{V_2}{V_1} = \frac{h_{21} R_L}{h_{12} h_{21} R_L - (1 + h_{22} R_L)(R_1 + h_{11})}$$

$$15.24 \quad A = \frac{-1}{\gamma}, \quad B = \frac{-Z_2}{\gamma}, \quad C = \frac{-1}{\gamma Z_1}, \quad D = \frac{-Z_2}{\gamma Z_1}$$


15.27 Answers: No answers given. On your own.

$$15.39 \quad A = 3, \quad B = j8 \Omega, \quad C = 3 - j1 \text{ S}, \quad D = 3 + j8$$

vol 7

15.2

Find the Y-parameters for the following

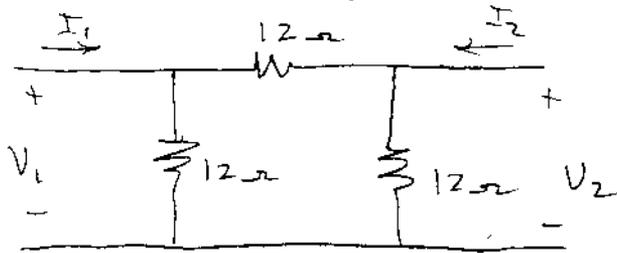


$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

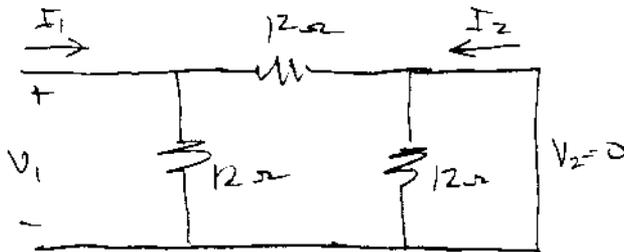

$$y_{11} = \frac{I_1}{V_1}, \text{ where } V_1 = I_1 \times 6$$

$$y_{11} = \frac{1}{6} \text{ S}$$

$$y_{21} = \frac{I_2}{V_1} \text{ where } V_1 = -12I_2$$

so

$$y_{12} = -\frac{1}{12} \text{ S}$$

continued


wkg

continue

15.2

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

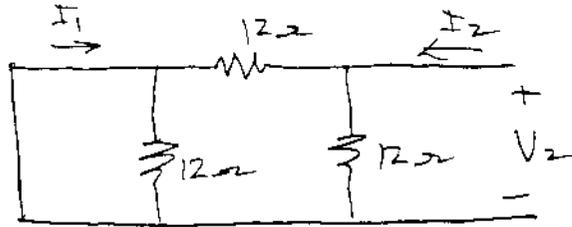

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} \quad \text{where } I_1 = \frac{-V_2}{12}$$

$$y_{12} = -\frac{1}{12} \text{ S}$$


$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} \quad \text{where } V_2 = I_2 \times 6$$

$$y_{22} = \frac{1}{6} \text{ S}$$

$$Y = \begin{bmatrix} \frac{1}{6} \text{ S} & -\frac{1}{12} \text{ S} \\ -\frac{1}{12} \text{ S} & \frac{1}{6} \text{ S} \end{bmatrix}$$


15.5

Find the Y parameters for the following.

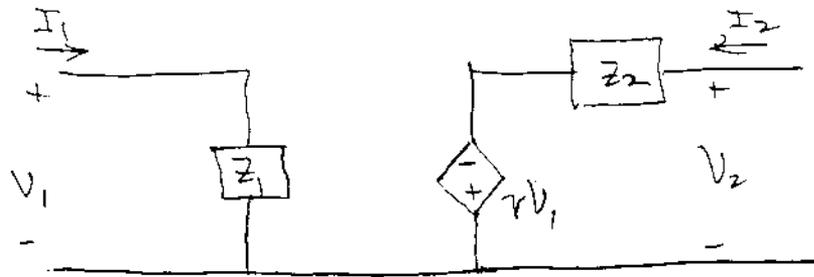

$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

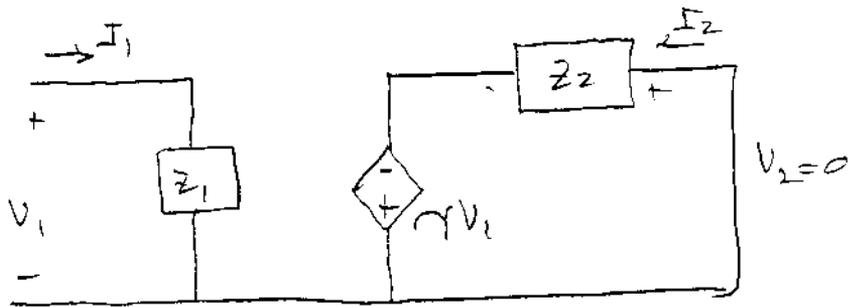

$$I_1 = \frac{V_1}{Z_1} ; \quad \frac{I_1}{V_1} = \frac{1}{Z_1}$$

$$y_{11} = \frac{1}{Z_1} \text{ S}$$

$$I_2 Z_2 - \gamma V_1 = 0$$

$$I_2 Z_2 = \gamma V_1$$

$$\frac{I_2}{V_1} = \frac{\gamma}{Z_2}$$


$$y_{21} = \frac{\gamma}{Z_2} \text{ S}$$

W8g

15.9

$$y_{21} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

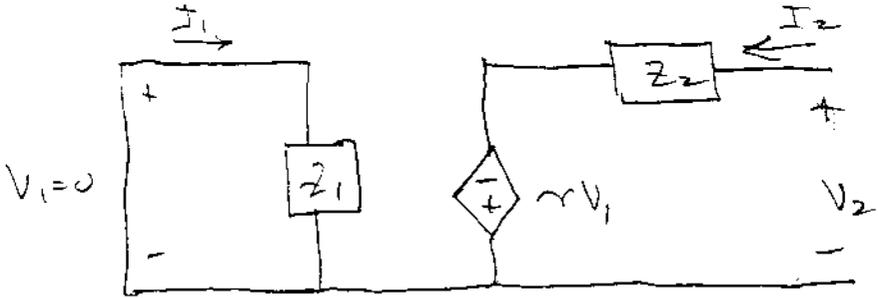

with  $V_1 = 0$ ,  $I_1 = 0$

$$\therefore \frac{I_1}{V_2} = 0$$

$$y_{21} = 0$$

$$-V_2 + I_2 Z_2 - rV_1 = 0$$

$$V_1 = 0$$

$$I_2 Z_2 = V_2$$

$$\frac{I_2}{V_2} = \frac{1}{Z_2}$$


$$y_{22} = \frac{1}{Z_2} \text{ S}$$

$$Y = \begin{bmatrix} \frac{1}{Z_1} \text{ S} & 0 \\ \frac{r}{Z_2} \text{ S} & \frac{1}{Z_2} \text{ S} \end{bmatrix}$$

w/g



15.7

Find the Y parameters for the following:

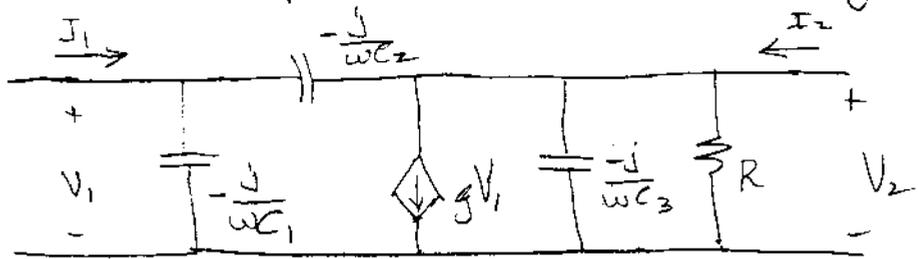

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

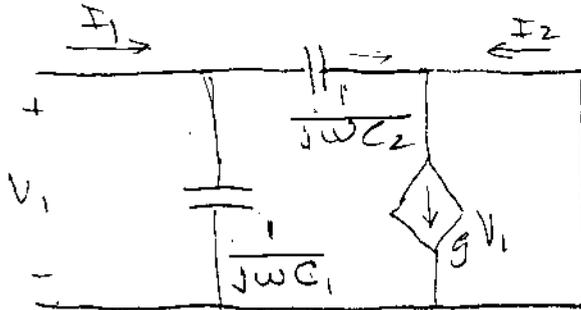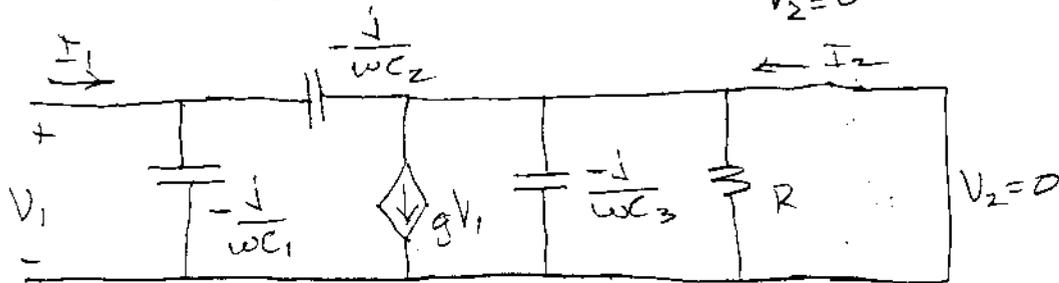

$$I_1 = V_1(j\omega C_1 + j\omega C_2) ; \frac{I_1}{V_1} = j\omega C_1 + j\omega C_2$$

$$Y_{11} = (j\omega C_1 + j\omega C_2) \text{ S}$$

$$I_2 + j\omega C_2 V_1 = g V_1$$

$$\frac{I_2}{V_2} = g - j\omega C_2$$

$$Y_{21} = (g - j\omega C_2) \text{ S}$$


wkg

continued

2

15.7

$$y_{21} = \frac{I_1}{V_2} \Big|_{V_1=0} \quad y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

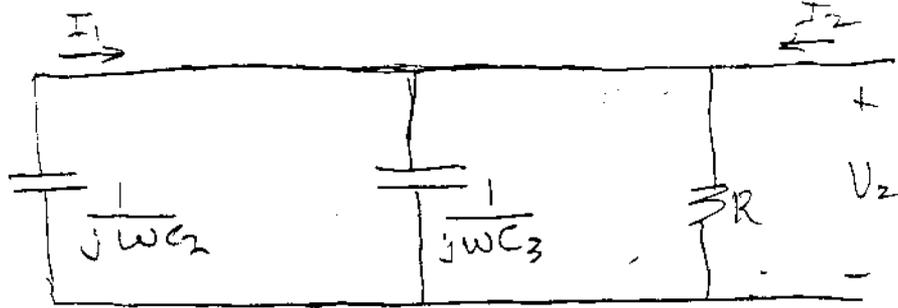

$$V_2 = -\frac{I_1}{j\omega C_2} \quad ; \quad \frac{I_1}{V_2} = -j\omega C_2$$

$$y_{21} = -j\omega C_2 \quad \text{S}$$

$$I_2 = \frac{V_2}{R} + j\omega C_3 V_2 + j\omega C_2 V_2$$

$$y_{22} = \frac{I_2}{V_2} = R + j\omega C_2 + j\omega C_3$$

$$Y = \begin{bmatrix} (j\omega C_1 + j\omega C_2)S & (-j\omega C_2)S \\ (j\omega C_2)S & (R + j\omega C_2 + j\omega C_3)S \end{bmatrix}$$


wly

ISEF-1

Given

$$Y = \begin{bmatrix} \frac{1}{14} s & -\frac{1}{21} s \\ -\frac{1}{21} s & \frac{1}{7} s \end{bmatrix}$$

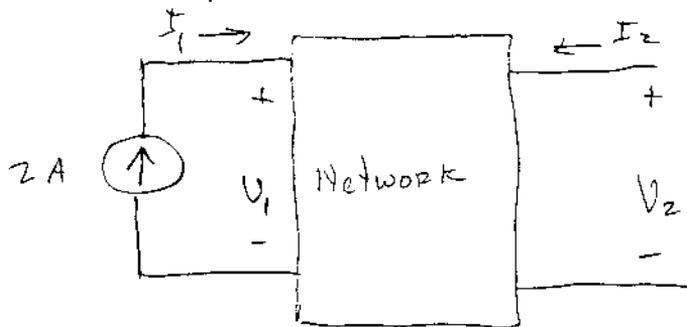A 2A current source is connected to the input terminals as shown below.



FIND  $V_1$ :

$$2 = \left(\frac{1}{14}\right) V_1 - \frac{1}{21} V_2 \quad (1)$$

$$0 = -\frac{1}{21} V_1 + \frac{1}{7} V_2 \quad (2)$$


multiply (1) by 3 and add

$$6 = \frac{3}{14} V_1 - \frac{1}{21} V_2$$

$$42 = \frac{3}{2} V_1 - \frac{V_2}{3} = \frac{9V_1 - 2V_2}{6}$$

$$V_1 = 36 \text{ V}$$

15.12

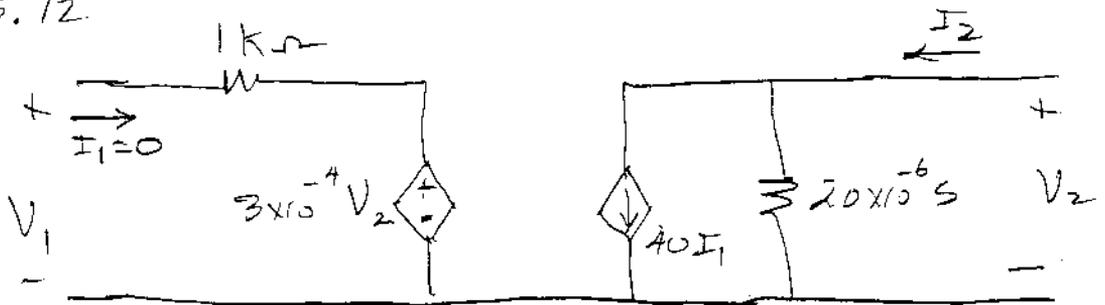

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$V_1 = 3 \times 10^{-4} V_2 \quad \text{but} \quad V_2 = \frac{I_2}{20 \times 10^{-6}}$$

$$V_1 = \frac{3 \times 10^{-4}}{20 \times 10^{-6}} I_2 = 3 \times 10^{-4} \times 50 \times 10^3 I_2$$

$$Z_{12} = 15 \, \Omega$$

with  $I_1 = 0$ ;


$$V_2 = 50 \times 10^3 \times I_2$$

$$Z_{22} = 50 \times 10^3 \, \Omega$$

slg

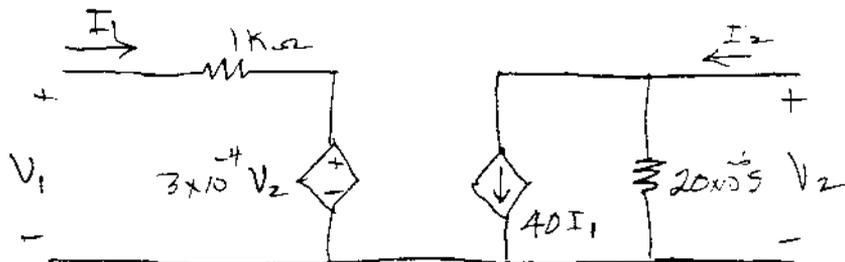15.12

Given the following circuit. Find the Z-parameters.



$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

$$z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$V_1 = 1 \times 10^3 I_1 + 3 \times 10^4 V_2 = 1 \times 10^3 I_1 + \frac{3 \times 10^4 (-40) I_1}{20 \times 10^5}$$

$$V_1 = 400 I_1 ; \quad \frac{V_1}{I_1} = z_{11}$$

$$z_{11} = 400 \Omega$$

Now,  $I_2 = 0$ , so


$$V_2 = -40 I_1 \times \frac{1}{20 \times 10^5} = -2 \times 10^6 I_1$$

$$z_{21} = -2 \times 10^6 \Omega \quad ?$$

continued

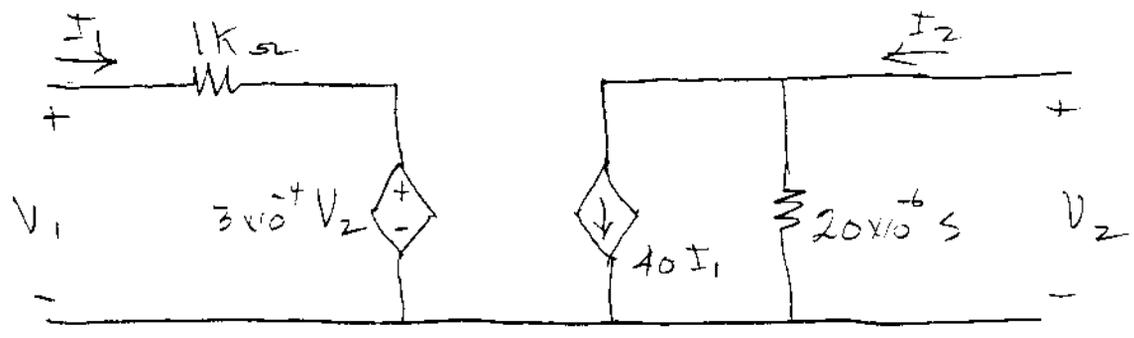15.12

Find the hybrid parameters for the following




$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

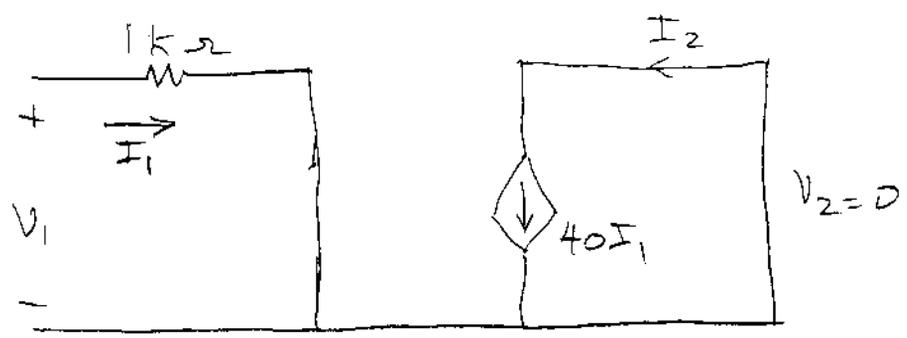

$$h_{11} = \frac{V_1}{I_1} = 1000 \Omega$$


$$I_2 = 40 I_1$$

$$h_{21} = 40$$

continued

15.12

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

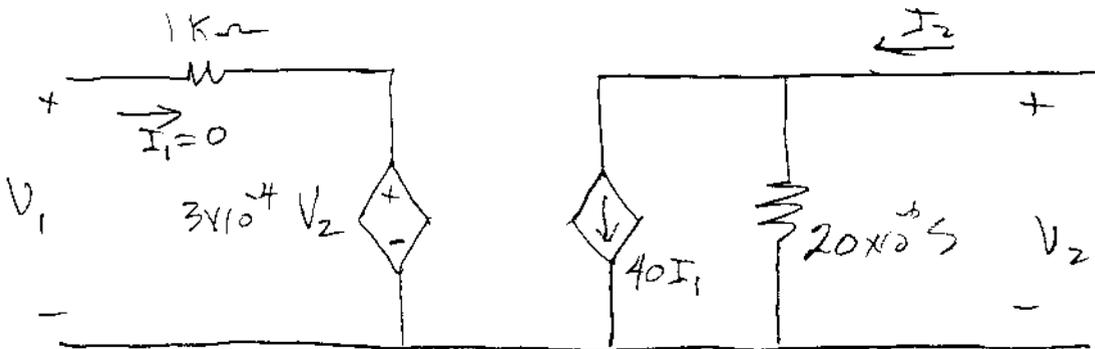

with  $I_1 = 0$

$$V_1 = 3 \times 10^{-4} V_2$$

$$h_{12} = \frac{V_1}{V_2} = 3 \times 10^{-4}$$

with  $I_1 = 0$


$$V_2 = \frac{I_2}{20 \times 10^{-6}}$$

$$\frac{I_2}{V_2} = 20 \times 10^{-6} \text{ S}$$

$$h_{22} = 20 \times 10^{-6} \text{ S}$$

$$H = \begin{bmatrix} 1\text{ k}\Omega & 3 \times 10^{-4} \\ 40 & 20 \times 10^{-6} \text{ S} \end{bmatrix}$$

5.18

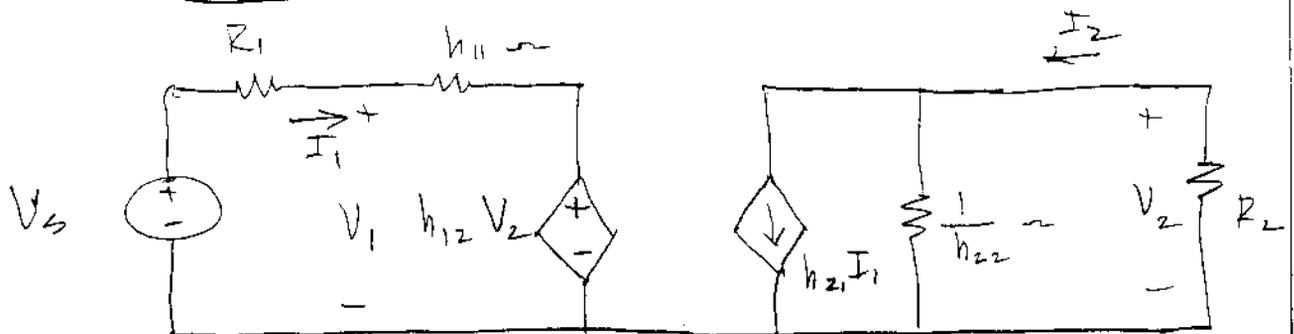GIVEN

We know

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

We know:

$$V_1 = V_s - I_1 R_1$$

$$V_2 = -R_L I_2 \rightarrow I_2 = -\frac{V_2}{R_L}$$

Determine  $V_2/V_s$ 

$$V_s - I_1 R_1 = h_{11} I_1 + h_{12} V_2$$

$$V_s = (R_1 + h_{11}) I_1 + h_{12} V_2$$

and

$$-\frac{V_2}{R_L} = h_{21} I_1 + h_{22} V_2$$

$$0 = h_{21} I_1 + \left( h_{22} + \frac{1}{R_L} \right) V_2$$

5.18 cont. used  
I.

$$\begin{bmatrix} R_1 + h_{11} & h_{12} \\ h_{21} & \frac{1 + h_{22}R_L}{R_L} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$

By Cramer's rule:

$$V_2 = \frac{\begin{vmatrix} R_1 + h_{11} & V_s \\ h_{21} & 0 \end{vmatrix}}{\begin{vmatrix} R_1 + h_{11} & h_{12} \\ h_{21} & \frac{1 + h_{22}R_L}{R_L} \end{vmatrix}}$$

$$V_2 = \frac{-h_{21}V_s}{\frac{1}{R_L}(R_1 + h_{11})(1 + h_{22}R_L) - h_{12}h_{21}}$$


$$V_2 = \frac{h_{21}R_L V_s}{h_{12}h_{21} - (1 + h_{22}R_L)(R_1 + h_{11})}$$

$$\frac{V_2}{V_s} = \frac{h_{21}R_L}{h_{12}h_{21} - (1 + h_{22}R_L)(R_1 + h_{11})}$$

wf g

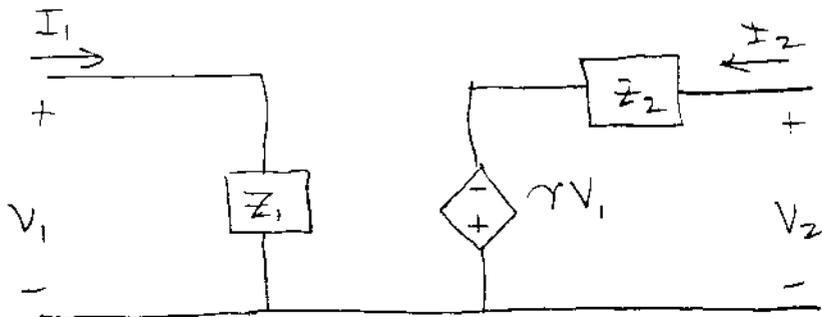15.24

Find the A, B, C, D parameters for the following



$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - D I_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

with  $I_2 = 0$

$$V_2 = -\gamma V_1 ; \quad \frac{V_1}{V_2} = -\frac{1}{\gamma}$$

$$\therefore \boxed{A = -\frac{1}{\gamma}}$$

#

with  $I_2 = 0$

$$V_2 = -\gamma V_1 = -\gamma (I_1 Z_1)$$

so

$$\frac{I_1}{V_2} = -\frac{1}{\gamma Z_1}$$

$$\boxed{C = -\frac{1}{\gamma Z_1}}$$


continued

2

15.24

$$B = \frac{V_1}{-I_2} \quad \left| \quad V_2 = 0 \right.$$

$$D = \frac{I_1}{-I_2} \quad \left| \quad V_2 = 0 \right.$$

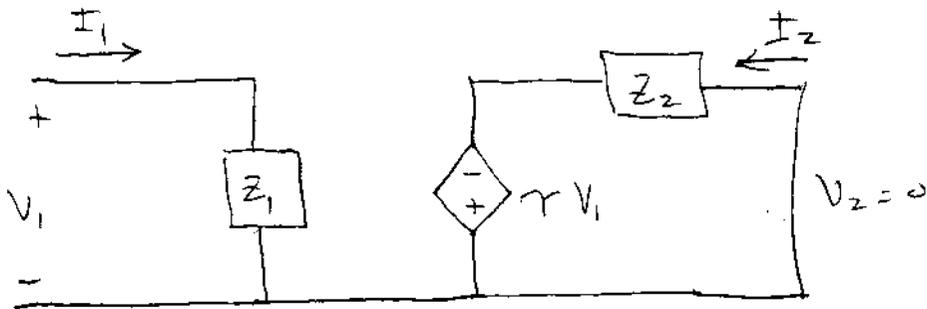

with  $V_2 = 0$

$$Z_2 I_2 - \gamma V_1 = 0$$

$$\frac{V_1}{-I_2} = -\frac{Z_2}{\gamma}$$

$$B = -\frac{Z_2}{\gamma}$$

Now

$$V_1 = \frac{Z_2}{\gamma} I_2$$

but  $V_1 = I_1 Z_1$  so

$$I_1 Z_1 = \frac{Z_2}{\gamma} I_2$$


$$D = \frac{I_1}{-I_2} = -\frac{Z_2}{Z_1 \gamma}$$

$$\begin{bmatrix} -\frac{1}{\gamma} & -\frac{Z_2}{\gamma} \\ -1 & -Z_2 \end{bmatrix}$$

w/q

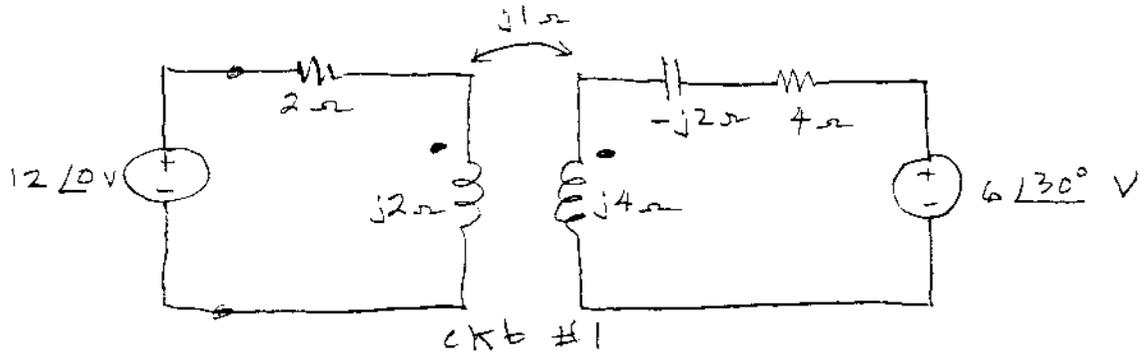15.27


Given the network below. Find the A, B, C, D parameters and then find  $I_0$  using terminal conditions.



$$A = \frac{V_1}{V_2} \Big|_{I_2=0}$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0}$$

DRAW circuit:

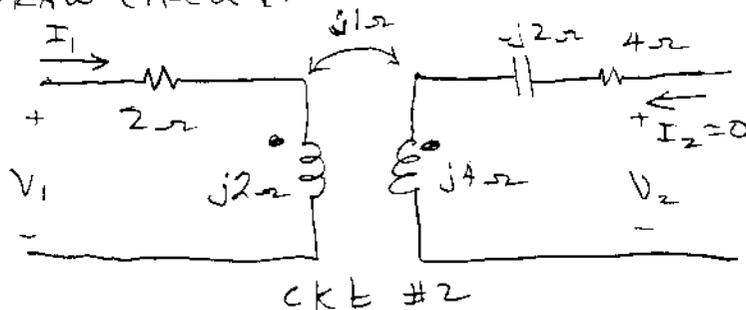

$$I_1 = \frac{V_1}{2 + j2} \quad (1)$$

and

$$V_2 = (j1) I_1 \quad (2)$$

substitute (1) into (2)

$$V_2 = \frac{(j1) V_1}{2 + j2} \quad (3)$$

$$\frac{V_1}{V_2} = \frac{2 + j2}{j} = 2 - j2$$

$$A = 2 - j2$$

15.27 cont. using from circuit 2

$$C = \frac{I_1}{V_2} \Big|_{I_2=0}$$

Now

$$V_2 = (j1) I_1 \quad (\text{induced})$$

$I_2 = 0$


$$\frac{I_1}{V_2} = \frac{1}{j} = -j \text{ S}$$

$$C = -j1 \text{ S}$$

~~≠~~

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0}$$

$$D = \frac{I_1}{-I_2} \Big|_{V_2=0}$$

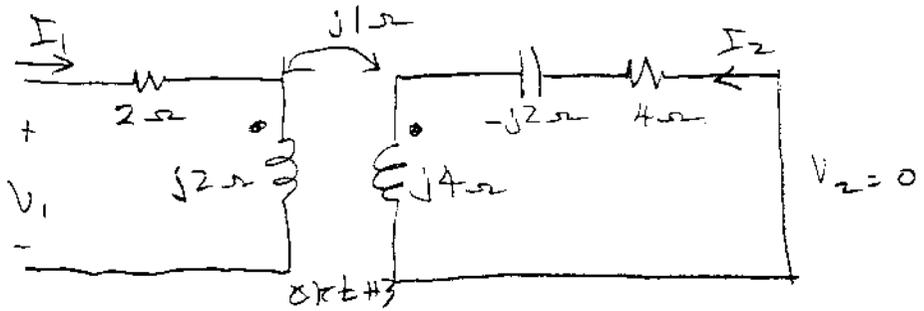

loop 1  $V_1 = (2 + j2) I_1 + (j1) I_2$  (4)

loop 2  $(4 + j2) I_2 + (j1) I_1 = 0$  (5)

or  $I_1 = -\frac{(4 + j2)}{j} I_2 = (-2 + j4) I_2$  (6)

substitute (6) into (4)

15.27

3

$$V_1 = (2+j2)(-2+j4)I_2 + (j1)I_2$$

$$V_1 = (-12+j4)I_2 + jI_2$$

$$V_1 = (-12+j5)I_2$$

$$\frac{V_1}{I_2} = -12+j5$$

$$\frac{V_1}{-I_2} = (+12-j5) \text{ S}$$

$$B = (+12-j5) \text{ S}$$

#

$$D = \frac{I_1}{-I_2}$$

From (6)

$$\frac{I_1}{I_2} = -2+j4$$

so

$$\frac{I_1}{-I_2} = (+2-j4) = D$$

$$\begin{bmatrix} 2-j2 & +12-j5 \text{ S} \\ -j1 \text{ S} & +2-j4 \end{bmatrix}$$

(7)

continued

15.27 continued

Attach  $V_1 = 12 \angle 0^\circ \text{ V}$

$V_2 = 6 \angle 30^\circ \text{ V}$

$I_0 = -I_2$

Solve for  $I_0$


$V_1 = (2 - j2)V_2 - (12 - j5)I_2$

$12 \angle 0 = (2 - j2)6 \angle 30 + (12 - j5)I_0$

$$I_0 = \frac{12 - (2 - j2)(6 \angle 30)}{(12 - j5)}$$

$I_0 = 0.48 \angle 157.6^\circ \text{ A}$   
 $I_0 = -0.48 \angle -22.4^\circ \text{ A}$

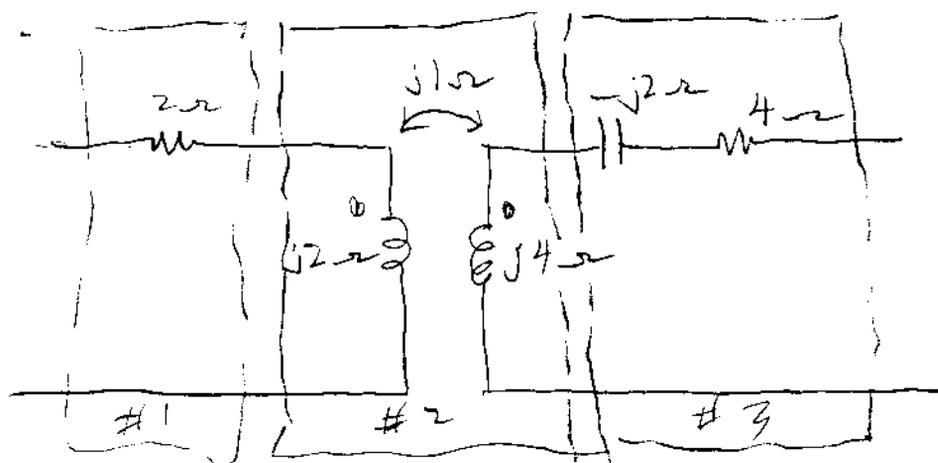As an alternate solution, break the network into 3 parts




15.27 CONT. Nue 2

5

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

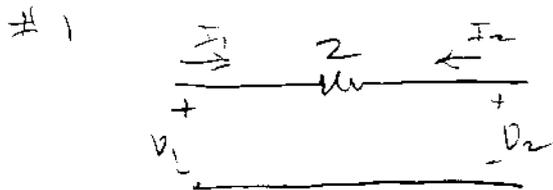


$$A_1 = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 1; \quad C_1 = \left. \frac{I_1}{V_2} \right|_{I_2=0} = 0; \quad B_1 = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = \frac{-2I_2}{-I_2} = 2$$

$$D_1 = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = \frac{-I_2}{-I_2} = 1$$
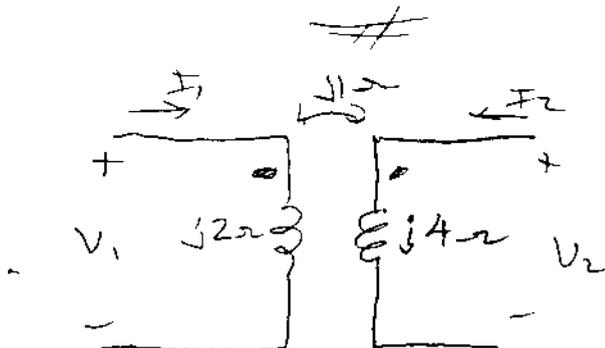
#1

$$\begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix}$$



$$A_2 = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{j2I_1}{j1I_1} = 2$$

$$C_2 = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{I_1}{j1I_1} = -j5$$

15.27 continued

$$B_2 = \frac{V_1}{-I_2} \Big|_{V_2=0}$$

$$j4I_2 + j1I_1 = 0 \quad (\text{loop 2})$$

$$I_1 = \frac{-j4I_2}{j} = -4I_2$$

$$V_1 = j2I_1 + jI_2 \quad (\text{loop 1})$$

$$V_1 = -j8I_2 + jI_2 = -j7I_2$$

$$\frac{V_1}{I_2} = -j7$$


$$\frac{V_1}{-I_2} = \boxed{j7 = B_2}$$

$$D = \frac{I_1}{-I_2} \Big|_{V_2=0} = \frac{-4I_2}{-I_2} = 4$$

#2

$$\begin{bmatrix} 2 & j7 \\ -j15 & 4 \end{bmatrix}$$

~~#~~

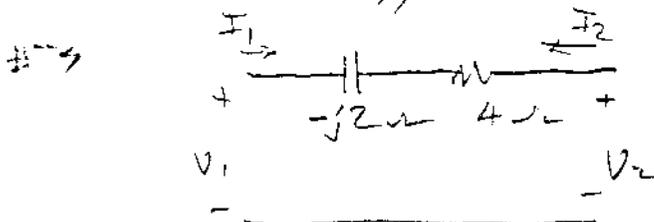

$$A_3 = \frac{V_1}{V_2} \Big|_{I_2=0} = 1, \quad C_3 = \frac{I_1}{V_2} \Big|_{I_2=0} = 0$$

$$B_{23} = \frac{V_1}{-I_2} \Big|_{V_2=0} = \frac{-(4-j2)I_2}{I_2} = 4-j2 \Omega$$

$$D_{22} = \frac{I_1}{-I_2} \Big|_{V_2=0} = \frac{-I_2}{-I_2} = 1$$

# 3

$$\begin{bmatrix} 1 & 4-j2 \Omega \\ 0 & 1 \end{bmatrix}$$

(# 1) (# 2) (# 3)

$$\begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 2 & j7 \\ -j & 4 \end{bmatrix} \begin{bmatrix} 1 & 4-j2 \\ 0 & 1 \end{bmatrix}$$

$$\begin{bmatrix} 2-j2 & 8+j7 \\ -j & 4 \end{bmatrix} \begin{bmatrix} 1 & 4-j2 \\ 0 & 1 \end{bmatrix}$$


$$\begin{bmatrix} 2-j2 & 12-j5 \\ -j & 2-j4 \end{bmatrix}$$

same as (7)

Proceed as before to solve for  $I_0$

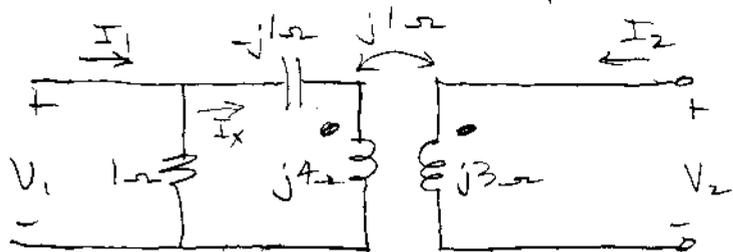15.39

Find the transmission parameters for the following.



$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

with  $V_2=0$ 

$$V_2 = (j1)I_x = j1 \left( \frac{V_1}{j3} \right) = \frac{V_1}{3}$$

so

$$\boxed{\frac{V_1}{V_2} = 3 = A}$$

#

From above diagram

$$I_x = \frac{I_1 \times 1}{1 + j3}$$

$$V_2 = j1(I_x) = \frac{(j1)I_1}{1 + j3}$$


$$\boxed{\frac{I_1}{V_2} = \frac{1 + j3}{j} = 3 - j1 = C}$$

continued

2

15.39

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0} \quad D = \frac{I_1}{-I_2} \Big|_{V_2=0}$$

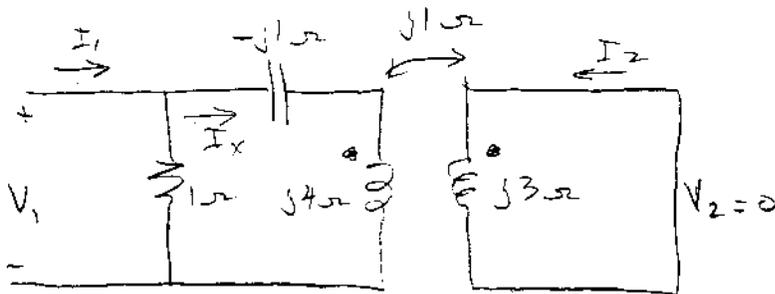

$$(j3)I_2 + (j1)I_x = 0 \quad (1)$$

but

$$V_1 = (-j1)I_x + j4I_x + jI_2 \quad (1A)$$

$$I_x = \frac{V_1 - jI_2}{j3} \quad (2)$$

(2) into (1)

$$j3I_2 + (j1) \left[ \frac{V_1 - jI_2}{j3} \right] = 0$$

or

$$j9I_2 + V_1 - jI_2 = 0$$

$$V_1 = -j8I_2$$

$$\frac{V_1}{-I_2} = j8\Omega = B$$

continued

wkg

continued

3

15.39

From (1A)

$$V_1 = jI_2 + j3I_x \quad (3)$$

and

$$V_1 = (I_1 - I_x)1 \quad (4)$$

Equate (3) to (4)

$$I_1 - I_x = jI_2 + j3I_x$$

$$I_x = \frac{I_1 - jI_2}{1 + j3} \quad (5)$$

Substitute (5) into (1)

$$j3I_2 + (j1)\left(\frac{I_1 - jI_2}{1 + j3}\right) = 0$$

$$j3(1 + j3)I_2 + jI_1 + I_2 = 0$$

$$(-8 + j3)I_2 = -jI_1$$

$$\frac{I_1}{I_2} = \frac{(-8 + j3)}{-j} = -3 - j8$$

$$\frac{I_1}{-I_2} = 3 + j8$$

$$D = \frac{I_1}{-I_2} = 3 + j8$$

$$\begin{bmatrix} 3 & j8 \Omega \\ 3 - j1 & 3 + j8 \end{bmatrix}$$