

ECE 300
Spring Semester, 2004
HW Set #5

February 26, 2004
wlg

Name **Dr.Green**

Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. **Do neat work. Underline your answers. Show how you got your equations. Be sure to show how you got your answers.** Each problem counts 5 points.

5.18		50t	V	
		-50t + 0.1	V	0 ≤ t ≤ 1 ms
		50t - 0.1	V	1 ms ≤ t ≤ 2 ms
	v(t) =	-50t + 0.2	V	2 ms ≤ t ≤ 3 ms
		50t - 0.2	V	3 ms ≤ t ≤ 4 ms
		50	mV	4 ms ≤ t ≤ 6 ms
				t ≥ 5 ms

5.32 $i(t) = 500t^2$ A $0 \leq t \leq 1$ ms

$i(t) = 2t - 500t^2 - 10^{-3}$ A $1\text{ms} \leq t \leq 2$ ms

$i(t) = 1$ ma $t > 2$ ms

5.45 $V_1 = 4$ V, $V_2 = 8$ V

5.58 $L = 4$ mH

5FE-3 $W = 3.84$ mJ

6.4 $i_o(t) = 2.67e^{-t/0.6}$ mA $v_c(t) = 5.33e^{-t/0.6}$ V $t > 0$

6.7 $v_o(t) = (48/11)(1 - e^{-11t/6})$ V $t > 0$; $v_o(t) = 0$ $t < 0$

6.23 $i_o(t) = -1.2$ A $t < 0$::::: $i_o(t) = 2 - 3.2e^{-3t}$ A $t > 0$


6.29 $i_o(t) = 2 + 0.5e^{-3.75t}$ mA

6.35 $v_o(t) = -6e^{-4t}$ V $t > 0$

w/q

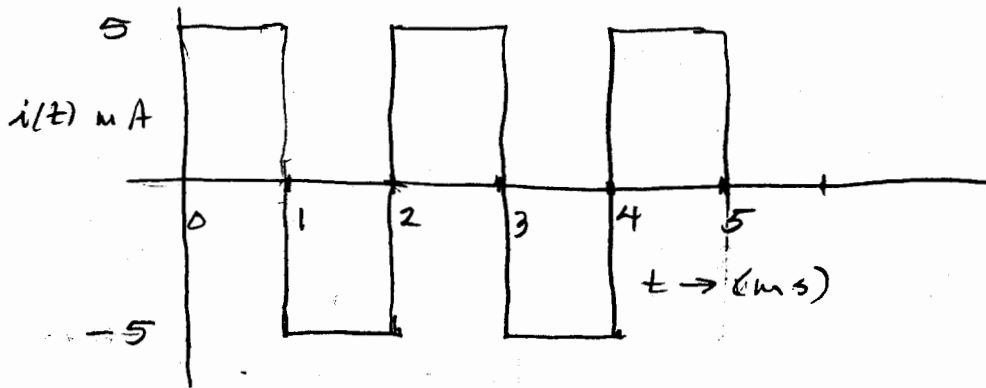5.18

Waveform for current in a $100\mu\text{F}$ initially uncharged capacitor is shown below. Determine the waveform for the capacitor voltage.



$$\boxed{0 \leq t \leq 1 \text{ ms}}$$

$$i(t) = C \frac{dV}{dt}$$

$$\int_{\tau=0}^{\tau=t} dV(\tau) = \frac{1}{C} \int_{\tau=0}^{\tau=t} i(\tau) d\tau \quad (1)$$

$$v(t) - v(0) = \frac{5 \times 10^{-3}}{0.1 \times 10^{-3}} \int_{\tau=0}^{\tau=t} d\tau = 50\tau \Big|_{\tau=0}^{\tau=t} = 50t$$

but $v(0) = 0 \Rightarrow$

$$\boxed{V(t) = 50t \quad 0 \leq t \leq 1 \text{ ms}} \quad (2)$$

$$\text{Now } v(1 \text{ ms}) = 50 \times 1 \times 10^{-3} = 0.05 \text{ V} \quad (3)$$

$$\boxed{1 \text{ ms} \leq t \leq 2 \text{ ms}}$$

$$\int_{\tau=1 \text{ ms}}^{\tau=t} dV(\tau) = 50 \int_{\tau=1 \text{ ms}}^{\tau=t} d\tau \quad (4)$$

3.18 cont.

From (4)

$$V(t) - V(1\text{ms}) = -50 \tau \Big|_{\tau=1\text{ms}}^{\tau=t} = -50(t - 1\text{ms})$$

$$V(t) - 0.05 = -50t + 0.05$$

$$\boxed{V(t) = -50t + 0.1} \quad 1\text{ms} \leq t \leq 2\text{ms} \quad (5)$$

Note:

$$V(2\text{ms}) = -50 \times 2 \times 10^{-3} + 0.1 = -0.1 + 0.1 = 0$$

$$\boxed{V(2\text{ms}) = 0\text{V}} \quad \text{use for next eq.}$$

$$2\text{ms} \leq t \leq 3\text{ms}$$

$$\int_{\tau=2\text{ms}}^{\tau=t} dV(\tau) = +50 \int_{\tau=2\text{ms}}^{\tau=t} d\tau = 50\tau \Big|_{\tau=2\text{ms}}^{\tau=t} = 50(t - 2\text{ms})$$

$$V(t) - V(2\text{ms}) = 50(t - 2\text{ms})$$

$$V(t) = 50t - 0.1 + 0$$

$$\boxed{V(t) = 50t - 0.1} \quad 2\text{ms} \leq t \leq 3\text{ms} \quad (6)$$

Note:

$$V(3\text{ms}) = 50 \times 3 \times 10^{-3} - 0.1 = 0.15 - 0.1$$

$$V(3\text{ms}) = 0.05\text{V} \quad \text{use next}$$

$$\boxed{3\text{ms} \leq t \leq 4\text{ms}}$$

$$\int_{\tau=3\text{ms}}^{\tau=t} dV(\tau) = -50 \int_{\tau=3\text{ms}}^{\tau=t} d\tau$$

5.18 continued

From previous equation:

$$v(t) - v(3\text{ms}) = -50 \tau \Big|_{\tau=3\text{ms}}^{\tau=t} = -50(t - 3\text{ms})$$

$$v(t) - 0.05 = -50t + 0.15$$

$$\boxed{v(t) = -50t + 0.2} \quad 3\text{ms} \leq t \leq 4\text{ms} \quad (7)$$

$$v(4\text{ms}) = -50 \times 4\text{ms} + 0.2 = -0.2 + 0.2 = 0$$

$$\boxed{v(4\text{ms}) = 0} \quad \text{use next}$$

$$4\text{ms} \leq t \leq 5\text{ms}$$

$$\int_{\tau=4\text{ms}}^{\tau=t} dv(\tau) = 50 \int_{\tau=4\text{ms}}^{\tau=t} d\tau$$

$$v(t) - v(4\text{ms}) = 50 \tau \Big|_{\tau=4\text{ms}}^{\tau=t} = 50(t - 4\text{ms})$$

$$v(t) = 50t - 0.2 + 0$$



$$\boxed{v(t) = 50t - 0.2} \quad 4\text{ms} \leq t \leq 5\text{ms} \quad (8)$$

$$v(5\text{ms}) = 50 \times 5\text{ms} - 0.2 = 0.25 - 0.2 = 0.05\text{V}$$

$$\boxed{v(5\text{ms}) = 50\text{mV}} \quad 5\text{ms} \leq t \quad (9)$$

Summary from (2), (5), (6), (7), (8) and (9)

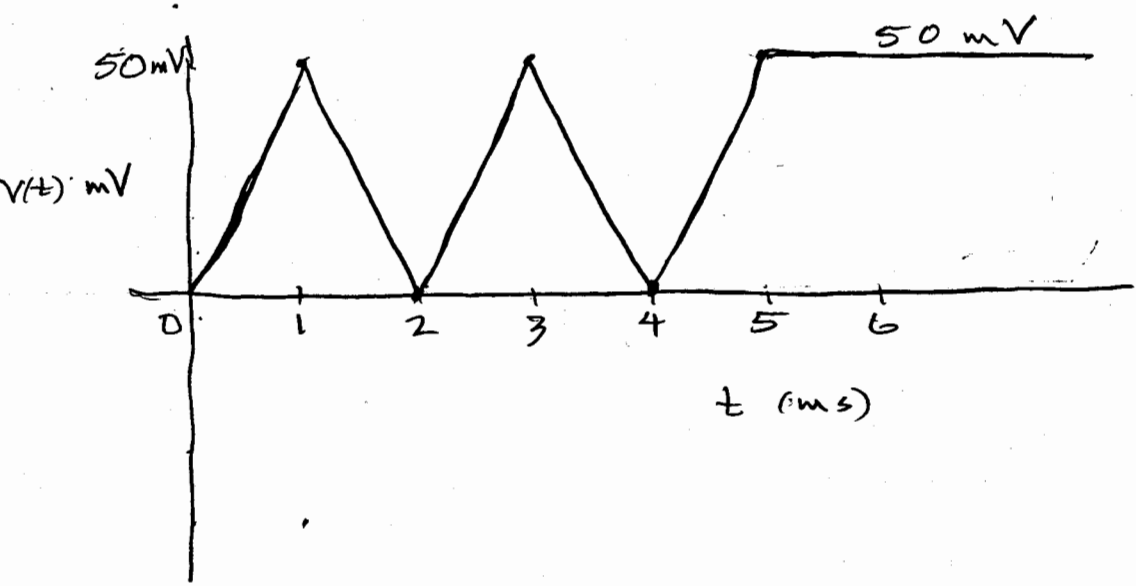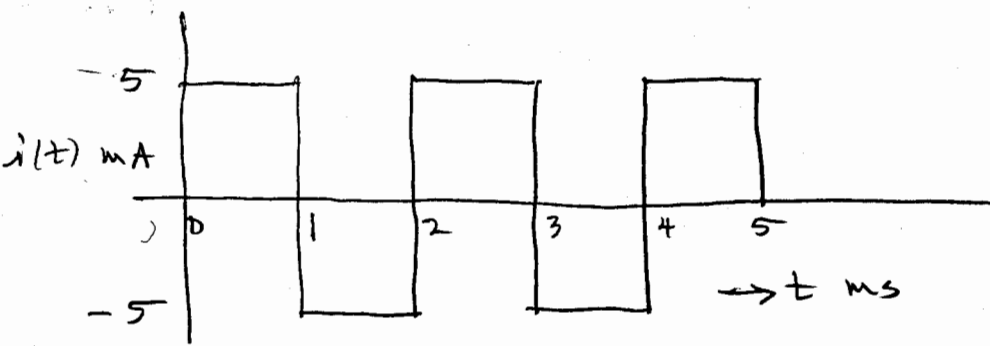
$$v(t) = \begin{cases} 50t & \text{V} & 0 \text{ms} \leq t \leq 1 \text{ms} \\ -50t + 0.1 & \text{V} & 1 \text{ms} \leq t \leq 2 \text{ms} \\ 50t - 0.1 & \text{V} & 2 \text{ms} \leq t \leq 3 \text{ms} \\ -50t + 0.2 & \text{V} & 3 \text{ms} \leq t \leq 4 \text{ms} \\ 50t - 0.2 & \text{V} & 4 \text{ms} \leq t \leq 5 \text{ms} \\ 50 \text{ mV} & & t \geq 5 \text{ms} \end{cases}$$



wlg

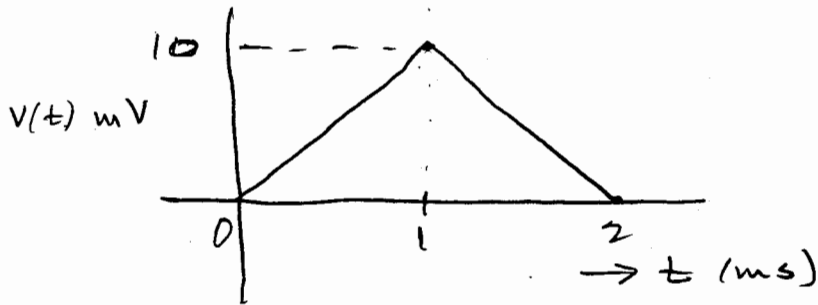5.32

The voltage across a 10 mH inductor is shown below. Determine the waveform for the inductor current. $v(t) = 0, t < 0$



For $0 \leq t \leq 1$ msec

$$v(t) = L \frac{di(t)}{dt}$$

$$\int_{\tau=0}^{\tau=t} di(\tau) = \frac{1}{L} \int_{\tau=0}^{\tau=t} v(\tau) d\tau \quad L = 10 \text{ mH}$$

over this range $v(\tau) = 10\tau$

so, integrating we have

$$i(t) - i(0) = \frac{10}{0.01} \int_{\tau=0}^{\tau=t} \tau d\tau = \frac{1000}{2} \tau^2 \Big|_{\tau=0}^{\tau=t}$$

$$i(0) = 0$$

$$i(t) = 500t^2 \quad 0 \leq t \leq 1 \text{ ms} \quad (1)$$

Note from above

$$i(1 \text{ ms}) = 500 (1 \times 10^{-3})^2 = 500 \times 1 \times 10^{-6}$$

$$i(1 \text{ msec}) = 0.5 \text{ mA} \quad (2)$$

use in next part.

wkg

5.32 continued

$$1 \text{ ms} \leq t \leq 2 \text{ ms}$$

$$\int_{\tau=1 \text{ ms}}^{\tau=t} \phi i(\tau) = \frac{1}{L} \int_{\tau=1 \text{ ms}}^{\tau=t} v(\tau) d\tau \quad (3)$$

$$L = 0.01$$

$$v(\tau) = -10(\tau - 2 \text{ ms}) \quad (4)$$

substitute (4) into 3 and integrate

$$i(t) - i(1 \text{ ms}) = -1000 \int_{\tau=1 \text{ ms}}^{\tau=t} (\tau - 2 \text{ ms}) d\tau$$

$$= -1000 \left[\frac{\tau^2}{2} - 2 \text{ ms} \tau \right] \Big|_{\tau=1 \text{ ms}}^{\tau=t}$$

$$= -500(t^2 + 1 \times 10^{-6}) + 2\tau \Big|_{1 \text{ ms}}^{\tau=t}$$

remember
 $i(1 \text{ ms}) = 0.5 \times 10^{-3} \text{ A}$

$$i(t) - i(1 \text{ ms}) = -500t^2 + 0.5 \times 10^{-3} + 2t - 2 \times 10^{-3}$$

$$i(t) = -500t^2 + 2t + 0.5 \times 10^{-3} - 2 \times 10^{-3} + 0.5 \times 10^{-3}$$

$$i(t) = (-500t^2 + 2t - 1 \times 10^{-3}) \text{ A} \quad 1 \text{ ms} \leq t < 2 \text{ ms}$$


$$i(2 \text{ ms}) = -500 \times (2 \times 10^{-3})^2 + 2 \times 2 \times 10^{-3} - 1 \times 10^{-3}$$

$$i(2 \text{ ms}) = -2 \times 10^{-3} + 4 \times 10^{-3} - 1 \times 10^{-3}$$

$$i(2 \text{ ms}) = 1 \times 10^{-3} \text{ A} \quad 2 \text{ ms} \leq t \leq \infty$$

wlg
5.45

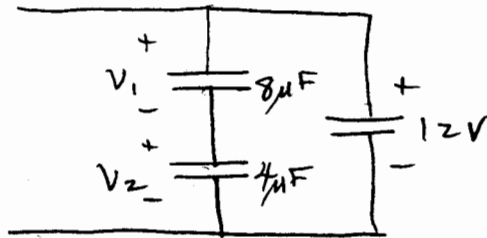The capacitors shown below have been connected for some time and have reached their present values. Find V_1 and V_2 .



C_q for the $8\mu\text{F}$ & $4\mu\text{F}$ in series is

$$\frac{4 \times 8}{4+8} = \frac{32}{12} = \frac{8}{3} \mu\text{F}$$

$$q_{8\mu\text{F}} = C_q \cdot 12 = \frac{8}{3} \mu\text{F} \times 12 = 32 \mu\text{C}$$

$$q_{8\mu\text{F}} = 32 \mu\text{C} = q_{4\mu\text{F}}$$

$$q_{8\mu\text{F}} = (32 \mu\text{C}) = C_8 V_8 = 8 \mu\text{F} V_8$$

$$V_{8\mu\text{F}} = \frac{32}{8} = 4 \text{V}$$

$$V_{8\mu\text{F}} = 4 \text{V} = V_1$$

$$V_{4\mu\text{F}} = 12 - V_{8\mu\text{F}} = 12 - 4 = 8 \text{V}$$



$$V_{4\mu\text{F}} = 8 \text{V} = V_2$$

wkg
5.58

FIND L in the ckt below so that

$$L_T = 2 \text{ mH}$$

Redrawing the ckt gives

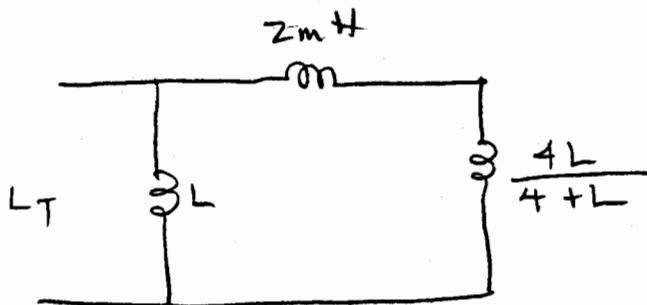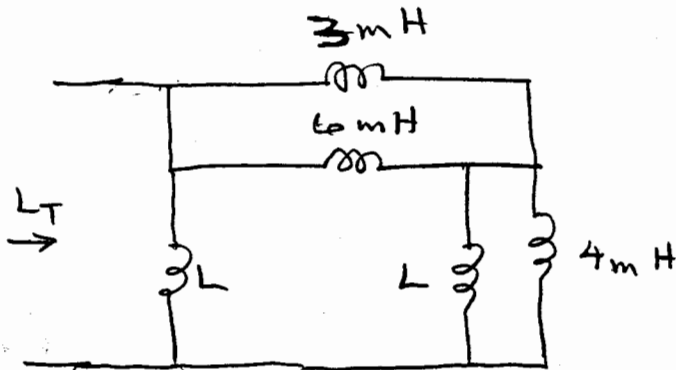

Assuming $L \rightarrow \text{mH's}$

$$L_T = L \parallel \left(2 \text{ mH} + \frac{4L(\text{mH})^2}{(4+L)\text{mH}} \right)$$

$$= L \parallel \left(\frac{8 + 2L + 4L}{4+L} \right) = L \parallel \frac{8+6L}{4+L}$$

$$= \frac{L \times \left(\frac{8+6L}{4+L} \right)}{L + \left(\frac{8+6L}{4+L} \right)} = \frac{L(8+6L)}{4L + L^2 + 8 + 6L}$$

$$2 \text{ mH} = \frac{6L^2 + 8L}{L^2 + 10L + 8}$$

$$2L^2 + 20L + 16 = 6L^2 + 8L$$

$$4L^2 - 12L - 16 = 0 \Rightarrow L^2 - 3L - 4$$


$$L_T = (L-4)(L+1) = 0$$

$$L_T = 4 \text{ mH}$$

W2g

5FE-3

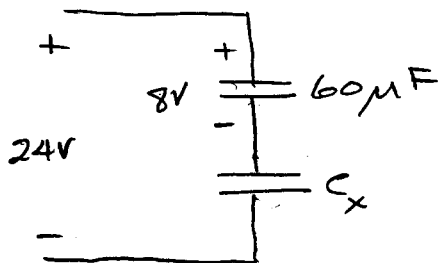Two capacitors below have been connected for a long time and have reached their present values. Determine C_x and the energy stored in C_x .



Upper capacitor:

$$q = CV = 60 \times 10^{-6} \times 8 = 0.48 \times 10^{-3} \text{ C}$$

Lower capacitor:

Voltage on the capacitor

$$V_{C_x} = 24 - 8 = 16 \text{ V}$$

$$q_{C_x} = q_{60\mu\text{F}} = 0.48 \times 10^{-3} \text{ C}$$


$$C_x = \frac{q_{C_x}}{V_{C_x}} = \frac{0.48 \times 10^{-3}}{16} = 0.03 \times 10^{-3} \text{ F}$$

$$C_x = 30 \mu\text{F}$$


$$W = \frac{1}{2} CV^2 = \frac{1}{2} \times 30 \times 10^{-6} \times (16)^2$$

$$W = 3.84 \text{ mJ}$$

6.4

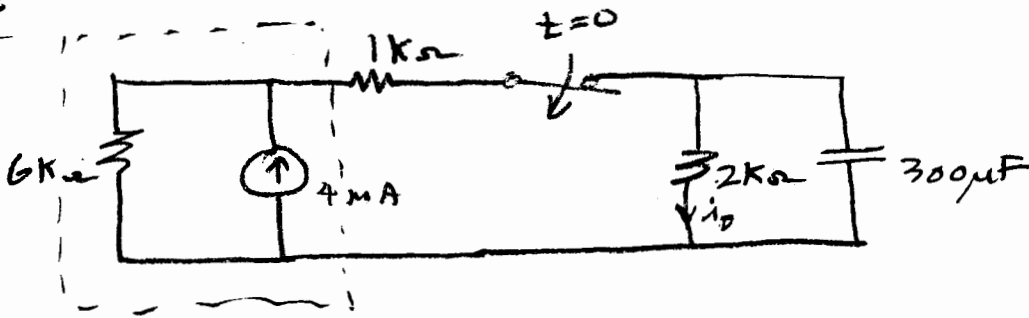


change current source to voltage source

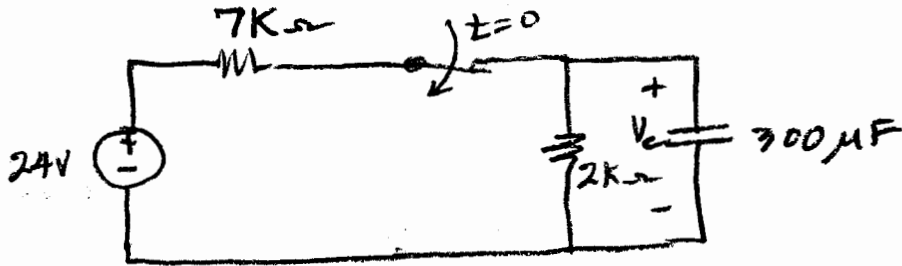

$$V_c(0^-) = \frac{24 \times 2K}{(2 + 7)K} = 5.33V$$

so $V_c(0^+) = V_c(0^-) = 5.33V$

After the switch opens

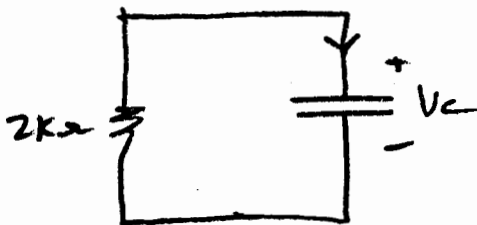

$$V_c(t) = V_c(0) e^{-\frac{t}{\tau}}$$


$$\tau = RC = (2K)(1.3 \times 10^{-3})$$

$$\tau = 0.6 = 6/10 = 3/5$$

$$V_c(t) = 5.33 e^{-\frac{5t}{3}} V$$

$$i_o(t) = \frac{V_c(t)}{2K} = 2.67 e^{-\frac{5t}{3}} mA$$

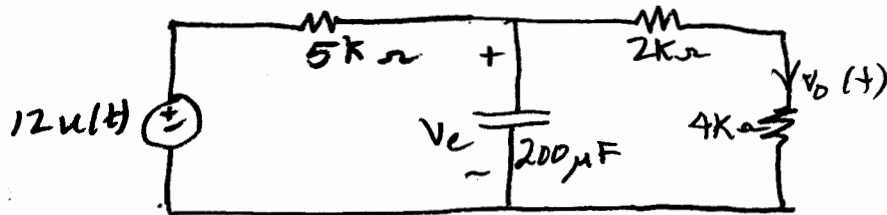
6.7 Use the d.e. approach to find $V_o(t)$ for the following. Prior to $t=0$, the circuit is set so that all IC's are zero. After the switch is closed, the circuit is as follows



If you find $V_c(t)$ then

$$V_o(t) = \frac{V_c(t) \times 4K}{4K + 2K} \quad (1)$$


REDRAW

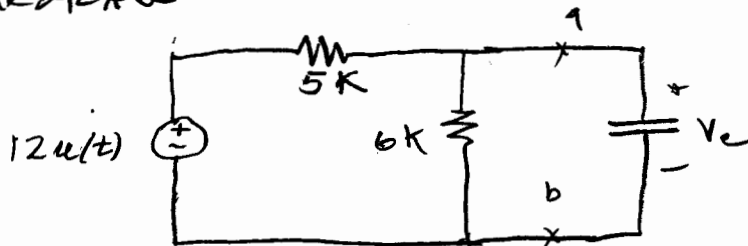

The Thevenin to the left of a-b

$$V_{TH} = \frac{12 \times 6}{11} = \frac{72}{11} = 6.55$$
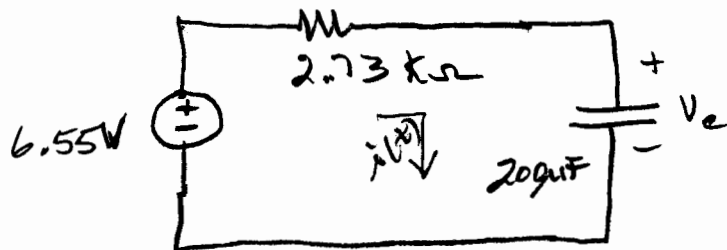
$$R_{TH} = 6K \parallel 5K = 2.73K\Omega$$



wlg

6.7 cont.

$$\tau = R_{eq} C = 2.73 \times 10^3 \times 0.2 \times 10^{-3}$$

$$\tau = 0.546$$

The d.e. for the ckt is

$$Ri(t) + V_c(t) = 6.55$$

$$RC \frac{dV_c}{dt} + V_c(t) = 6.55$$

$$\frac{dV_c}{dt} + \frac{V_c}{0.546} = \frac{6.55}{0.546}$$

$$\frac{dV_c}{dt} + 1.83 V_c(t) = 12 \quad (2)$$

$$V_c(t) = V_f(t) + V_n(t)$$

$$V_f(t) = K$$

Assume this; substitute back into (2) gives

$$(K) 1.83 = 12$$

$$K = 6.56$$

$$V_c(t) = 6.56 + K_2 e^{-1.83t}$$

$$\text{At } t = 0^+ \quad V_c(0^+) = V_c(0^-) = 0$$

$$\therefore K_2 = -6.56$$


$$V_c(t) = 6.56 (1 - e^{-1.83t}) \quad \forall u(t)$$

using (1)

$$V_o(t) = 4.37 (1 - e^{-1.83t}) \quad \forall u(t)$$

wly

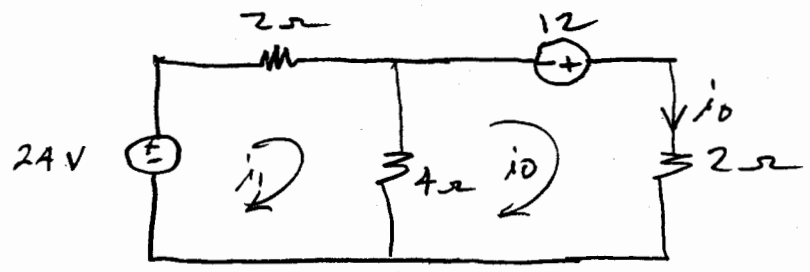6.23 WORK using d.e. approach. Find $i_o(t)$ for $t > 0$ and just prior to $t = 0$.
 $t < 0$ circuit is as below (coil shorted)




$$\begin{bmatrix} 6 & -4 \\ -4 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_o \end{bmatrix} = \begin{bmatrix} 24 \\ 12 \end{bmatrix}$$

$$i_1(0^-) = 9.6 \text{ A}$$

$$i_o(0^-) = 8.4 \text{ A}$$

$$\therefore i_L(0^-) = i_1(0^-) - i_o(0^-) = 1.2 \quad (1)$$

FOR $t > 0$

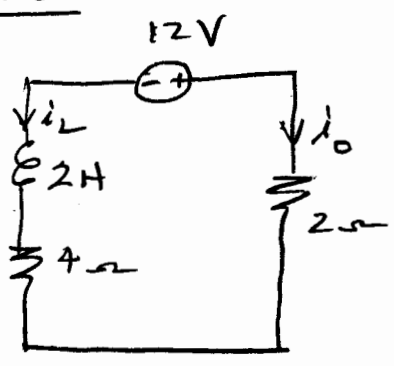

$$i_L(t) = -i_o(t)$$

$$2 \frac{di_o}{dt} + 6 i_o(t) = 12$$

$$\frac{di_o}{dt} + 3 i_o(t) = 6 \quad (2)$$

$\lambda_{op} = K$ substitute into (2)

$$\text{get } K = 2$$

w/9
6.23 cont.

$$i_0(t) = 2 + K_2 e^{-\frac{t}{\tau}}$$

$$R_{eq} = 6\Omega, \quad L = 2H$$

$$\tau = \frac{L}{R} = \frac{2}{6} = \frac{1}{3} \text{ sec}$$

$$i_0(t) = 2 + K_2 e^{-3t}$$

$i_0(0^+) = -i_2(0^-)$; current through L cannot change inst. so current through 2Ω is the negative of $i_2(0^-)$. From (1)

$$-1.2 = 2 + K_2 e^{-3t} \Big|_{t=0}$$


$$-1.2 = 2 + K_2$$

$$K_2 = -3.2$$

$$i_0(t) = 2 - 3.2 e^{-3t} \text{ A} \quad t \geq 0$$

wlg
6.29

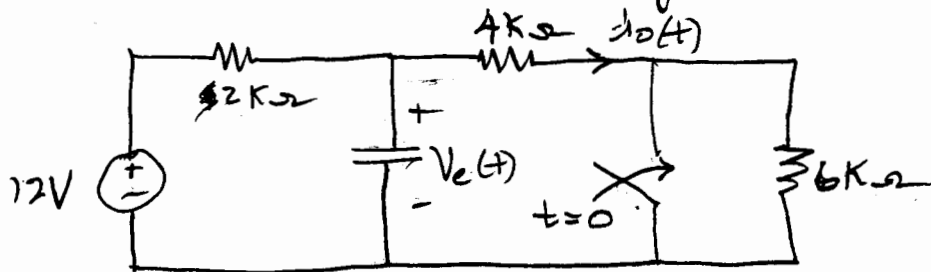
Use step-by-step method to find $i_o(t)$ for $t > 0$ in the following networks



Before the switch is closed, $v_c(t)$ can be found by using voltage division:

$$v_c(0^-) = \frac{12V \times 10K}{10K + 2K} = 10V$$

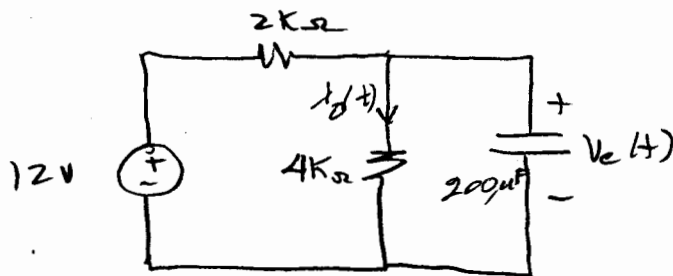After the switch is closed the ckt becomes



FIND $v_c(t)$, divide by $4k\Omega$ to get $i_o(t)$.

$$R_{eq} = 4K \parallel 2K = \frac{4 \times 2}{16} = 1.33K$$

$$\tau = R_{eq} \times C = (1.33 \times 10^3)(0.2 \times 10^{-3}) = 0.267$$

$$v_c(\infty) = \frac{12 \times 4K}{16K} = 3V$$

$$v_c(0^+) = v_c(0^-) = 10V$$

$$i_o(t) = K_1 + K_2 e^{-3.75t}$$

$$i_o(\infty) = \underline{K_1} = \frac{12}{6K} = 2mA$$

$$i_o(0^+) = \frac{v_c(0^+)}{4K} = \frac{10}{4} mA = 2.5mA$$

$$2.5mA = K_1 + K_2$$

wlog

6.29 cont

$$K_2 = 2.5 \text{ mA} - K_1 = 2.5 \text{ mA} - 2 \text{ mA}$$


$$K_2 = 0.5 \text{ mA}$$

$$i_0(t) = \left[2 + 0.5 e^{-3.75t} \right] \text{ mA } u(t)$$

wlg


6.35 Use step-by-step to find $V_0(t)$ for $t > 0$

For $t < 0$ circuit is

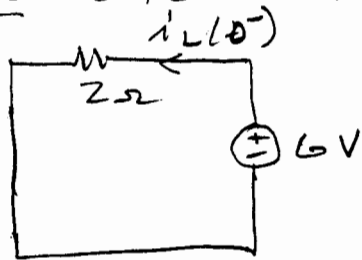

$$i_L(0^-) = \frac{6}{2} = 3A$$

For $t > 0$

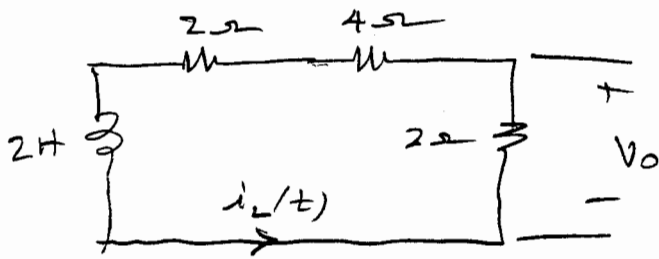

$$R_{eq} = 2 + 4 + 2 = 8\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{2}{8} = 0.25 \text{ sec}$$

$$V_0 = K_1 + K_2 e^{-4t}$$

$$V_0(\infty) = 0 \quad \therefore K_1 = 0$$

$$V_0(0^+) = -i_L(0^+) \cdot 2 = -3 \times 2 = -6V$$

$$\therefore V_0(0) = K_2 = -6$$

$$V_0(t) = -6 e^{-4t} u(t)$$