

ECE 301
Fall Semester, 2002
HW Set #4

Due: September 26, 2002
wlg (wlg@utk.edu)

Name _____
Print (last, first)

All the problems on this set are to be submitted for grading. Use engineering paper. Work only on one side of the paper. Use this sheet as your cover sheet, placed on top of your work and stapled in the top left-hand corner. Number the problems at the top of the page, in the center of the sheet. Do neat work. **Underline your answers. Show how you got your equations.** Each problem counts 10 points. **Be sure to show how you got your answers.**

4.11 $W_{1F} = 72 \text{ J}$, $W_{1H} = 50 \text{ J}$, $W_{2H} = 4 \text{ J}$, $W_{2F} = 576 \text{ J}$

4.14 $i_L(15\mu\text{s}) = -13.67 \text{ mA}$

4.25 $V_{\text{avg}} = -4 \text{ V}$, $V_{\text{rms}} = 6.4 \text{ V}$

4.26 $i_{\text{rms}} = 6.12 \text{ A}$, $P_{1\Omega} = 37.5 \text{ W}$

4.28 $i_{\text{rms}} = 1.15 \text{ A}$