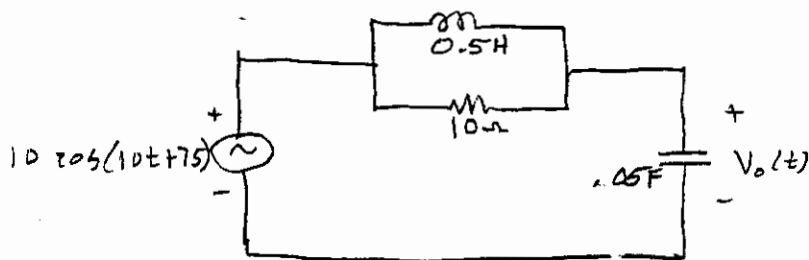


H.W. # 4

(1) Determine  $V_o(t)$  in the following ckt.




change to a phasor circuit.  $\omega = 10 \text{ rad/sec}$

$$.5 \text{ H} \rightarrow j10 \times .5 = j5 \Omega$$

$$.05 \text{ F} \rightarrow \frac{-j}{10 \times .05} = -j2 \Omega$$

Redraw the circuit:

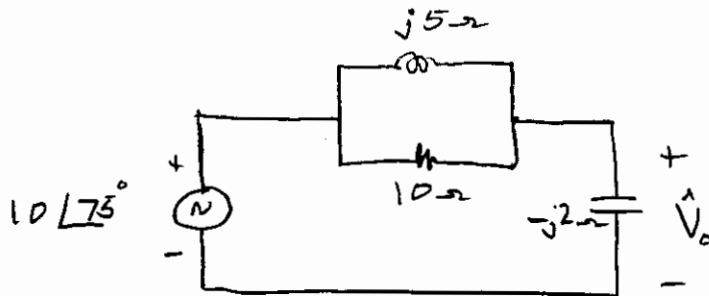


Apply voltage division:

$$\hat{V}_o = \frac{(10 \angle 75^\circ)(2 \angle -90^\circ)}{\frac{10 \times (5 \angle 90^\circ)}{10 + j5} - j2} = \frac{20 \angle -15^\circ}{2 + j2}$$

$$\hat{V}_o = 7.07 \angle -60^\circ$$

$$\therefore V_o(t) = 7.07 \cos(10t - 60^\circ) \text{ V}$$

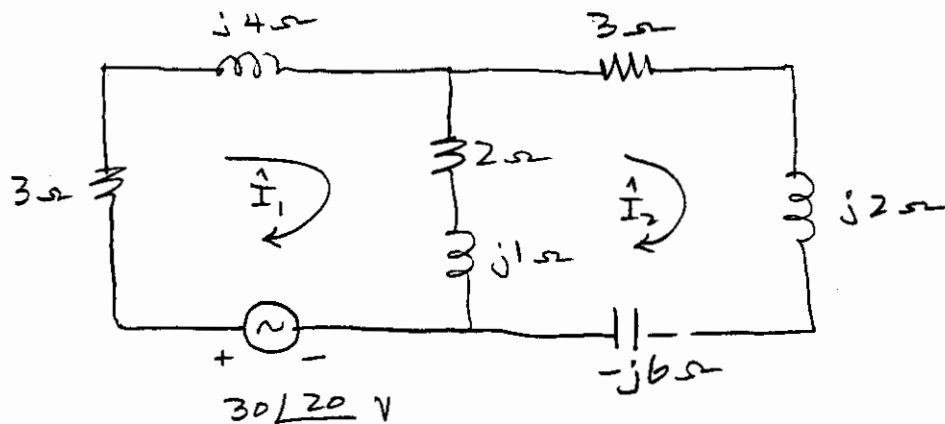(2) Use mesh analysis to find  $\hat{I}_1$  and  $\hat{I}_2$  in the circuit below.



$$3\hat{I}_1 + j4\hat{I}_1 + 2(\hat{I}_1 - \hat{I}_2) + j1(\hat{I}_1 - \hat{I}_2) = 30\angle 20^\circ$$

$$(5 + j5)\hat{I}_1 - (2 + j1)\hat{I}_2 = 30\angle 20^\circ$$


$$(2 + j)(\hat{I}_2 - \hat{I}_1) + (3 - j4)\hat{I}_2 = 0$$

$$-(2 + j)\hat{I}_1 + (5 - j3)\hat{I}_2 = 0$$

$$\begin{bmatrix} 5 + j5 & -2 - j1 \\ -2 - j1 & 5 - j3 \end{bmatrix} \begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \begin{bmatrix} 30\angle 20^\circ \\ 0 \end{bmatrix}$$

$$\hat{I}_1 = 4.67 \angle -20.2^\circ \text{ A} \quad \hat{I}_2 = 1.79 \angle 37.4^\circ \text{ A}$$

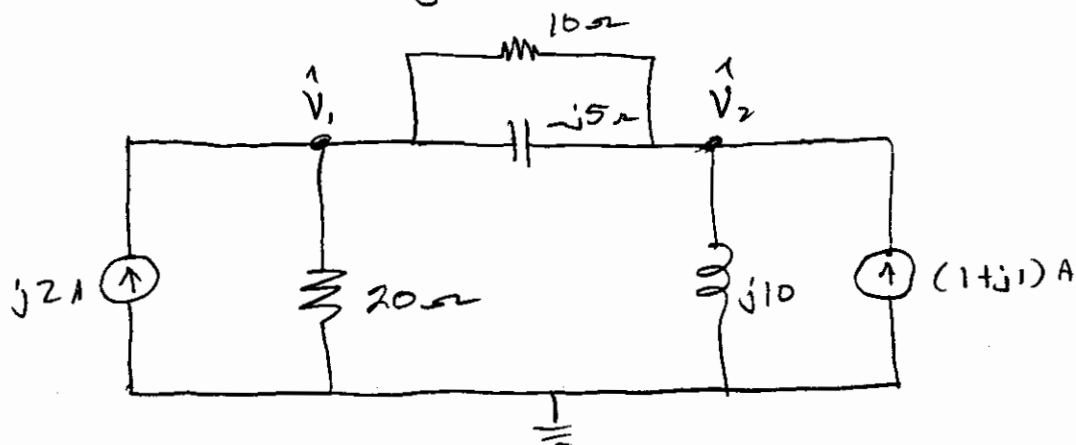(3) Use Nodal analysis to find  $\hat{V}_1$  and  $\hat{V}_2$ .



$$10 \parallel (-j5) = \frac{(50 \angle -90^\circ)}{(10 - j5)} = 2 - j4 = 4.47 \angle -63.4^\circ$$

At  $\hat{V}_1$

$$\frac{\hat{V}_1}{20} + \frac{(\hat{V}_1 - \hat{V}_2)}{4.47 \angle -63.4^\circ} = 2 \angle 90^\circ$$

$$.05 \hat{V}_1 + (-1 + j.2) \hat{V}_1 + (-.1 - j.2) \hat{V}_2 = 2 \angle 90^\circ$$

$$\boxed{(-.15 + j.2) \hat{V}_1 + (-.1 - j.2) \hat{V}_2 = 2 \angle 90^\circ}$$

At  $\hat{V}_2$


$$\frac{\hat{V}_2 - \hat{V}_1}{4.47 \angle -63.4^\circ} + \frac{\hat{V}_2}{j10} = (1 + j1)$$

$$(.1 + j.2) \hat{V}_2 + (-.1 - j.2) \hat{V}_1 - j0.1 \hat{V}_2 = 1 + j1$$

$$\boxed{(-.1 - j.2) \hat{V}_1 + (0.1 + j0.1) \hat{V}_2 = (1 + j1)}$$

$$\hat{V}_1 = 22.9 \angle 132.3^\circ \text{ V} \quad \hat{V}_2 = 27.9 \angle 140.6^\circ \text{ V}$$

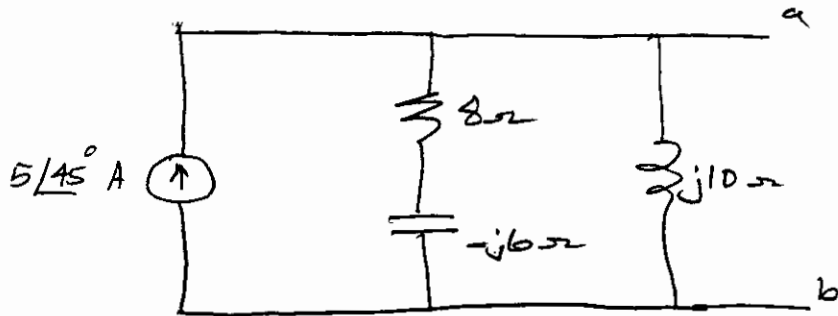(4) Find the Thevenin circuit looking into terminals a-b



First,  $Z_{TH}$ : Open the current source, look into a-b and find the impedance,


$$\hat{Z}_{TH} = (j10) \parallel (8 - j6) = \frac{(10 \angle 90^\circ)(8 - j6)}{j10 + 8 - j6}$$

$$\hat{Z}_{TH} = 10 + j5 = 11.18 \angle 26.6^\circ \Omega$$


Find  $V_{TH}$ : Find the current in  $j10$  using current splitting. Then multiply this current by  $j10$ .

$$\hat{V}_{TH} = \left( \frac{(5 \angle 45^\circ)(8 - j6)}{8 - j6 + j10} \right) \times j10$$
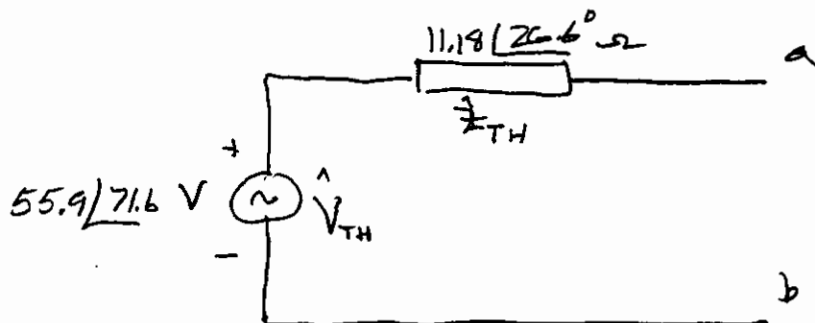
$$\hat{V}_{TH} = 55.9 \angle 71.6^\circ \text{ V}$$



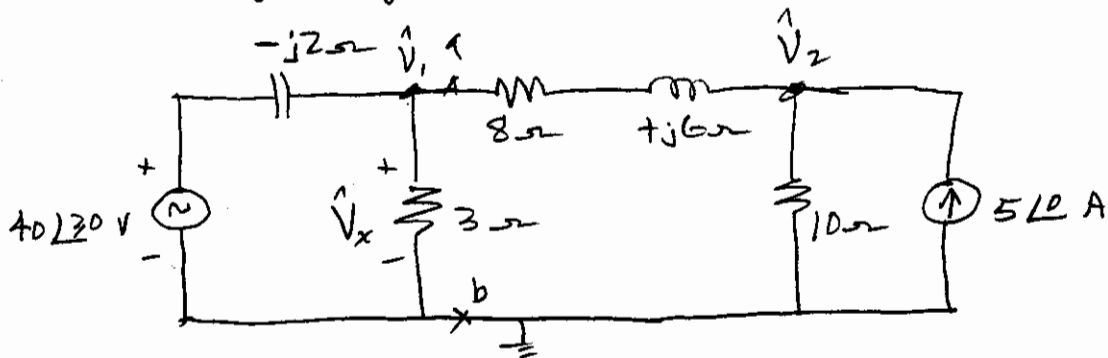(5) Determine  $\hat{V}_x$  in the following circuit using any method.



Use nodal analysis (my choice)

At  $\hat{V}_1$

$$\frac{V_1 - 40 \angle 30}{-j2} + \frac{\hat{V}_1}{3} + \frac{\hat{V}_1 - \hat{V}_2}{8 + j6} = 0$$

$$j0.5V_1 + 20 \angle -60 + 0.333V_1 + (0.08 - j0.06)V_1 - (0.08 - j0.06)V_2 = 0$$

$$(0.413 + j0.44)\hat{V}_1 + (-0.08 + j0.06)\hat{V}_2 = -20 \angle -60$$

At  $\hat{V}_2$

$$\frac{\hat{V}_2 - \hat{V}_1}{8 + j6} + \frac{\hat{V}_2}{10} = 5 \angle 0$$

$$(0.08 - j0.06)V_2 - (0.08 - j0.06)\hat{V}_1 + 0.1\hat{V}_2 = 5 \angle 0$$

$$(-0.08 + j0.06)\hat{V}_1 + (0.18 - j0.06)\hat{V}_2 = 5 \angle 0$$

$$\hat{V}_1 = \hat{V}_x = 29.4 \angle 62.9^\circ \text{ V}$$