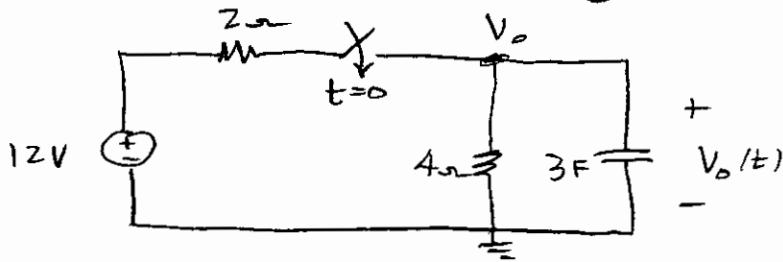


HOME WORK #5

①

Find $V_o(t)$ for the following circuit.



$V_o(0^+) = 0$ voltage across the capacitor cannot change instantaneously.

$$V_o(\infty) = \frac{12 \times 4}{6} = 8 \text{ V}$$

Write a node equation;

$$3 \frac{dV_o}{dt} + \frac{V_o}{4} + \frac{V_o - 12}{2} = 0$$

$$3 \frac{dV_o}{dt} + 0.75V_o = 6$$

$$\frac{dV_o}{dt} + 0.25V_o = 2$$

$$V_{op} = K$$

$$.25K = 2$$

$$K = 8$$


$$V_o = 8 + K_c e^{-0.25t}$$

$$V_o(0) = 0 = 8 + K_c$$

$$K_c = -8$$

$$V_o(t) = 8(1 - e^{-0.25t})$$


① 2nd solution:

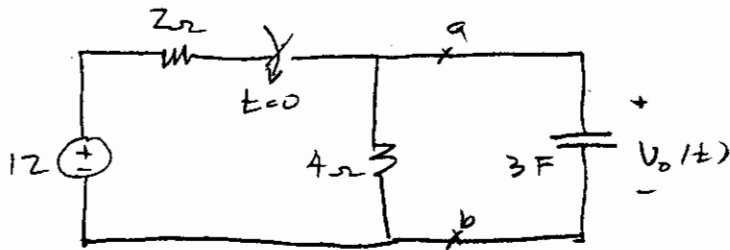

Form the Thevenin equivalent to the left of a-b.

$$R_{TH} = \frac{4 \times 2}{4 + 2} = \frac{8}{6} = \frac{4}{3} \Omega$$
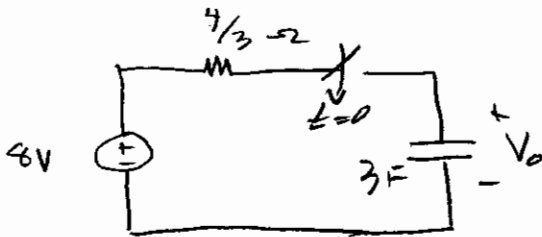
$$V_{TH} = \frac{12 \times 4}{4 + 2} = 8V$$



Using

$$V_o(t) = V_o(\infty) + [V_o(0^+) - V_o(\infty)] e^{-\frac{t}{\tau}}$$


$$\tau = R_{eq} C = \frac{4}{3} \times 3 = 4$$

$$V_o(\infty) = 8V, \quad V_o(0^+) = 0$$

$$V_o(t) = 8(1 - e^{-0.25t}) V$$

(2)

For the following circuit;

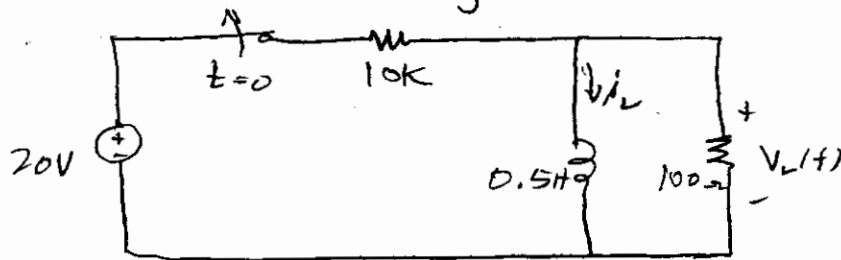


(a) Develop the DE that allows you to solve for $V_L(t)$.

With the switch closed, i_L reach steady state. The inductor looks like a short circuit.

$$i_L(0^-) = \frac{20}{10k} = 2 \times 10^{-3} \text{ A}$$

After the switch is open we have

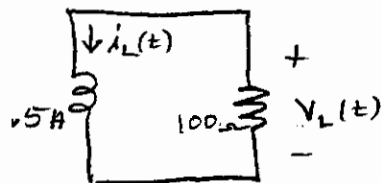

$$L \frac{di_L(t)}{dt} + R i_L(t) = 0 \quad L=0.5, R=100\Omega$$

$$(b) \quad \frac{di_L(t)}{dt} + \frac{R}{L} i_L(t) = 0$$

$$\frac{di_L(t)}{dt} + 200 i_L(t) = 0$$

$$i_L(t) = k e^{-200t}$$

$$i_L(0^-) = i_L(0^+) = 2 \times 10^{-3}$$

$$i_L(t) = 0.002 e^{-200t} \text{ A}$$

(2) continued

(c) What is the time constant?

$$\tau = \frac{L}{R} = \frac{0.5}{100} = 0.005 \text{ sec}$$

$$\tau = 5 \text{ msec}$$

(d) When will the current reach 0.001 A

Take

$$i_L(t) = 0.002 e^{-200t}$$

Set it equal to 0.001

$$0.001 = 0.002 e^{-200t}$$

So,

$$e^{-200t} = 0.5$$


$$-200t \ln e = \ln 0.5 = -0.693$$

$$\ln e = 1$$


$$-200t = -0.693$$

$$t = 0.003 \text{ seconds}$$

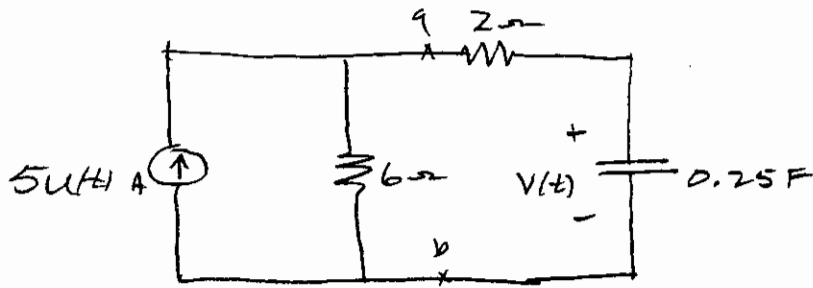③ For the following circuit, find $V(t)$, $t \geq 0$.



Make a Thevenin to the left of a-b

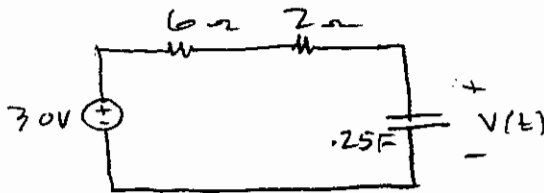

$$0.25 \times 8 \frac{dV_c}{dt} + V_c = 30$$

$$\frac{dV_c}{dt} + 0.5V_c = 15$$

Solution:

$$V_c(t) = 30(1 - e^{-0.5t}) \text{ V}$$

~~##~~

step-by-step

$$V(t) = V(\infty) + [V(0^+) - V(\infty)] e^{-\frac{t}{\tau}}$$


$$\tau = R_{\text{eq}} C = 8 \times 0.25 = 2$$

$$V(\infty) = 30 \text{ V}, \quad V(0) = 0$$


\therefore

$$V(t) = 30(1 - e^{-0.5t}) \text{ V}$$

④ Find $i_L(t)$ in the circuit below.

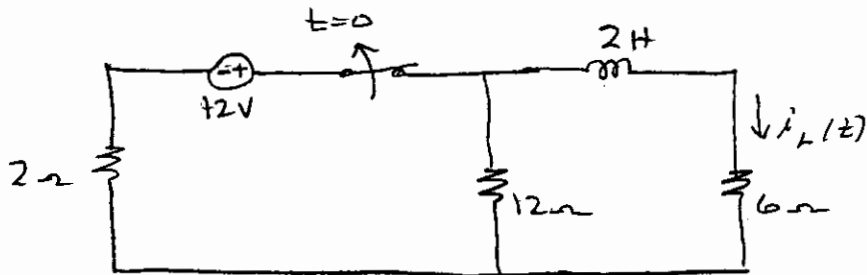

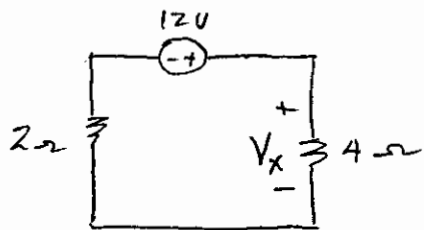With the switch closed for a long time, the inductor is a short circuit. We can find $i_L(0^-)$ from the following:




$$6 \parallel 12 = \frac{72}{18} = 4 \Omega$$

$$V_x = \frac{12 \times 4}{6} = 8 \text{ V}$$

$$\therefore i_L(0^-) = \frac{8 \text{ V}}{6 \Omega} = \frac{4}{3} \text{ A} = i_L(0^+)$$

After the switch is opened we have

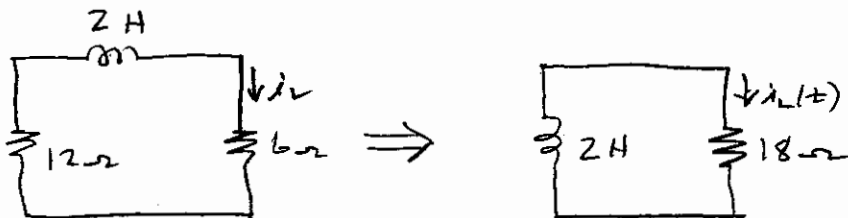

$$L \frac{di_L}{dt} + R i_L = 0$$


$$2 \frac{di_L}{dt} + 18 i_L = 0$$

$$\frac{di_L}{dt} + 9 i_L = 0 \Rightarrow i_L = k e^{-9t} \text{ A}$$


$$i_L = \frac{4}{3} e^{-9t} \text{ A}$$

5) Determine $V_o(t)$ for the circuit below.

Assume $V_o(0^-) = 0$

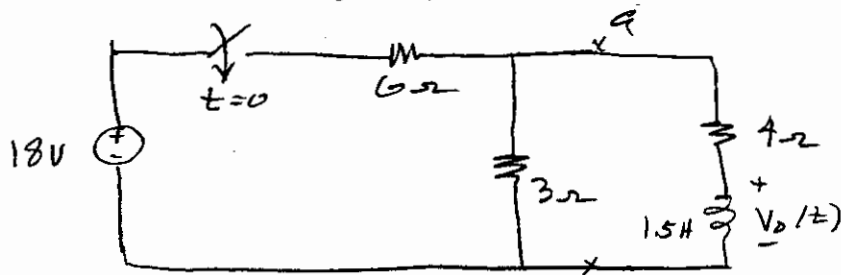

Use Thevenin to the left of a-b.

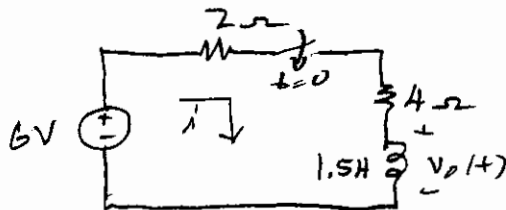

$$V_o(t) = L \frac{di}{dt}$$

$$di = \frac{1}{L} V_o(t) dt$$

$$\int_0^t di = \frac{1}{L} \int_0^t V_o(t) dt$$

$$i(t) = \frac{1}{L} \int_0^t V_o(t) dt + i(0) \quad \text{Assume } i(0) = 0$$

For the circuit;

$$6i(t) + V_o(t) = 6$$

$$6 \times \frac{1}{1.5} \int_0^t V_o(t) dt + V_o(t) = 0 \quad (1)$$

Take the derivative of (1)

$$4V_o(t) + \frac{dV_o(t)}{dt} = 0$$

$$\frac{dV_o(t)}{dt} + 4V_o(t) = 0 \quad (2)$$

(5) continue

The solution to Eq (2) is

$$V_o(t) = k e^{-4t}$$

We need to know $V_o(0^+)$. We know $V_o(0^-) = 0$. However, the voltage across an inductor can change instantaneously.

From circuit 2 we know that when the 6 volts is applied, the current cannot change instantaneously. That means the voltage drops across the 2 Ω and 4 Ω resistors are zero, therefore all the 6V applied is across the inductor. Thus, $V_o(0^+) = 6V$

$$V_o(0^+) = 6 = k e^0 = k$$

so

$$\underline{V_o(t) = 6e^{-4t} \text{ V}}$$

3