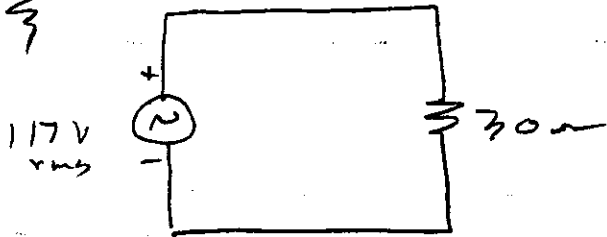


wk 7


N.W. # 7

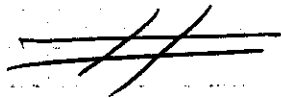7.1
3




Find P_{30} :

$$P_{30} = \frac{V_{rms}^2}{30} = \frac{(117)^2}{30} = 456.3 \text{ W}$$



7.6
3

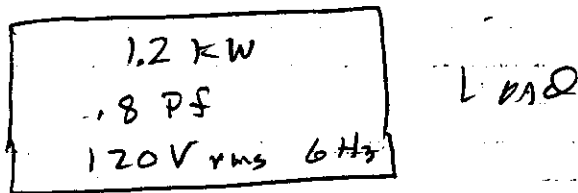

(a) Find I_{rms}

$$P = 12 \text{ kW} = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

$$\theta_v = 0 \quad \theta_i = \cos^{-1} 0.8$$

$$I_{rms} = \frac{1.2 \times 10^3}{120 \times 0.8} = \underline{12.5 \text{ A}}$$

$$(b) \theta = \cos^{-1}(0.8) = \underline{36.87^\circ}$$


$$(c) Z = \frac{120}{12.5 \angle \pm 36.87^\circ} = \underline{9.6 \angle \pm 36.87}$$

$$(d) P = 1200 = I_{rms}^2 R$$


$$R = 7.7 \Omega$$

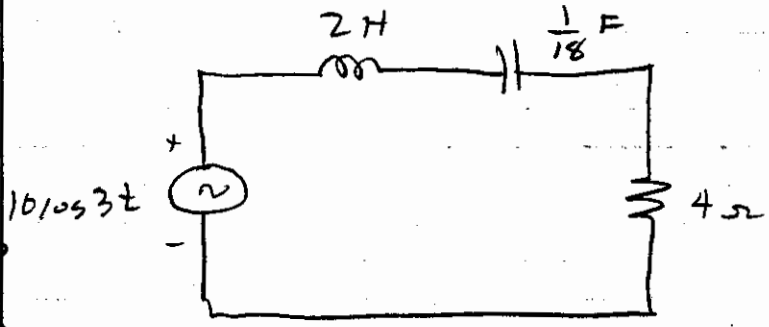7.12 Find the real power and reactive power supplied by the source in the following circuit. Repeat if the frequency is increased by a factor of 3.

$\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)$




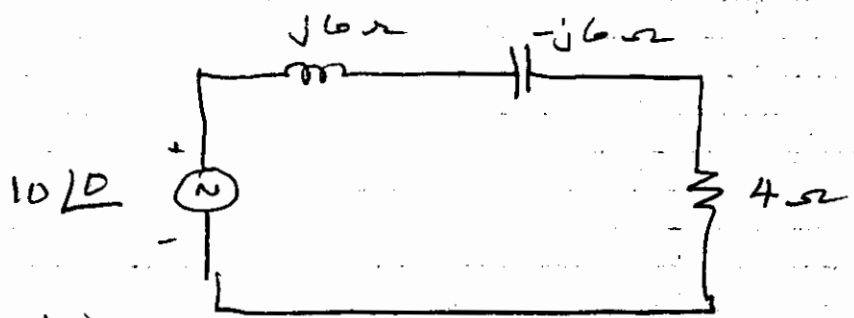$X_L = \omega L = 3 \times 2 = 6, X_C = \frac{1}{\omega C} = -6$



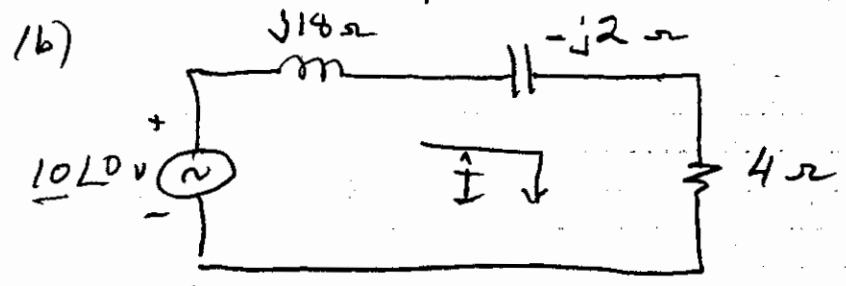(a) $\theta_v = \theta_i = 0$


$P = \frac{10}{\sqrt{2}} \times \frac{10/\sqrt{2}}{4} = 12.5 \text{ W} \quad Q = 0$



$I = \frac{10}{4 + j16} = 0.147 - j0.588 = 0.606 \angle -75.96^\circ$

$P = \frac{10 \times 0.606 \cos(75.96)}{2} = 0.735 \text{ W} \quad Q = \frac{10 \times 0.606 \sin(75.96)}{2} = 2.94 \text{ VAR}$

7.15

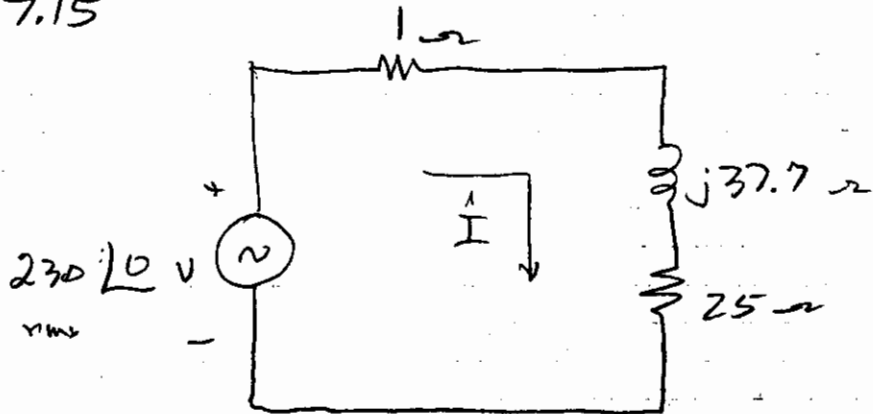

$$\hat{I} = \frac{230}{26 + j37.7} = 5.02 \angle -55.41^\circ \text{ A rms}$$

(b)

$$|S| = (230)(5.02) = \underline{\underline{1.155 \text{ kVA}}}$$

(c)

$$\begin{aligned} \hat{S}_L &= V_L \hat{I}_L^* = (\underline{I}_L \underline{I}_L^*) \underline{Z} = |\hat{I}|^2 (25 + j37.7) \\ &= 1140 \angle 56.5^\circ \end{aligned}$$


$$|S_L| = \underline{\underline{1.14 \text{ kVA}}}$$

(d)


$$\text{pf} = \cos(55.41) \text{ lagging}$$

$$\underline{\underline{\text{pf} = 0.5677 \text{ lagging}}}$$


7.20

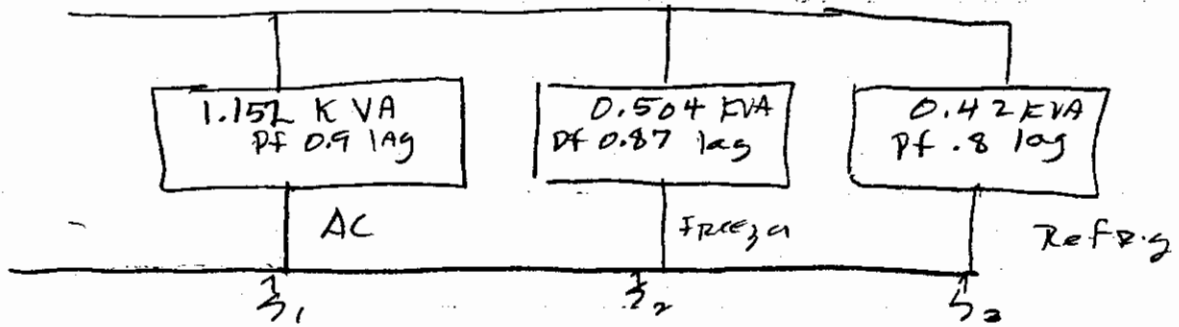

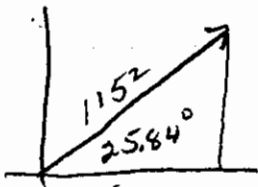
$$\vec{S} = \vec{S}_1 + \vec{S}_2 + \vec{S}_3$$


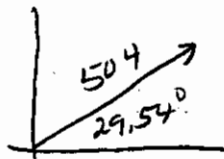
$$S_1 = 1152 \angle 25.84^\circ \text{ VA}$$


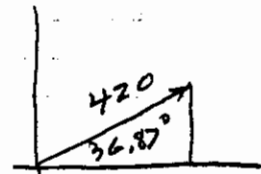
$$S_2 = 504 \angle 29.54^\circ \text{ VA}$$




$$S_3 = 420 \angle 36.87^\circ$$

$$\vec{S} = 1152 \angle 25.84^\circ + 504 \angle 29.54^\circ + 420 \angle 36.87^\circ$$

$$\vec{S} = 1811.3 + j1002.6 \text{ VA}$$

7.25

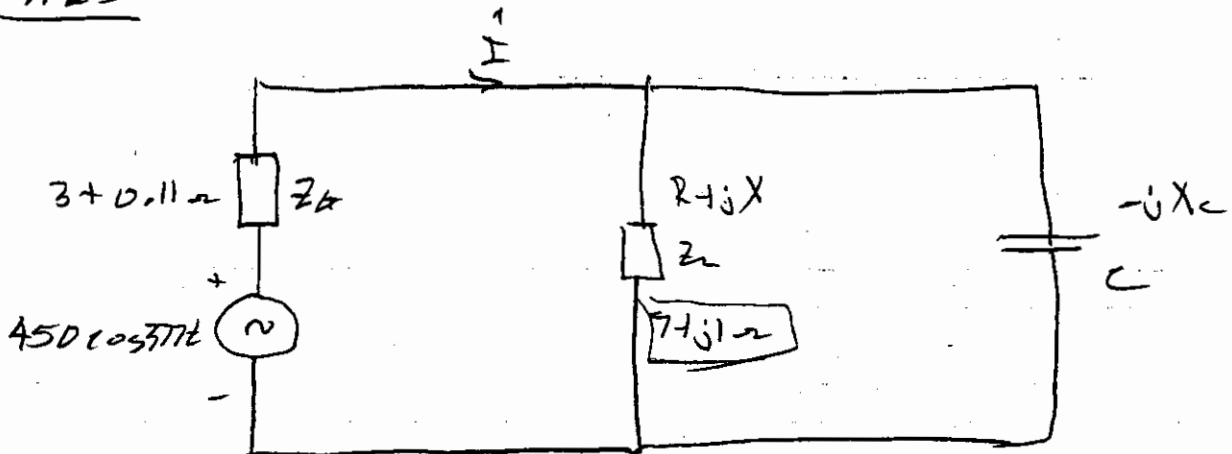

ADD C so that P.F. = 1

To make the P.F. = 1, we want the load impedance to be real (No j term)

$$\frac{(R + jX)(-jX_C)}{R + j(X - X_C)} = R_{eq} + jX_{eq} \Rightarrow X_{eq} = 0$$

$$\frac{(-X X_C - j R X_C)(R - j(X - X_C))}{R^2 + (X - X_C)^2}$$

$$\frac{R X X_C - R X_C (X - X_C) - (j R^2 X_C + X X_C (X - X_C))}{R^2 + (X - X_C)^2} = 0$$

$$\text{so } R^2 X_C + X X_C (X - X_C) = 0$$


$$X_C = \frac{R^2 + X^2}{X} = \frac{7^2 + 1^2}{1} = \frac{49 + 1}{1}$$

$$X_C = 50 = \frac{1}{\omega C}$$

$$C = \frac{1}{50 \times 377} = 53.05 \mu F$$



EX #1

Find \hat{V}_0 for the following circuit

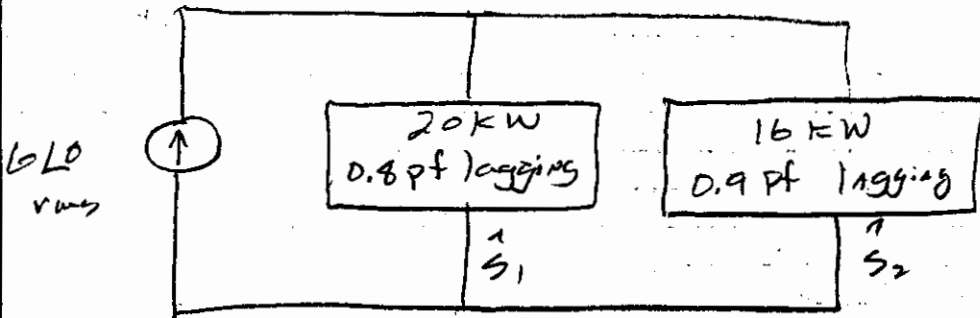

$$\hat{S} = V_{rms} \hat{I}_{rms}^* = 60 \cdot \hat{I}_0^*$$

$$\hat{S} = \hat{S}_1 + \hat{S}_2$$

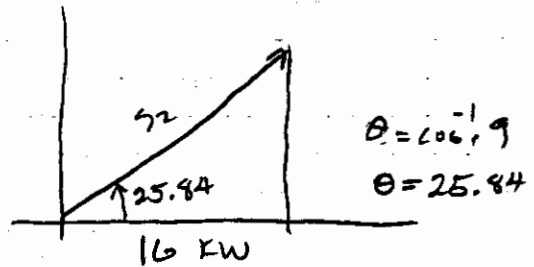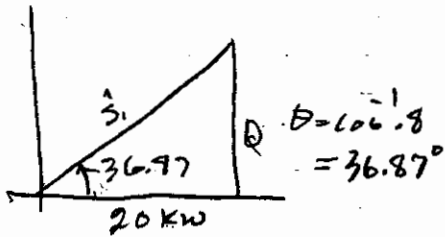

$$\hat{S}_1 = (20 + j20 \tan 36.87) \text{ kVA}$$

$$\hat{S}_2 = (16 + j16 \tan 25.84) \text{ kVA}$$

$$\hat{S}_1 = (20 + j15) \text{ kVA}$$

$$\hat{S}_2 = (16 + j7.75) \text{ kVA}$$

$$\hat{S} = (20 + j15 + 16 + j7.75) \text{ kVA}$$

$$\hat{S} = (36 + j22.75) \text{ kVA} = 42.59 \angle 32.3 \text{ kVA}$$



$$\hat{V}_0 = \frac{42.59 \angle 32.3 \times 10^3}{6} = \underline{\underline{7.098 \angle 32.3 \text{ kV}}}$$

$$\text{P.f.} = \cos(32.3) \text{ lagging}$$

$$\text{P.f.} = 0.8453 \text{ lagging}$$



Ex # 2

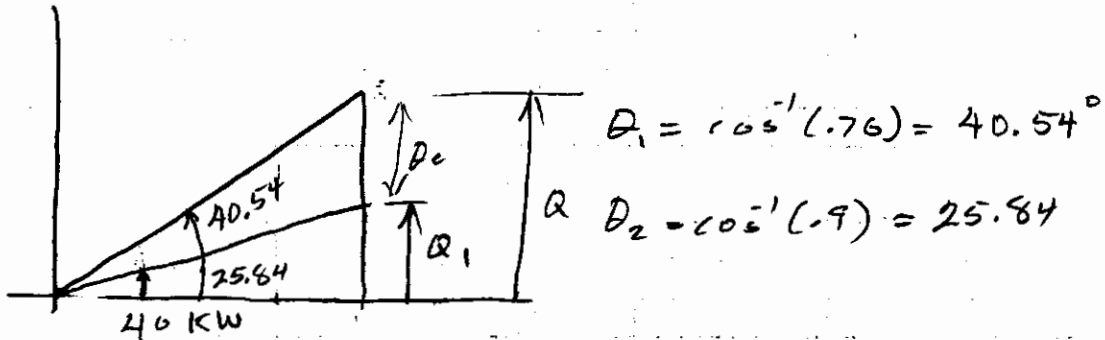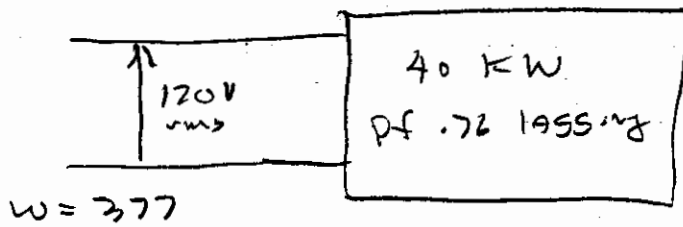

(a)

$$Q_c = Q - Q_1 = P (\tan 40.54 - \tan 25.84)$$

$$Q_c = 14.84 \text{ kVARs}$$

$$\therefore C = \frac{14.84 \times 10^3}{120^2 \times 377} = \underline{2.73 \text{ mF}}$$

(b) To bring to unity power factor:

$$Q_c = 40 \text{ kW} [\tan 40.54 - \tan(0)]$$

$$Q_c = 34.2 \text{ kVARs}$$

$$C = \frac{34.2 \times 10^3}{120^2 \times 377}$$

$$C = \underline{6.3 \text{ mF}}$$