
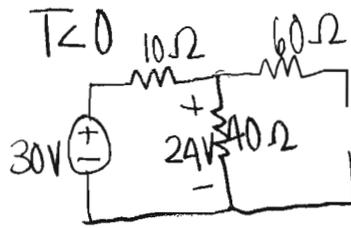


8.16

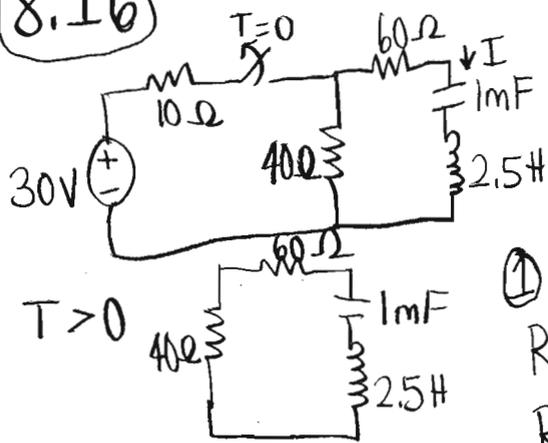

$$V_C(0^-) = 24V$$

$$I_L(0^-) = 0A$$

$$I_C = C \frac{dV/dT}$$

$$V_L = L \frac{dI/dT}$$

$$\textcircled{1} 40\Omega \cdot i + 60\Omega \cdot i + L \frac{di}{dT} + V_C = 0$$

$$R = 40\Omega + 60\Omega \quad V_C = \frac{1}{C} \int_{-\infty}^T i dt$$

$$Ri + L \frac{di}{dT} + \frac{1}{C} \int_{-\infty}^T i dt = 0$$

$$d^2i/dT^2 + \frac{R}{L} \frac{di}{dT} + \frac{1}{LC} = 0 \Rightarrow s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s_1, s_2 = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} \Rightarrow \frac{-\frac{R}{L} \pm \sqrt{(\frac{R}{L})^2 - 4(\frac{1}{LC})}}{2}$$

However, easier to do this

$$\frac{1}{2}s^2 + (\frac{R}{2L})s + \frac{1}{2} \cdot \frac{1}{LC} = 0 \quad \text{divide both sides by 2}$$

$$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{(\frac{R}{2L})^2 - 4(\frac{1}{2LC})(\frac{1}{4})} \quad \text{which gives}$$

$$s_1, s_2 = -\frac{R}{2L} \pm \sqrt{(\frac{R}{2L})^2 - (\frac{1}{\sqrt{LC}})^2} \rightarrow \omega_0$$

$$\alpha = \frac{R}{2L} = \frac{100}{5} = 20 \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10^{-3} \cdot 2.5}} = 20$$

$$s_1 = s_2$$

$$I(t) = (A + Bt)e^{-\alpha t} \Rightarrow (A + Bt)e^{-20t} u(t) \quad A$$

$$I(0) = (A + B \cdot 0) \cdot 1 = A = 0$$

$$\frac{dI}{dT} = -20BTe^{-20T} + Be^{-20T}$$

Using $\textcircled{1}$


$$\frac{di}{dT} = \frac{1}{L}(-Ri - V_C) = \frac{1}{2.5}(-100(0) - 24) = -9.6$$

$$-9.6 = -20B \cdot 0 \cdot 1 + B \cdot 1 \Rightarrow B = -9.6$$

$$I(t) = (-9.6t)e^{-20t} u(t) \quad A$$

HW 7

8.20

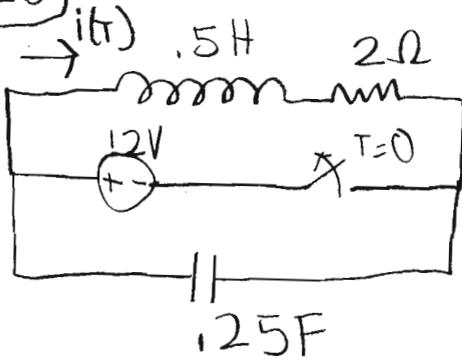

$$V_L = L \frac{di}{dt}$$


$$I_{C0} = 0A$$

$$I_C = C \frac{dV}{dt}$$

$$V_{L0} = 0V$$

$$I_0 = \frac{12V}{2\Omega} = 6A$$

$$V_{C0} = 12V$$

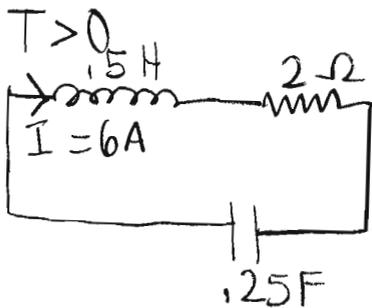

$$Ri + L \frac{di}{dt} + V_C = 0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\alpha = \frac{2\Omega}{2 \cdot 0.5H} = 2 \quad \omega_0 = \frac{1}{\sqrt{0.25 \cdot 0.5}} = 2.828$$

$$s_1, s_2 = \alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 = 2 + j2$$

$$s_2 = 2 - j2$$

$$i(t) = (A_1 \cos 2t + A_2 \sin 2t) e^{-2t} A u(t)$$

$$A_1 = i(0) = 6A$$

$$\frac{di}{dt} = -\frac{1}{L}(-Ri - V_C) = -2(-12 + 12) = 0$$

$$\frac{di}{dt} = -2(A_1 \cos 2t + A_2 \sin 2t) e^{-2t} + (-2A_1 \sin 2t + 2A_2 \cos 2t) e^{-2t}$$

$$\frac{di}{dt} = -2A_1 + 2A_2$$

$$2A_1 = 2A_2 \quad A_2 = 6A$$

$$i(t) = [6 \cos 2t + 6 \sin 2t] e^{-2t} A u(t)$$

8.24

HW 7




$$V_L = L \frac{di}{dt}$$

$$I_C = C \frac{dv}{dt}$$

$$I_0 = 4A$$

$$V_{C0} = 0V$$

$$V_{L0} = 0V$$

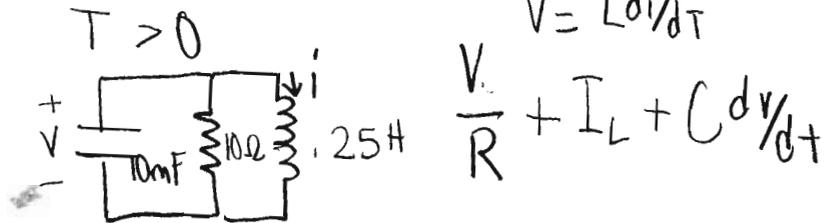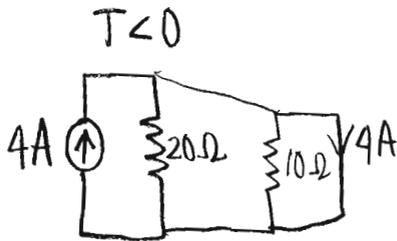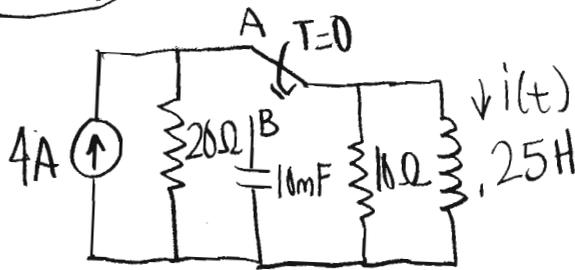

$$\frac{L}{R} \frac{di}{dt} + i + CL \frac{d^2 i}{dt^2} \Rightarrow \frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{i}{LC} = 0$$

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0 \Rightarrow s_1, s_2 = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \left(\frac{1}{LC}\right)^2}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2} \cdot 10 \Omega \cdot 10 \times 10^{-3} F = 5 \quad \omega_0 = \frac{1}{\sqrt{L \cdot C}} = \frac{1}{\sqrt{.25 \cdot 10^{-3}}} = 20$$

$$s_1 = 5 + j19.4$$

$$s_2 = 5 - j19.4$$

$$i(t) = e^{-5t} (A_1 \cos 19.4t + B \sin 19.4t) u(t)$$

$$i(0) = 4 = A_1$$

$$\frac{di}{dt} = (-5A_1 \cos 19.4t - 5B \sin 19.4t - 19.4A_1 \sin 19.4t + 19.4B \cos 19.4t) e^{-5t}$$


$$\frac{di(0)}{dt} = \frac{V}{L} = \frac{0}{.25H} = 0$$

$$5 \cdot 4 = 19.4 B \quad B = 1.03$$

$$i(t) = (4 \cdot \cos 19.4t + 1.03 \sin 19.4t) e^{-5t} u(t) \text{ A}$$


HW 7

8.31

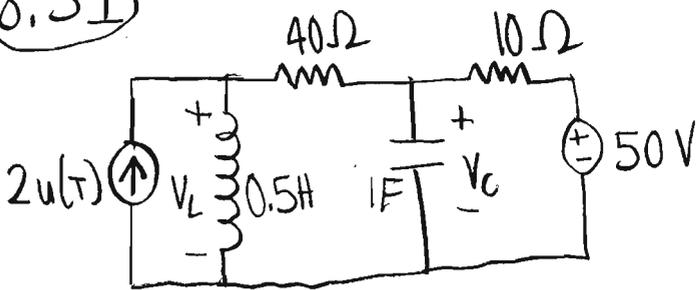

$$I_c = C \frac{dV}{dt}$$

$$V_L = L \frac{di}{dt}$$

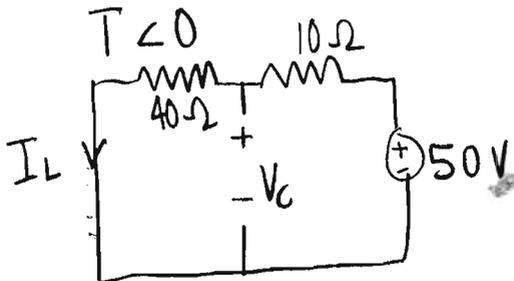


$$I_L(0^-) = 1 \text{ A}$$

$$V_c(0^-) = 40 \text{ V}$$

$$V_L(0^-) = 0 \text{ V}$$

$$I_c(0^-) = 0 \text{ A}$$

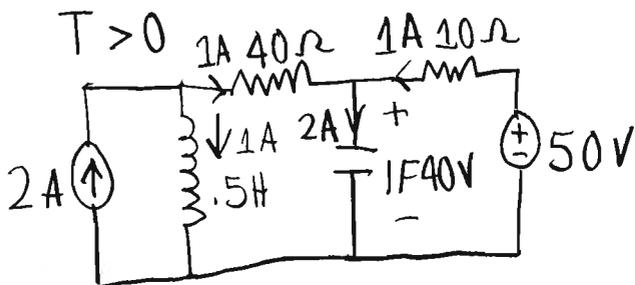

$$V_c(0^-) = V_c(0^+)$$

$$V_c(0^+) = 40 \text{ V}$$

$$I_c(0^+) = 2 \text{ A}$$

$$I_L(0^-) = I_L(0^+) = 1 \text{ A}$$

$$V_L = 40\Omega \cdot 1 \text{ A} + 40 \text{ V} = 80 \text{ V}$$

$$V_L(0^+) = 80 \text{ V}$$


$$I_L(0^+) = 1 \text{ A}$$

$$V_c(0^+) = 40 \text{ V}$$

$$I_c(0^+) = 2 \text{ A}$$


HW 7

8.35

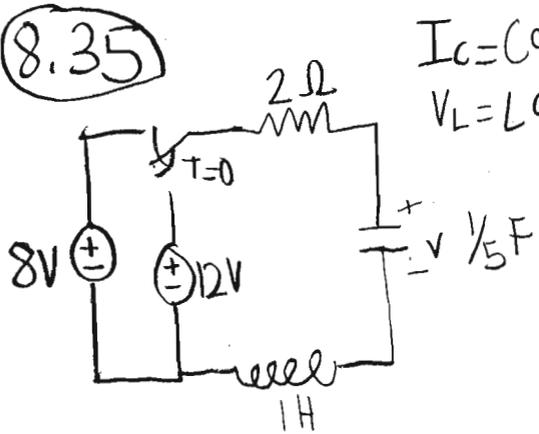

$$I_C = C \frac{dv}{dt}$$

$$V_L = L \frac{di}{dt}$$

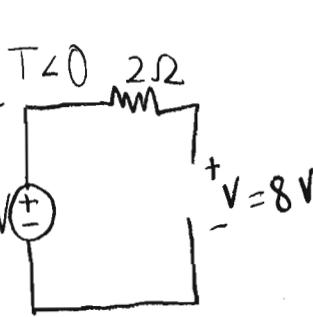


$$I_{L0^-} = 0A$$


$$V_{C0^-} = 8V$$

$$V_{L0^-} = 0V$$

$$I_{C0^-} = 0A$$

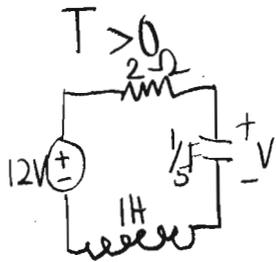

$$\frac{dV(0)}{dt} = 0$$

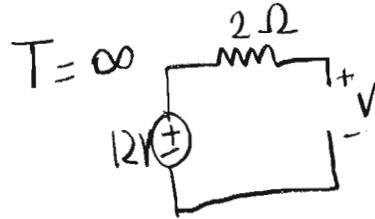

$$-12V + 2\Omega \cdot I + V + L \frac{dI}{dt}$$

$$\frac{d^2 V}{dt^2} + \frac{R}{L} \frac{dV}{dt} + \frac{V}{LC} = \frac{12V}{LC} \Rightarrow s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$\alpha = R/2L = 2\Omega/2H = 1 \quad \omega_0 = 1/\sqrt{LC} = 1/\sqrt{1 \cdot 1/5} = 2.236$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -1 + j2$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -1 - j2$$

$$V(t) = 12 - (A \cos 2t + B \sin 2t) e^{-t} u(t) \text{ V}$$


$$V(0^+) = 8V = 12 - A \quad A = 4$$

$$\frac{dV}{dt} = (-A \cos 2t - B \sin 2t - 2A \sin 2t + 2B \cos 2t) e^{-t}$$

$$\frac{dV}{dt} = -A + 2B \quad B = 2$$


$$V(t) = 12 - (4 \cos 2t + 2 \sin 2t) e^{-t} u(t) \text{ V}$$

8.40

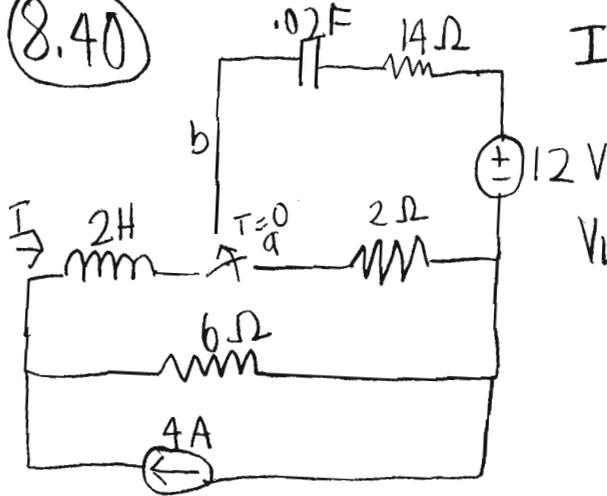

$$I_c = C \frac{dV_c}{dt} \quad T < 0$$

$$V_L = L \frac{dI}{dt}$$

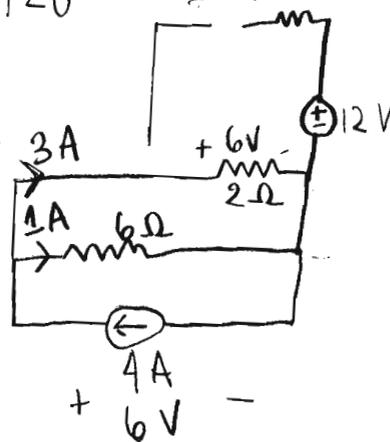



$$V_c(0^-) = 0V$$

$$I_L(0^-) = 3A$$

$$V_L(0^-) = 0V$$

$$I_c(0^-) = 0A$$


$T > 0$

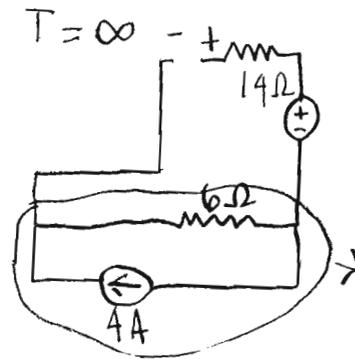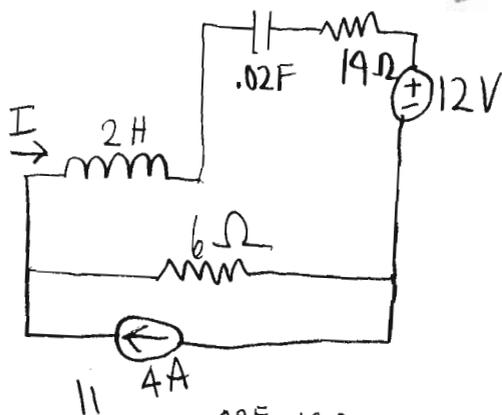

$$I(\infty) = 0$$

$$\frac{dI}{dt} = \frac{1}{L} (-20 \cdot 3A + 12V)$$

$$\frac{dI}{dt} = -24$$

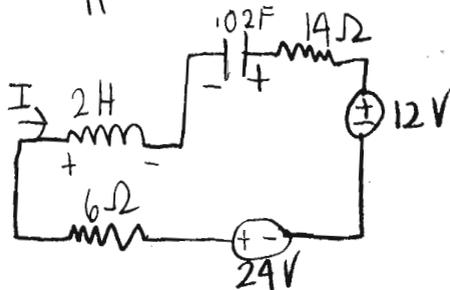

$$-24V + 6\Omega \cdot I + L \frac{dI}{dt} - V_c + 14\Omega \cdot I + 12V = 0 \Rightarrow \frac{d^2 I}{dt^2} + \frac{R}{L} \frac{dI}{dt} + \frac{1}{LC} I = \frac{12V}{LC}$$

$$\alpha = R/2L = \frac{6\Omega + 14\Omega}{2 \cdot 2H} = 5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.02 \cdot 2}} = 5$$

$$I(t) = (A + Bt) e^{-5t} u(t) \text{ A}$$

$$I(0) = A = 3$$

$$\frac{dI}{dt} = -5Bt e^{-5t} - 5A e^{-5t} + B e^{-5t} \Rightarrow \frac{dI}{dt} = -5A + B$$

$$B = -24 + 15 = -9$$

$$I(t) = (3 - 9t) e^{-5t} u(t) \text{ A}$$