


ECE 300  
Spring Semester, 2007  
Test #1

wlg Test A

Name wlg  
Print (last, first)

Work the exam on your own engineering paper. Work on one side of your paper only. Attach your work to the back of this exam sheet and staple in the top left hand corner. Each problem 20%.

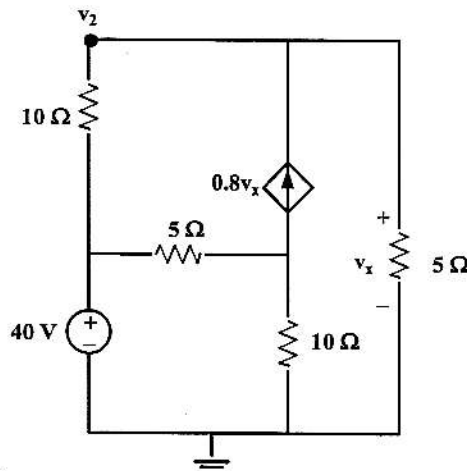(1) You are given the circuit of Figure 1. Use any method to find the voltage  $v_2$ .



At node  $v_2$ :

$$\frac{v_2 - 40}{10} + \frac{v_2}{5} - 0.8v_x = 0$$

note:  
 $v_x = v_2$

$$v_2 - 40 + 2v_2 - 8v_2 = 0$$

$$5v_2 = -40$$

$$v_2 = -8V$$

Test A

Figure 1: Circuit for problem 1.

- (2) Use any method to find the voltage  $V_{ab}$  in the circuit of Figure 2.

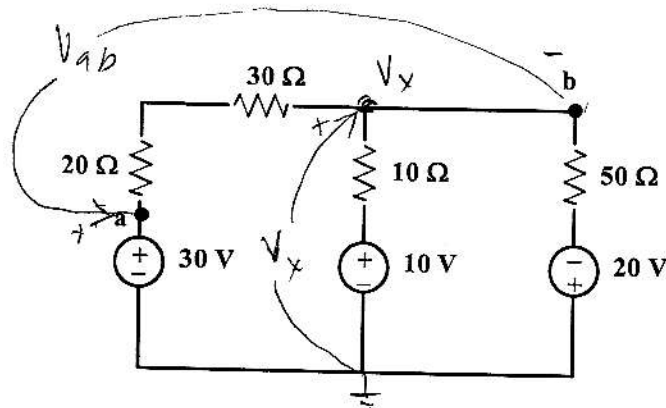


Figure 2: Circuit for problem 2.

Solve for the node voltage,  $V_x$

$$\frac{V_x - 30}{50} + \frac{V_x - 10}{10} + \frac{V_x + 20}{50} = 0$$

$$V_x - 30 + 5V_x - 50 + V_x + 20 = 0$$

$$7V_x = 60$$

$$V_x = 8.57 \text{ V}$$

Applying KVL


$$V_{ab} - 30 + V_x = 0$$

$$V_{ab} = 30 - V_x = 30 - 8.57$$

$$V_{ab} = 21.43 \text{ V}$$

# Test A

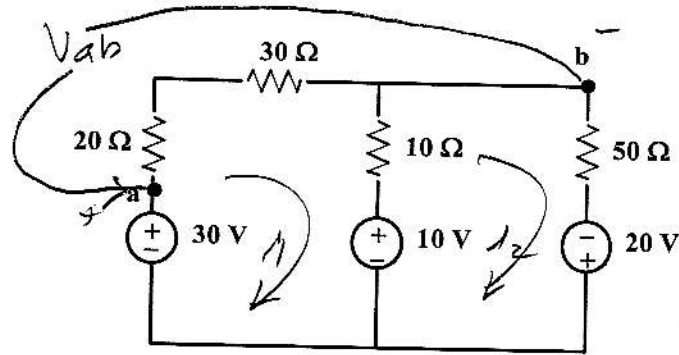(2) Use any method to find the voltage  $V_{ab}$  in the circuit of Figure 2.



Another solution using mesh

By inspection

$$\begin{bmatrix} 60 & -10 \\ -10 & 60 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 30 \end{bmatrix}$$

$$i_1 = 0.4286 \text{ A}$$

$$V_{ab} - 0.4286(20 + 30) = 0$$


$$V_{ab} = 21.43 \text{ V}$$

# Test A


3

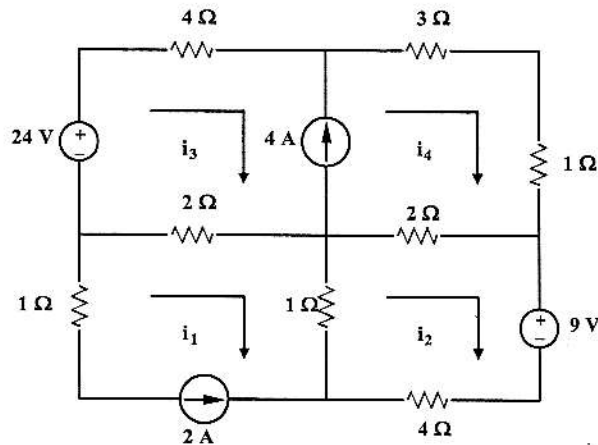(3) You are given the circuit of Figure 3.

- Use mesh analysis to find the currents  $i_1$ ,  $i_2$ ,  $i_3$  and  $i_4$ .
- How much power is supplied by the 9 V source?
- How much power is dissipated by the  $3\ \Omega$  resistor?



Redraw

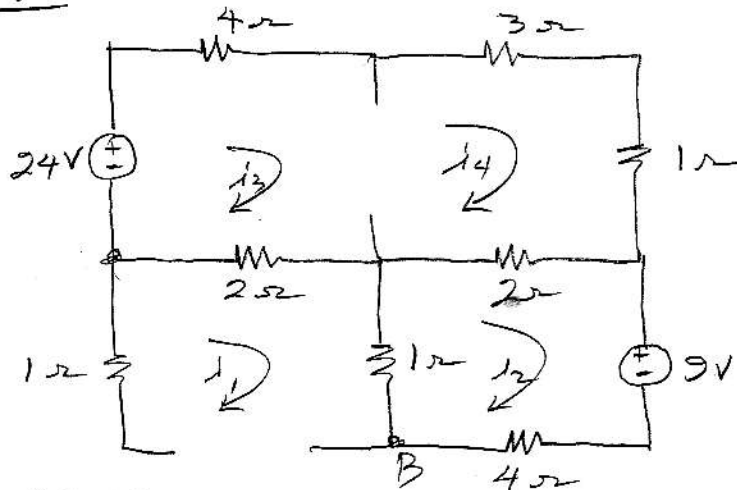

At A,  $\sum \text{cw } \Sigma \text{ drops} = 0$

$$-24 + 4i_3 + 4i_4 + 2(i_4 - i_2) + 2(i_3 - i_1) = 0$$

$$\boxed{-2i_1 - 2i_2 + 6i_3 + 6i_4 = 24}$$

At B,  $\sum \text{cw } \Sigma \text{ drops} = 0$

$$1(i_2 - i_1) + 2(i_2 - i_4) + 9 + 4i_2 = 0$$

$$\boxed{-i_1 + 7i_2 + 0i_3 - 2i_4 = -9}$$

Test A

3.2

Problem #3 continued

Constraint 1

$$i_1 = -2A$$

$$i_1 + 0i_2 + 0i_3 + 0i_4 = -2$$

Constraint 2

$$i_4 - i_3 = 4$$

$$0i_1 + 0i_2 - i_3 + i_4 = 4$$

$$\begin{bmatrix} -2 & -2 & 6 & 6 \\ -1 & 7 & 0 & -2 \\ 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 24 \\ -9 \\ -2 \\ 4 \end{bmatrix}$$

$$i_1 = -2A$$

$$i_2 = -0.55A$$

$$i_3 = -0.425A$$


$$i_4 = 3.58A$$

$$(b) P_{50\Omega} = -i_2 \times 9 = .55 \times 9 = 4.95W$$

$$(c) P_{2.5\Omega} = i_4^2 \times 3 = (3.58)^2 \times 3 = 38.45W$$

cut A

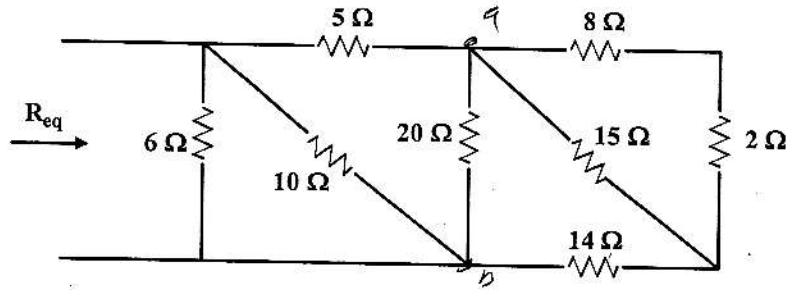
(4) Find  $R_{eq}$  for the circuit of Figure 4.





Working right to left

$$10 \parallel 15 = \frac{10 \times 15}{10 + 15} = 6 \Omega$$

Right of a-b then  $6 + 14 = 20 \Omega$

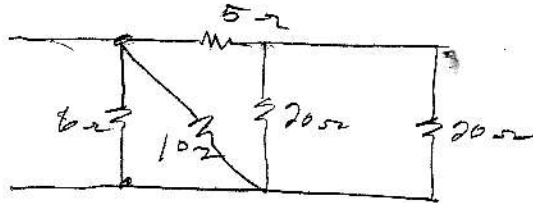

then

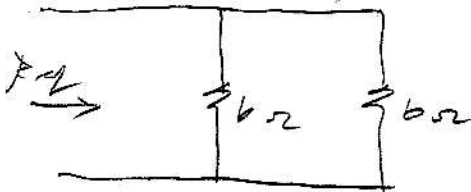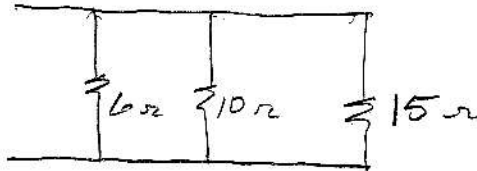


$$R_{eq} = 6 \parallel 6$$

$$R_{eq} = 3 \Omega$$

## Test A

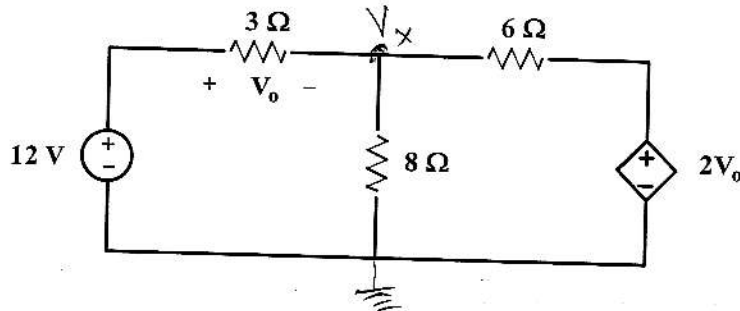- (5) Use any method of your choice to answer the following questions about the circuit of Figure 5.
- Determine the voltage  $V_0$  as shown in Figure 5.
  - How much power is absorbed by the  $8\ \Omega$  resistor shown in Figure 5.



Using nodal at  $V_x$

$$\frac{V_x - 12}{3} + \frac{V_x}{8} + \frac{V_x - 2V_0}{6} = 0$$

but  $V_0 = 12 - V_x$

so

$$24 \left( \frac{V_x - 12}{3} + \frac{V_x}{8} + \frac{V_x - 2(12 - V_x)}{6} = 0 \right)$$

$$8V_x - 96 + 3V_x + 12V_x = 96$$

$$23V_x = 192$$

$$V_x = 8.35\text{ V}$$

$$\therefore V_0 = 12 - 8.35 = 3.65\text{ V}$$

(a)  $V_0 = 3.65\text{ V}$


(b)  $P_8 = \frac{V_x^2}{8} = \frac{8.35^2}{8} = 8.72\text{ W}$

$P_8 = 8.72\text{ W}$

# Test A

(5)  $B_n$  mesh

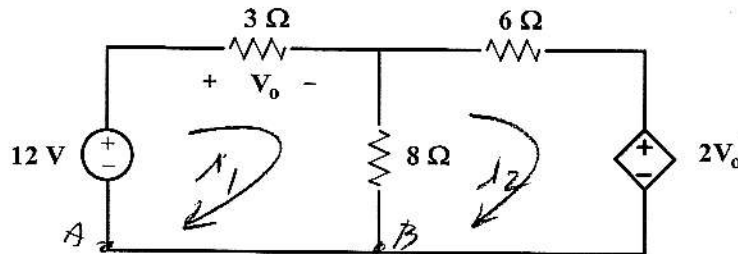- (5) Use any method of your choice to answer the following questions about the circuit of Figure 5.  
 (a) Determine the voltage  $V_o$  as shown in Figure 5.  
 (b) How much power is absorbed by the  $8\ \Omega$  resistor shown in Figure 5.



At A,  $\sum \text{cw, } \sum \text{drops} = 0$

$$-12 + 3i_1 + 8(i_1 - i_2) = 0$$

$$\boxed{11i_1 - 8i_2 = 12}$$

At B,  $\sum \text{cw, } \sum \text{drops} = 0$

$$8(i_2 - i_1) + 6i_2 + 2V_o = 0$$

$$V_o = 3i_1$$

$$8(i_2 - i_1) + 6i_2 + 2(3i_1) = 0$$

$$\boxed{-2i_1 + 14i_2 = 0}$$

$$\begin{bmatrix} 11 & -8 \\ -2 & 14 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \end{bmatrix}$$

$$i_1 = 1.217\text{ A}, \quad i_2 = 0.1739\text{ A}$$

(a)  $\boxed{V_o = 3i_1 = 3.65\text{ V}}$  OK


(b)  $\boxed{P_8 = (i_1 - i_2)^2 \times 8 = 8.71\text{ W}}$  OK



7/10/18



(6) This problem is for extra credit. Part (a) is for 1 point. Part (b) is for 1 point. There is no partial credit given. In each case, the answer is either correct or not correct.

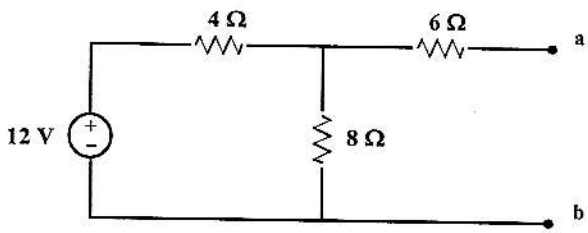(a) Find the voltage  $V_{ab}$  indicated in the diagram of Figure 6 (a)



$$V_{ab} = \frac{12 \times 8}{4 + 8} = 8V$$

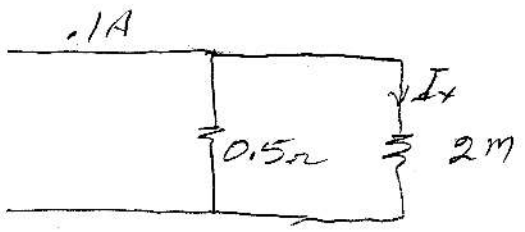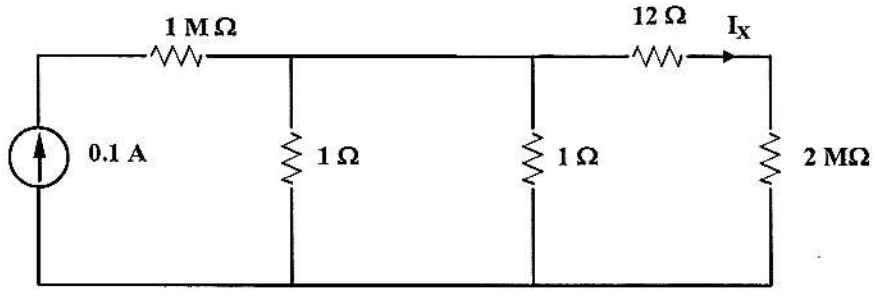(b) Give the value of the current  $I_x$  in the 12 Ω resistor, up to the second significant decimal place, for the circuit shown Figure 6b.



$$I_x = \frac{0.1 \times 0.5}{2m} = 2.5 \times 10^{-8} A$$

$I_x = 0$  for 2 significant digits