

Desk copy

ECE 300
Fall Semester, 2007
Test #2

wlg Test A

Name

wlg

Print (last, first)

Work the exam on the paper provided.

- (1) You are given the circuit of Figure 1.
(a) Find the Thevenin equivalent circuit to the left of terminals a-b.
(b) Draw your Thevenin circuit using your V_{TH} and R_{TH} .

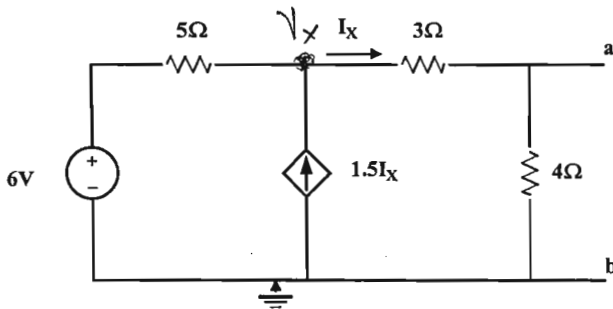


Figure 1: Circuit for problem 1.

For open circuit voltage:

$$\frac{V_x - 6}{5} + \frac{V_x}{7} - 1.5I_x = 0$$

$$\text{but } I_x = \frac{V_x}{7}$$

so

$$35 \left(\frac{V_x - 6}{5} + \frac{V_x}{7} - \frac{1.5V_x}{7} \right) = 0$$

$$7V_x - 42 + 5V_x - 7.5V_x = 0$$

$$4.5V_x = 42$$

$$V_x = 9.33 \text{ V}$$

$$V_{OC} = V_{TH} = \frac{9.33 \times 4}{3 + 4} = 5.33 \text{ V}$$

∴


$$V_{TH} = 5.33 \text{ V}$$

Test A
Problem 1

2

Now for I_{sc}

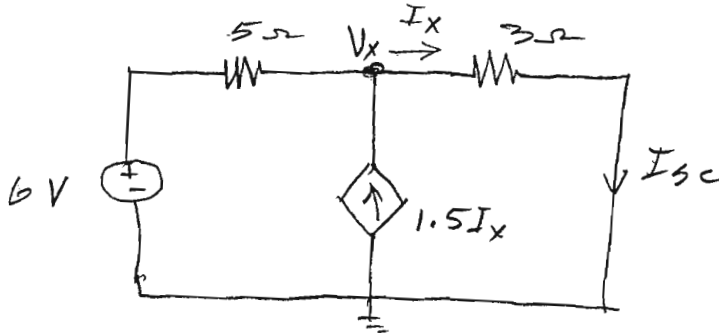Shorting terminals a-b shorts out the 4Ω resistor. We have



$$\left(\frac{V_x - 6}{5} + \frac{V_x}{3} - 1.5I_x = 0 \right) ; \quad I_x = \frac{V_x}{3}$$

$$15 \left(\frac{V_x - 6}{5} + \frac{V_x}{3} - \frac{1.5V_x}{3} \right) = 0$$

$$3V_x - 18 + 5V_x - 7.5V_x = 0$$


$$.5V_x = 18$$

$$V_x = 36$$

$$I_{sc} = I_N = \frac{V_x}{3} = 12A$$

$$R_{TH} = \frac{V_{OS}}{I_{sc}} = \frac{5.33}{12} = 0.44\Omega$$

(b)

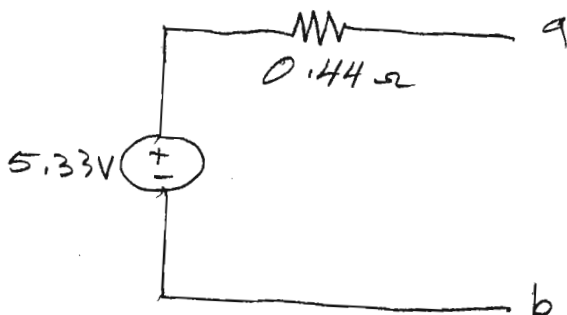


Thevenin
Circuit

Test A

11)

3

Alternate way to find R_{TH} .

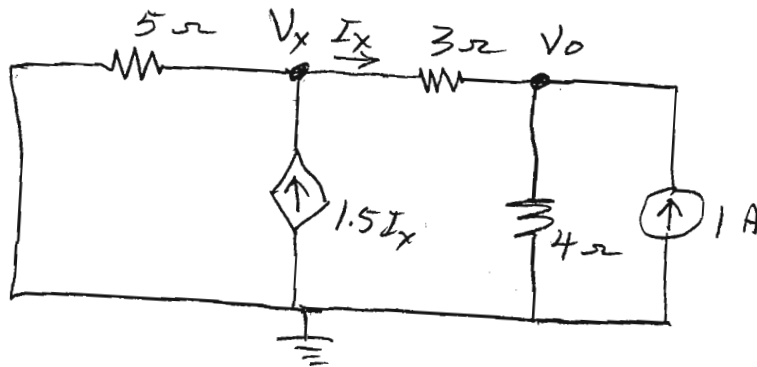

At V_x

$$\frac{V_x}{5} + \frac{V_x - V_o}{3} - \frac{1.5(V_x - V_o)}{3} = 0$$

$$\frac{V_x}{5} - \frac{V_x}{6} + \frac{V_o}{6} = 0$$

$$6V_x - 5V_x + 5V_o = 0$$

$$\boxed{V_x + 5V_o = 0}$$

At V_o

$$12 \left(\frac{V_o - V_x}{3} + \frac{V_o}{4} = 1 \right)$$

$$4V_o - 4V_x + 3V_o = 12$$

$$\boxed{-4V_x + 7V_o = 12}$$

$$V_o = 0.444 \text{ V}$$

$$R_{TH} = \frac{V_o}{1}$$

$$R_{TH} = 0.444 \Omega \quad \text{check}$$

- (2) You are given the circuit of Figure 2. Find the value of R that will result in maximum power being delivered to this resistor.


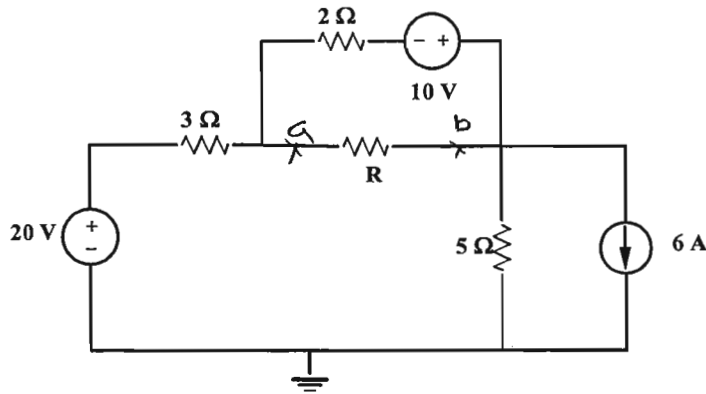


Figure 2: Circuit for problem 2.

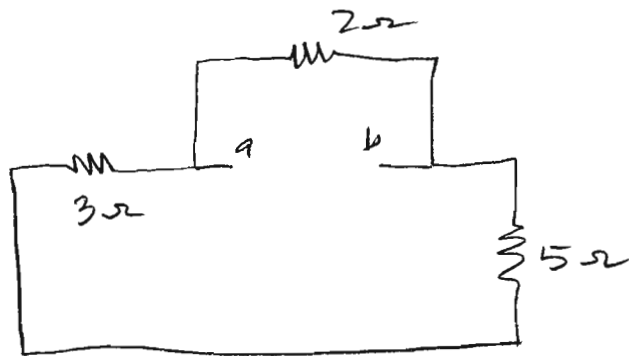Looking into a-b with independent sources deactivated, gives the following circuit.



$$R = 2 \parallel 8 = \frac{16}{10} = 1.6 \Omega$$

So R for maximum power transfer is

$$R = 1.6 \Omega$$

(3) You are given the circuit of Figure 3. Determine the relationship between V_o and I_o . Circle the correct answer from the following list.

(a) $V_o = 24 - 5I_o$

(c) $V_o = 14 + 3I_o$

(e) $V_o = 36I_o$

(b) $V_o = 18I_o$

(d) $V_o = 24I_o$

(f) $V_o = 32I_o - 2$

10%


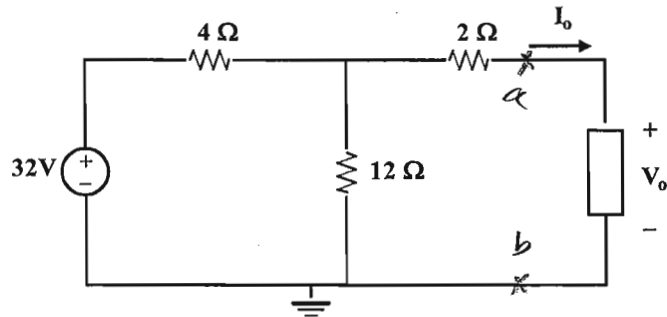



Figure 3: Circuit for problem 3.

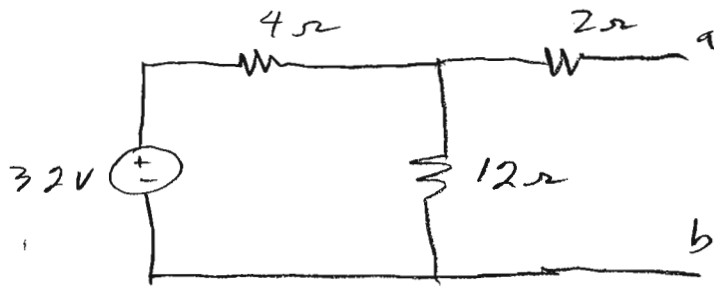Remove the load and find V_{TH} , R_{TH} looking into a-b



$$V_{ab} = V_{TH} = \frac{32 \times 12}{12 + 4} = 24V ; R_{TH} = (12 || 4) + 2$$

$$R_{TH} = 3 + 2 = 5\Omega$$

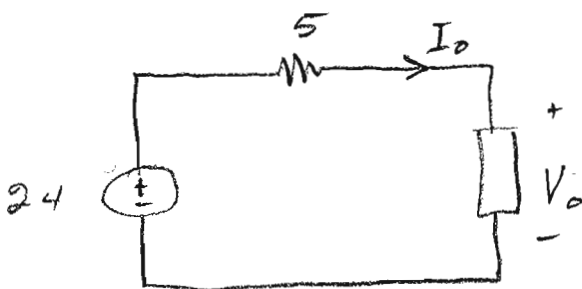

$$V_o = 24 - 5I_o$$

- (4) You are given the circuit of Figure 4.
 (a) Find the Norton equivalent circuit looking into terminals a-b.
 (b) Draw the Norton equivalent circuit using your values of I_N and R_N .

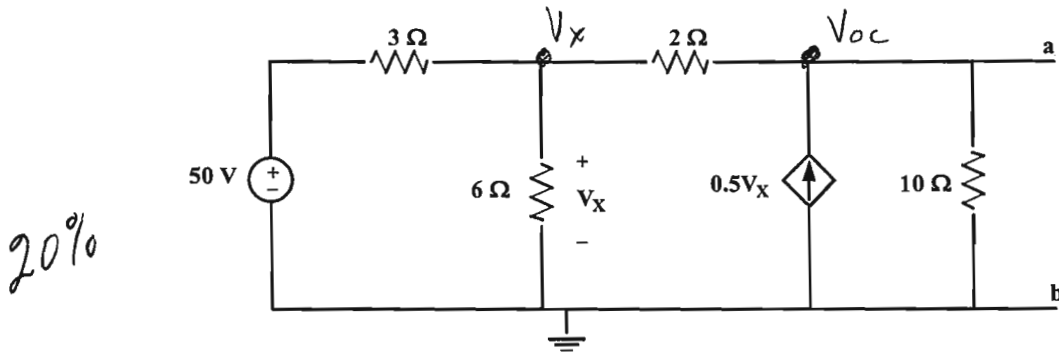


Figure 4: Circuit for problem 4.

Find V_{oc} : Use Nodal

At V_x

$$6 \left(\frac{V_x - 50}{3} + \frac{V_x}{6} + \frac{V_x - V_{oc}}{2} = 0 \right)$$

$$2V_x - 100 + V_x + 3V_x - 3V_{oc} = 0$$

$$\boxed{6V_x - 3V_{oc} = 100} \quad (1)$$

At V_{oc}

$$10 \left(\frac{V_{oc} - V_x}{2} + \frac{V_{oc}}{10} - 0.5V_x = 0 \right)$$

$$5V_{oc} - 5V_x + V_{oc} - 5V_x = 0$$


$$\boxed{-10V_x + 6V_{oc} = 0} \quad (2)$$

FROM (1) & (2)

$$\begin{bmatrix} 6 & -3 \\ -10 & 6 \end{bmatrix} \begin{bmatrix} V_x \\ V_{oc} \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \end{bmatrix}$$

$$\boxed{V_o = V_{TH} = 166.67 \text{ V}}$$

Now find I_{sc}

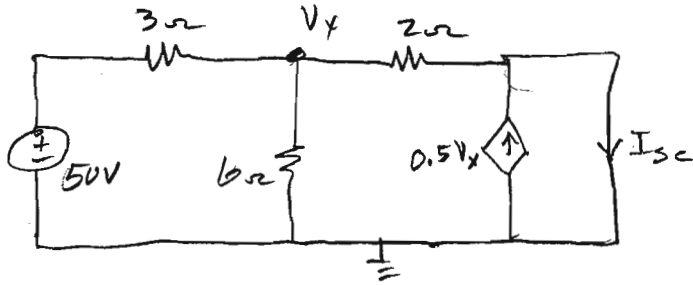

$$6 \left(\frac{V_x - 50}{3} + \frac{V_x}{6} + \frac{V_x}{2} = 0 \right)$$


$$2V_x - 100 + V_x + 3V_x = 0$$

$$6V_x = 100$$


$$V_x = 16.67 \text{ V}$$

$$I_{sc} = \frac{V_x}{2} + 0.5V_x = \frac{50}{6} + \frac{50}{6} = \frac{100}{6} = 16.67 \text{ A}$$
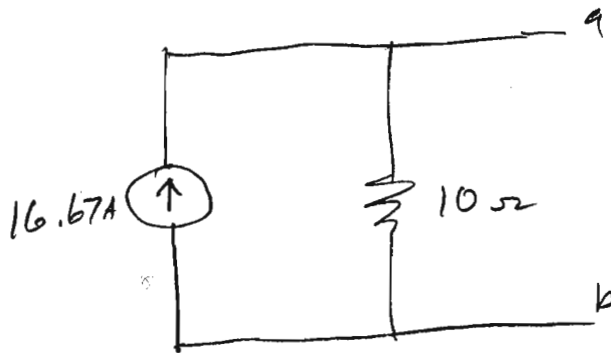
$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{166.67}{16.67} = 10 \Omega$$



4

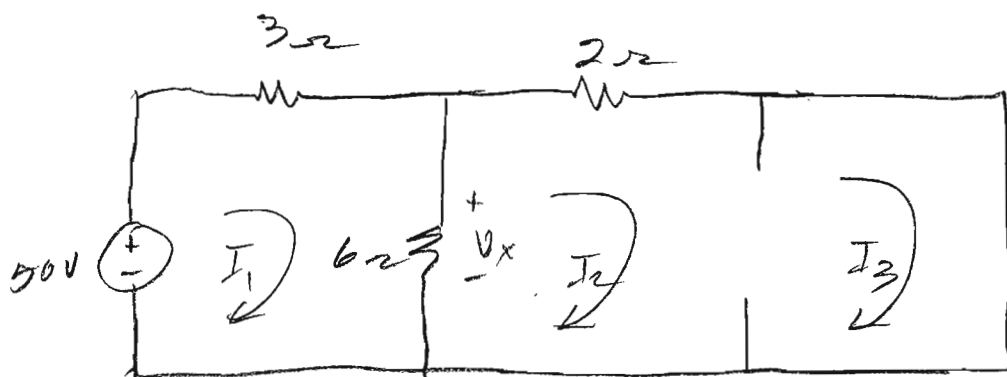

$$-50 + 9I_1 - 6I_2 + 0I_3 = 0$$

$$9I_1 - 6I_2 + 0I_3 = 50$$

$$-6I_1 + 8I_2 + 0I_3 = 0$$

$$0.5V_x = I_3 - I_2$$

$$0.5(6(I_1 - I_2)) = I_3 - I_2$$


$$3I_1 - 3I_2 - I_3 + I_2 = 0$$

$$3I_1 - 2I_2 - I_3 = 0$$

$$\begin{bmatrix} 9 & -6 & 0 \\ -6 & 8 & 0 \\ 3 & -2 & -1 \end{bmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 50 \\ 0 \\ 0 \end{pmatrix}$$

$$I_3 = I_{sc} = 16.67 \text{ A}$$

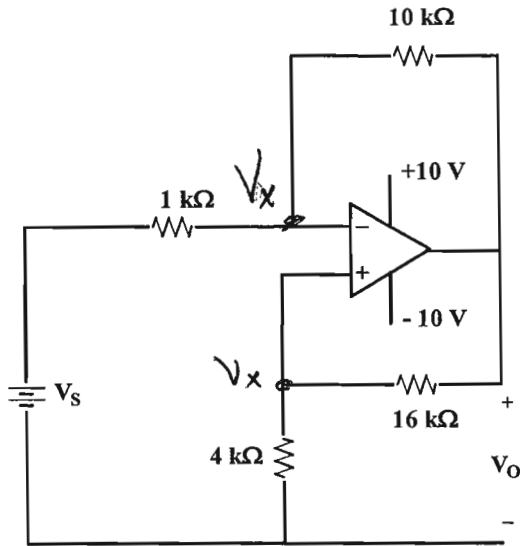- (5) You are given the op amp circuit shown in Figure 5.
 (a) What is the rail-to-rail voltage of the circuit?
 (b) If $V_S = 1.5\text{ V}$, what is the value of V_O ?



(a) Rail to Rail:
 $+10\text{ V}$
 -10 V

Figure 5: Circuit for problem 5.

At V_x

$$\frac{V_x - V_S}{1\text{ k}} + \frac{V_x - V_O}{10\text{ k}} = 0$$

but $V_x = \frac{V_O \times 4\text{ k}}{4\text{ k} + 16\text{ k}} = 0.2 V_O$

$$\frac{0.2 V_O - V_S}{1} + \frac{0.2 V_O - V_O}{10} = 0$$

$$2 V_O - 10 V_S + 0.2 V_O - V_O = 0$$

$$1.2 V_O = 10 V_S$$

$$V_O = 8.33 V_S \Big|_{V_S = 1.5\text{ V}} = 12.5\text{ V} \text{ but limited to } 10\text{ V}$$

$$V_O = 10\text{ V}$$

(6) You are given the op amp circuit of Figure 6.

(a) Find the relationship for $\frac{V_o}{i_s}$ in terms of R.

(b) If $R = 1 \text{ k}\Omega$, what is the maximum value allowable for i_s in order not to saturate the op amp?

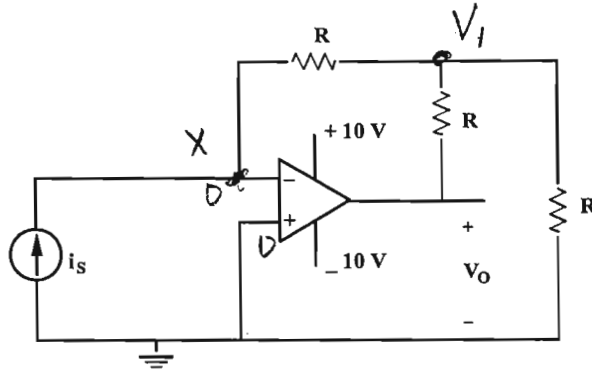


Figure 6: Circuit for problem 6.

20%

(a)

At X

$$\frac{0 - V_1}{R} = i_s \Rightarrow V_1 = -R i_s \quad (1)$$

At V_1

$$\frac{V_1 - 0}{R} + \frac{V_1 - V_o}{R} + \frac{V_1}{R} = 0$$

$$V_o = 3V_1$$

Using (1)

$$V_o = -3R i_s$$

(b)

$$V_o = -3R i_s \Big|_{V_o = 10} = -3k i_s$$

$$R = 1k$$

$$i_s = \pm \frac{10}{3k} = \pm 3.33 \text{ mA}$$