

Desk Copy


ECE 300
Fall Semester, 2007
Test #2

wlg Test B

Name wlg
Print (last, first)

Work the exam on the paper provided.

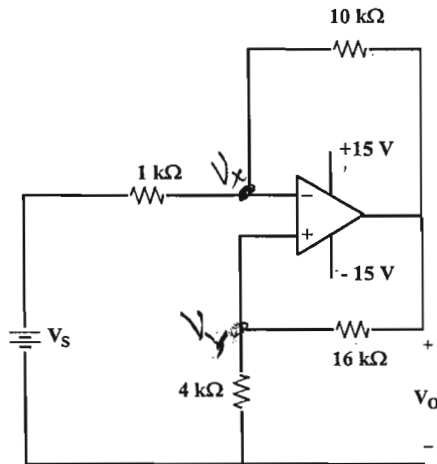- (1) You are given the op amp circuit shown in Figure 1.
 - (a) What is the rail-to-rail voltage of the circuit?
 - (b) If $V_s = 2.2$ V, what is the value of V_o ?



(a) rail to rail
-15 to +15 volts

Figure 1: Circuit for problem 1.

At V_x

$$\frac{V_x - V_s}{1K} + \frac{V_x - V_o}{10K} = 0 \quad (1)$$

∴ but

$$V_y = V_x = \frac{4V_o}{4 + 16} = 0.2V_o$$

substitute into (1)

$$\frac{0.2V_o - V_s}{1} + \frac{0.2V_s - V_o}{10} = 0$$

$$2V_o - 10V_s + 0.2V_s - V_o = 0$$

$$1.2V_o = 10V_s$$

$$V_o = 8.33V_s \quad = 18.33V$$

$$V_s = 2.2$$

but limited to 15V

$$V_o = 15V$$

(2) You are given the circuit of Figure 2. Determine the relationship between V_o and I_o . Circle the correct answer from the following list.

(a) $V_o = 24 - 5I_o$

(c) $V_o = 14 + 3I_o$

(e) $V_o = 40I_o$

(b) $V_o = 18I_o$

(d) $V_o = 30 - 7I_o$

(f) $V_o = 40I_o - 4$

10%



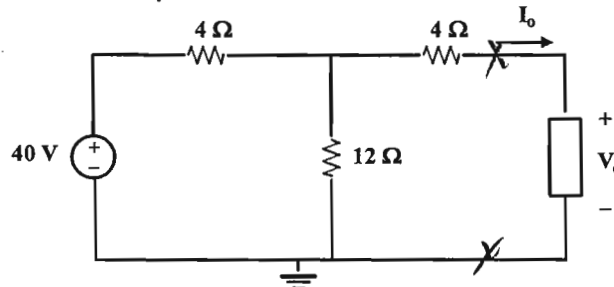


Figure 2: Circuit for problem 2.

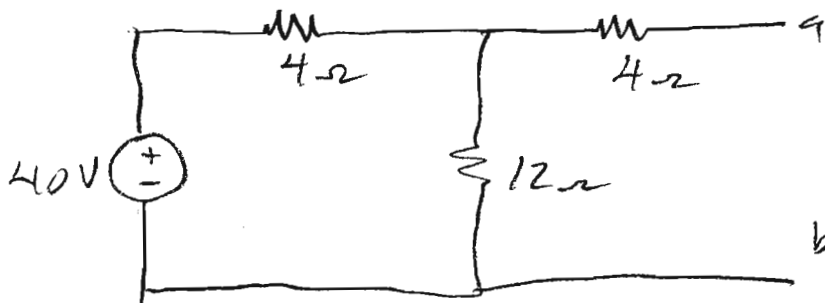

$$V_{ab} = V_{TH} = \frac{40 \times 12}{4 + 12} = 30V; \quad R_{TH} = 4 + 12 \parallel 4$$

$$R_{TH} = 7\Omega$$

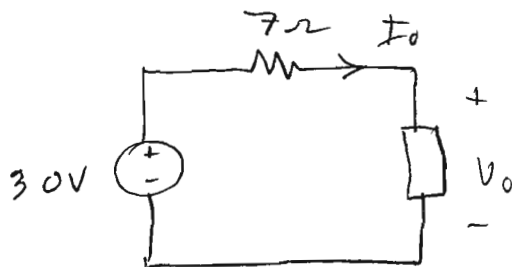

$$V_o = 30 - 7I_o$$

- (3) You are given the circuit of Figure 3.
 (a) Find the Thevenin equivalent circuit to the left of terminals a-b.
 (b) Draw your Thevenin circuit using your V_{TH} and R_{TH} .

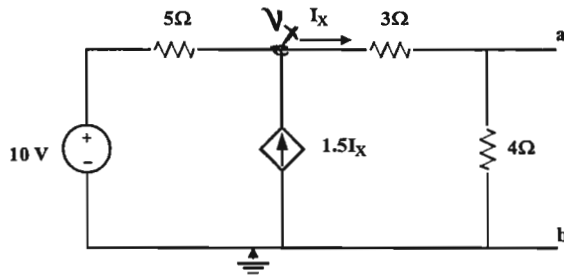


Figure 3: Circuit for problem 3.

20%

FOR V_{oc}

$$\frac{V_x - 10}{5} + \frac{V_x}{7} - 1.5I_x = 0$$

but

$$I_x = \frac{V_x}{7}$$

$$35 \left(\frac{V_x - 10}{5} + \frac{V_x}{7} - \frac{1.5V_x}{7} = 0 \right)$$

$$7V_x - 70 + 5V_x - 7.5V_x = 0$$

$$4.5V_x = 70$$

$$V_x = 15.56 \text{ V}$$

$$V_{oc} = \frac{15.56 \times 4}{4 + 3} = 8.87 \text{ V}$$


$$V_{oc} = V_{TH} = 8.87 \text{ V}$$

To find R_{TH} , find I_{sc} and use

$$R_{TH} = \frac{V_{oc}}{I_{sc}}$$

Test B
Prob 3

Shorting a-b leaves the following ckt.

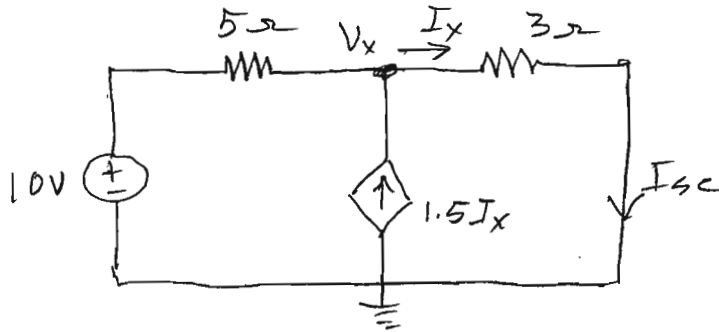

$$\frac{V_x - 10}{5} + \frac{V_x}{3} - 1.5I_x = 0 \quad I_x = \frac{V_x}{3}$$

$$15 \left(\frac{V_x - 10}{5} + \frac{V_x}{3} - \frac{1.5V_x}{3} = 0 \right)$$

$$3V_x - 30 + 5V_x - 7.5V_x = 0$$


$$0.5V_x = 30$$

$$V_x = 60$$

$$I_{sc} = \frac{V_x}{3} = 20 \text{ A}$$

$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{8.87}{20} = 0.444 \Omega$$


(b)

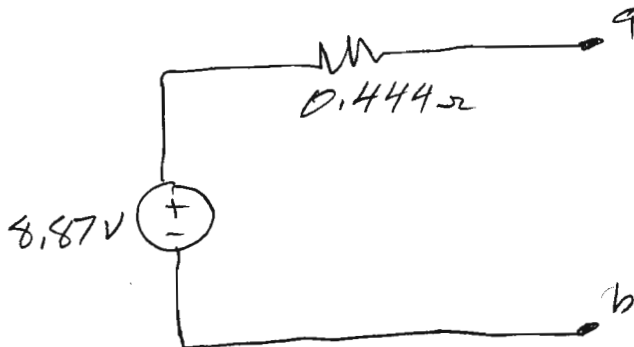

Thevenin Equivalent
Circuit

Test B
 Prob 3
 Alternate solution
 For R_{TH}

Apply 1 Amp

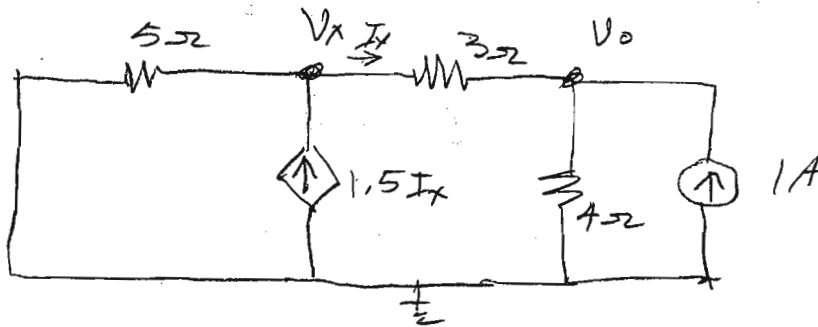

At V_x

$$\frac{V_x}{5} + \frac{V_x - V_0}{3} - 1.5 I_x \quad ; \quad I_x = \frac{V_x - V_0}{3}$$

$$\left(\frac{V_x}{5} + \frac{V_x - V_0}{3} - \frac{1.5(V_x - V_0)}{3} = 0 \right)$$

$$30 \left(\frac{V_x}{5} - \frac{V_x}{6} + \frac{V_0}{6} = 0 \right)$$

$$6V_x - 5V_x + 5V_0 = 0$$

$$\boxed{V_x + 5V_0 = 0}$$

At V_0

$$12 \left(\frac{V_0 - V_x}{3} + \frac{V_0}{4} = 1 \right)$$

$$4V_0 - 4V_x + 3V_0 = 12$$

$$\boxed{-4V_x + 7V_0 = 12}$$

$$V_0 = 0.444 \text{ V}$$

$$\boxed{R_{TH} = \frac{V_0}{1} = 0.444 \Omega}$$

check

- (4) You are given the circuit of Figure 4. Find the value of R that will result in maximum power being delivered to this resistor.


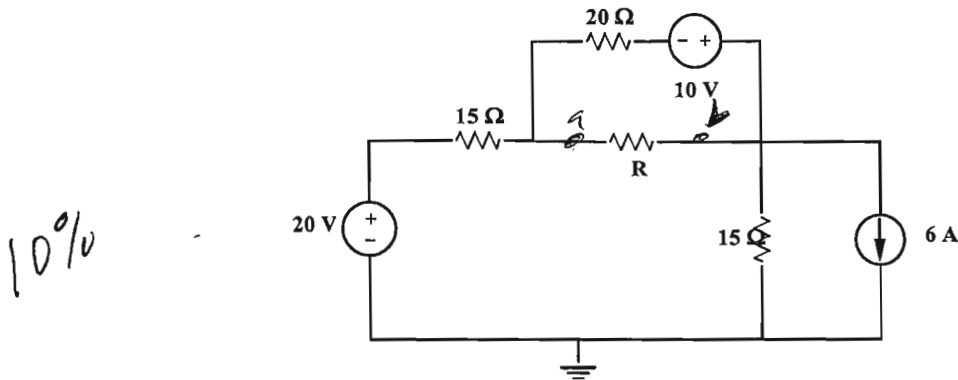


Figure 4: Circuit for problem 4.

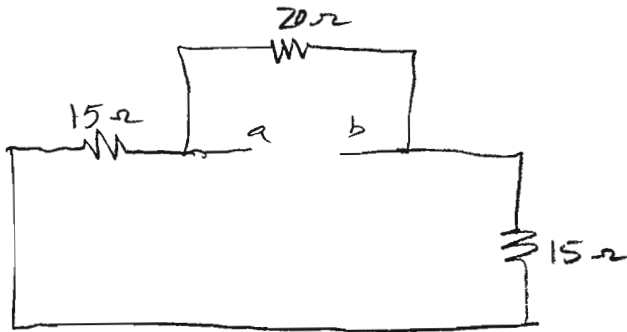For maximum power transfer, R must be R_{TH} . To get R_{TH} look into terminals a-b with R removed and all independent sources deactivated. This gives the circuit below.




$$R_{ab} = R_{TH} = 20 \parallel (15 + 15) = 12 \Omega$$

(5) You are given the op amp circuit of Figure 5.

(a) Find the relationship for $\frac{V_o}{i_s}$ in terms of R.

(b) If $R = 1 \text{ k}\Omega$, what is the maximum value allowable for i_s in order not to saturate the op amp?

20%

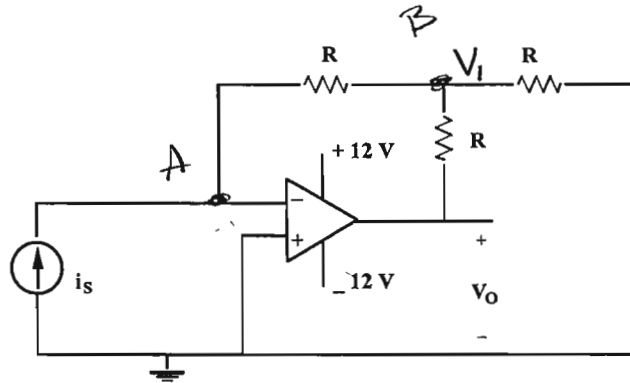

(a)

Figure 5: Circuit for problem 5.

At A

$$i_s = -\frac{V_1}{R} \quad \text{or} \quad V_1 = -R i_s \quad (1)$$

At B

$$\frac{V_1}{R} + \frac{V_1}{R} + \frac{V_1 - V_o}{R} = 0$$

$$V_o = 3V_1$$


substitute from Eq. (1).

$$V_o = -3R i_s \quad (2)$$

(b) use (2) with $V_o = \pm 12$

$$i_s = \mp \frac{12}{1\text{k} \times 3} = \mp 4 \text{ mA}$$

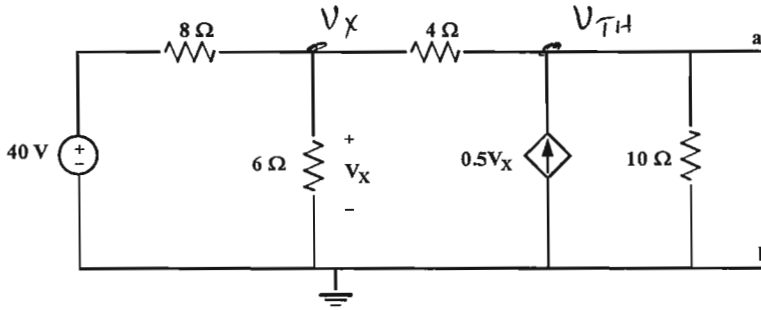- (6) You are given the circuit of Figure 6.
 (a) Find the Norton equivalent circuit looking into terminals a-b.
 (b) Draw the Norton equivalent circuit using your values of I_N and R_N .



20%

HW
Problem

Figure 6: Circuit for problem 6.

Find $V_{OC} = V_{TH}$; Find I_{SC} ; $R_{TH} = \frac{V_{OC}}{I_{SC}}$

$$24 \left(\frac{V_x - 40}{8} + \frac{V_x}{6} + \frac{V_x - V_{TH}}{4} = 0 \right)$$

$$3V_x - 120 + 4V_x + 6V_x - 6V_{TH} = 0$$

$$\boxed{13V_x - 6V_{TH} = 120}$$

Find V_{TH}

$$20 \left(\frac{V_{TH} - V_x}{4} + \frac{V_{TH}}{10} - 0.5V_x = 0 \right)$$


$$5V_{TH} - 5V_x + 2V_{TH} - 10V_x = 0$$

$$\boxed{-15V_x + 7V_{TH} = 0}$$

$$\begin{bmatrix} 13 & -6 \\ -15 & 7 \end{bmatrix} \begin{bmatrix} V_x \\ V_{TH} \end{bmatrix} = \begin{bmatrix} 120 \\ 0 \end{bmatrix}$$

$$V_x = 840V; \quad V_{TH} = 1800V$$

Now Find I_{sc}

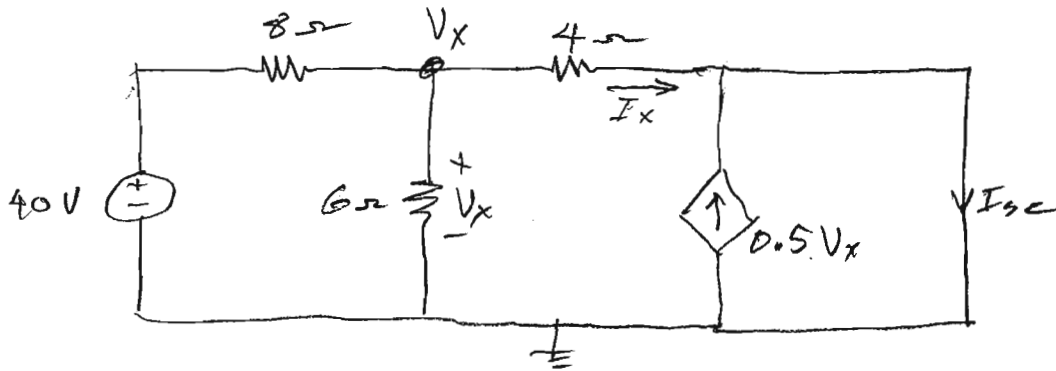

$$24 \left(\frac{V_x - 40}{8} + \frac{V_x}{6} + \frac{V_x}{4} = 0 \right)$$

$$3V_x - 120 + 4V_x + 6V_x = 0$$

$$13V_x = 120$$


$$V_x = \frac{120}{13}$$

$$I_x = \frac{V_x}{4} = \frac{30}{13}$$

$$\underline{I_{sc}} = I_x + 0.5V_x = \frac{30}{13} + \frac{60}{13} = \frac{90}{13} = \underline{6.92 A}$$


$$\underline{R_{TH}} = \frac{V_{oc}}{I_{sc}} = \frac{1800}{6.92} = \underline{260 \Omega}$$

(b) $I_N = I_{sc}$

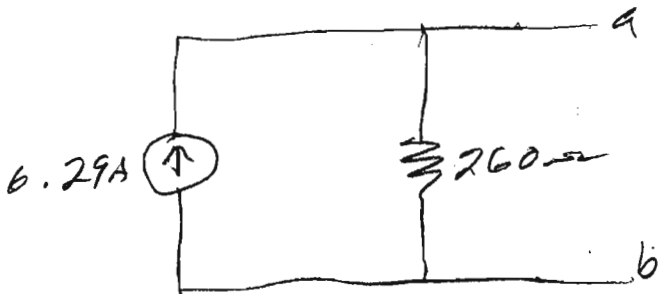

#6

Finding I_{sc} another way

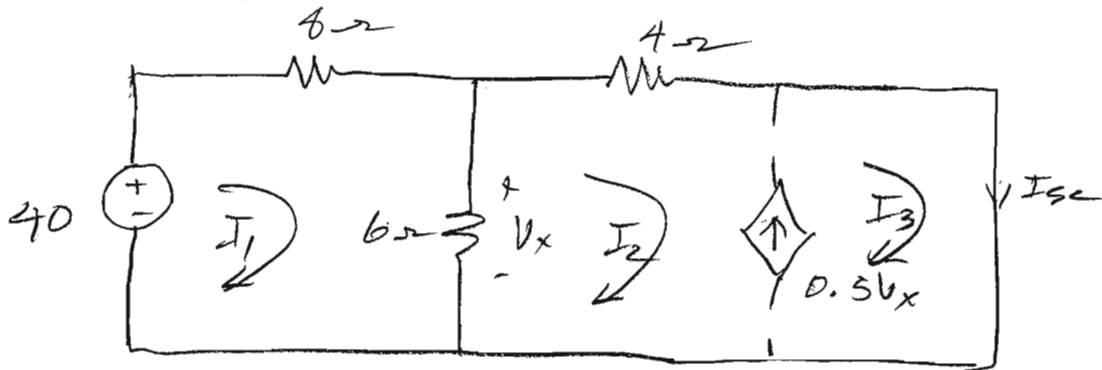

$$I_{sc} = I_3$$

$$-40 + 14I_1 - 6I_2 + 0I_3 = 0$$

$$14I_1 - 6I_2 + 0I_3 = 40$$

$$-6I_1 + 10I_2 + 0I_3 = 0$$

$$0.5V_x = I_3 - I_2$$

$$0.5(6(I_1 - I_2)) = I_3 - I_2$$


$$3I_1 - 3I_2 = I_3 - I_2$$

$$3I_1 - 2I_2 - I_3 = 0$$

$$\begin{bmatrix} 14 & -6 & 0 \\ -6 & 10 & 0 \\ 3 & -2 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 40 \\ 0 \\ 0 \end{bmatrix}$$

$$I_3 = I_{sc} = 6.923 \text{ A check}$$

#6 Verify R_{TH} , second method

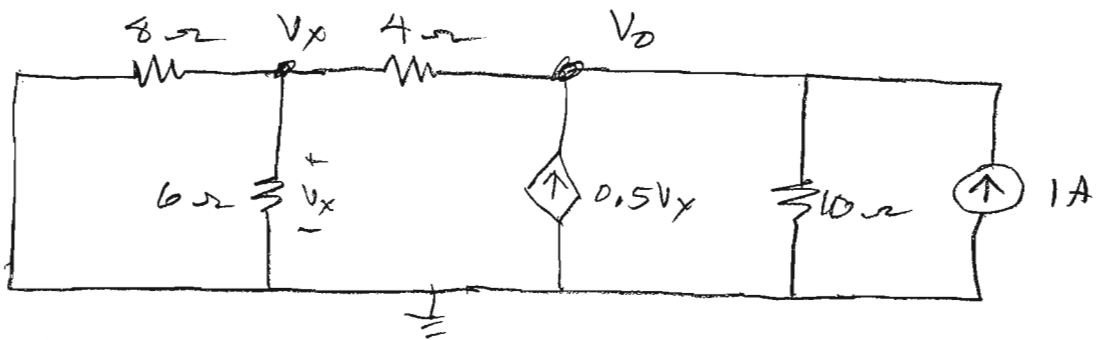

$$R_{TH} = \frac{V_o}{1}$$

At V_x

$$24 \left(\frac{V_x}{8} + \frac{V_x}{6} + \frac{V_x}{4} - V_o \right) = 0$$

$$3V_x + 4V_x + 6V_x - 6V_o = 0$$

$$13V_x - 6V_o = 0$$

At V_o

$$20 \left(\frac{V_o - V_x}{4} + \frac{V_o}{10} \right) - 0.5V_x = 1$$

$$5V_o - 5V_x + 2V_o - 10V_x = 20$$


$$-15V_x + 7V_o = 20$$

$$\begin{bmatrix} 13 & -6 \\ -15 & 7 \end{bmatrix} \begin{bmatrix} V_x \\ V_o \end{bmatrix} = \begin{bmatrix} 0 \\ 20 \end{bmatrix}$$

$$V_o = 260 \text{ V}$$

$$R_{TH} = \frac{260}{1} = 260 \Omega \text{ check}$$

Test B
(6)

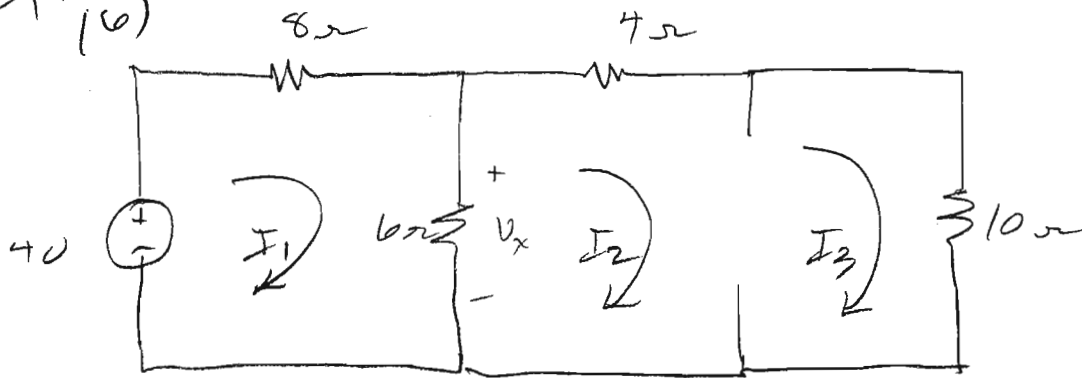

Constraint: $0.5 V_x = I_3 - I_2$

$V_x = 2I_3 - 2I_2$

$$14I_1 - 6I_2 + 0I_3 = 40$$

$$-6I_1 + 10I_2 + 10I_3 = 0$$

$$V_x = 6I_1 - 6I_2 = 2I_3 - 2I_2$$

$$+6I_1 - 4I_2 - 2I_3 = 0$$

$$\begin{bmatrix} 14 & -6 & 0 \\ -6 & 10 & 10 \\ 6 & -4 & -2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 40 \\ 0 \\ 0 \end{bmatrix}$$

$$I_3 = 180$$

$$V_{TH} = 1800V \quad \text{check}$$